

Compensating Amplifiers That Are Stable at Gain ≥ 10 to Operate at Lower Gains

By Charly El-Khoury

This article shows how compensating an amplifier—such as the [ADA4895-2](#), which is normally stable for a gain higher than +9—to operate with a gain as low as +2 provides higher slew rate and faster settling time than an equivalent internally compensated amplifier. Two methods will be presented, and advantages and disadvantages of each circuit will be highlighted.

The ADA4895-2, a device in the same family as the [ADA4896-2](#), [ADA4897-1](#), and [ADA4897-2](#), is a dual low-noise, high-speed, voltage-feedback amplifier with rail-to-rail outputs. Stable with a minimum gain of 10, it features 1.5-GHz gain-bandwidth product, 940-V/ μ s slew rate, 26-ns settling time to 0.1%, 2-nV/ $\sqrt{\text{Hz}}$ 1/f noise at 10 Hz, 1-nV/ $\sqrt{\text{Hz}}$ wide band noise, and -72-dBc spurious-free dynamic range at 2 MHz. Operating with a 3-V to 10-V supply, it draws a quiescent current of 3 mA per amplifier.

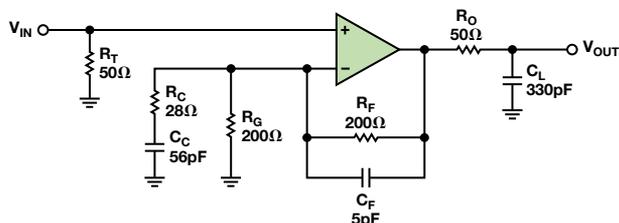


Figure 1. Method 1: Compensating the ADA4895-2 for a stable gain of +2.

Method 1, shown in Figure 1, adds a simple RC circuit ($R_C = 28 \Omega$ and $C_C = 56 \text{ pF}$) to the inverting input and a feedback capacitor ($C_F = 5 \text{ pF}$) in parallel with the feedback resistor. The circuit has a noise gain of +9 at high frequencies and a gain of +2 at frequencies below the resonance frequency, $1/2\pi R_C C_C = 100 \text{ MHz}$. Even though the noise gain at higher frequencies is approximately +9, the total output noise can be kept low as long as the low-pass filter, formed with R_O and C_L , blocks the high-frequency content. This allows the amplifier to operate at a gain of +2 while keeping the total output noise very low (3.9 nV/ $\sqrt{\text{Hz}}$).

This configuration is scalable to accommodate any gain between +2 and +9. Table 1 shows the component values and total wideband output noise for each gain setting.

Table 1. Component Values Used for Gain < +10. $R_T = R_O = 49.9 \Omega$.

Gain	R_C (Ω)	C_C (pF)	R_G (Ω)	R_F (Ω)	C_L (pF)	Total Output Noise ¹ (nV/ $\sqrt{\text{Hz}}$)
+2	28.6	56	200	200	330	3.88
+3	33.3	56	100	200	270	5.24
+4	40	56	66.7	200	200	6.60
+5	50	56	50	200	150	7.96
+6	66.7	40	40	200	150	9.32
+7	113	30	37.5	226	120	10.82
+8	225	20	32.1	226	120	12.18
+9	N/A	N/A	31.1	249	100	13.67

¹See the complete total noise equation below.

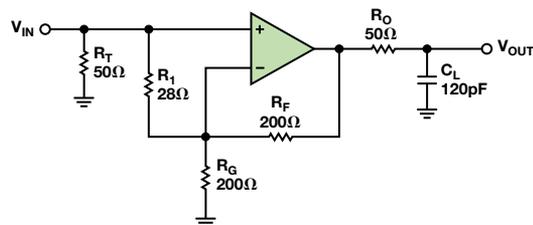


Figure 2. Method 2: Compensating the ADA4895-2 for a stable gain of +2.

Method 2, shown in Figure 2, adds a resistor ($R_1 = 28 \Omega$) between the inverting and noninverting inputs to increase the amplifier's noise gain to +9. No voltage appears across R_1 , so no current flows through it. Thus, the input impedance looking into R_1 in parallel with the noninverting input will remain high. The input-to-output signal gain is equal to $1 + R_F/R_G$, or +2 in this case. No capacitor is used in the compensation circuit, so there is no frequency dependency. This means that the wideband output noise is always higher at lower frequencies as compared to the first method.

This configuration is also scalable to accommodate any gain between +2 and +9. Table 2 shows the component values and total wideband output noise for each gain setting.

Table 2. Component Values Used for Gain < +10. $R_T = R_O = 49.9 \Omega$, $C_L = 120 \text{ pF}$.

Gain	R_1 (Ω)	R_G (Ω)	R_F (Ω)	Total Output Noise ¹ (nV/ $\sqrt{\text{Hz}}$)
+2	28.6	200	200	13.39
+3	33.3	100	200	13.39
+4	40	66.5	200	13.39
+5	49.9	49.9	200	13.39
+6	66.5	40	200	13.39
+7	113	37.4	226	13.53
+8	225	32.4	226	13.53
+9	N/A	30.9	249	13.67

¹See the complete total noise equation below.

Figure 3 shows the small signal and large signal frequency responses of the circuits shown in Figure 1 and Figure 2 into a 50- Ω analyzer, with $G = +5 \text{ V/V}$ or 14 dB. As shown, both circuits are very stable, and the peaking is a little over 1 dB. This stability will apply throughout the range of gains between +2 and +9 as long as the values in Table 1 and Table 2 are used.

For better total output noise, the low-pass RC filter at the output can be adjusted to cut the bandwidth of this circuit at 50 MHz or below, depending on the application.

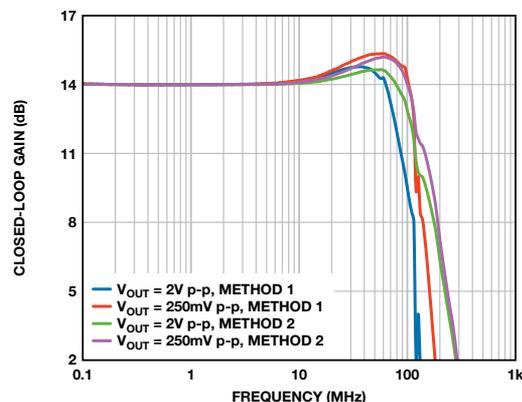


Figure 3. Frequency response for $G = +5$.

Equation for Method 1: total output noise =

$$\sqrt{\left(\sqrt{4KTR_T} \times \left(1 + \frac{R_F}{R_G}\right)\right)^2 + \left(e_n \times \left(1 + \frac{R_F}{R_G}\right)\right)^2 + \left(i_n \times 10^{-3} \times R_T \times \left(1 + \frac{R_F}{R_G}\right)\right)^2 + \left(\sqrt{4KTR_G} \times \left(\frac{R_F}{R_G}\right)\right)^2 + \left(i_n \times 10^{-3} \times R_F\right)^2 + \left(\sqrt{4KTR_F}\right)^2 + \left(\sqrt{4KTR_O}\right)^2}$$

Equation for Method 2: total output noise =

$$\sqrt{\left(\sqrt{4KTR_T} \times \left(1 + \frac{R_F}{R_E}\right)\right)^2 + \left(e_n \times \left(1 + \frac{R_F}{R_E}\right)\right)^2 + \left(i_n \times 10^{-3} \times R_T \times \left(1 + \frac{R_F}{R_E}\right)\right)^2 + \left(\sqrt{4KTR_E} \times \left(\frac{R_F}{R_E}\right)\right)^2 + \left(i_n \times 10^{-3} \times R_F\right)^2 + \left(\sqrt{4KTR_F}\right)^2 + \left(\sqrt{4KTR_O}\right)^2}$$

Why the Output Noise Is Better in Method 1 as Compared to Method 2

The output noise of Method 1 is much lower than that of Method 2, especially at gains below +7, because the noise gain of Method 1 is only high at high frequencies. At this point, a low-pass filter can be used to eliminate the high-frequency noise content. In Method 2, on the other hand, the amplifier is always operating at a noise gain of +9, even at low frequencies. Thus, the total output noise does not vary with the gain, as shown in Table 2. The equations above correspond to the two methods (note: $R_E = R_G/R_I$).

Advantages and Disadvantages of Each Method

We have shown two different methods, using a few external components, to make an amplifier that is designed for stability at higher gains operate stably at lower gain. Method 1 uses more passive components, which can increase board space and add cost as compared to Method 2. In return, the total output noise of the first circuit is lower than that of the second circuit. Therefore, the circuit choice will be determined by the application and its required specifications.

As shown in Figure 4, the decompensated ADA4895-2 provides a higher slew rate (300 V/μs vs. 100 V/μs) and faster settling time as compared to the internally compensated ADA4897-2, which is stable for gains $\geq +1$. These advantages increase as the circuit gain increases.

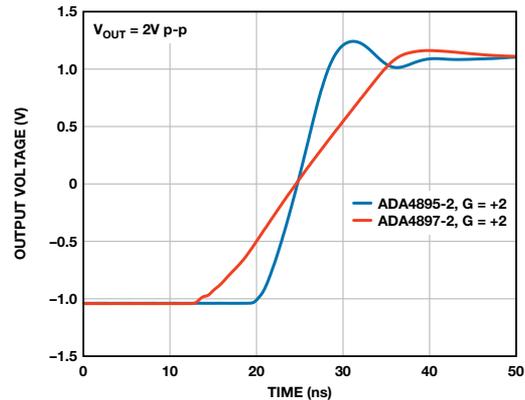


Figure 4. Comparing the compensated and decompensated amplifiers at $G = +2$.

Conclusion

A decompensated amplifier, such as the ADA4895-2, which is stable for $G \geq +10$, can be compensated to allow operation at lower gains. The two methods presented here trade complexity for total wideband noise. Both provide higher slew rate and faster settling time than the equivalent internally compensated ADA4897-2, which is stable for $G \geq +1$.

Author

Charly El-Khoury [charly.el-khoury@analog.com] is an applications engineer in the High Speed Amplifier Group. He has worked at ADI since graduating with a master's in ECE from Worcester Polytechnic Institute (WPI) in 2006.

