

DESIGN NOTES

Dual Micropower Comparator with Integrated 400mV Reference Simplifies Monitor and Control Functions – Design Note 321

Jon Munson

Introduction

The LT[®]6700 dual comparator incorporates features to reduce part count in space-critical designs, including a trimmed on-chip 400mV bandgap derived reference and internal hysteresis mechanisms. The LT6700 also features low voltage micropower single supply operation (1.4V to 18V, 7 μ A typical) and Over-The-Top[®] I/O capability to maximize versatility and provide solutions especially useful in portable battery-powered applications. The outputs are open collector to permit logical wire-AND functionality, and can drive relatively heavy loads (up to 40mA) such as relays or LED indicators.

The LT6700 supports a wide range of design configurations, but still offers a minimum pin count package (ThinSOT[™], 6-lead). This is made possible by offering the LT6700 in three different versions, each with a different input configuration. The LT6700-1 provides the designer with one inverting and one noninverting input, especially useful in window detection functions; the LT6700-2 provides two inverting inputs; and the LT6700-3 offers two noninverting inputs. The internal reference is connected to one of the inputs of each comparator section, as shown in Figure 1, and the remaining two connections are brought out for signal sensing by the user.

“Gas Gauge” Battery Monitor

It is easy to create a simple and accurate battery monitor using the LT6700, thanks to the accurate internal reference ($\pm 2\%$ over temperature). Figure 2 shows an

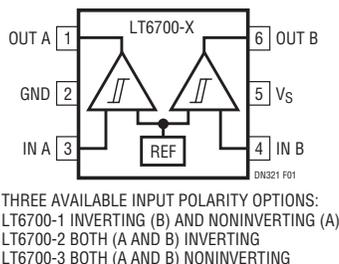


Figure 1. Pin Functions of the LT6700 Family

implementation of a 2-threshold “alkaline-cell” battery monitor. For the resistor values shown, the Pin 1 output goes low when the pack voltage falls below 2V (1V per cell) which corresponds to about 30% capacity remaining. The Pin 6 output goes low as well at 1.6V (0.8V per cell) as the battery pack reaches its rated end-of-life voltage. The number of threshold points may easily be increased by extending the resistor-divider chain and using additional comparators.

Simple Window-Function Status Monitor

The LT6700-1 lends itself nicely to window comparison applications, where the output wire-AND feature can be exploited. Figure 3 shows a 48V power bus monitor that provides an optoisolated alarm indication when voltage limits are exceeded. The micropower operation of the circuit allows it to derive operating power directly from the monitored voltage using simple Zener diode techniques.

LT, LT, LTC, LTM, Linear Technology, the Linear logo and Over-The-Top are registered trademarks and ThinSOT is a trademark of Linear Technology Corporation. All other trademarks are the property of their respective owners.

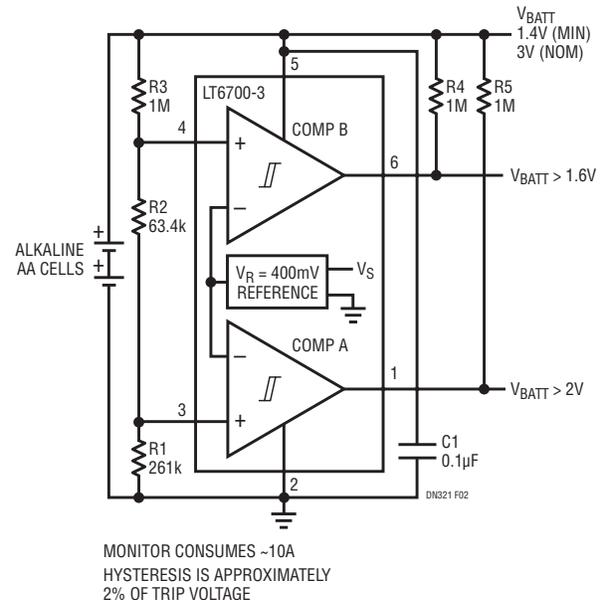


Figure 2. Micropower “Gas Gauge” Battery Monitor

