

Creating a Constant Envelope Signal Using the **ADL5331** RFVGA and **AD8319** Log Detector

CIRCUIT FUNCTION AND BENEFITS

Overall performance of a transmitter, wired or wireless, is a strong function of the output power of the amplifier. If the signal is weak, bit error rate (BER) or modulation error rate (MER) degrades due to low signal-to-noise ratio (SNR). If the signal is too strong, distortion causes the same issues. The circuit shown in Figure 1 uses the **ADL5331** variable gain amplifier (VGA), the **AD8319** power detector, and the **AD5621** low power *nano*DAC® to generate output power control accurate to 12 bits.

The **AD8319** has high temperature stability to compensate for any gain variation over temperature of the VGA, resulting in accurate power control over a wide temperature range. Because the **AD8319** control input, V_{SET} , and output, V_{OUT} , are related to the radio frequency (RF) input on a volts/dB scale and the **AD5621** *nano*DAC has a linear transfer function, the resulting output power control is linear in dB vs. digital-to-analog converter (DAC) input code.

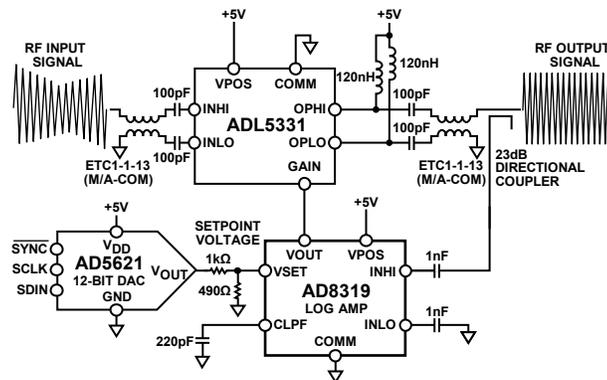


Figure 1. **ADL5331** Operating in an Automatic Gain Control Loop in Combination with the **AD8319** and **AD5621** (Simplified Schematic)

TABLE OF CONTENTS

Circuit Function and Benefits.....	1	Common Variations.....	4
Revision History	2	References.....	4
Circuit Description.....	3		

REVISION HISTORY

12/2017—Rev. 0 to Rev. A

Document Title Changed from CN0082 to AN-1527.....	Universal
Changes to Figure 1	1
Changes to Circuit Description Section	3

7/2009—Revision 0: Initial Version

CIRCUIT DESCRIPTION

The **ADL5331** VGA provides accurate gain control. However, an automatic gain control (AGC) achieves a more precise regulation of output power. Figure 1 shows the **ADL5331** operating in an AGC loop. The addition of the **AD8319** logarithmic amplifier allows the AGC to have improved temperature stability over a wide output power control range.

To operate the **ADL5331** VGA in an AGC loop, a sample of the output RF is back to the detector (typically using a directional coupler and additional attenuation). A setpoint voltage is applied by the **AD5621** DAC to the VSET input of the detector while V_{OUT} is connected to the GAIN pin of the **ADL5331**. Based on the defined linear in dB relationship of the detector between V_{OUT} and the RF input signal, the detector adjusts the voltage on the GAIN pin (the V_{OUT} pin of the detector is an error amplifier output) until the level at the RF input corresponds to the applied setpoint voltage. The GAIN pin settles to a value that results in the correct balance between the input signal level at the detector and the setpoint voltage.

The basic connections for operating the **ADL5331** in an AGC loop with the **AD8319** are shown in Figure 1. The **AD8319** is a 1 MHz to 10 GHz precision demodulating logarithmic amplifier. It offers a dynamic detection range of 40 dB with ± 1 dB temperature stability. The V_{OUT} pin of the **AD8319** controls the gain control pin, GAIN, of the **ADL5331**. In this application, when the **AD8319** is in controller mode, the V_{OUT} pin of the **AD8319** can drive the **ADL5331** GAIN pin over its full linear range of 0 V to 1.4 V. Under low power RF input conditions, outside the linear control range of the loop, the V_{OUT} pin of the **AD8319** can be driven to its maximum value, close to the value of the positive input voltage, V_{POS} . To avoid overdrive recovery issues with the **ADL5331** GAIN input, place a voltage divider between V_{OUT} on the **AD8319** and GAIN on the **ADL5331**. This can have a slight effect on the overall speed of the loop, for instance, when the input power to the **ADL5331** is stepped.

A coupler with an attenuation of 23 dB matches the desired output power range from the VGA to the linear operating range of the **AD8319**. In this case, the desired output power range of the VGA is -15 dBm to $+15$ dBm. With the given coupler and attenuation, the range of power to the **AD8319** RF input is -8 dBm to -38 dBm, within the specified range of -3 dBm to -43 dBm for a ± 1 dB error.

The error amplifier of the detector uses a ground referenced capacitor pin, CLFP, to integrate the error signal in the form of a current. Connect a capacitor to the CLFP pin to set the loop bandwidth and to ensure loop stability.

Figure 2, Figure 3, and Figure 4 show the transfer function of the **ADL5331** output power vs. the **AD5621** DAC code for a 100 MHz sine wave with an input power of 0 dBm, -10 dBm, and -20 dBm. The power control of the **AD8319** has a negative sense. Decreasing the DAC code, which corresponds to demanding a higher signal from the **ADL5331**, increases the gain.

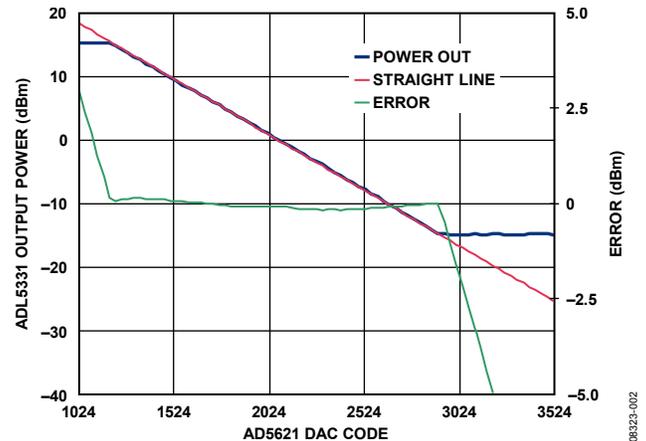


Figure 2. **ADL5331** Output Power vs. **AD5621** DAC Code with RF Input Signal = 0 dBm

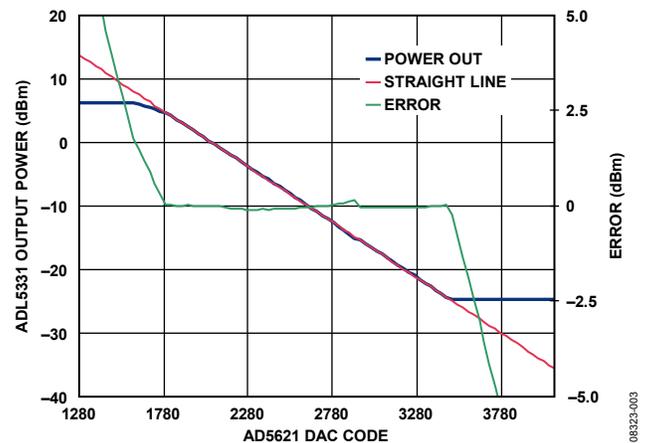


Figure 3. **ADL5331** Output Power vs. **AD5621** DAC Code with RF Input Signal = -10 dBm

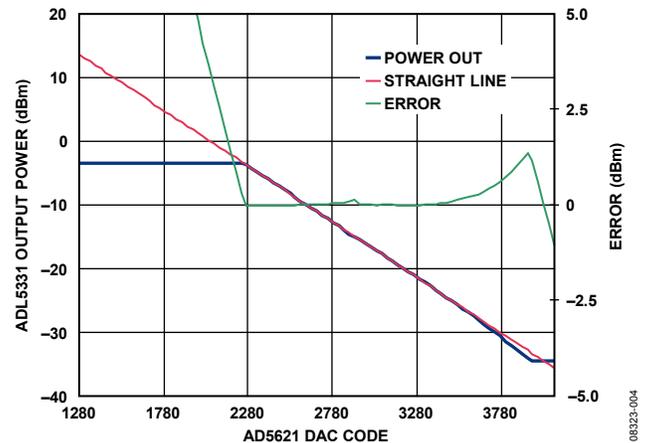


Figure 4. **ADL5331** Output Power vs. **AD5621** DAC Code with RF Input Signal = -20 dBm

For the AGC loop to remain in equilibrium, the [AD8319](#) must track the envelope of the [ADL5331](#) output signal and provide the necessary voltage levels to the gain control input of the [ADL5331](#). Figure 5 shows an oscilloscope measurement of the AGC loop in Figure 1. A 100 MHz sine wave with 50% amplitude modulation (AM) is applied to the [ADL5331](#). The output signal from the [ADL5331](#) is a constant envelope sine wave with amplitude corresponding to a setpoint voltage at the [AD8319](#) of 1.5 V. The gain control response of the [AD8319](#) to the changing input envelope is also shown in Figure 5.

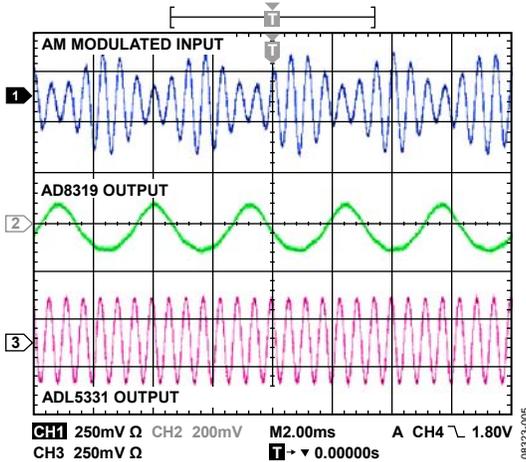


Figure 5. Oscilloscope Showing an AM Modulated Input Signal

Figure 6 shows the response of the AGC RF output to a pulse on the VSET pin. As the VSET pin decreases to 1 V, the AGC loop responds with an RF burst. Response time and the amount of signal integration are controlled by the capacitance at the [AD8319](#) CLFP pin. This function is analogous to the feedback capacitor around an integrating amplifier. An increase in the capacitance results in a slower response time.

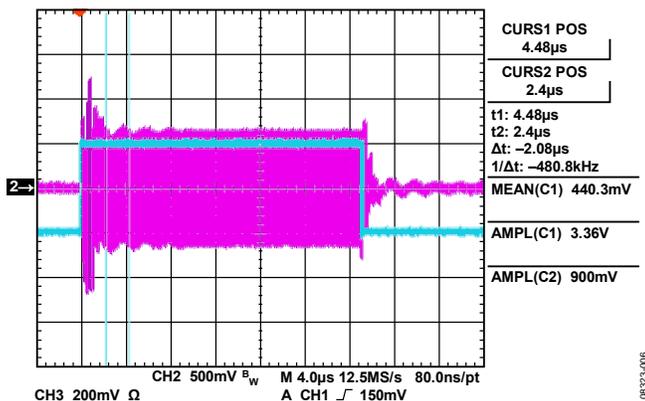


Figure 6. Oscilloscope Showing the [ADL5331](#) Output

Construct the circuit on a multilayer printed circuit board (PCB) with a large area ground plane. Use proper layout, grounding, and decoupling techniques to achieve optimum performance (see [MT-031](#), [MT-101](#), and the [EVAL-ADL5331](#) and [EVAL-AD8319](#) evaluation board layouts).

On the bottom of the [ADL5331](#) and [AD8319](#) chip scale packages, there are exposed compressed paddles. These paddles are internally connected to the ground of the chips. Solder the paddles to the low impedance ground plane on the PCB to ensure the specified electrical performance and to provide thermal relief. It is also recommended that the ground planes on all layers under the paddle be stitched together with vias to reduce thermal impedance.

COMMON VARIATIONS

This circuit can implement a constant power out function (fixed setpoint with variable input power) or a variable power out function (variable setpoint with fixed or variable input power). If a higher output power control range is desired, the [AD8318](#) logarithmic amplifier (60 dB power detection range) can be used in place of the [AD8319](#). For a constant output power function, the lower dynamic range of the [AD8319](#) is adequate because the loop always servos the input power of the detector to a constant level.

The [ADL5331](#) VGA, which is optimized for transmit applications, can also be replaced by the [AD8368](#) VGA. The [AD8368](#) is optimized for low frequency receive applications up to 800 MHz and provides 34 dB of linear in dB, voltage controlled variable gain.

REFERENCES

- [MT-031 Tutorial, Grounding Data Converters and Solving the Mystery of "AGND" and "DGND."](#) Analog Devices.
- [MT-073 Tutorial, High Speed Variable Gain Amplifiers.](#) Analog Devices.
- [MT-077 Tutorial, Log Amp Basics.](#) Analog Devices.
- [MT-078 Tutorial, High Speed Log Amps.](#) Analog Devices.
- [MT-101 Tutorial, Decoupling Techniques.](#) Analog Devices.
- Whitlow, Dana. *Design and Operation of Automatic Gain Control Loops for Receivers in Modern Communications Systems.* Chapter 8, Analog Devices Wireless Seminar (2006).