

If the voltage at DCIN drops below 9.75V, DCIN is deselected and the battery voltage is routed to the output. If the battery voltage is less than 5.9V, each switch is made to mimic a diode, allowing power to flow from the highest potential source to the output. In this “2-diode” mode, the first half of each PowerPath switch pair is turned on, and the second half is turned off. Thus, two diodes are formed by the body diodes of the MOSFET switches that are turned off.

The inrush current limit of 6A is selected with a 0.033Ω R_{SENSE} resistor. The fault timer is set to 1.1ms with a 4700pF C_{TIMER} capacitor. If a MOSFET switch is in current limit for more than 1.1ms, an internal latch in the LTC1473 is set and the MOSFET switch is turned off.

The LTC1442 shown in Figure 1 is an ultralow power dual comparator with a precision 1.182V reference. This comparator monitors the voltage at DCIN and the battery voltage and selects which MOSFET switch to turn on. Simple logic, comprising CMOS NAND gates, decodes the comparator outputs to control the inputs of the LTC1473. A 7.5V Zener shunt regulator in series

with a 500k resistor supplies power for both the CMOS NAND gates and the LTC1442.

Power Routing Circuit for Microprocessor Controlled Dual Battery Systems

The microprocessor controlled dual battery system shown in Figure 2 uses two LTC1473s to provide input power routing and battery charging multiplexing. The two batteries can be of different chemistries. One LTC1473 is used to connect the output of the charger to the battery; the other connects the battery to the input of the system switching regulator.

The power-management microprocessor provides overall control of the power management system in concert with the two LTC1473s and the auxiliary power-management systems. The microprocessor decides which battery to connect to the input of the system switching regulator and which battery is in need of recharging. To charge a battery, the microprocessor selects the charging algorithm for that particular battery chemistry.

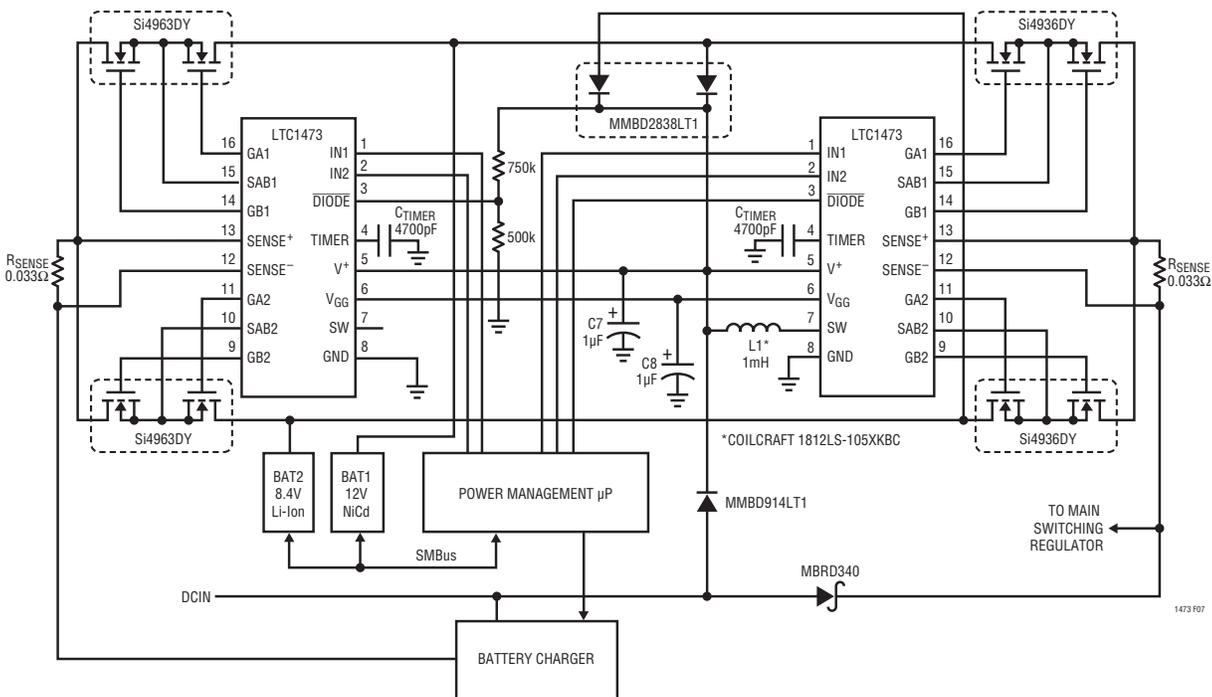


Figure 2. Power Routing Circuit for Microprocessor Controlled Dual Battery System

Data Sheet Download

www.linear.com

For applications help,
call (408) 432-1900

Linear Technology Corporation
1630 McCarthy Blvd., Milpitas, CA 95035-7417
(408) 432-1900 • FAX: (408) 434-0507 • www.linear.com

dn160f_conv LT/TP 0897 185K • PRINTED IN THE USA

LINEAR
TECHNOLOGY
© LINEAR TECHNOLOGY CORPORATION 1997