

Circuits from the Lab™ tested circuit designs address common design challenges and are engineered for quick and easy system integration. For more information and/or support, visit www.analog.com/CN0175.

Devices Connected/Referenced

AD7607	8-Channel DAS with 14-Bit, Bipolar Input, Simultaneous Sampling ADC
ADR421	Precision, Low Noise, 2.500 V XFET® Voltage Reference

A Low Cost, 8-Channel, Simultaneously Sampled, Data Acquisition System with 84 dB SNR and Excellent Channel-to-Channel Matching

CIRCUIT FUNCTION AND BENEFITS

Cost sensitive, high channel count applications that require wide dynamic range can effectively use the [AD7607](#) 8-channel integrated data acquisition system (DAS) with on-chip 14-bit SAR ADCs to achieve greater than 80 dB dynamic range.

A typical application for the DAS is in power-line measurement and protection equipment, where large numbers of current and voltage channels of multiphase distribution and transmission networks must be sampled simultaneously.

Many low voltage power-line measurement and protection systems do not require full 16-bit ADC resolution (such as provided by the [AD7606](#) DAS); however, they still require more than 80 dB dynamic range to capture the under- and over-voltage/current conditions. Simultaneous sampling is also needed to maintain the phase information between the current and voltage channels on a multiphase power line.

The [AD7607](#) 8-Channel DAS with 14-Bit, bipolar input, simultaneous sampling SAR ADC has 84 dB signal-to-noise ratio (SNR) to meet the requirements for these types of low voltage protection and measurement systems. The circuit shown in Figure 1 also uses an external [ADR421](#) precision, low drift, low noise reference for high channel count applications that require absolute accuracy performance.

CIRCUIT DESCRIPTION

The [AD7607](#) is an integrated data acquisition system with input amplifiers, overvoltage protection, analog antialiasing filter, 14-bit SAR ADC, and a digital filter all included on chip. This circuit consists of the [AD7607](#) in conjunction with the [ADR421](#) 2.5 V reference. Symmetrical layout around the analog input channels and device decoupling is critical for good channel-to-channel matching.

The following section outlines the recommended layout for the [AD7607](#) and [ADR421](#) to achieve excellent channel-to-channel matching as well as 84 dB SNR performance.

Rev. 0

Circuits from the Lab™ circuits from Analog Devices have been designed and built by Analog Devices engineers. Standard engineering practices have been employed in the design and construction of each circuit, and their function and performance have been tested and verified in a lab environment at room temperature. However, you are solely responsible for testing the circuit and determining its suitability and applicability for your use and application. Accordingly, in no event shall Analog Devices be liable for direct, indirect, special, incidental, consequential or punitive damages due to any cause whatsoever connected to the use of any Circuits from the Lab circuits. (Continued on last page)

100-9293-001

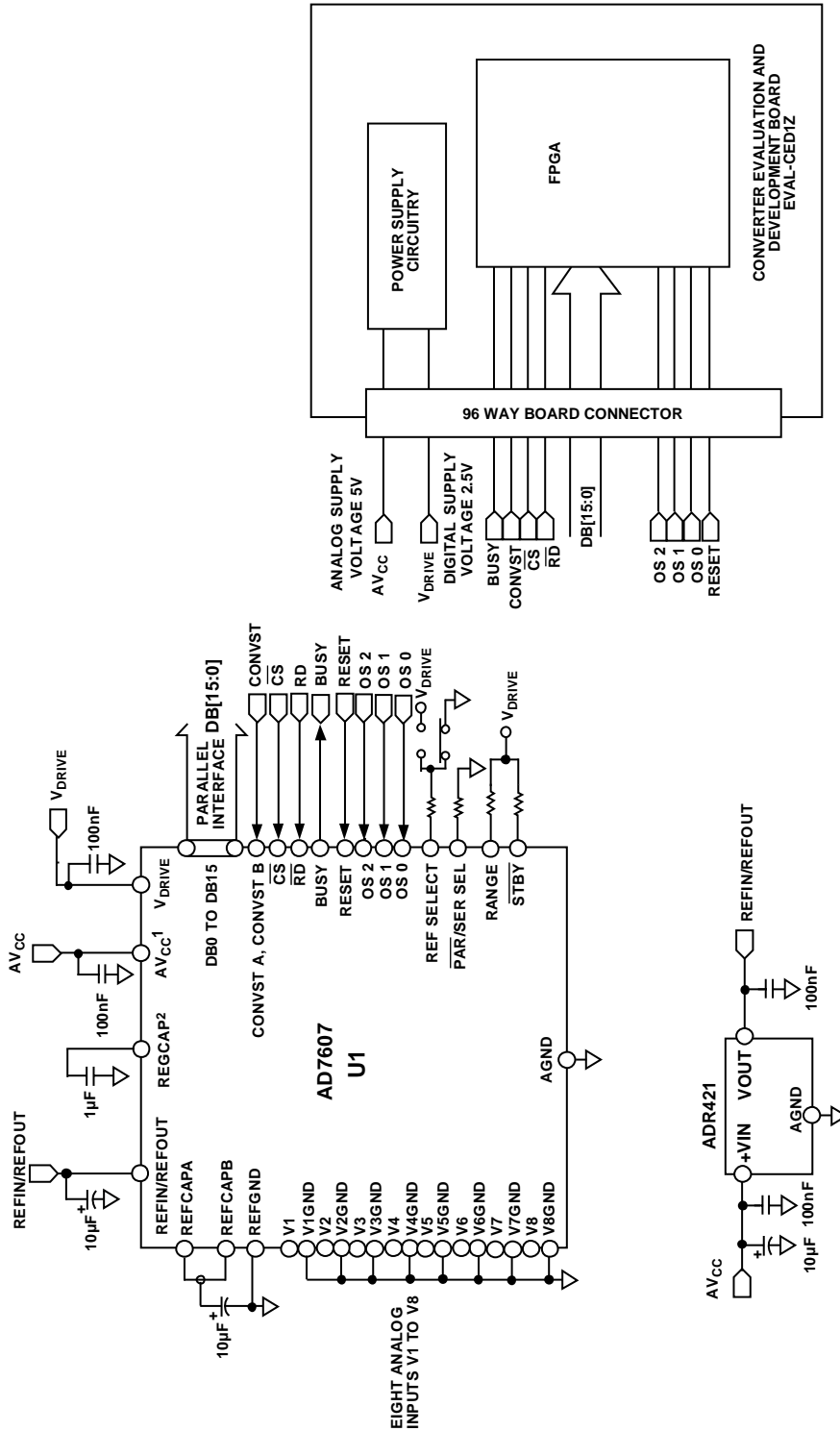


Figure 1. Low Cost, 8-Channel, Simultaneously Sampled, Data Acquisition System (Simplified Schematic: All Connections and Decoupling Not Shown)

¹DECOUPLING SHOWN ON THE AV_{CC} PIN APPLIES TO EACH AV_{CC} PIN (PIN 1, PIN 37, PIN 38, PIN 48).
²DECOUPLING SHOWN ON THE REGCAP PIN APPLIES TO EACH REGCAP PIN (PIN 36, PIN 39).

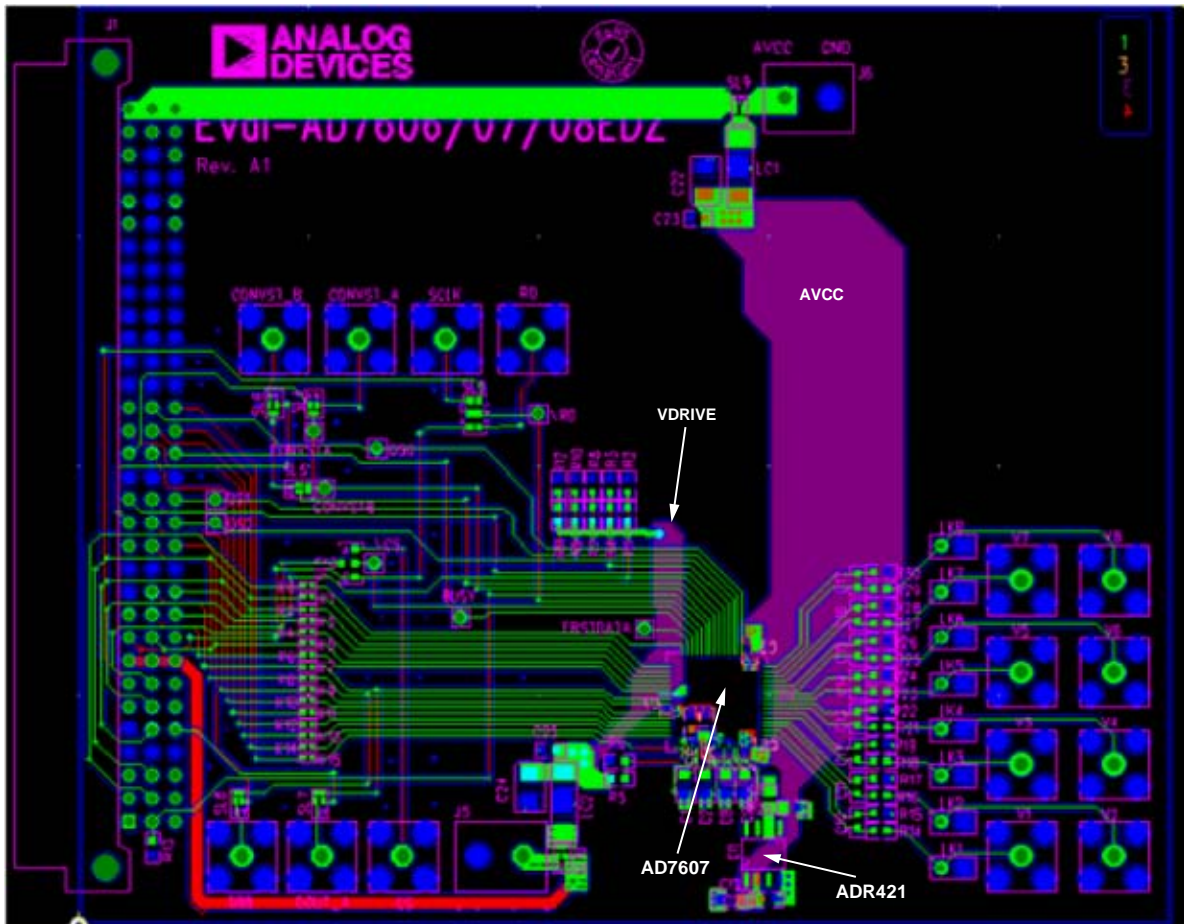


Figure 2. PCB Layout Showing the AD7607 DAS and ADR421 Reference

AD7607 Evaluation Board Layout

To ensure good channel-to-channel matching, a symmetrical layout of the analog input channels is important. In a system that contains multiple AD7607 devices, to ensure good device-to-device performance matching, a symmetrical layout between the AD7607 devices is important.

Figure 2 shows an optimum board layout of the AD7607 and the ADR421. The AVCC supply plane runs to the right of the AD7607. The VDRIVE supply track runs to the left of the AD7607. The ADR421 reference is positioned to the south of the AD7607. A solid ground plane layer is used.

These symmetrical layout principles should also be applied to a system that contains multiple AD7607 devices. The AD7607 devices should be placed in a north-south direction with the reference voltage located midway between the AD7607 devices, and running in the north-south direction similar to Figure 2. Details of a system using multiple AD7606 (16-bit 8-channel DAS) devices can be found in Circuit Note CN-0148.

Good decoupling is also important to lower the supply impedance presented to the AD7607 and to reduce the magnitude of the supply spikes. The decoupling capacitors should be placed as close as possible to the DUT power pins

and their corresponding ground pins. The decoupling capacitors for the REFIN/REFOUT pin and the REFCAPA and REFCAPB pins are also critical decoupling capacitors and should be placed as close as possible to their respective AD7607 pins and, where possible, they should be placed on the same side of the board as the AD7607 device. Figure 3 shows the recommended decoupling on the top layer of the AD7607 board.

The four ceramic capacitors on the top layer of the board are the decoupling caps for REFIN/REFOUT pin and the REFCAPA and REFCAPB pins. These capacitors are placed in a north-south direction to get as close to their respective pins as possible. Figure 4 shows the bottom layer decoupling which is used for the four AVCC pins and the VDRIVE pin. Multiple vias are used to connect the pins to their respective decoupling capacitors. Symmetrical layout of the decoupling capacitors around the AD7607 devices helps with part-to-part performance matching. Multiple vias are used to connect capacitor pads and pin pads to ground and supply planes and the reference track.

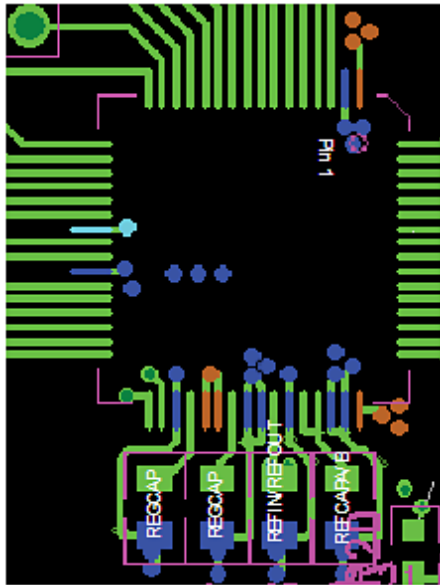


Figure 3. Top Layer Decoupling

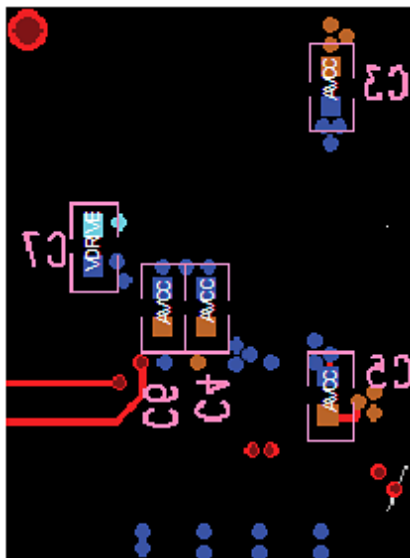


Figure 4. Bottom Layer Decoupling

Channel-to-Channel Matching

In a high channel count system, good channel-to-channel and part-to-part performance matching greatly simplifies calibration routines. Symmetrical layout of the AD7607 devices, the analog input channels, and the decoupling capacitors aids performance matching between multiple devices. The use of a common system reference further enhances matching performance in the system. Figure 5 shows the matching measured for the eight channels on the board when all inputs are grounded. There is a maximum histogram spread of three codes, with each channel histogram centered on Code 1.

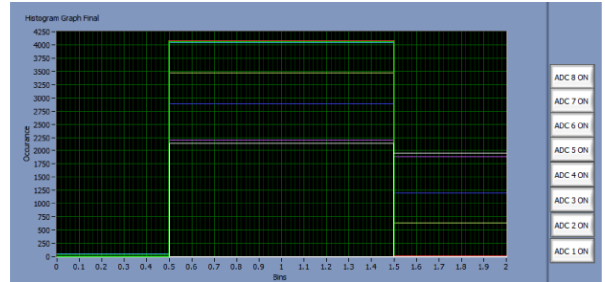


Figure 5. Histogram for Eight Channels with Inputs Grounded

AC Performance

In this circuit, the AD7607 is configured to operate in the external reference mode. The ADR421 provides the 2.5 V reference to the REFIN/REFOUT pin of the AD7607. A 1 kHz signal is applied to Channel 1 of the AD7607. The AD7607 is configured for the ±5 V input range. Sampling at 200 kSPS on all eight channels, the AD7607 achieves 84.12 dB SNR. This performance equates to approximately 13.7 effective number of bits (ENOB), where $ENOB = (SNR - 1.76 \text{ dB})/6.02$.

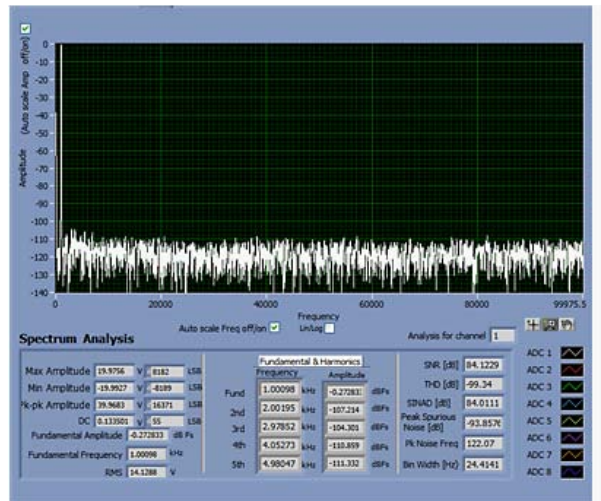


Figure 6. FFT Showing SNR of 84.12 dB, Input = 1 kHz, fs = 200 kSPS

To further increase the SNR performance and increase the ENOB of the system, the AD7607 is configured to operate in an 8x oversampling mode. In this mode, the SNR increases to 85.25 dB, therefore increasing the effective number of bits to 13.9 bits. When using the AD7607 in an 8x oversampling mode, the throughput rate on each channel is reduced to 25 kSPS.

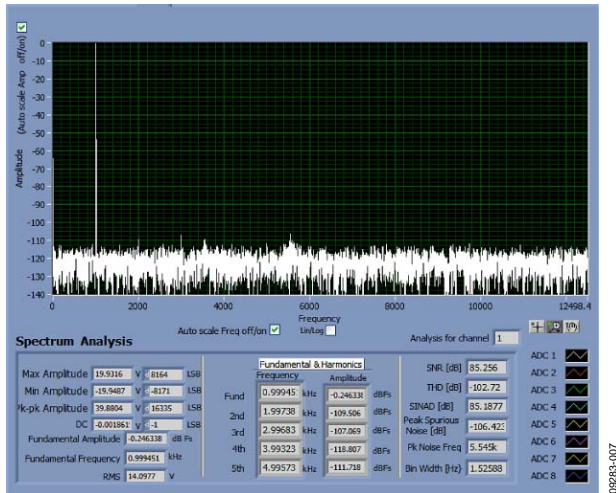


Figure 7. FFT Showing 85.26 dB SNR with Oversampling-by-8 and $f_s = 25$ kSPS

The layout suggested above ensures good channel-to-channel matching on a single [AD7607](#) and also good part-to-part matching between multiple [AD7607](#)s on the same PCB board. The [AD7607](#) and [ADR421](#) achieve 84 dB SNR, satisfying the need for greater than 80 dB dynamic range for low voltage protection and measurement applications in substation automation equipment.

COMMON VARIATIONS

The [AD7607](#) is an 8-channel, 14-bit DAS. Also available are the [AD7606-6](#) (6-channel, 16-bit DAS) and [AD7606-4](#) (4-channel, 16-bit DAS). The [AD7608](#) is an 8-channel 18-bit DAS.

Alternate voltage references can be chosen using the [Voltage Reference Selection and Evaluation Tool](#).

For more details on layout and performance issues involving multiple [AD7606](#) 16-bit devices on the same board, see Circuit Note [CN-0148](#).

LEARN MORE

[MT-021 Tutorial, Successive Approximation ADCs.](#)
Analog Devices.

[MT-031 Tutorial, Grounding Data Converters and Solving the Mystery of "AGND" and "DGND."](#) Analog Devices.

[MT-101 Tutorial, Decoupling Techniques.](#) Analog Devices.
[Voltage Reference Selection and Evaluation Tool.](#)
Analog Devices.

Data Sheets and Evaluation Boards

[AD7606](#)

[AD7606 Evaluation Board](#)

[AD7607](#)

[AD7607 Evaluation Board](#)

[AD7608](#)

[AD7608 Evaluation Board](#)

[EVAL-CED1Z Converter Evaluation and Development Board](#)

[ADR421](#)

REVISION HISTORY

11/10—Revision 0: Initial Version

(Continued from first page) Circuits from the Lab circuits are intended only for use with Analog Devices products and are the intellectual property of Analog Devices or its licensors. While you may use the Circuits from the Lab circuits in the design of your product, no other license is granted by implication or otherwise under any patents or other intellectual property by application or use of the Circuits from the Lab circuits. Information furnished by Analog Devices is believed to be accurate and reliable. However, "Circuits from the Lab" are supplied "as is" and without warranties of any kind, express, implied, or statutory including, but not limited to, any implied warranty of merchantability, noninfringement or fitness for a particular purpose and no responsibility is assumed by Analog Devices for their use, nor for any infringements of patents or other rights of third parties that may result from their use. Analog Devices reserves the right to change any Circuits from the Lab circuits at any time without notice but is under no obligation to do so.

©2010 Analog Devices, Inc. All rights reserved. Trademarks and registered trademarks are the property of their respective owners.
CN09283-0-12/10(0)



www.analog.com