

Circuits from the Lab™
Reference Circuits

Circuits from the Lab™ reference circuits are engineered and tested for quick and easy system integration to help solve today's analog, mixed-signal, and RF design challenges. For more information and/or support, visit www.analog.com/CN0198.

Devices Connected/Referenced

| | |
|---------|--|
| AD5755 | 16-Bit Quad Channel, Voltage Output DAC with Dynamic Power Control |
| ADP2300 | 700 kHz Nonsynchronous Step-Down Switching Regulator |

5 V Regulator Supplies High Transient Current for Dynamic Power Controlled DAC

EVALUATION AND DESIGN SUPPORT

Circuit Evaluation Boards

- [AD5755 Evaluation Board \(EVAL-AD5755SDZ\)](#)
- [System Demonstration Platform \(EVAL-SDP-CB1Z\)](#)
- [ADP2300 Evaluation Board \(ADP2300-EVALZ\)](#)

Design and Integration Files

- [Schematics, Layout Files, Bill of Materials](#)

CIRCUIT FUNCTION AND BENEFITS

The circuit shown in Figure 1 provides a unique power saving solution for a digital-to-analog converter (DAC)-based, 4 mA to 20 mA output circuit. To provide sufficient headroom for typical resistive loads between 10 Ω and 1000 Ω, traditional 4 mA to 20 mA output driver stages must operate on at least 20 V (plus

some additional headroom) to provide a sufficient voltage to drive high value resistive loads. For low value resistive loads, however, the fixed value, high voltage supply results in significant internal power dissipation that can affect DAC accuracy and require additional heat sinking.

The AD5755 quad 16-bit DAC has four independent high efficiency, internal dc-to-dc converters that drive the four output stages at a dynamically adjusted boost voltage based on sensing the actual output voltage of the 4 mA to 20 mA driver. The boost circuit maintains several volts of headroom on the output stage, regardless of the load resistance, thereby reducing the maximum internal power dissipation by a factor of approximately 4× for a 24 mA output current into a 10 Ω load.

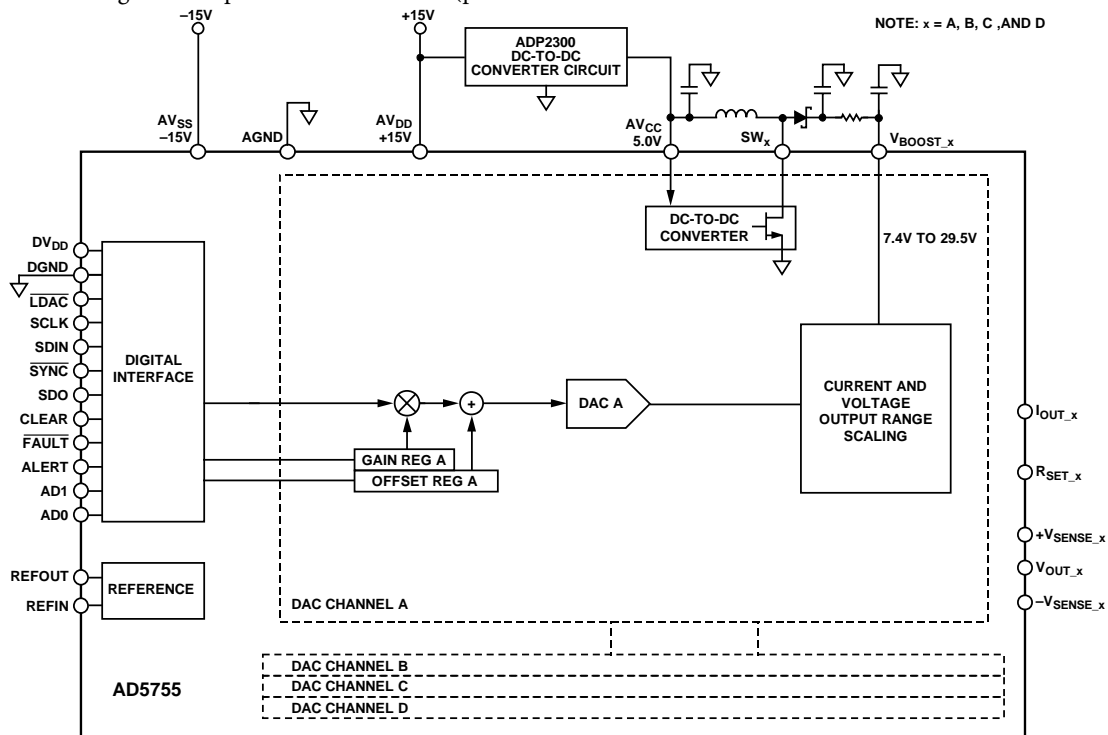


Figure 1. Current and Voltage Output DAC with Modified Power Scheme (Simplified Schematic: All Connections and Decoupling Not Shown)

Rev. 0

Circuits from the Lab™ circuits from Analog Devices have been designed and built by Analog Devices engineers. Standard engineering practices have been employed in the design and construction of each circuit, and their function and performance have been tested and verified in a lab environment at room temperature. However, you are solely responsible for testing the circuit and determining its suitability and applicability for your use and application. Accordingly, in no event shall Analog Devices be liable for direct, indirect, special, incidental, consequential or punitive damages due to any cause whatsoever connected to the use of any Circuits from the Lab circuits. (Continued on last page)

The internal dc-to-dc converters require an external 5 V supply and can draw significant currents when the DAC outputs full-scale slew. A high efficiency external dc-to-dc converter circuit based on the ADP2300 is driven from the 15 V and supplies this voltage. The ADP2300 has excellent transient response to large current steps up to 800 mA and ensures proper operation of the boost converters as well as eliminating the need for a separate 5 V supply.

The entire circuit operates on ± 15 V supplies that allow the DAC to provide voltage outputs that cover the industrial signal level range of up to ± 10 V in addition to the 4 mA to 20 mA outputs. This combination of parts is a low cost, power efficient solution that minimizes the number of external components required and that ensures 16-bit performance for varying load conditions.

CIRCUIT DESCRIPTION

This circuit enhances the slew rate control and dynamic power control features of the AD5755 to create a more complete and robust DAC solution. By implementing a simple step-down dc-to-dc converter using the ADP2300, the circuit can provide higher than normal supply currents that are required when slewing the AD5755 outputs.

The AD5755 behaves like any standard DAC converting digital data to analog current (for example, 0 mA to 20 mA, 4 mA to 24 mA, or 0 mA to 24 mA) or voltage outputs (0 V to 5 V, 0 V to 10 V, ± 5 V, or ± 10 V). The AD5755 operates with an extended AV_{SS} power supply range to -26.4 V, and an AV_{DD} range to $+33.0$ V.

Power Dissipation Control

In standard, current controlled module or actuator designs, the load resistor value can range from typically 50Ω to 750Ω , but it can be as low as 10Ω or as high as $1 \text{ k}\Omega$. The 4 mA to 20 mA output driver stage must operate on a supply voltage that provides sufficient headroom for the full range of the load resistor values. For example, when driving 24 mA into a $1 \text{ k}\Omega$ load, a supply voltage of greater than 27 V is required, assuming a 3 V headroom is needed. In this case, the internal package power dissipation due to the output driver is $3 \text{ V} \times 24 \text{ mA} = 72 \text{ mW}$. However, when driving a 10Ω load with the same 27 V supply voltage, the internal power dissipation of the driver is approximately $27 \text{ V} \times 24 \text{ mA} = 648 \text{ mW}$. For a quad DAC, this is greater than 2.5 W.

The AD5755 circuitry senses the output voltage and dynamically regulates the boost supply voltage to meet supply voltage requirements plus a sufficient amount of headroom. For 24 mA output into 10Ω , the boost voltage of 7.4 V results in an internal power dissipation of only $7.4 \text{ V} \times 24 \text{ mA} = 178 \text{ mW}$. This represents nearly a 4 \times reduction in power vs. the unregulated case.

A separate boost supply voltage is generated for each of the four DAC outputs by four independent dc-to-dc converters operating on a 5 V input.

DC-to-DC Converters

The AD5755 contains four independent, on-board dc-to-dc converters. They provide dynamic control of the V_{BOOST_X} supply voltage for each individual channel. Figure 2 shows the discrete components needed for the dc-to-dc circuitry, and the following sections describe the operation of this circuitry.

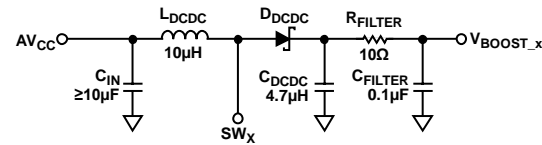


Figure 2. DC-to-DC External Circuit

It is recommended to place a 10Ω , 100 nF low-pass RC filter after C_{DCDC} . This consumes a small amount of power; however, it reduces the amount of ripple on the V_{BOOST_X} supply. The suggested component values for L_{DCDC} , C_{DCDC} , and D_{DCDC} are given in Table 1.

Table 1. Discrete Components for DC-to-DC Converter

| Symbol | Component | Value | Manufacturer |
|-------------------|--------------------|--------------------|--------------|
| L_{DCDC} | XAL4040-103 | $10 \mu\text{H}$ | Coilcraft |
| C_{DCDC} | GRM32ER71H475KA88L | $4.7 \mu\text{F}$ | Murata |
| D_{DCDC} | PMEG3010BEA | 0.38 V_f | NXP |

DC-to-DC Converter Operation

The on-board dc-to-dc converters use a constant frequency, peak current mode control scheme to step up an AV_{CC} input of 4.5 V to 5.5 V to drive the AD5755 output channel. These are designed to operate in discontinuous conduction mode (DCM) with a duty cycle of $<90\%$ typical.

Discontinuous conduction mode refers to a mode of operation where the inductor current goes to zero for an appreciable percentage of the switching cycle. The dc-to-dc converters are nonsynchronous; that is, they require an external Schottky diode.

DC-to-DC Converter Output Voltage

When a channel current output is enabled, the converter regulates the V_{BOOST_X} supply to 7.4 V ($\pm 5\%$) or $(I_{\text{OUT}_X} \times R_{\text{LOAD}} + \text{Headroom})$, whichever is greater. The value of the headroom voltage is approximately 3 V. In the voltage output mode with the output disabled, the converter regulates the V_{BOOST_X} supply to $+15 \text{ V}$ ($\pm 5\%$). In current output mode with the output disabled, the converter regulates the V_{BOOST_X} supply to 7.4 V ($\pm 5\%$).

Within a channel, the V_{OUT_X} and I_{OUT_X} stages share a common V_{BOOST_X} supply so that the outputs of the I_{OUT_X} and V_{OUT_X} stages can be tied together.

DC-to-DC Converter Settling Time

When in current output mode, the settling time for a step greater than approximately 1 V ($I_{OUT} \times R_{LOAD}$) is dominated by the settling time of the dc-to-dc converter. The exception to this is when the required voltage at the I_{OUT_X} pin plus the compliance voltage is below 7.4 V ($\pm 5\%$). The settling time for smaller loads is faster. The settling time for current steps less than 24 mA is also faster.

DC-to-DC Converter V_{MAX} Functionality

The maximum V_{BOOST_X} voltage is set in the dc-to-dc control register. On reaching this maximum voltage, the dc-to-dc converter is disabled, and the V_{BOOST_X} voltage is allowed to decay by approximately 0.4 V. After the V_{BOOST_X} voltage has decayed, the dc-to-dc converter is reenabled, and the voltage ramps up again to V_{MAX} , if still required.

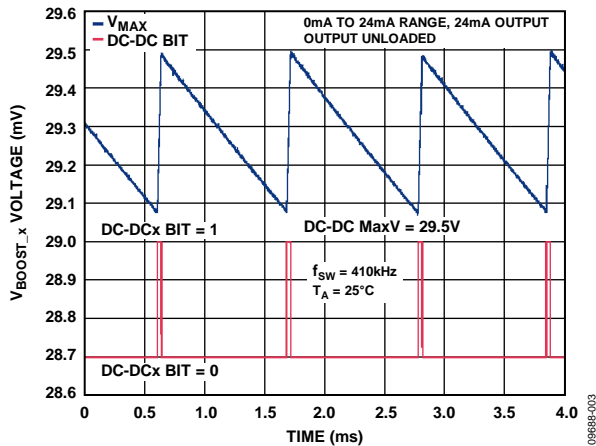


Figure 3. V_{MAX} Operation

As seen in Figure 3, the DC-DCx bit in the status register asserts when the AD5755 is ramping to the V_{MAX} value and deasserts when the voltage is decaying to $V_{MAX} - 0.4$ V.

AV_{CC} Supply Static Current Requirements

The dc-to-dc converter is designed to supply a V_{BOOST_X} voltage of

$$V_{BOOST} = I_{OUT} \times R_{LOAD} + \text{Headroom}$$

This means that, for a fixed load and output voltage, the dc-to-dc converter output current can be calculated by

$$AI_{CC} = \frac{\text{Power Out}}{\text{Efficiency} \times AV_{CC}} = \frac{I_{OUT} \times V_{BOOST}}{\eta_{V_{BOOST}} \times AV_{CC}}$$

where:

I_{OUT} is the output current from I_{OUT_X} in amps.

$\eta_{V_{BOOST}}$ is the efficiency at V_{BOOST_X} as a fraction.

AV_{CC} Supply Slewing Current Requirements-

The AI_{CC} current requirement while slewing is greater than in static operation because the output power increases to charge the output capacitance of the dc-to-dc converter. If not enough AI_{CC} current is provided, the AV_{CC} voltage drops. Due to this AV_{CC} drop, the AI_{CC} current required to slew increases further. This means that the voltage at AV_{CC} drops further, and the V_{BOOST_X} voltage, and thus the output voltage, may never reach its intended value. Because this AV_{CC} voltage is common to all channels, this may also affect other channels.

ADP2300 AV_{CC} Supply

The ADP2300 and several discrete components are used to create a simple 5 V rail that meets the supply current demands of the AD5755 as previously described. The output voltage is set externally by a resistive voltage divider from the output voltage to the FB pin, as show in Figure 4.

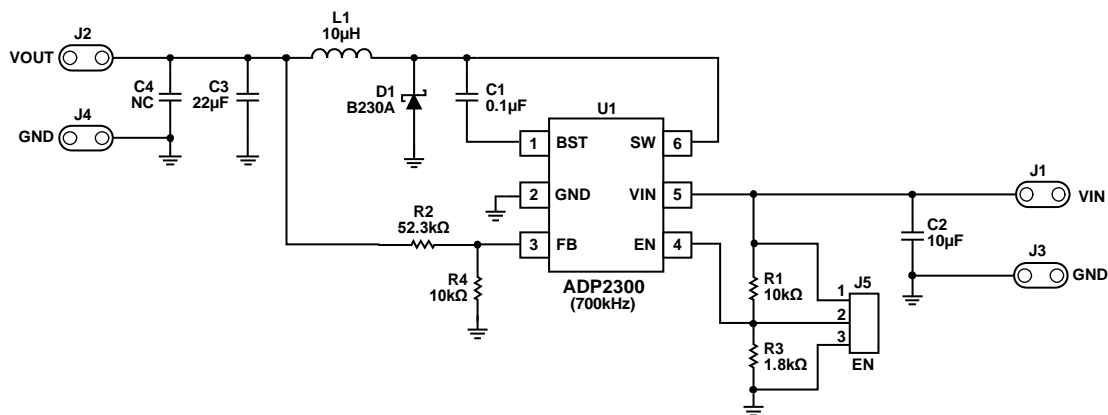


Figure 4. ADP2300 Typical Application (ADP2300 Evaluation Board)

Test Data and Results

All test data was gathered using the [EVAL-AD5755SDZ](#), [EVAL-SDP-CB1Z](#), and [ADP2300-EVALZ](#) boards. The integral nonlinearity (INL), differential nonlinearity (DNL), and total unadjusted error (TUE) of the system using the [ADP2300](#) circuit is shown in Figure 5, Figure 6, and Figure 7, respectively. The [AD5755](#) boost regulators were active for all the measurements.

Complete documentation for the system can be found in the [CN0198 Design Support](#) package.

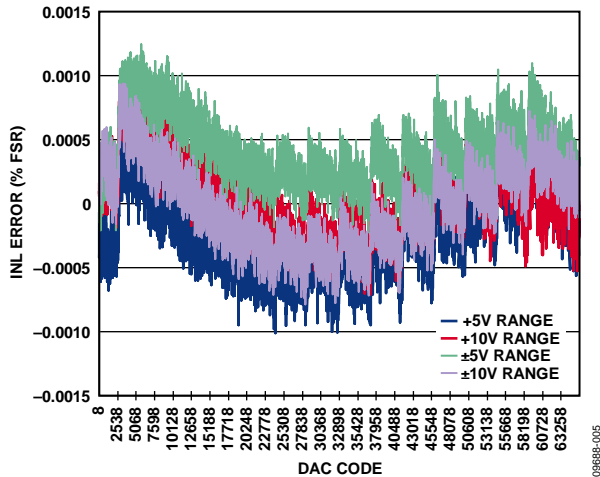


Figure 5. INL for Voltage Outputs

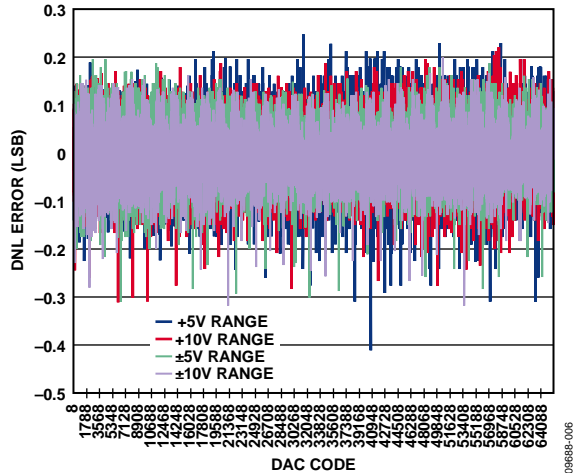


Figure 6. DNL for Voltage Outputs

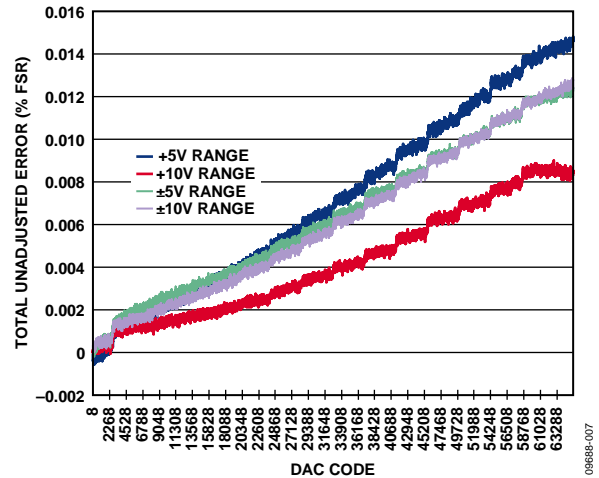


Figure 7. TUE for Voltage Outputs

COMMON VARIATIONS

The [AD5755-1](#) is similar to the [AD5755](#); however, it has HART connectivity. Each channel has a corresponding CHARTx pin so that HART signals can be coupled onto the current outputs of the [AD5755-1](#).

CIRCUIT EVALUATION AND TEST

This circuit uses the [EVAL-AD5755SDZ](#) circuit board and the [EVAL-SDP-CB1Z](#) System Demonstration Platform (SDP) evaluation board. The two boards have 120-pin mating connectors, allowing for the quick setup and evaluation of the performance of the circuit.

The [EVAL-AD5755SDZ](#) circuit board contains the circuit to be evaluated, and the SDP evaluation board is used with the [AD5755 Evaluation Software](#) to capture data.

Equipment Needed

The following equipment is needed:

- A PC with a USB port and Windows® XP, Windows Vista® (32-bit), or Windows 7 (32-bit)
- The [EVAL-AD5755SDZ](#) circuit board
- The [EVAL-SDP-CB1Z](#) SDP evaluation board
- The [ADP2300-EVALZ](#) evaluation board
- The [AD5755 Evaluation Software](#)
- A power supply: ±15 V
- A digital multimeter (that is, Agilent 34401A)
- A GPIB-to-USB cable (only required for capturing analog data from the DAC and transferring it to the PC).

Getting Started

Load the evaluation software by placing the [AD5755 Evaluation Software](#) CD into the PC. Using **My Computer**, locate the drive that contains the evaluation software CD and open the **Readme** file. Follow the instructions contained in the **Readme** file for installing and using the evaluation software.

Functional Block Diagram

Figure 8 shows the test setup block diagram, and the **EVAL-CN0198-SDPZ-SCH-RevX.pdf** file has the circuit schematics. This file is contained in the [CN0198 Design Support Package](#).

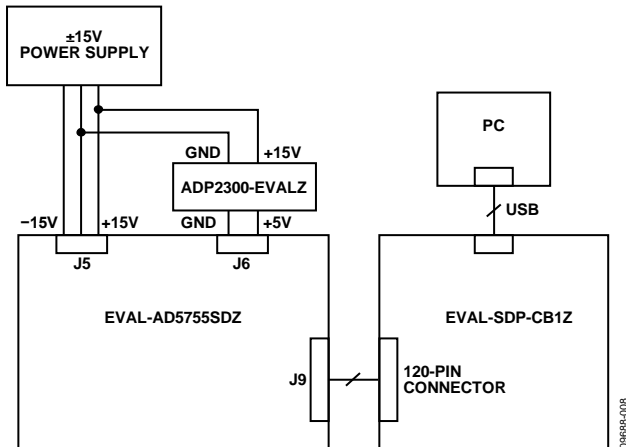


Figure 8. Photo Test Setup Block Diagram

Setup

Connect the 120-pin connector on the [EVAL-AD5755SDZ](#) to the **CON A** connector on the [EVAL-SDP-CB1Z](#). Used nylon hardware to firmly secure the two boards, using the holes provided at the ends of the 120-pin connectors.

With power to the supply off, do the following:

- Connect a ± 15 V power supply to J5 terminal block on the [EVAL-AD5755SDZ](#).
- Connect a 15 V power supply to the inputs of the [ADP2300-EVALZ](#).
- Connect the output pins to the J6 connector of the [EVAL-AD5755SDZ](#).
- Connect a ± 15 V power supply to the J5 connector on the [EVAL-AD5755SDZ](#).
- Connect the USB cable supplied with the SDP board to the USB port on the PC. Note: Do not connect the USB cable to the mini-USB connector on the SDP board at this time.

Test

Apply power to the [ADP2300-EVALZ](#) and the [EVAL-AD5755SDZ](#) supplies.

Connect the USB cable from the PC to the mini-USB connector on the SDP board and launch the evaluation software.

Once USB communications are established, the SDP board can be used to send and receive data from the [EVAL-AD5755SDZ](#).

Information regarding the [EVAL-SDP-CB1Z](#) can be found in the [SDP User Guide](#).

Information and details regarding test setup and how to use the evaluation software for data capture can be found in the [CN-0198 User Guide](#).

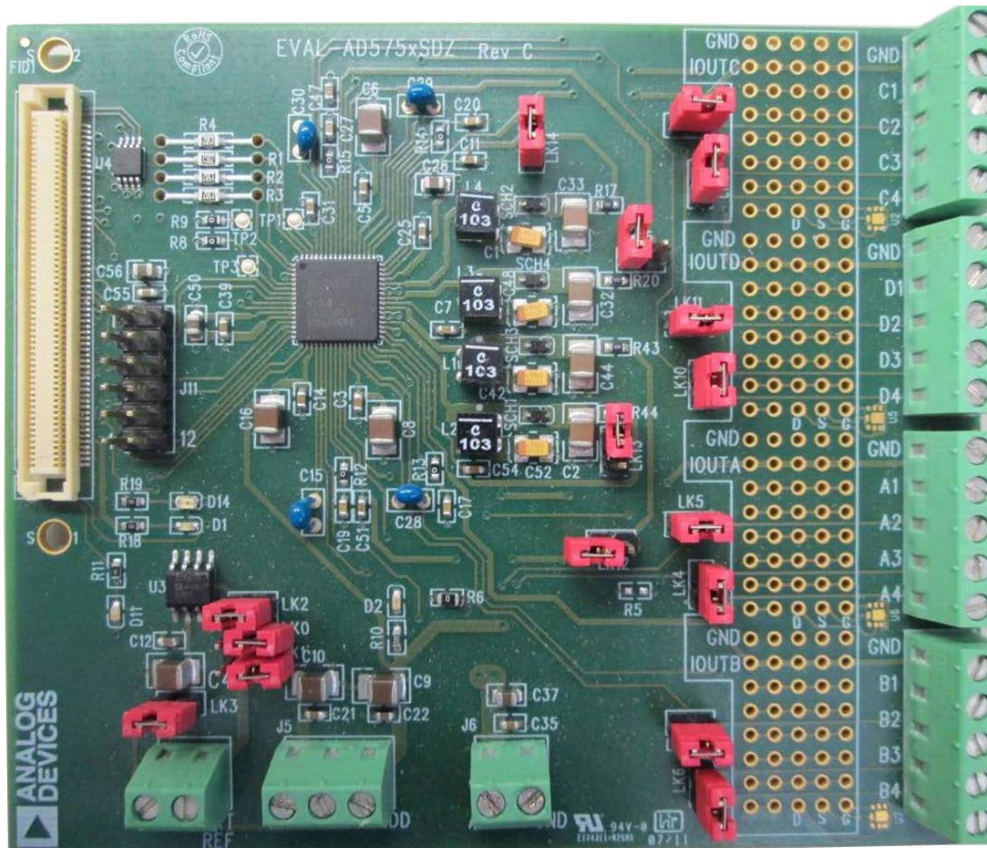


Figure 9. Photo of the EVAL-AD5755SDZ Board

LEARN MORE

CN0198 Design Support Package:

<http://www.analog.com/CN0198-DesignSupport>.

UG-244 (EVAL-AD5755SDZ Evaluation Board User Guide).

Evaluation Board for a Quad-Channel, 16-Bit, Serial Input, 4 mA to 20 mA, Voltage Output DAC with Dynamic Power Control and HART Connectivity. Analog Devices, Inc., 2011.

UG-179 (ADP2300-EVALZ Evaluation Board User Guide).

Evaluation Board for the 1.2 A, 20 V Nonsynchronous Step-Down Regulators. Analog Devices, 2010.

ADIsimPower

MT-031 Tutorial, *Grounding Data Converters and Solving the Mystery of "AGND" and "DGND"*, Analog Devices.

MT-101 Tutorial, *Decoupling Techniques*, Analog Devices.

Data Sheets and Evaluation Boards

[AD5755 Data Sheet](#)

[AD5755 Evaluation Board](#)

[ADP2300 Data Sheet](#)

[ADP2300 Evaluation Board](#)

REVISION HISTORY

12/12—Revision 0: Initial Version

(Continued from first page) Circuits from the Lab circuits are intended only for use with Analog Devices products and are the intellectual property of Analog Devices or its licensors. While you may use the Circuits from the Lab circuits in the design of your product, no other license is granted by implication or otherwise under any patents or other intellectual property by application or use of the Circuits from the Lab circuits. Information furnished by Analog Devices is believed to be accurate and reliable. However, Circuits from the Lab circuits are supplied "as is" and without warranties of any kind, express, implied, or statutory including, but not limited to, any implied warranty of merchantability, noninfringement or fitness for a particular purpose and no responsibility is assumed by Analog Devices for their use, nor for any infringements of patents or other rights of third parties that may result from their use. Analog Devices reserves the right to change any Circuits from the Lab circuits at any time without notice but is under no obligation to do so.

©2012 Analog Devices, Inc. All rights reserved. Trademarks and registered trademarks are the property of their respective owners.
CN09688-0-12/12(0)

