

Devices Connected/Referenced

ADAU1761	SigmaDSP® Stereo, Low Power, 96 kHz, 24-Bit Audio Codec with Integrated PLL
ADAV801/ADAV803	Audio Codec for Recordable DVD (SPI/I ² C Control Interface)

S/PDIF and I²S Interface for a SigmaDSP Codec Using the [ADAV801/ADAV803](#) Audio Codec

EVALUATION AND DESIGN SUPPORT

Circuit Evaluation Boards

[ADAU1761 Evaluation Board \(EVAL-ADAU1761Z\)](#)

[USBi USB Interface Board \(EVAL-ADUSB2EBZ\)](#)

(Included with [EVAL-ADAU1761Z Board](#))

[ADAV801 Evaluation Board \(EVAL-ADAV801EBZ\)](#) or

[ADAV803 Evaluation Board \(EVAL-ADAV803EBZ\)](#)

Design and Integration Files

[Schematics, Layout Files, Bill of Materials](#)

CIRCUIT FUNCTION AND BENEFITS

S/PDIF (Sony/Philips Digital Interface) is a high quality digital audio format that is commonly used in consumer electronics and is used to interconnect audio equipment. Many audio codecs/DSPs only support I²S as digital audio input/output, which is a problem when using these parts in circuits that need to support both S/PDIF or the AES (Audio Engineering Society) professional standard.

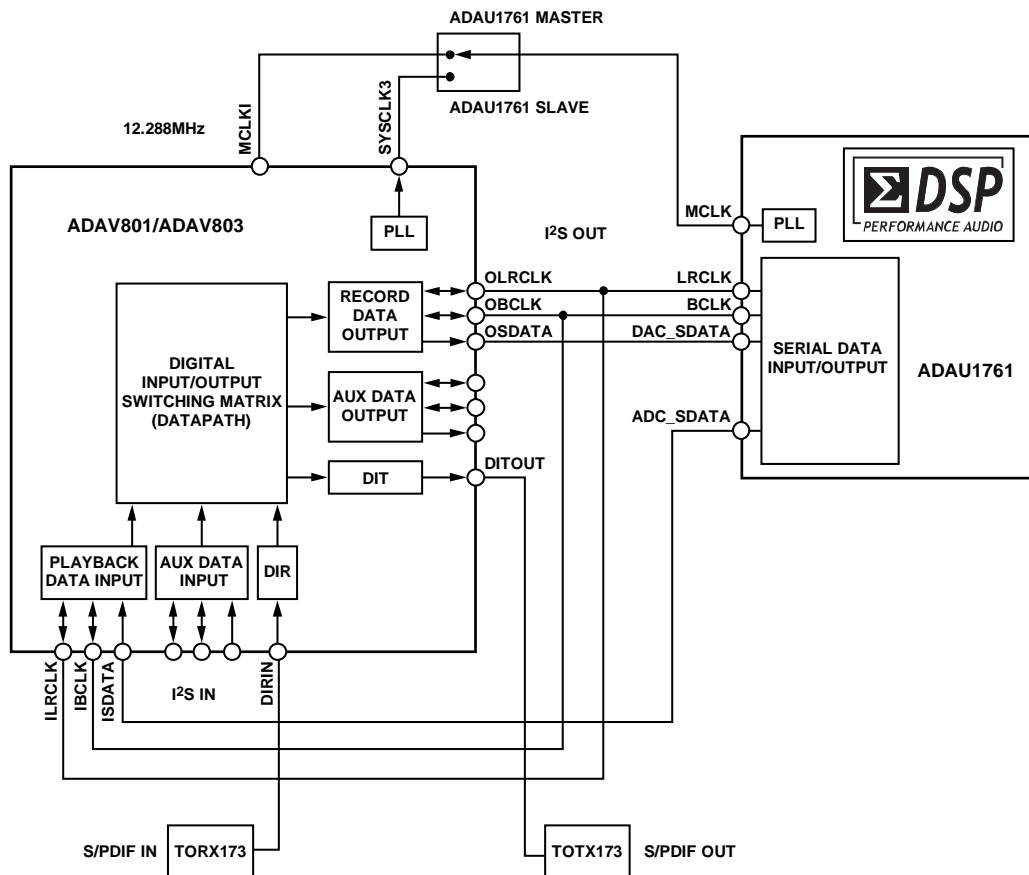


Figure 1. [ADAV801/ADAV803](#) Connections for S/PDIF In/Out to ADAU1761 SigmaDSP (Simplified Schematic: Power Supply Decoupling and All Connections Not Shown)

Rev.0

Circuits from the Lab™ circuits from Analog Devices have been designed and built by Analog Devices engineers. Standard engineering practices have been employed in the design and construction of each circuit, and their function and performance have been tested and verified in a lab environment at room temperature. However, you are solely responsible for testing the circuit and determining its suitability and applicability for your use and application. Accordingly, in no event shall Analog Devices be liable for direct, indirect, special, incidental, consequential or punitive damages due to any cause whatsoever connected to the use of any Circuits from the Lab circuits. (Continued on last page)

The circuit, in Figure 1, shows how to overcome this problem by connecting the [ADAV801](#) or the [ADAV803](#) audio codec to a SigmaDSP® device, such as the [ADAU1761](#).

The audio input in S/PDIF format is converted to I²S before processing by the [ADAV1761](#), and the processed audio output in I²S format is converted back to S/PDIF by the [ADAV801/ADAV803](#). The [ADAV801/ADAV803](#) has a flexible digital input/output routing matrix that allows it to process audio in either I²S or S/PDIF format and output it in either format as a master or slave with the use of an onboard SRC (sample rate converter). The [ADAV801/ADAV803](#) support the consumer audio standard, and channel status data can be embedded in the audio stream by writing to the relevant registers in the [ADAV801/ADAV803](#). This is a useful feature for passing configuration information between devices. The [ADAV801/ADAV803](#) has a stereo DAC/ADC that can also be used to process audio as needed.

CIRCUIT DESCRIPTION

The [ADAV801/ADAV803](#) has two sets of input/output I²S ports, either of which can be used. In the configuration shown in Figure 1, the playback port ILRCLK and record port OLRCLK pins are connected to the LRCLK pin of the [ADAU1761](#). The IBCLK and OBCLK pins are connected to the BCLK pin of the [ADAU1761](#). The ISDATA pin is connected to the ADC_SDATA pin of the [ADAU1761](#), and the OSDATA is connected to the DAC_SDATA pin of the [ADAU1761](#).

The S/PDIF input comes from the TORX173 fiber optic receiver module into the DIRIN pin and is then output to the [ADAU1761](#) on the record port in I²S format. Once the audio is processed by the [ADAU1761](#) SigmaDSP® device it is output on the ADC_SDATA pin to the playback port of the [ADAV801/ADAV803](#) in I²S format. It is then converted to S/PDIF format on the DITOUT pin and fed to the TOTX173 fiber optical transmitter module.

The circuit is powered from a 3.3 V AVDD supply. The master clock for the circuit is generated either by the [ADAV801/ADAV803](#) or by an external oscillator, depending on whether the [ADAU1761](#) is to be configured as master or slave. In the case where the [ADAU1761](#) is a slave, i.e. the BCLK and LRCLK are driven by the [ADAV801/ADAV803](#), the MCLK is 256× the recovered audio clock from the S/PDIF stream. It can also be configured to be 512× the recovered clock. This clock is accessed on the SYSCLK3 pin of the [ADAV801/ADAV803](#) and connected to the MCLK pin of the [ADAU1761](#).

When the [ADAU1761](#) is master, the MCLK is generated by an onboard oscillator and is supplied to the [ADAV801/ADAV803](#) on the MCLKI pin. In this case, the [ADAU1761](#) drives the LRCLK and BCLK lines, and the SRC on the [ADAV801/](#)

[ADAV803](#) is used to synchronize the audio between the I²S port and the S/PDIF port.

Register Settings

A complete design support documentation package for this circuit note can be found at www.analog.com/CN0219-DesignSupport. This includes register setting files for both master and slave configuration for the [ADAV801/ADAV803](#) and [ADAU1761](#). These register settings files can be loaded using the relevant evaluation board software.

COMMON VARIATIONS

This circuit can also be set up with any part that has a SigmaDSP processor core and requires an S/PDIF/AES audio interface, including the [ADAU1401A](#), [ADAU1701](#), and [ADAU1781](#). Although not described in this circuit note, the above circuit can be modified to work with the AES audio format. Instead of optical connectors, XLR connectors would be used, and transformers would be required to convert from differential to single-ended signals and vice versa.

CIRCUIT EVALUATION AND TEST

This circuit is tested using the [ADAV801/ADAV803](#) ([EVAL-ADAV801EBZ](#) or [EVAL-ADAV803EBZ](#)) and [ADAU1761](#) ([EVAL-ADAU1761Z](#)) evaluation boards. The necessary connections between the two boards and link configurations are contained in [the design support documentation](#). Figure 2 shows the full test setup using both evaluation boards.

Equipment Needed

The [ADAU1761](#) evaluation board is programmed using SigmaStudio thru a USBI board ([EVAL-ADUSB2EBZ](#)). The SigmaStudio GUI software requires a PC with the following: Windows® 7, Windows Vista, or Windows XP Professional or Home Edition with SP2, 128 MB of RAM (256 MB recommended), 50 MB of available hard disk space, 1024 × 768 screen resolution, and USB 1.1/2.0 data port. The [ADAV801/ADAV803](#) board is controlled using the printer port of a PC with its own software that can be downloaded from the ADI website. Two optical connectors are needed to connect the S/PDIF input/output to the [ADAV801/ADAV803](#) board. Eight single pin jumper cables are needed to make the necessary connections between the two evaluation boards.

Getting Started

From this point, follow the documentation for the [EVAL-ADAU1761Z](#) and [EVAL-ADAV801/ADAV803EBZ](#) regarding software installation, setup, and operation of the system.

The SigmaStudio software is used to program and tune the registers and SigmaDSP core in the **ADAU1761**. SigmaStudio can be downloaded from www.analog.com/sigmastudio. The software for the **ADAV801/ADAV803** can also be downloaded from the ADI website. Once the software is

installed, the register setting files in the design documentation can be loaded to program both boards depending on whether you want the **ADAU1761** device to be master or slave. The **ADAU1761** SigmaStudio project has just a simple audio pass-thru with volume control for the purposes of testing the circuit of Figure 1.

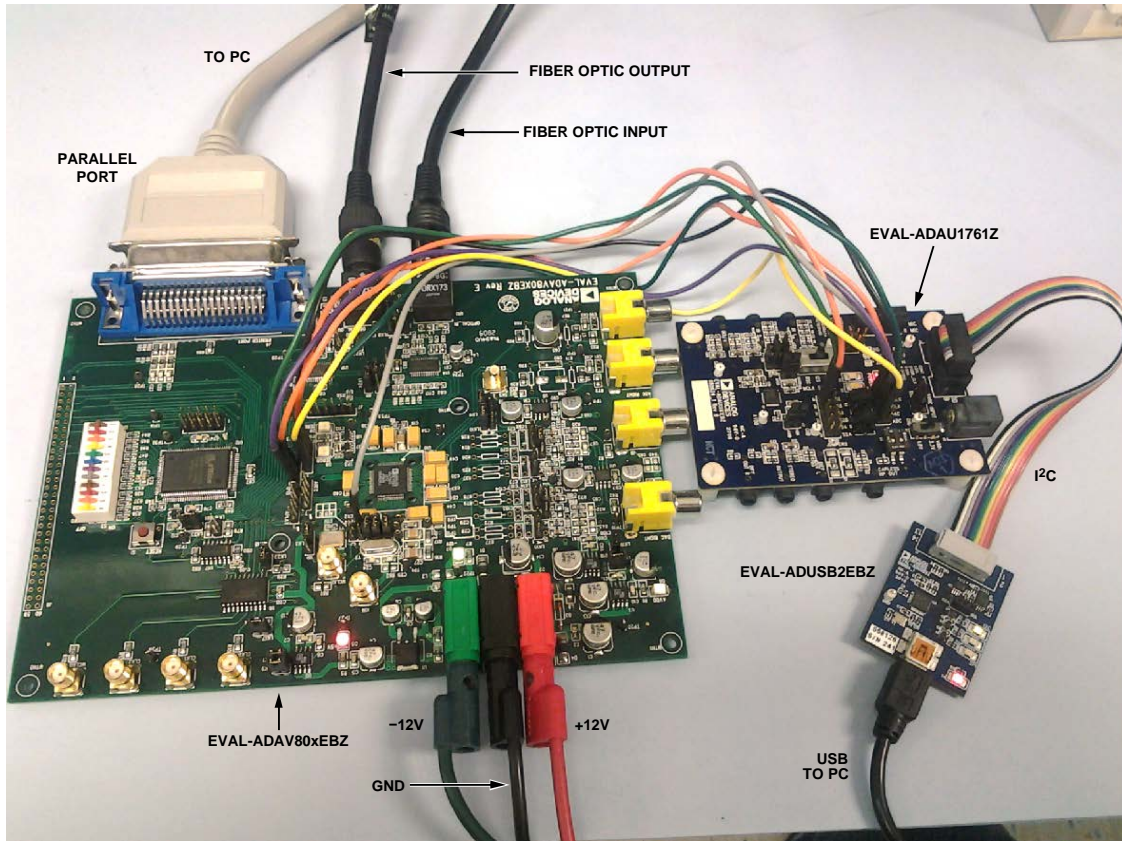


Figure 2. Test Setup for Connecting the **ADAV801/ADAV803** Board to the **ADAU1761** Board

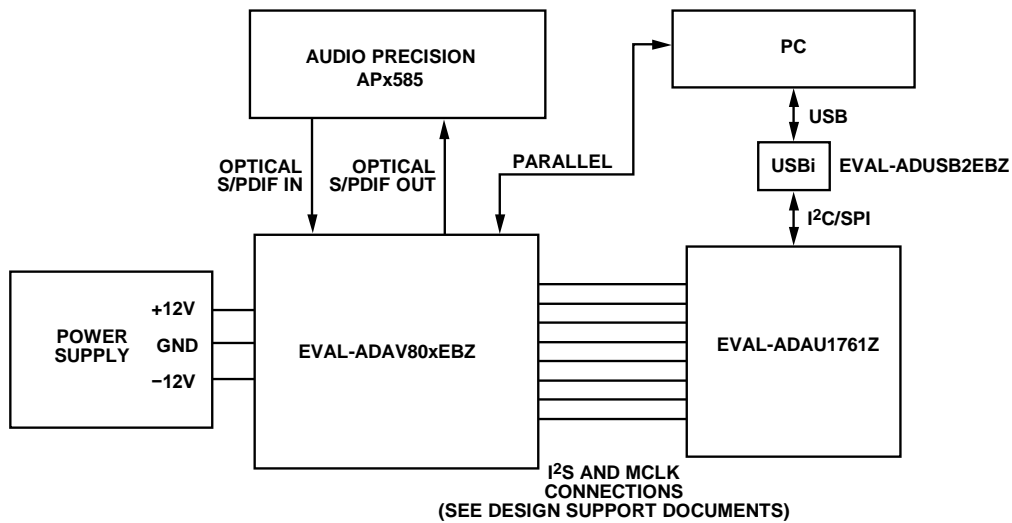


Figure 3. Functional Diagram of Test Setup

Setup and Test

An Audio Precision APx585 multichannel audio analyzer can be used to generate the S/PDIF input and capture the S/PDIF output. With the [ADAU1761](#) as master and a full-scale 1 kHz input tone, the THD + N should be ~130 dB at the S/PDIF output. In slave mode, the THD + N should be ~142 dB, since there is no SRC needed to synchronize the S/PDIF stream to the [ADAU1761](#) I²S stream.

LEARN MORE

CN0219 Design Support Package:

www.analog.com/CN0219-DesignSupport

Gildersleeve, Brett, *Using the EVAL-ADUSB2EBZ*, Application Note AN-1006, Analog Devices.

SigmaStudio™ Graphical Development Tool:

www.analog.com/sigmastudio

Data Sheets and Evaluation Boards

[ADAU1761 Data Sheet](#)

[ADAU1761 Evaluation Board](#)

[ADAV801 Data Sheet](#)

[ADAV803 Data Sheet](#)

[ADAV801/ADAV803 Evaluation Board and Software](#)

REVISION HISTORY

10/11—Revision 0: Initial Version

(Continued from first page) Circuits from the Lab circuits are intended only for use with Analog Devices products and are the intellectual property of Analog Devices or its licensors. While you may use the Circuits from the Lab circuits in the design of your product, no other license is granted by implication or otherwise under any patents or other intellectual property by application or use of the Circuits from the Lab circuits. Information furnished by Analog Devices is believed to be accurate and reliable. However, "Circuits from the Lab" are supplied "as is" and without warranties of any kind, express, implied, or statutory including, but not limited to, any implied warranty of merchantability, noninfringement or fitness for a particular purpose and no responsibility is assumed by Analog Devices for their use, nor for any infringements of patents or other rights of third parties that may result from their use. Analog Devices reserves the right to change any Circuits from the Lab circuits at any time without notice but is under no obligation to do so.

©2011 Analog Devices, Inc. All rights reserved. Trademarks and registered trademarks are the property of their respective owners.
CN09970-0-10/11(0)



www.analog.com