

**Circuits from the Lab<sup>®</sup>**  
Reference Designs

*Circuits from the Lab<sup>®</sup> reference designs are engineered and tested for quick and easy system integration to help solve today's analog, mixed-signal, and RF design challenges. For more information and/or support, visit [www.analog.com/CN0237](http://www.analog.com/CN0237).*

### Devices Connected/Referenced

<a href="#">ADA4940-1/ADA4940-2</a>	Single/Dual, Ultralow Power, Low Distortion Differential ADC Driver
<a href="#">AD7982</a>	18-Bit, 1 MSPS PulSAR ADC
<a href="#">ADR435</a>	Ultralow Noise XFET Voltage Reference with Current Sink and Source Capability

## Ultralow Power, 18-Bit, Differential PulSAR ADC Driver

### EVALUATION AND DESIGN SUPPORT

#### Design and Integration Files

[Schematics](#), [Layout Files](#), [Bill of Materials](#)

### CIRCUIT FUNCTION AND BENEFITS

The circuit shown in Figure 1 uses the ultralow power [AD7982](#) 18-bit, 1 MSPS analog-to-digital converter (ADC) driven by the [ADA4940-1](#), a low power fully differential amplifier. The [ADR435](#) low noise precision 5.0 V voltage reference is used to supply the 5 V needed for the ADC. All the ICs shown in Figure 1 are available in small packages, either 3 mm × 3 mm LFCSP or 3 mm × 5 mm MSOP, which helps to reduce board cost and space.

Power dissipation of the [ADA4940-1](#) in the circuit is typically 6.25 mW. The 18-bit, 1 MSPS [AD7982](#) ADC consumes only 7 mW at 1 MSPS. This power also scales with the throughput. The [ADR435](#) consumes only 4.7 mW, making the total power dissipated by the system less than 18 mW.

### CIRCUIT DESCRIPTION

Modern high resolution SAR ADCs, such as the [AD7982](#) 18-bit, 1 MSPS PulSAR<sup>®</sup> ADC, require a differential driver for optimum performance. In such applications, the ADC driver takes either a differential or single-ended signal and performs the level shifting required to drive the input of the ADC at the right level.

Figure 1 shows the [ADA4940-1](#) differential amplifier level shifting and driving the 18-bit [AD7982](#) differential input successive approximation PulSAR ADC. Using four resistors, the [ADA4940-1](#) can either buffer the signal with a gain of 1 or amplify the signal for more dynamic range. The ac and dc performances are compatible with those of the [AD7982](#) 18-bit, 1 MSPS PulSAR<sup>®</sup> ADC and other 16-bit and 18-bit members of the family, which have sampling rates of up to 2 MSPS. This circuit can also accept a single-ended input signal to generate the same fully differential output signal.

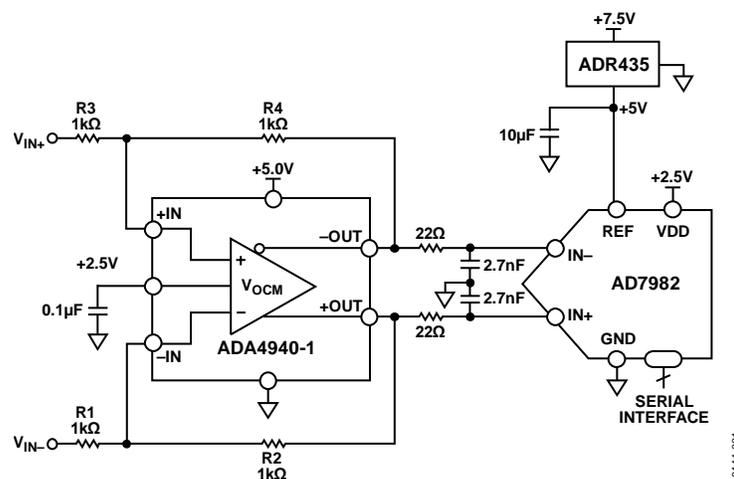


Figure 1. High Performance 18-Bit Differential ADC Driver (Simplified Schematic: All Connections and Decoupling Not Shown)

#### Rev. A

Circuits from the Lab reference designs from Analog Devices have been designed and built by Analog Devices engineers. Standard engineering practices have been employed in the design and construction of each circuit, and their function and performance have been tested and verified in a lab environment at room temperature. However, you are solely responsible for testing the circuit and determining its suitability and applicability for your use and application. Accordingly, in no event shall Analog Devices be liable for direct, indirect, special, incidental, consequential or punitive damages due to any cause whatsoever connected to the use of any Circuits from the Lab circuits. (Continued on last page)

The AD7982 operates on a single VDD supply of 2.5 V. It contains a low power, high speed, 18-bit sampling ADC and a versatile serial interface port. The reference voltage (REF) is applied externally from the ADR435 precision low dropout (0.3 V) band gap reference, and can be set independently of the supply voltage.

The ADA4940-1 operates from a 5 V single supply and offers sufficient headroom on the outputs, which swing from 0 V to 5 V with a 2.5 V common-mode and accommodate a full-scale input to the ADC. The ADA4940-1 is dc-coupled on the input and the output, and its outputs drive the inputs of the AD7982. It also allows single-ended to differential conversion if needed.

The gain is set by the ratio of the feedback resistor ( $R_2 = R_4$ ) to the gain resistor ( $R_1 = R_3$ ). For  $R_1 = R_2 = R_3 = R_4 = 1\text{ k}\Omega$ , the single-ended input impedance is approximately 1.33 k $\Omega$ . In addition, the circuit can be used to convert either single-ended or differential inputs to a differential output. If needed, a termination resistor in parallel with the input can be used. Whether the input is a single-ended input or differential input, the input impedance of the amplifier can be calculated as shown in the MT-076 Tutorial and in the DiffAmpCalc™ Differential Amplifier Calculator ([www.analog.com/DiffAmpCalc](http://www.analog.com/DiffAmpCalc)).

A single-pole, 2.7 MHz, RC (22  $\Omega$ , 2.7 nF) noise filter is placed between the op amp output and the ADC input to help limit the noise at the ADC input and to reduce the effect of kickbacks coming from the capacitive DAC input of the SAR ADC.

For the tests on this circuit, the signal generator provided a 10 V p-p differential output. The  $V_{OCM}$  input is bypassed for noise reduction and set externally with 1% resistors to maximize the output dynamic range on the 5 V reference. With an output common-mode voltage of 2.5 V, each ADA4940-1 output swings between 0 V and 5 V, opposite in phase, providing a gain of 1 and a 10 V p-p differential signal to the ADC input.

The FFT performance is shown in Figure 3 and is summarized as follows:

- Dynamic range = 97.33 dB
- SNR = 96.67 dBFS
- SINAD = 96.52 dBFS
- THD = -111.03 dBFS

Figure 2 shows the typical INL and DNL performance of the AD7982.

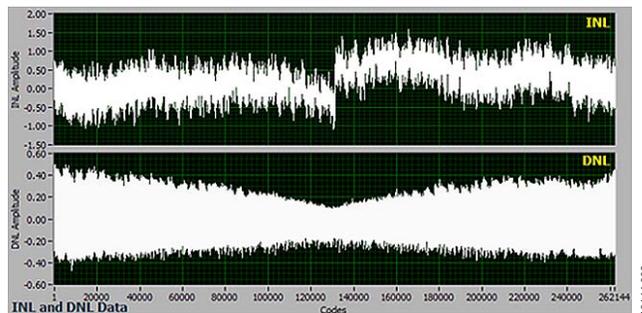


Figure 2. INL and DNL Plot for 20 kHz Signal, with Sampling Frequency of 1 MSPS (Min/Max INL = +1.6 LSB/-1.1 LSB and DNL =  $\pm 0.5$  LSB)

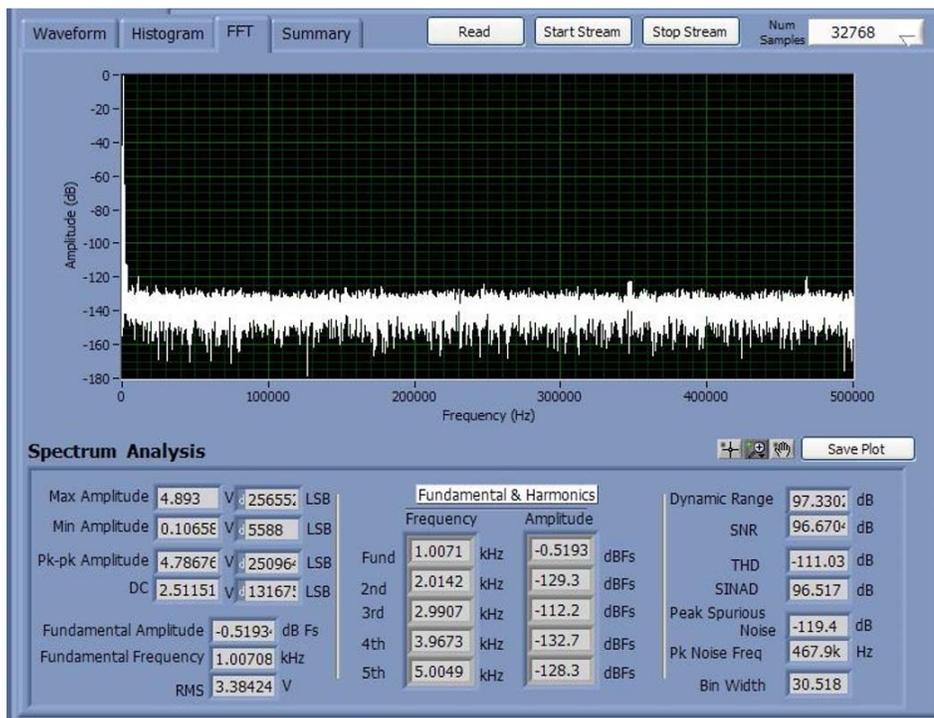


Figure 3. FFT Plot for 1 kHz Signal, 0.5 dB Below Full Scale, with Sampling Frequency of 1 MSPS

## COMMON VARIATIONS

The circuit is proven to work with good stability and accuracy with the component values shown. Other ADCs can be used in place of the [AD7982](#) to achieve the maximum desired performance. The [ADA4940-1/ADA4940-2](#) are optimal for driving 16-bit and 18-bit ADCs with minimal degradation in performance. Faster sampling 18-bit ADCs include the [AD7984](#) (1.33 MSPS) and [AD7986](#) (2 MSPS). Differential 16-bit ADCs include the [AD7688](#) (500 kSPS) and the [AD7693](#) (500 kSPS).

The [ADA4940-1/ADA4940-2](#) rail-to-rail outputs can be driven to within 0.5 V of each power rail without significant ac performance degradation. Other differential ADC drivers such as the [AD8137](#) and [ADA4941-1](#) can also be used to replace the [ADA4940-1](#) for applications when speed, input impedance, or other factors dictate.

## CIRCUIT EVALUATION AND TEST

This circuit was tested using a [EVAL-AD7982SDZ](#) PulSAR [AD7982](#) evaluation board connected to the [EVAL-SDP-CB1Z](#) system demonstration platform.

The [EVAL-AD7982SDZ](#) is a user evaluation board intended to ease standalone testing of performance and functionality for the 18-bit [AD7982](#) PulSAR ADC.

The [EVAL-SDP-CB1Z](#) board is a platform intended for use in evaluation, demonstration, and development of systems using Analog Devices, Inc. precision converters. It provides the necessary communications between the converter and the PC, programming or controlling the device, transmitting or receiving data over a USB link as shown in Figure 4 and Figure 5.

## Equipment Needed

In addition to the two evaluation boards, external 5 V power supplies are required for the [ADA4940-1](#). A wall wart supplies the 9 V dc voltage for the [EVAL-SDP-CB1Z](#). Other appropriate voltages are supplied to the [AD7982](#) evaluation board from the [EVAL-SDP-CB1Z](#).

A low distortion signal source, the Audio Precision® SYS-2702, was used to achieve the required performance. A PC with Windows® XP or Windows 7 equipped with an USB port was used to run the PulSAR evaluation software.

## Getting Started

Install the evaluation software as described at the [EVAL-SDP-CB1Z](#) and [EVAL-AD7982SDZ](#) product pages.

Connect the [ADA49xx-1 EVAL-BRDZ](#), [EVAL-AD7982SDZ](#), and [EVAL-SDP-CB1Z](#) boards together as shown in Figure 5. Connect a 9 V wall wart to the [EVAL-AD7982SDZ](#), connect the USB cable to [EVAL-SDP-CB1Z](#), and connect the external 5 V power supply to the [ADA49xx-1 EVAL-BRDZ](#).

For more information on differential amplifier evaluation boards like the [ADA49xx-1 EVAL-BRDZ](#), see the [UG-132](#).

## Setup and Test

An Audio Precision SYS-2702 source was used to provide the input signal to the [EVAL-AD7982SDZ](#). The PulSAR evaluation software was used to monitor the ADC output results.

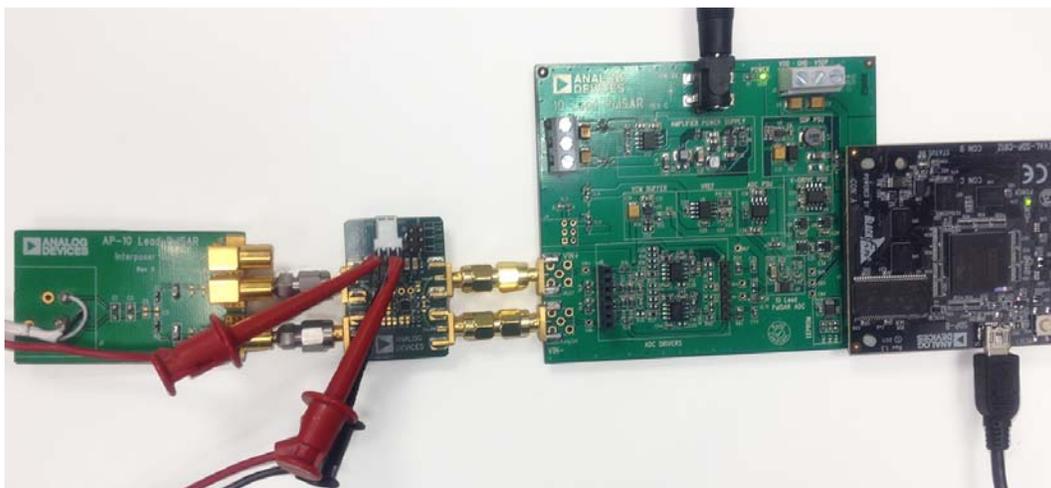


Figure 4. PulsAR ADC Evaluation Platform

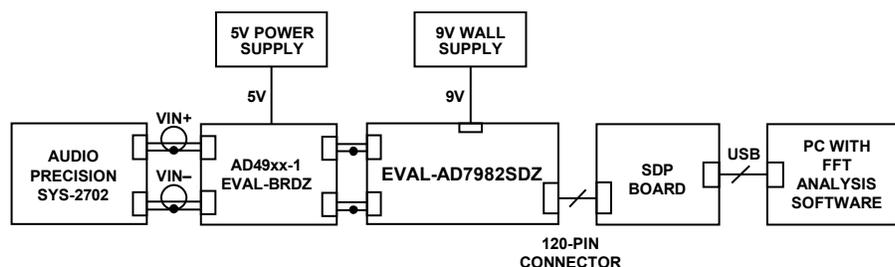


Figure 5. Test Setup Functional Block Diagram

**LEARN MORE**

CN-0237 Design Support Package:

[www.analog.com/CN0237-DesignSupport](http://www.analog.com/CN0237-DesignSupport)

DiffAmpCalc™ Differential Amplifier Calculator

Ardizzoni, John. *A Practical Guide to High-Speed Printed-Circuit-Board Layout*, Analog Dialogue 39-09, September 2005.

MT-031 Tutorial. *Grounding Data Converters and Solving the Mystery of “AGND” and “DGND”*. Analog Devices.

MT-074 Tutorial. *Differential Drivers for Precision ADCs*. Analog Devices.

MT-075 Tutorial. *Differential Drivers for High Speed ADCs Overview*. Analog Devices.

MT-076 Tutorial. *Differential Driver Analysis*. Analog Devices.

MT-101 Tutorial. *Decoupling Techniques*. Analog Devices.

**Data Sheets and Evaluation Boards**

[ADA4940-1 Data Sheet](#)

[ADA4940-2 Data Sheet](#)

[ADA4940 Evaluation Board](#)

[AD7982 Data Sheet](#)

[AD7982 Evaluation Board](#)

[ADR435 Data Sheet](#)

**REVISION HISTORY****2/15—Rev. 0 to Rev. A**

Reorganized Layout.....	Universal
Changes to Circuit Function and Benefits Section and Figure 1 .....	1
Changes to Circuit Description Section, Figure 2, and Figure 3 .....	2
Changes to Circuit Evaluation and Test Section, Figure 4, and Figure 5 .....	3

**10/11—Revision 0: Initial Version**

(Continued from first page) Circuits from the Lab reference designs are intended only for use with Analog Devices products and are the intellectual property of Analog Devices or its licensors. While you may use the Circuits from the Lab reference designs in the design of your product, no other license is granted by implication or otherwise under any patents or other intellectual property by application or use of the Circuits from the Lab reference designs. Information furnished by Analog Devices is believed to be accurate and reliable. However, Circuits from the Lab reference designs are supplied "as is" and without warranties of any kind, express, implied, or statutory including, but not limited to, any implied warranty of merchantability, noninfringement or fitness for a particular purpose and no responsibility is assumed by Analog Devices for their use, nor for any infringements of patents or other rights of third parties that may result from their use. Analog Devices reserves the right to change any Circuits from the Lab reference designs at any time without notice but is under no obligation to do so.