

**Circuits
from the Lab™
Reference Circuits**

Circuits from the Lab™ reference circuits are engineered and tested for quick and easy system integration to help solve today's analog, mixed-signal, and RF design challenges. For more information and/or support, visit www.analog.com/CN0263.

Devices Connected/Referenced

| | |
|---------------------------|--|
| ADV7180 | 10-Bit, 4× Oversampling SDTV Video Decoder |
| ADA4830-1 | High Speed Difference Amplifier with Input Short-to-Battery Protection |

A Robust Video Receiver with Input Short-to-Battery Protection

EVALUATION AND DESIGN SUPPORT

Circuit Evaluation Boards

[CN-0263 Circuit Evaluation Board \(EVAL-CN0263-EB1Z\)](#)

Design and Integration Files

[Schematics, Layout Files, Bill of Materials](#)

CIRCUIT FUNCTION AND BENEFITS

The circuit shown in Figure 1 provides a very robust solution, with integrated overvoltage (short-to-battery [STB]) protection, for receiving CBVS video signals in harsh environments. It uses the [ADA4830-1](#) low cost, low power, unipolar, differential receiver to convert a fully differential or pseudo differential (ground referenced single-ended) video signal to a single-ended signal before being digitized by the [ADV7180](#).

The [ADA4830-1](#) is used to eliminate the common-mode noise and phase noise caused by the ground potential differences between an incoming video signal source and the receive circuit. More importantly, the [ADA4830-1](#) and [ADV7180](#) combination provides a very robust input that operates in the harsh automotive environment, and this combination provides protection from and detection of short-to-battery events and meets the strict requirements of automotive manufacturers.

This robust receiver circuit using the [ADA4830-1](#) and [ADV7180](#) follows the traditional, proven architecture of isolating/separating a low voltage integrated circuit like the [ADV7180](#) from the outside world and using an amplifier circuit for signal conditioning and protection.

The [ADA4830-1](#) (single) is a monolithic, high speed difference amplifier that integrates input overvoltage (short-to-battery) protection of up to 18 V with a wide input common-mode voltage range and excellent ESD robustness. It is intended for use as a receiver for differential or pseudo differential CVBS and other high speed video signals in harsh, noisy environments, such as

automotive infotainment and vision systems. The [ADA4830-1](#) combines high speed and precision, which allows for accurate reproduction of CVBS video signals, yet rejects unwanted common-mode error voltages.

The combination of STB protection/detection, robust ESD tolerance, and wide input common-mode voltage range allows the [ADA4830-1](#) to be used as an automotive analog video receiver in systems such as rear-view cameras and rear seat entertainment.

The [ADV7180](#) and [ADA4830-1](#) are fully automotive qualified, which makes both products ideal for infotainment and vision-based safety systems for automotive applications. The [ADV7180](#) and the [ADA4830-1](#) are available in a very small LFCSP package which is ideal for space critical applications.

CIRCUIT DESCRIPTION

The [ADA4830-1](#) is a monolithic high speed difference amplifier that is specifically designed for automotive applications. Its design is based on the traditional, four resistor difference amplifier, which is then optimized to eliminate the pitfalls while enhancing the benefits of this standard amplifier application circuit.

The short-to-battery protection that is integrated into the [ADA4830-1](#) employs fast switching circuitry to clamp and hold internal voltage nodes at a safe level when an input overvoltage condition is detected. This protection allows the inputs of the [ADA4830-1](#) to be directly connected to a remote video source, such as a rear-view camera, without the need for large expensive series capacitors.

Most video decoders, such as the [ADV7180](#), are built on very low voltage processes and thus have a limited input voltage range. The [ADA4830-1](#) has a signal gain of 0.5 V/V and is designed to keep the video signal within the allowed input range of the video decoder, which is typically 1 V p-p or less.

Rev. 0

Circuits from the Lab™ circuits from Analog Devices have been designed and built by Analog Devices engineers. Standard engineering practices have been employed in the design and construction of each circuit, and their function and performance have been tested and verified in a lab environment at room temperature. However, you are solely responsible for testing the circuit and determining its suitability and applicability for your use and application. Accordingly, in no event shall Analog Devices be liable for direct, indirect, special, incidental, consequential or punitive damages due to any cause whatsoever connected to the use of any Circuits from the Lab circuits. (Continued on last page)

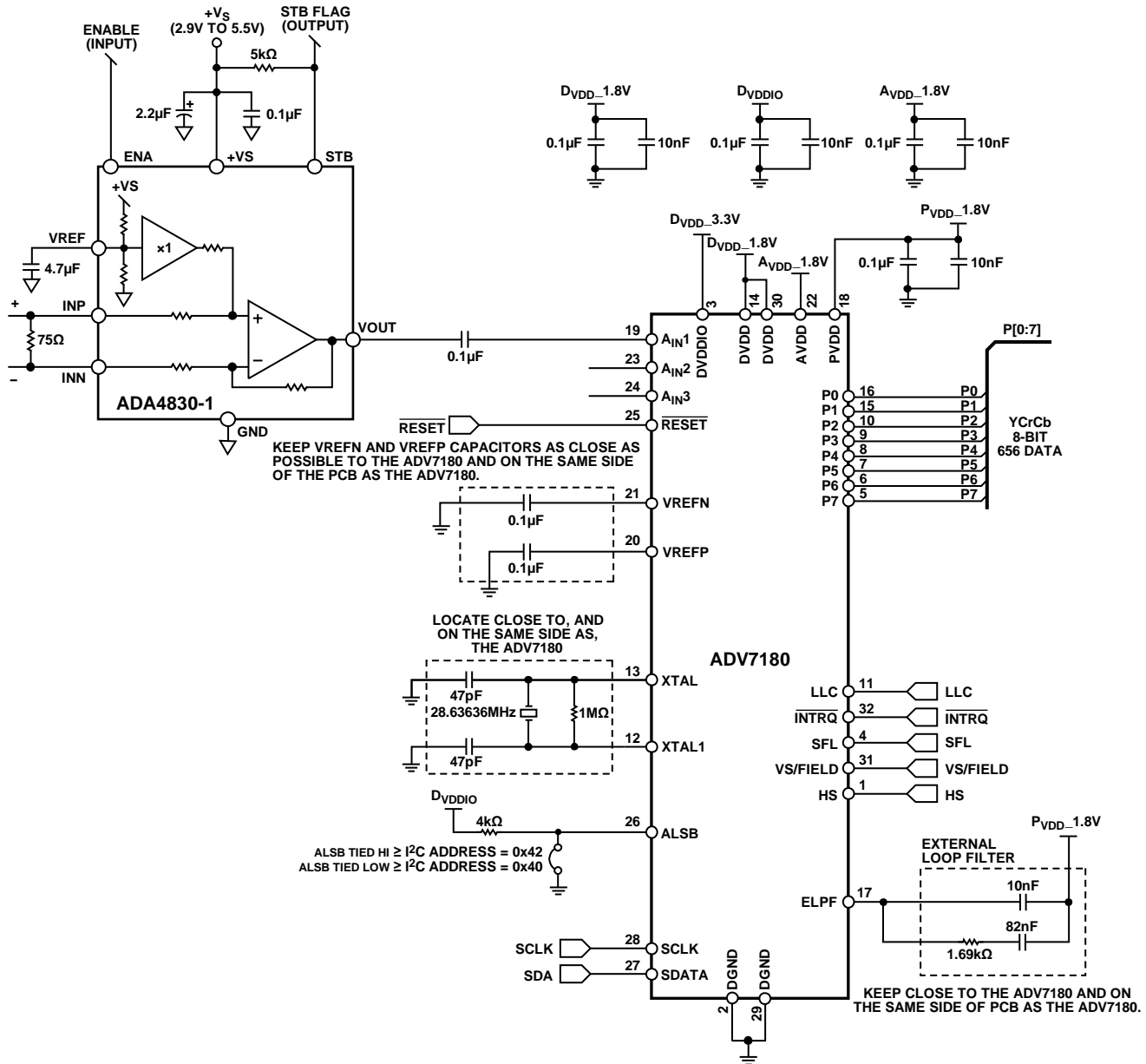


Figure 1. Robust Differential Video Receiver with the ADA4830-1 and the ADV7180 (All Connections and Decoupling Not Shown)

Input Common-Mode Voltage Range

In a standard, four resistor difference amplifier with 0.5 V/V gain, the input common-mode (CM) range is three times the CM range of the core amplifier. The input common-mode of the ADA4830-1 has been extended to more than ±8.5 V around ground (with a 5 V supply). This very wide common-mode range allows the ADA4830-1 and the ADV7180 to operate in the presence of very large common-mode offsets and noise without any adverse effects on image quality.

Wire Diagnostic

The ADA4830-1/ADV7180 combination shown in Figure 1 offers a short-to-battery wire diagnostic by connecting the STB output on the ADA4830-1 to one of the GPIO ports of the ADV7180. During a short-to-battery event, the STB output is a logic low signal. The ADV7180 reads this low and generates an interrupt that can be read by a microcontroller in the system. The short-to-battery output flag (STB pin) is functionally independent of the short-to-battery protection. Its purpose is to indicate an overvoltage condition on either input. Because protection is provided passively, it is always available; the flag merely indicates the presence or absence of a fault condition.

Input ESD Protection

The protection architecture at the inputs of the [ADA4830-1](#) uses a new technology for bidirectional asymmetrical blocking voltage. It is immune to short-to-battery conditions and able to provide ESD robustness above the 8 kV HBM level. For added ESD protection up to 15 kV, external transient suppressors are recommended.

Common-Mode Noise Rejection

The on-chip resistors integrated into the [ADA4830-1](#) are inherently well matched, improving its common-mode rejection (CMR) performance over a wide frequency range. The CMR vs. frequency of the [ADA4830-1](#) is shown in Figure 2 and is typically 65 dB at low frequencies, which enables the recovery of video signals in the presence of large levels of common-mode noise.

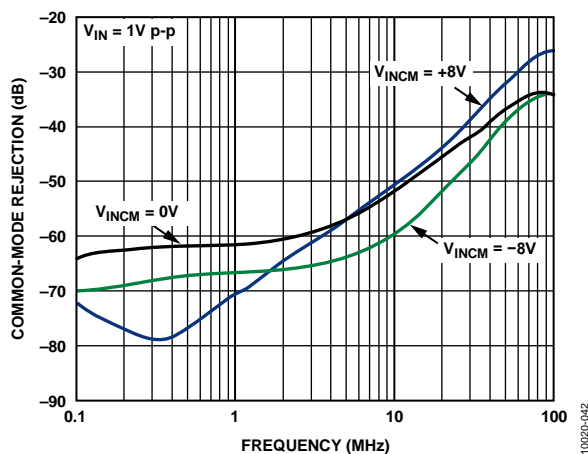


Figure 2. CMR vs. Frequency Response for Various Input Common-Mode Voltages

Common-mode errors, whether dc offsets or ac signals, degrade video image quality. Figure 3 and Figure 4 display a single large black stripe with a white background. Figure 3 shows the effects that a 500 kHz, 1 V p-p common-mode noise signal has on video image quality. Figure 4 shows the improved video image quality by adding the [ADA4830-1](#) input stage to remove common-mode noise.

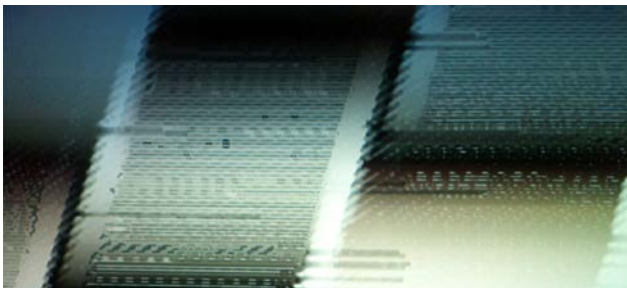


Figure 3. Video Display of a Black Stripe with 1 V p-p, 500 kHz Common-Mode Noise Inserted and [ADA4830-1](#) Bypassed



Figure 4. Video Display of Black Stripe Showing 1 V p-p, 500 kHz Common-Mode Noise Rejected by the [ADA4830-1](#)

The [ADV7180](#) automatically detects and converts standard analog baseband television signals compatible with worldwide NTSC, PAL, and SECAM standards into 4:2:2 component video data compatible with the 8-bit ITU-R.656 interface standards. The accurate 10-bit analog-to-digital conversion provides professional quality video performance for consumer applications with true 8-bit data resolution. Three analog video input channels accept standard composite, S-Video, or component video signals, supporting a wide range of consumer video sources. Automatic gain control (AGC) and clamp restore circuitry allow an input video signal peak-to-peak range of up to 1.0 V.

Printed Circuit Board (PCB) Layout Considerations

In any circuit where accuracy is crucial, it is important to consider the power supply and ground return layout on the board. The PCB should isolate the digital and analog sections as much as possible. The PCB was constructed in a 4-layer stack up with large area ground plane layers and power plane polygons. See the [MT-031 Tutorial](#) for more discussion on layout and grounding and the [MT-101 Tutorial](#) for information on decoupling techniques.

Decouple the power supply to the [ADV7180](#) with 10 μF and 0.1 μF capacitors. In addition, decouple the [ADA4830-1](#) with 0.1 μF and 22 μF capacitors to properly suppress noise and reduce ripple. Place the capacitors as close to the device as possible to ensure that the 0.1 μF capacitor has a low ESR value. Ceramic capacitors are recommended for all high frequency decoupling.

Ensure that power supply lines have as large a trace width as possible to provide low impedance paths and reduce glitch effects on the supply line. Shield clocks and other fast switching digital signals from other parts of the board by digital ground.

A complete design support package for this circuit note, including board layouts, complete schematic, and bill of materials, can be found at <http://www.analog.com/CN0263-DesignSupport>.

COMMON VARIATIONS

If multiple channels are required, the [ADA4830-1](#) is also available in a 2-channel version, the [ADA4830-2](#).

CIRCUIT EVALUATION AND TEST

This circuit uses the [EVAL-CN0263-EB1Z](#) circuit board, which contains the circuit to be evaluated, as described in this note. The board also contains an [ADV7391](#) video encoder that allows reconstruction of the input video signal. Consult the [CN-0264](#) circuit note for a description of the output circuit. A Cypress USB microcontroller is used to configure and load software to and from the [EVAL-CN0263-EB1Z](#) board.

Equipment Needed

The following equipment is needed:

- A PC with a USB port and Windows® XP or Windows Vista® (32-bit), or Windows® 7 (32-bit).
- An Astrodesign VG-828 programmable video signal generator.
- A video source for signal and common-mode error voltage. For the test described in this circuit note, the [AD8137](#) differential amplifier was used to convert single-ended video from the VG-828 to differential video, and the 500 kHz, 1 V p-p common-mode signal was applied to the V_{OCM} input of the [AD8137](#). The resulting differential signal with the added common-mode voltage was applied to the input of the evaluation board.
- A Hewlett-Packard 3314A function generator.
- An Agilent E3631A power supply.
- The [EVAL-CN0263-EB1Z](#) board.
- The [CN-0263](#) evaluation software.
- A power supply: 7.5 V or 7.5 V wall wart.
- A video display for observing the analog video output of the [EVAL-CN0263-EB1Z](#) board.

Getting Started

Load the evaluation software by placing the [CN-0263](#) evaluation software CD into the PC. Using **My Computer**, locate the drive that contains the evaluation software CD and open the **Readme** file. Follow the instructions contained in the **Readme** file for installing and using the evaluation software.

Functional Block Diagram

See Figure 1 of this circuit note for the circuit block diagram and the [EVAL-CN0263-EB1Z-SCH.pdf](#) file for the circuit schematics. This file is located in the [CN0263 Design Support Package](#).

Setup

With power to the supply off, connect a 7.5 V power supply to the +7.5 V and GND pins on the board. If available, a 7.5 V wall wart can be connected to the barrel connector on the board and used in place of the 7.5 V power supply. Connect the USB cable to the USB port on the PC. Do not connect the USB cable to the mini-USB connector on the board at this time.

Test

Apply power to the 7.5 V supply (or wall wart) connected to the [EVAL-CN0263-EB1Z](#) circuit board. Launch the evaluation software and connect the USB cable from the PC to the mini-USB connector on the PCB.

Information and details regarding how to use the evaluation software for data capture can be found in the [CN-0263](#) evaluation software **Readme** file.

LEARN MORE

[CN0263 Design Support Package:](#)

<http://www.analog.com/CN0263-DesignSupport>

[CN-0264 Circuit Note. A Robust Solution for Transmitting Composite Video with Output Short-to-Battery Protection.](#) Analog Devices, Inc., 2012.

[AN-617 Application Note. Wafer Level Chip Scale Package.](#) Analog Devices, Inc., 2012.

[MT-031 Tutorial. Grounding Data Converters and Solving the Mystery of "AGND" and "DGND."](#) Analog Devices, Inc., 2009.

[MT-101 Tutorial. Decoupling Techniques.](#) Analog Devices, Inc., 2009.

Data Sheets and Evaluation Boards

[CN-0263 Circuit Evaluation Board \(EVAL-CN0263-EB1Z\)](#)

[ADV7180 Data Sheet](#)

[ADV7180 Evaluation Board](#)

[ADA4830-1 Data Sheet](#)

[ADA4830-1 Evaluation Board](#)

REVISION HISTORY

7/12—Revision 0: Initial Version

(Continued from first page) Circuits from the Lab circuits are intended only for use with Analog Devices products and are the intellectual property of Analog Devices or its licensors. While you may use the Circuits from the Lab circuits in the design of your product, no other license is granted by implication or otherwise under any patents or other intellectual property by application or use of the Circuits from the Lab circuits. Information furnished by Analog Devices is believed to be accurate and reliable. However, Circuits from the Lab circuits are supplied "as is" and without warranties of any kind, express, implied, or statutory including, but not limited to, any implied warranty of merchantability, noninfringement or fitness for a particular purpose and no responsibility is assumed by Analog Devices for their use, nor for any infringements of patents or other rights of third parties that may result from their use. Analog Devices reserves the right to change any Circuits from the Lab circuits at any time without notice but is under no obligation to do so.