

**Circuits from the Lab**  
Reference Designs

*Circuits from the Lab® reference designs are engineered and tested for quick and easy system integration to help solve today's analog, mixed-signal, and RF design challenges. For more information and/or support, visit [www.analog.com/CN0305](http://www.analog.com/CN0305).*

### Devices Connected/Referenced

AD7988-5	16-Bit, 500 kSPS PuLSAR ADC
OP1177	Precision Low Noise, Low Input Bias Current Op Amp
ADR435	Ultralow Noise XFET® 5.0 V Voltage

## 16-Bit, 300 kSPS Low Power Data Acquisition System Optimized for Sub-Nyquist Input Signals up to 4 kHz

### EVALUATION AND DESIGN SUPPORT

#### Circuit Evaluation Boards

[CN-0305 Circuit Evaluation Board \(EVAL-CN0305-SDPZ\)](#)  
[System Demonstration Platform \(EVAL-SDP-CB1Z\)](#)

#### Design and Integration Files

[Schematics, Layout Files, Bill of Materials](#)

### CIRCUIT FUNCTION AND BENEFITS

The circuit shown in Figure 1 is a 16-bit, 300 kSPS successive approximation analog-to-digital converter (ADC) system that has a drive amplifier that is optimized for a low system power dissipation of 10.75 mW for input signals up to 4 kHz and sampling rates of 300 kSPS.

This approach is highly useful in portable battery powered or multichannel applications, or where power dissipation is critical. It also provides benefits in applications where the ADC is idle most of the time between conversion bursts.

Drive amplifiers for high performance successive approximation ADCs are typically selected to handle a wide range of input

frequencies. However, when an application requires a lower sampling rate, considerable power can be saved because reducing the sampling rate reduces the ADC power dissipation proportionally.

To take full advantage of the power saved by reducing the ADC sampling rate, a low bandwidth, low power amplifier is required.

For example, the 80 MHz [ADA4841-1](#) op amp (12 mW at 10 V) is recommended for inputs up to approximately 100 kHz with the [AD7988-5](#) 16-bit successive approximation register (SAR) ADC (3.5 mW at 500 kSPS and 2.1 mW at 300 kSPS). The total system power dissipation including the [ADR435](#) reference (4.65 mW at 7.5 V) is 18.75 mW at 300 kSPS.

For input bandwidths less than 4 kHz and sampling rates less than 300 kSPS, the 1.3 MHz [OP1177](#) op amp (4 mW at 10 V) offers excellent signal-to-noise ratio (SNR) and total harmonic distortion (THD) performance and reduces total system power from 18.75 mW to 10.75 mW, which is a 43% power savings at 300 kSPS.

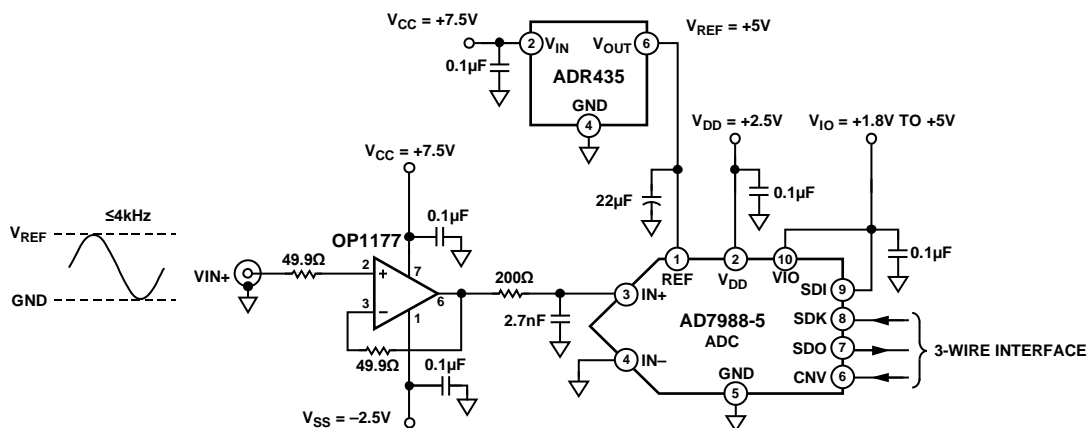


Figure 1. System Circuit Diagram of Low Power [OP1177](#) Amplifier Driving the [AD7988-5](#) ADC (Simplified Schematic: All Connections Not Shown)

#### Rev. A

Circuits from the Lab® reference designs from Analog Devices have been designed and built by Analog Devices engineers. Standard engineering practices have been employed in the design and construction of each circuit, and their function and performance have been tested and verified in a lab environment at room temperature. However, you are solely responsible for testing the circuit and determining its suitability and applicability for your use and application. Accordingly, in no event shall Analog Devices be liable for direct, indirect, special, incidental, consequential or punitive damages due to any cause whatsoever connected to the use of any Circuits from the Lab circuits. (Continued on last page)

## CIRCUIT DESCRIPTION

The circuit comprises the [AD7988-5](#) ADC, [OP1177](#) amplifier, and [ADR435](#) reference. The [AD7988-5](#) is a 16 bit, 500 kSPS SAR ADC whose low power is scalable with sampling rate and consumes 3.5 mW at 500 kSPS. Its low power also comes with industry-leading ac performance: SNR = 91 dB and THD = -114 dBc.

The driving amplifier is the low power, precision [OP1177](#) that has a supply current of 400  $\mu$ A and a gain bandwidth product of 1.3 MHz. The [OP1177](#) can be driven with supplies ranging from 5 V to 30 V. The reference for the ADC is the [ADR435](#), which is a high precision, low noise, 5 V XFET voltage reference. The [ADR435](#) has a very low temperature coefficient of 3 ppm/ $^{\circ}$ C at a low supply current of 620  $\mu$ A. The total power for this circuit is 10.75 mW at 300 kSPS. The SNR is 90.6 dBFS, and the THD is -102 dBc with an input frequency up to 4 kHz.

The [OP1177](#) is configured as a unity-gain buffer and has an RC filter (200  $\Omega$ , 2.7 nF) with a 295 kHz cutoff frequency between it and the [AD7988-5](#). The filter allows the use of a higher noise amplifier, such as the [OP1177](#), at 8 nV/ $\sqrt{\text{Hz}}$  while still getting the benefits of much lower power consumption. The tradeoff of higher noise for lower power causes only 0.4 dB reduction in the SNR performance of the system. The higher value of R (200  $\Omega$ ) relative to the recommended data sheet value (20  $\Omega$ ) means the [OP1177](#) can drive the large 2.7 nF input capacitor. The higher R value limits the maximum input bandwidth to a few kHz for low distortion.

This compares favorably to the 16-bit distortion performance (THD less than -100 dBc) of the [OP1177](#) for up to 5 kHz inputs. Distortion increases beyond 5 kHz so that it is not advisable to use this circuit with higher input frequencies or to use this amplifier in a multiplexed application due to the long settling time. Note that the [OP1177](#) requires at least 1.5 V of input headroom/footroom and 1 V of output headroom/footroom when setting the supplies. In addition, note that the [OP1177](#) cannot be used to drive the [AD7988-5](#) above 300 kSPS because the driver settling time is not sufficient for the shorter ADC acquisition time (see Figure 3).

## Performance Results

The goal of this circuit is to deliver good ac performance at the lowest ADC driver power level possible for input frequencies less than 4 kHz at a sampling rate of 300 kSPS. Figure 2 shows an FFT plot of the circuit performance for a 4 kHz input. The SNR is 90.6 dBFS, and the THD is -102 dBc. The main reason for the slight reduction in SNR from the 91 dBFS specification of the [AD7988-5](#) is the higher noise of the [OP1177](#) of 8 nV/ $\sqrt{\text{Hz}}$  vs. 2 nV/ $\sqrt{\text{Hz}}$  for the [ADA4841-1](#). The total system power is 10.75 mW: 2.1 mW for the ADC (running at 300 kSPS), 4 mW for the amplifier, and 4.65 mW for the reference. This represents a 43% reduction in power from using the [ADA4841-1](#), which consumes 12 mW for a total system power of 18.75 mW.

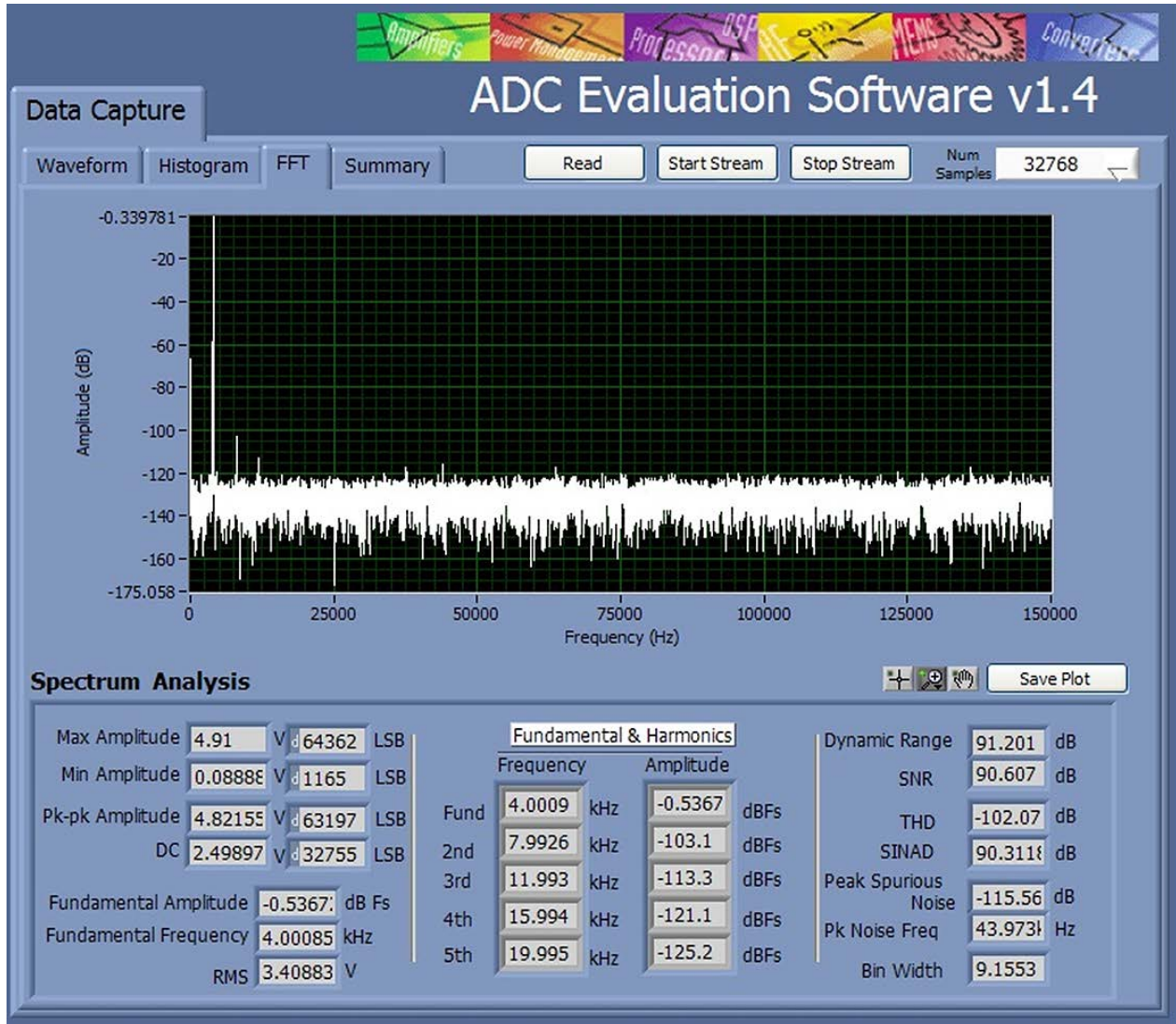


Figure 2. System Circuit Performance of Using the OP1177 Amplifier Driving the AD7988-5

Figure 3 shows how the system THD increases and the SNR decreases at higher sampling rates above 300 kSPS. For this reason, operate the ADC at 300 kSPS or lower for best performance.

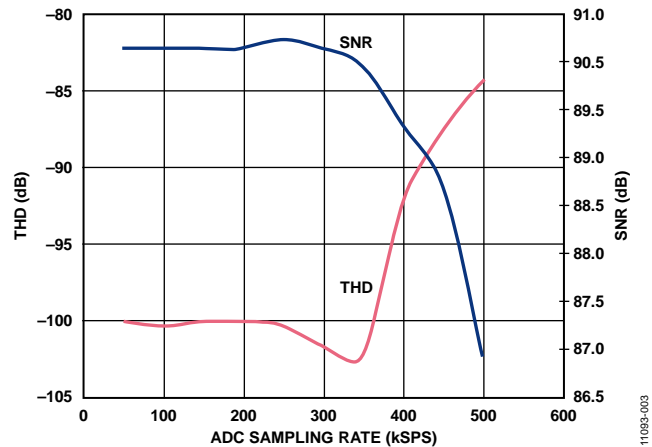


Figure 3. THD and SNR vs. ADC Sampling Rate for OP1177 Amplifier Driving the AD7988-5

Figure 4 shows how the system THD increases and the SNR decreases with input frequencies above 4 kHz. This is due to the amplifier distortion as can be seen in the THD+N vs. frequency plot shown in Figure 5.

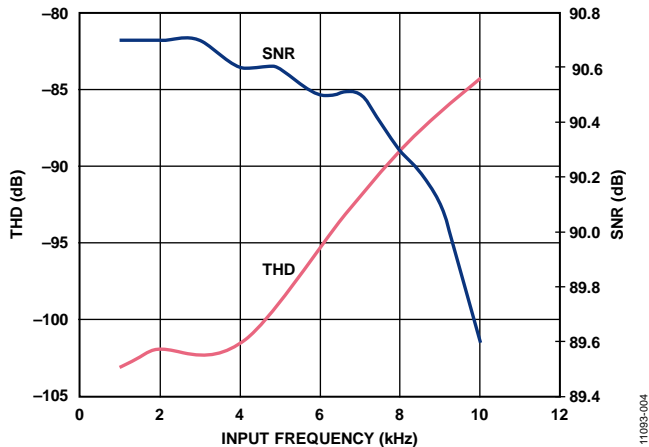


Figure 4. THD and SNR vs. Input Frequency for *OP1177* Amplifier Driving the *AD7988-5*

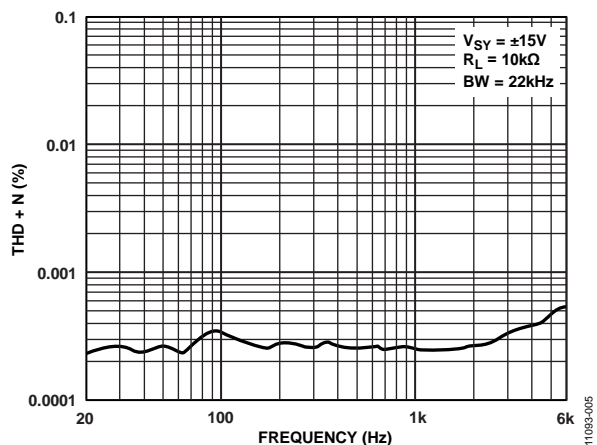


Figure 5. THD+N vs. Input Frequency Performance the *OP1177* Amplifier

**COMMON VARIATIONS**

The *OP1177* amplifier can be used to drive pin-compatible ADCs like the *AD7988-1* up to 100 kSPS and the *AD7980* up to 300 kSPS. The *AD8641* amplifier can be used to drive the *AD7988-5* at half the power (200  $\mu$ A); however, only up to 100 kSPS with reduced ac performance and a lower input frequency range (see the [CN-0306 circuit note](#)).

**CIRCUIT EVALUATION AND TEST**

**Equipment Needed (Equivalents Can Be Substituted)**

The following equipment is needed:

- The [EVAL-CN0305-SDPZ](#) evaluation board
- The System Demonstration Board ([EVAL-SDP-CB1Z](#))
- A function generator/signal source, such as the Audio Precision SYS-2522 used in these tests
- The 9 V wall power supply included with the [EVAL-CN0305-SDPZ](#) evaluation board
- A PC with a USB port, a USB cable, and the 10-lead PulSAR software installed

**Setup and Test**

Install the 10-lead PulSAR software downloadable from the [AD7988-5](#) product page on the Analog Devices, Inc., website using the installation guide in the [UG-340](#) user guide. The block diagram of the measurement setup is shown in Figure 6. Connect the 9 V wall power supply to the evaluation board power terminal. To measure the frequency response, connect the equipment as shown in Figure 6. Set the Audio Precision SYS-2522 signal generator for a 4 kHz frequency and a 5 V p-p sine wave with a 2.5 V dc offset. Set the ADC sample rate in the software window to 300 kSPS. Record the data using the evaluation board software. The software analysis is part of the evaluation board software that allows the user to capture and analyze ac and dc performance. This software and its features are described in detail in the [UG-340](#) user guide.

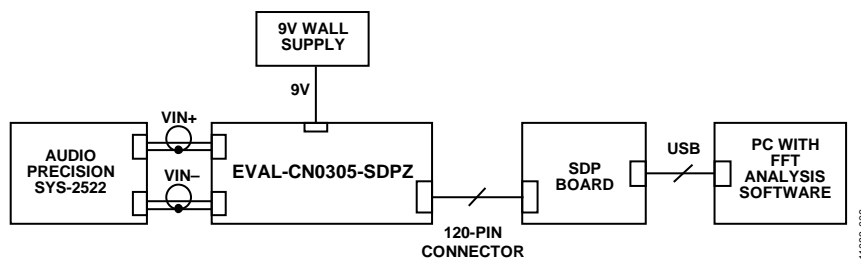


Figure 6. Functional Diagram of Test Setup

**LEARN MORE**

CN0305 Design Support Package:  
<http://www.analog.com/CN0305-DesignSupport>  
 UG-340 User Guide, *Evaluation Board for the 8-/10-Lead Family of 14-/16-/18-Bit PulSAR ADCs*, Analog Devices.  
 EVAL-SDP-CB1Z System Demonstration Platform (SDP)  
 MT-021 Tutorial, *Successive Approximation ADCs*, Analog Devices  
 MT-031 Tutorial, *Grounding Data Converters and Solving the Mystery of "AGND" and "DGND,"* Analog Devices.  
 MT-101 Tutorial, *Decoupling Techniques*, Analog Devices.  
 Voltage Reference Selection and Evaluation Wizard, Analog Devices

**Data Sheets and Evaluation Boards**

CN-0305 Circuit Evaluation Board (EVAL-CN0305-SDPZ)  
 System Demonstration Platform (EVAL-SDP-CB1Z)  
 AD7988-1 Data Sheet  
 AD7988-5 Data Sheet  
 AD7980 Data Sheet  
 ADR435 Data Sheet  
 AD8641 Data Sheet  
 OP1177 Data Sheet  
 ADA4841-1 Data Sheet

**REVISION HISTORY**

12/13—Rev. 0 to Rev. A  
 Changes to Title..... 1

11/12—Rev. 0: Initial Version

(Continued from first page) Circuits from the Lab reference designs are intended only for use with Analog Devices products and are the intellectual property of Analog Devices or its licensors. While you may use the Circuits from the Lab reference designs in the design of your product, no other license is granted by implication or otherwise under any patents or other intellectual property by application or use of the Circuits from the Lab reference designs. Information furnished by Analog Devices is believed to be accurate and reliable. However, Circuits from the Lab reference designs are supplied "as is" and without warranties of any kind, express, implied, or statutory including, but not limited to, any implied warranty of merchantability, noninfringement or fitness for a particular purpose and no responsibility is assumed by Analog Devices for their use, nor for any infringements of patents or other rights of third parties that may result from their use. Analog Devices reserves the right to change any Circuits from the Lab reference designs at any time without notice but is under no obligation to do so.

©2012–2013 Analog Devices, Inc. All rights reserved. Trademarks and registered trademarks are the property of their respective owners.  
 CN11093-0-12/13(A)

