

**Circuits from the Lab**<sup>®</sup>  
Reference Designs

*Circuits from the Lab*<sup>®</sup> reference designs are engineered and tested for quick and easy system integration to help solve today's analog, mixed-signal, and RF design challenges. For more information and/or support, visit [www.analog.com/CN0432](http://www.analog.com/CN0432).

### Devices Connected/Referenced

AD9139	Single Channel, 1.6 GSPS, 16-Bit, TxDAC <sup>®</sup> Digital-to Analog Converter
ADL5375	Broadband Quadrature Modulator
AD9516-1	14-Output Clock Generator with Integrated 2.5 GHz VCO

## Wideband Baseband I/Q Transmitter Design Using Two AD9139 Devices with Multi-DAC Synchronization

### EVALUATION AND DESIGN SUPPORT

#### Circuit Evaluation Boards

[AD9139/ADL5375 Evaluation Board \(AD9139-DUAL-EBZ\)](#)

[Digital Pattern Generator Evaluation Board \(AD-DPG3\)](#)

#### Design and Integration Files

[Schematics, Layout Files, Bill of Materials, Software](#)

### CIRCUIT FUNCTION AND BENEFITS

This circuit shown in Figure 1 provides a synchronized, wide-band transmitter, which can support a very wide I/Q bandwidth of up to 1150 MHz. The design proves high in-band signal performance such as high spurious-free dynamic range (SFDR), low error vector magnitude (EVM), and flat frequency response over a wide band.

The synchronization performance between multiple channels is especially critical for the quadrantal error correction (QEC).

The delay mismatch between the converters can be within one clock cycle when multichip synchronization is enabled, and a well-aligned sync clock is present.

The challenge of high speed synchronization is to reach the accuracy of digital-to-analog (DAC) clock cycles over process, voltage, and temperature (PVT). To achieve that accuracy, a synchronization logic block is implemented on the DAC, and a careful layout and clock scheme on board must be designed to work with the synchronization logic block.

This circuit can be used to support wideband point-to-point applications in E-band, which ensures both zero intermediate frequency (ZIF) and complex intermediate frequency (CIF). The excellent synchronization performance makes it possible to support the strict alignment requirements found in applications like radar.

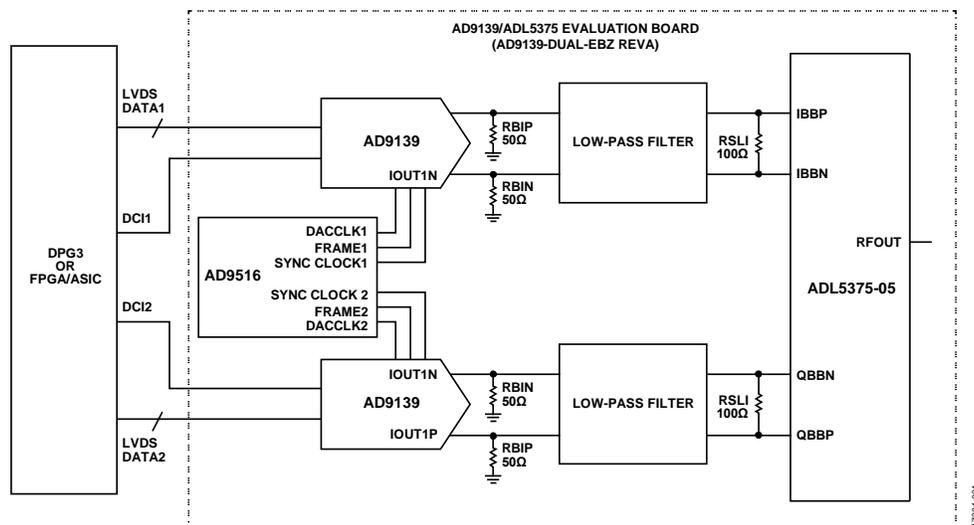


Figure 1. Block Diagram of AD9139-DUAL-EBZ Evaluation Board

#### Rev. 0

Circuits from the Lab<sup>®</sup> reference designs from Analog Devices have been designed and built by Analog Devices engineers. Standard engineering practices have been employed in the design and construction of each circuit, and their function and performance have been tested and verified in a lab environment at room temperature. However, you are solely responsible for testing the circuit and determining its suitability and applicability for your use and application. Accordingly, in no event shall Analog Devices be liable for direct, indirect, special, incidental, consequential or punitive damages due to any cause whatsoever connected to the use of any Circuits from the Lab circuits. (Continued on last page)

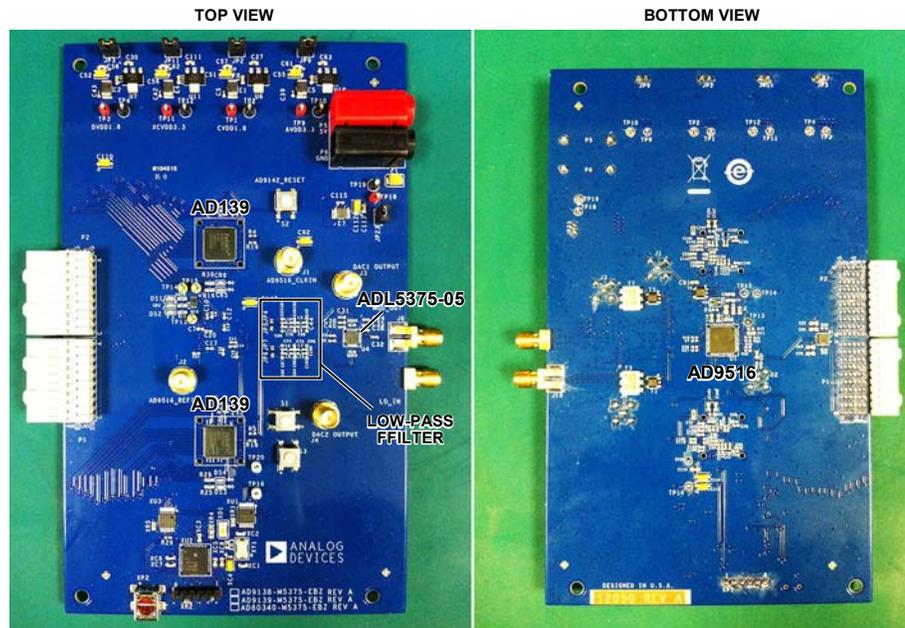


Figure 2. AD9139-DUAL-EBZ Evaluation Board for Circuit Implementation

## CIRCUIT DESCRIPTION

The board shown in Figure 2 uses the dual AD9139 single-channel TxDAC, the ADL5375-05 wideband quadrature modulator, and the AD9516-1 clock generator.

The maximum data clock input (DCI) frequency of the AD9139 can be up to 575 MHz. Because the data captured at both rising edge and falling edge feeds to one single DAC, the maximum data rate at 1× mode can reach as high as 1150 MSPS. To support quadrature data, two AD9139 devices are used to generate baseband data. The analog output of every channel goes to its own low-pass filter, respectively. Therefore, the reference design can support a maximum complex bandwidth of up to 1150 MHz, as shown in Figure 3. The flatness over such a wide range is critical. Because the AD9139 includes an inverse sinc filter that cancels the effect of the DAC's inherent sinc roll off, the flatness of the filter after DAC becomes important to the total flatness. A DDR clock frequency of 575 MHz is very high for a parallel low voltage differential signals (LVDS) interface. The timing of the LVDS interface needs to be designed carefully.

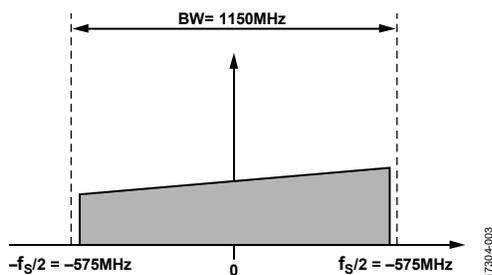


Figure 3. Maximum Bandwidth of Dual AD9139 Devices

## Quadrature Modulator

The ADL5375-05 is a broadband quadrature modulator with an output frequency range of 400 MHz to 6 GHz. The ADL5375-05 interfaces with the AD9139 as the I/Q modulator, which covers a wide frequency range from 400 MHz to 6 GHz. The output of the AD9139 and the input of the ADL5375-05 share the same common mode level of 0.5 V.

## Clock Generation and Considerations

Considering the synchronization requirements, the DACCLK, sync clock, and frame clock of both AD9139 devices must be well aligned. The AD9516-1 supports the necessary clock distribution functions, as well as a voltage controlled oscillator (VCO) and phase-locked loop (PLL) integrated for higher frequency generation. With the VCO and PLL disabled and the AD9516-1 in clock distribution mode, the phase noise of the clocks is better for the high speed alignment. In clock distribution mode, the additive phase noise at 10 MHz offset with divider = 1 and 1 GHz output is  $-147$  dBc/Hz. The Rohde & Schwartz SMA100A has excellent phase noise performance; used as the input of the AD9516-1, the total phase noise at the AD9516-1 output is close to the limit of the minimum value of the AD9516-1 in clock distribution mode.

## Multichip Synchronization of AD9139

The synchronization between dual channels is critical to QEC. Layout symmetry between DACCLK and sync clock is required. In addition, the phase between DACCLK and sync clock must not fall in the setup and hold time window (also called the keep out window (KOW)).

The mechanism of synchronization can reach the performance of less than one DAC clock cycle mismatch between multiple channels over PVT on the DAC output. The following are guidelines to achieve the test performance:

1. DACCLK 1 and DACCLK 2 must be well aligned on the pins of the AD9139. Mismatch between DACCLK 1 and DACCLK 2 is added to the final mismatch on the output.
2. Sync Clock 1 and Sync Clock 2 must be well aligned, and they are sampled by DACCLK1 and DACCLK2, respectively, and used as the reference.
3. The relative phase between DACCLK and sync clock must not fall in the KOW, as shown in Figure 4.

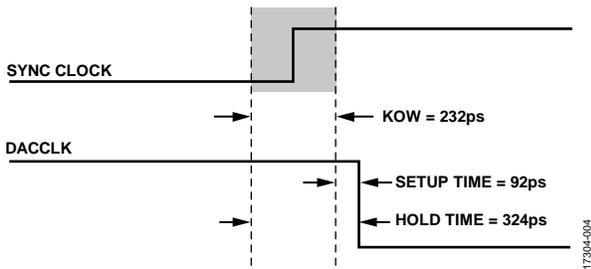


Figure 4. Timing Requirement Between DACCLK and Sync Clock

### LVDS Interface Design

When DCI = 575 MHz, it is usually a challenge for LVDS interface design over PVT. This section shows how to design and optimize the interface through one example.

In Figure 5, as an example, DCI = 491 MHz. If the edge of DCI and DATA are well aligned on the pin of the AD9139, based on the AD9139 data sheet specifications, the KOW (setup time + hold time) can be placed in the middle of the valid window when the delay locked loop (DLL) phase is set to zero.

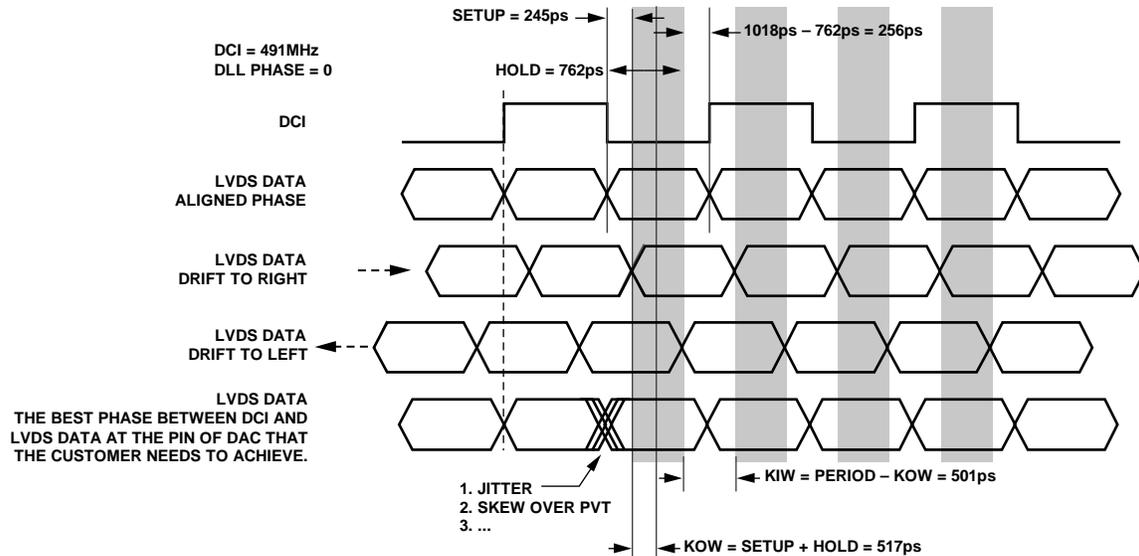


Figure 5. LVDS Timing Requirement

The data valid margin is defined by the following equation.

$$T_{DATA\ VALID\ MARGIN} = T_{DATA\ PERIOD} - T_{DATA\ SKEW} - T_{DATA\ JITTER} - (T_{HOLD} + T_{SETUP})$$

Over process variation, voltage, and temperature,  $T_{DATA\ VALID\ MARGIN}$  must be  $> 0$  to make sure that the data is sampled correctly.

When DCI = 491 MHz (see Figure 5),

- $T_{DATA\ PERIOD} = 1018\ ps$
- $T_{HOLD} + T_{SETUP} = 517\ ps$
- $T_{DATA\ SKEW} + T_{DATA\ JITTER}$  must be less than 501 ps over PVT, which is the requirement for the user's implementation.  $T_{DATA\ SKEW}$  includes LVDS data bus delay mismatch, the skew between DCI and DATA bus over PVT, and so on.

To optimize the interface design, the user can do the following:

- Route the tracks with equal length and as short as possible on the printed circuit board (PCB).
- Optimize the programmable field gate array (FPGA) by ensuring the following:
  - The edges of DCI and DATA are well aligned on the pins of the AD9139.
  - The drift between DCI and DATA is as small as possible over temperature and voltage.
  - The jitter of DCI and DATA is as small as possible.

With the DLL phase swept, the sample error detection (SED) function of the AD9139 can also be used to check the timing relationship between DCI and DATA.

**Low-Pass Filter Design**

For experimental purposes, in order not to limit the performance of AD9139 due to the filter, a filter with good flatness and group delay performance within 240 MHz was designed on the board. The out-of-band rejection can be enhanced by increasing the order of the filter in real product development.

The filter topology shown in Figure 6 is a fifth-order Butterworth filter with a 900 MHz corner frequency. The simulated response of the filter is shown in Figure 7. The simulated flatness is  $\pm 0.1$  dB from dc to 240 MHz. The simulated group delay of the filter is shown in Figure 7.

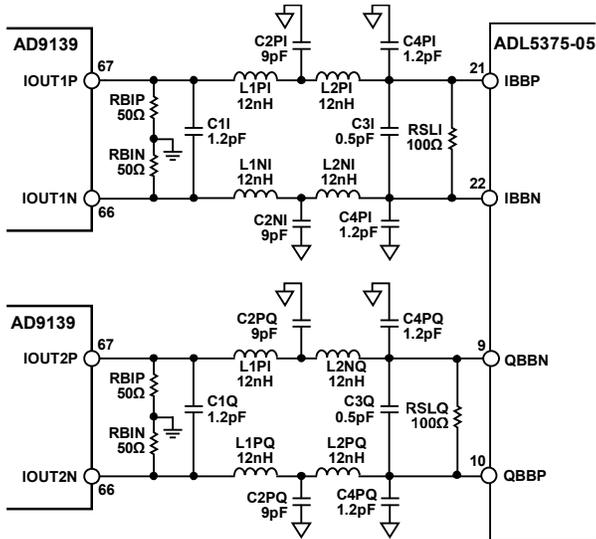


Figure 6. Recommended DAC Modulator Interface Topology with  $F_c = 900$  MHz Fifth-Order, Butterworth Filter

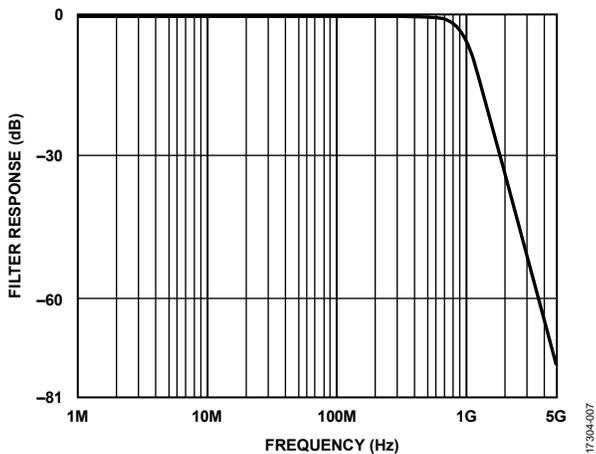


Figure 7. Frequency Response for DAC Modulator Interface with 900 MHz Fifth-Order Butterworth Filter (Simulated)

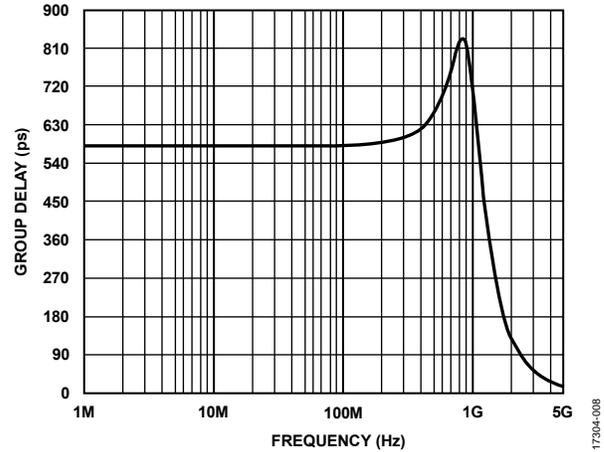


Figure 8. Group Delay of the Filter

**Layout Recommendations**

Special care must be taken in the layout of the AD9139 and ADL5375 interface. The following are some recommendations for good noise and spurious performance. Figure 9 shows a top-level layout, which follows these recommendations:

- Place the DAC, filter, and modulator on the same side of the PCB.
- Tightened filter layout: cut down the keep out margin of L and C.
- Triple ground the shunt caps to the GND plane.
- Shorten the distance from DAC to the modulator.
- Keep all I/Q differential trace lengths well matched.
- Place the filter termination resistor as close as possible to the modulator input.
- Place the DAC output 50  $\Omega$  resistors as close as possible to the DAC.
- Use 0402 size for L and C.
- Thicken the trace widths through the filter network to reduce signal loss.
- Place vias around all the DAC output traces, filter networks, modulator output traces, and LO input traces.
- Route the local oscillator (LO) and modulator outputs on different layers or at 90° angle to each other to prevent coupling.

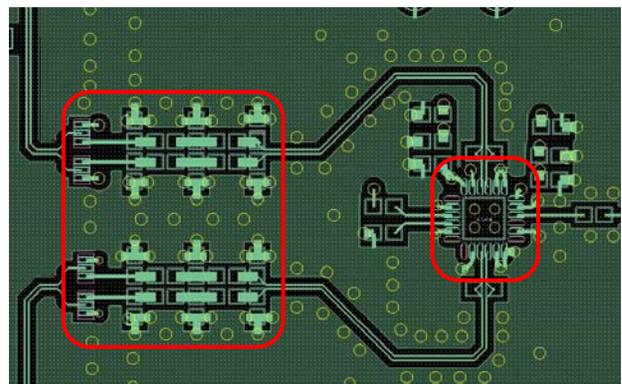


Figure 9. General Layout Recommendations

Further information on proper layout can be found in the [AD9139-DUAL-EBZ](#) layout files included in the design support package at [www.analog.com/CN0432-DesignSupport](http://www.analog.com/CN0432-DesignSupport).

## CIRCUIT EVALUATION AND TEST

The following section describes how to set up and test the board. These steps outline the basic steps required to replicate the demo and results. For more detailed information, see the [AD9139-DUAL-EBZ Evaluation Board Quick Start Guide](#).

### Required Equipment

The following hardware is required:

- [AD9139-DUAL-EBZ](#)
- [AD-DPG3](#)
- Agilent E3631A power supply (or equivalent)
- Spectrum Analyzer PXA N9030A
- Rohde & Schwarz SMA100A signal generator
- PC with USB port
- USB cable

The following software is required:

- DPG downloader
- [ACE](#) software

### Test Setup

The following section describes details of measuring adjacent channel power (ACP) and modulation error ratio (MER) performance with the digital modulation of 64 QAM. The test setup is flexible and allows other measurements to be performed. The test setup is shown as below in Figure 10.

The hardware of the [AD9139-DUAL-EBZ](#) evaluation board, SPI software, quick start guide (QSG), and DPG3 hardware and software are all released.

One Keysight E3631 is used to provide the 5 V power supply of the board on P5/P6. One R&S SMA100A provides the input clock to the [AD9516-1](#) on the board. A second R&S SMA100A provides the LO clock to [ADL5375-05](#). The [AD9139](#) is programmed by serial peripheral interface (SPI) software. The vector transmitted by the [AD9139](#) is generated and downloaded to the DPG3 by [DPGDownloader](#), which runs on the PC. The output of the [ADL5375-05](#) feeds to the Keysight PXA N9030A.

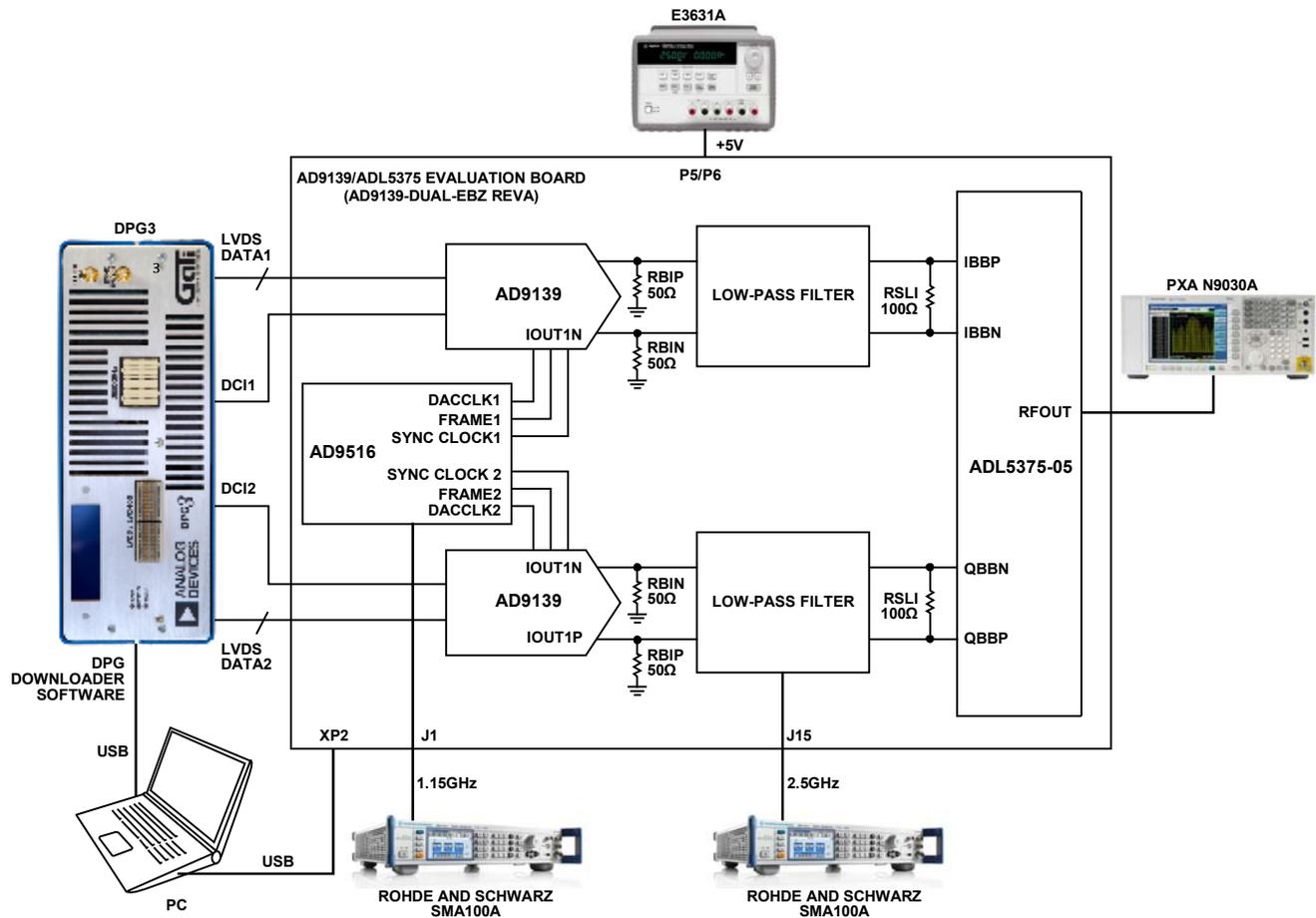


Figure 10. Test Setup Functional Block Diagram

Measured Results

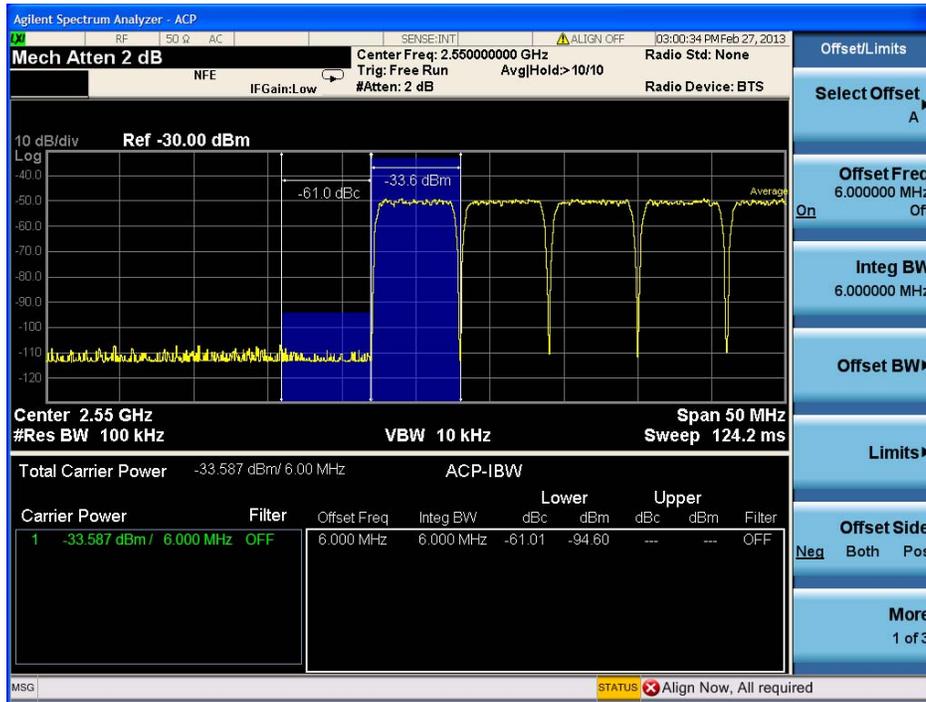


Figure 11. ACP Measurement with LO = 2.5 G and BW = 6 × 80 = 480 MHz (CIF)

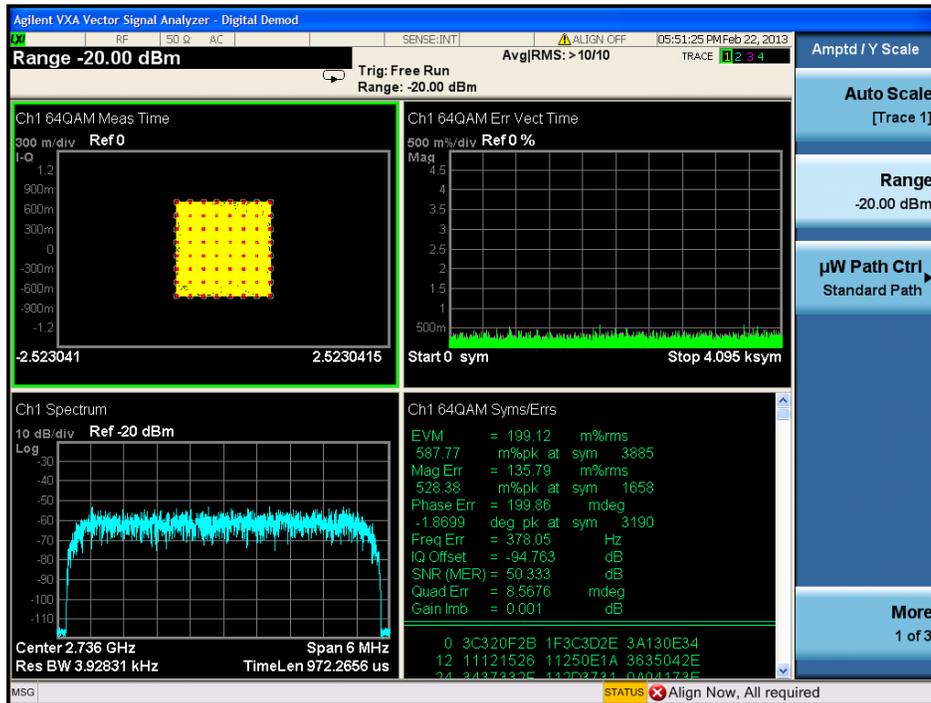


Figure 12. MER/EVM Measurement with LO = 2.5 G and BW = 6 × 80 = 480 MHz (CIF)

**LEARN MORE**

CN-0432 Design Support Package:

[www.analog.com/CN0432-DesignSupport](http://www.analog.com/CN0432-DesignSupport)

[CN-0205 Interfacing the ADL5375 I/Q Modulator to the](#)

[AD9122 Dual Channel, 1.2 GSPS High Speed DAC, Analog Devices](#)

[CN-0243 High Dynamic Range RF Transmitter Signal Chain Using Single External Frequency Reference for DAC Sample Clock and IQ Modulator LO Generation, Analog Devices.](#)

[ADIsimPLL Design Tool](#)

[ADIsimRF Design Tool](#)

[AD9139-DUAL Evaluation Board Quick Start Guide](#)

[Analog Devices Data Pattern Generator \(DPG\)](#)

**Data Sheets and Evaluation Boards**

[AD9139 Data Sheet](#)

[ADL5375 Data Sheet](#)

[AD9139-DUAL Evaluation Board](#)

[ADL5375-05 Evaluation Board](#)

**REVISION HISTORY**

**9/2019—Revision 0: Initial Version**

(Continued from first page) Circuits from the Lab reference designs are intended only for use with Analog Devices products and are the intellectual property of Analog Devices or its licensors. While you may use the Circuits from the Lab reference designs in the design of your product, no other license is granted by implication or otherwise under any patents or other intellectual property by application or use of the Circuits from the Lab reference designs. Information furnished by Analog Devices is believed to be accurate and reliable. However, Circuits from the Lab reference designs are supplied "as is" and without warranties of any kind, express, implied, or statutory including, but not limited to, any implied warranty of merchantability, noninfringement or fitness for a particular purpose and no responsibility is assumed by Analog Devices for their use, nor for any infringements of patents or other rights of third parties that may result from their use. Analog Devices reserves the right to change any Circuits from the Lab reference designs at any time without notice but is under no obligation to do so.

©2019 Analog Devices, Inc. All rights reserved. Trademarks and registered trademarks are the property of their respective owners.  
CN17304-0-9/19(0)

