

Circuits from the Lab[®] Reference Designs

Circuits from the Lab[®] reference designs are engineered and tested for quick and easy system integration to help solve today's analog, mixed-signal, and RF design challenges. For more information and/or support, visit www.analog.com/CN0602.

Devices Connected/Referenced

ADMT4000	True Power-On Multiturn Sensor
LT3467	1.1A Step-Up DC/DC Converter with Integrated Soft-Start

ADMT4000 TSSOP Industrial Reference Design

EVALUATION AND DESIGN SUPPORT

- Design and Integration Files
 - [Schematics, Layout Files, Bill of Materials](#)

CIRCUIT FUNCTIONS AND BENEFITS

This reference design provides a highly integrated development platform for the [ADMT4000](#) true power-on multiturn sensor in its thin shrink small outline package (TSSOP) package. Designed for easy prototyping and rapid evaluation, the board combines functionality, diagnostics, and modularity—eliminating the need for early-stage custom PCB layout. It allows designers to validate the ADMT4000 in conditions that closely mimic final production, including accurate pin mapping, signal integrity, thermal behavior, and packaging nuances. The board includes a plug-and-play interface featuring SPI connectivity and magnetic reset capability.

The turn count sensor in the ADMT4000 is comprised of a spiral of giant magneto resistance (GMR) resistors, by which the magnet-

ization pattern in these resistors is used to determine the turn count and the absolute position of a system. If the maximum allowed magnetic field (B_{MAX}) is exceeded, the GMR spiral may be corrupted. This scenario does not damage the device, but a reset of the spiral will be required. The reset can be achieved by rotating the system magnet more than 46 turns in the clockwise direction, or by applying a magnetic field greater than 60 mT in the 315° direction. Implementing the reset circuit with the specified components will ensure that the reset coil is energized sufficiently to generate the required magnetic field to reset the GMR turn count sensor.

The circuit shown in [Figure 1](#) provides an in-built coil and a pulse generator which is used, in combination with the system magnet, to reset the GMR sensor.

The circuit consists of the following key blocks:

- ADMT4000 Configuration
- Pulse Generator for the GMR Magnetic Reset Coil

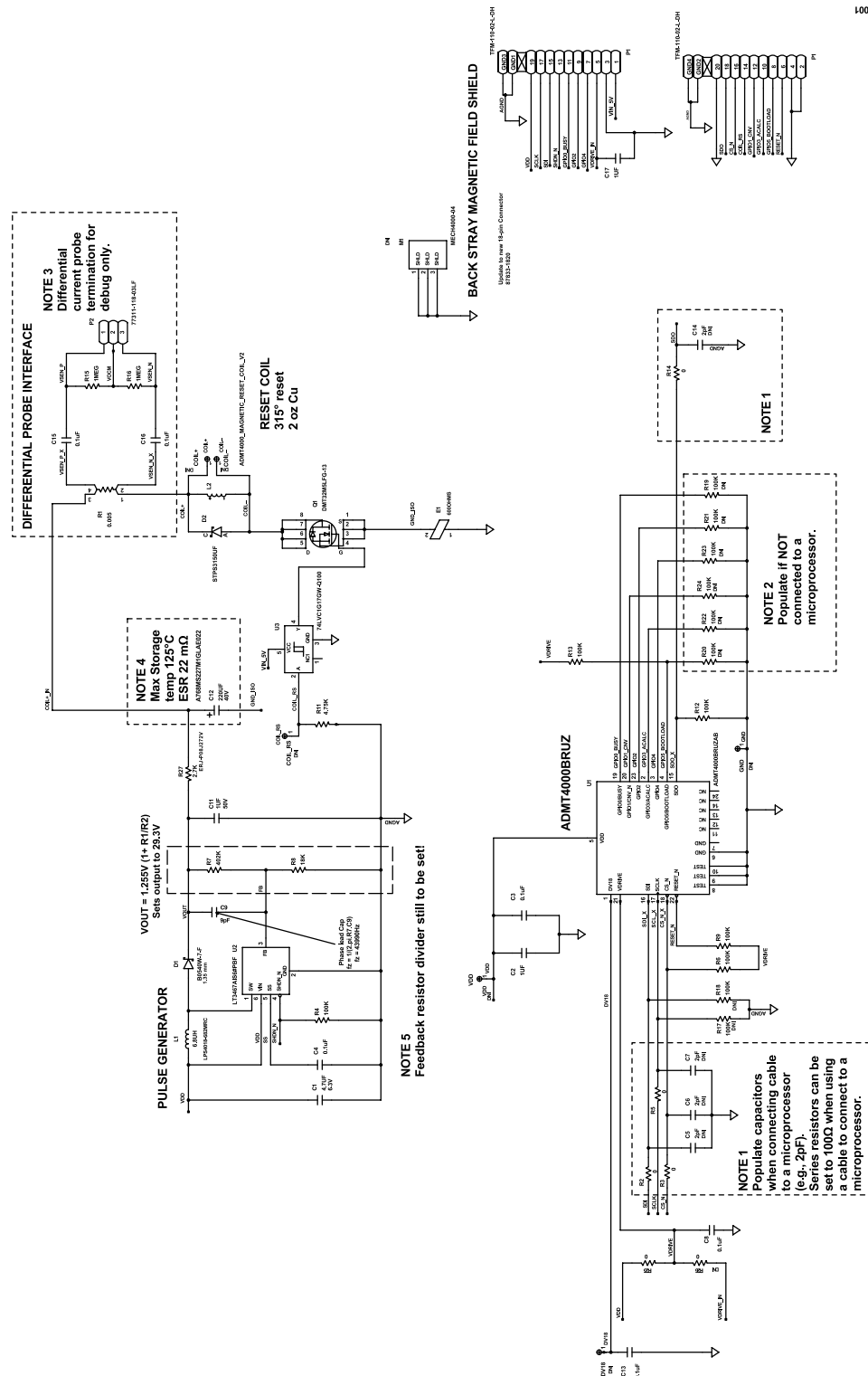


Figure 1. Circuit Diagram Illustrating the Use of a Pulse Generator and Coil for GMR Sensor Magnetic Reset

CIRCUIT DESCRIPTION

SPI INTERFACE

The ADMT4000 has an SPI interface, which can be used to control all the functions of the part and obtain the absolute position of a system on power-up. The general-purpose input/output (GPIO) pins are multifunctional pins and can be configured by setting a register to a specific function. For example, GPIO1 can be configured as an input, output, or convert start (CNV) pin.

Figure 2 shows the configuration when none of the GPIO pins are required. If the GPIO pins are not used, they should be tied to ground via a 100 k Ω resistor, except for GPIO5, which should be tied to V_{DRIVE} via a 100 k Ω resistor.

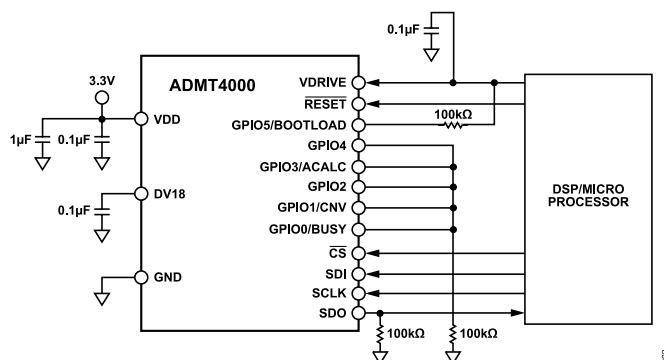


Figure 2. System Configuration for Applications That Do Not Require GPIO Functionality

As depicted in Figure 3, pull-down resistors are not needed when the GPIOs are connected to a microprocessor.

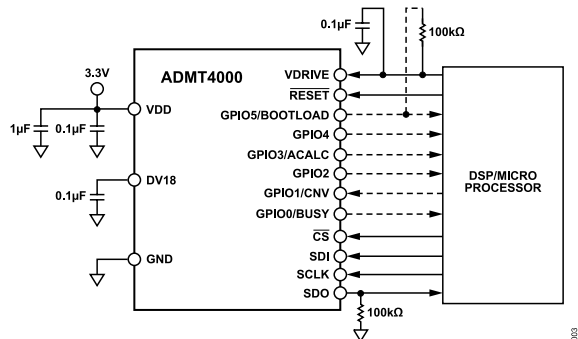


Figure 3. System Configuration for Applications Requiring GPIO Functionality

The circuit shown in Figure 1 can be configured with any combination of GPIOs being used or not. In most cases, the SPI interface should be connected directly to a microprocessor located on the same PCB. While it is possible to drive the SPI interface through a cable, different cable characteristics may necessitate an RC filter. This circuit note does not specify the values required to drive the SPI interface over a cable, but does provide the footprints on the PCB to add the resistors and capacitors.

During normal operation, the ADMT4000 is typically connected directly to a microprocessor via the SPI interface. In this configuration, the resistors and capacitors identified by Note 1 on Figure 1 are not required. However, if the ADMT4000 is controlled by an off-board microprocessor, an RC filter may be necessary—depending on the characteristics of the connecting cable—to ensure reliable SPI communication. Additionally, the GPIO ports should be terminated in accordance with the guidelines provided in the ADMT4000 data sheet.

PULSE GENERATOR

The pulse generator circuit for the reset coil is split into six key sections:

1. Voltage Boost Circuit

The voltage boost circuit based around the LT3467 step-up DC/DC converter is configured to boost the 5 V supply to 29.3 V. The converter charges the low ESR capacitor C12 to 29.3 V.

2. Current Limiting

Resistor R27 is used to control the inrush current to C12. If a power supply with a higher current rating is available, R27 can be reduced to shorten the capacitor's charge time.

3. Current Sensing

While not required in the final application, a sense resistor R1 is included to allow measurement of the current pulse through the reset coil using a differential probe.

4. Reset Coil Configuration

The reset coil, L2, is a planar coil integrated into the PCB, see AN-2610 Application Note for further details of the coil layout. A reverse-biased diode, D2, is used across the integrated coil to provide a path for the inductive kickback from the coil.

5. Pulse Discharge Path

The capacitor C12 is discharged through L2 via the n-channel MOSFET Q1. The MOSFET is selected for a low on-resistance (R_{on}) with a low gate-source voltage (V_{GS}). Although the chosen MOSFET should be fully switched on at 3.3 V, it was found necessary to drive V_{GS} at 5 V to give a reliable reset pulse.

6. Ground Noise Mitigation

To minimize ground noise during capacitor discharge, a ferrite bead E1 was used to separate the coil reset ground from the rest of the circuit.

COMMON VARIATIONS

Depending on the available supply voltages, the DC-DC converter used to charge the capacitor in the reset pulse generator may be modified. The CN0602 circuit uses an electrolytic capacitor with an ESR of 22 mΩ at 100 kHz. This capacitor can be replaced with a tantalum capacitor, provided its ESR remains within the same range.

CIRCUIT EVALUATION AND TEST

The GMR turn count sensor can be reset by applying an external magnetic field with a field strength greater than 60 mT at the 315° orientation. A common method for generating this field is through the use of an electromagnet. In the CN0602 reference design, this is implemented using a wire coil positioned close to the sensor and embedded within the circuit board. A capacitor is used to charge and discharge through the coil, thereby producing the necessary magnetic field to reset the sensor.

Figure 4 presents oscilloscope plots of key signals involved in achieving a successful reset of the GMR turn count sensor:

- ▶ Channel 1 displays the level-shifted 5 V coil reset signal.
- ▶ Channel 2 shows the original 3.3 V coil reset signal prior to buffering.
- ▶ Channel 3 illustrates the discharge of capacitor C12 through the coil to generate a strong magnetic field.
- ▶ Channel 4 captures the coil current, which peaks at nearly 200 A. This current produces a magnetic field exceeding 60 mT at a 315° orientation, sufficient to reset the GMR sensor.

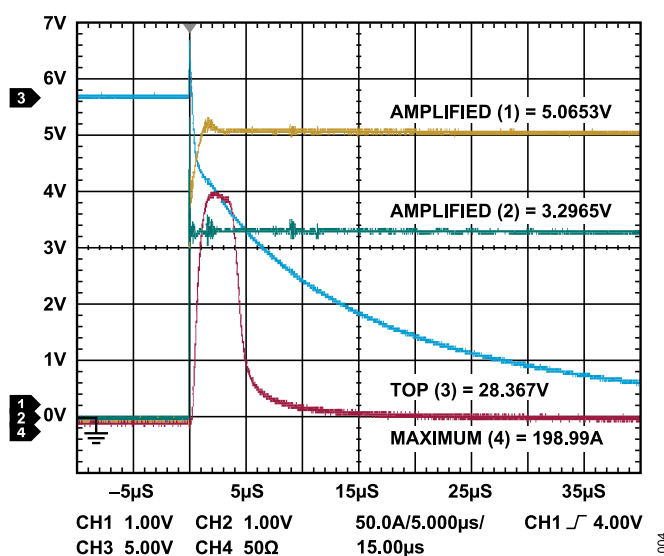


Figure 4. Scope Capture Showing the Current Pulse Used to Excite the Magnetic Reset Coil

LEARN MORE[CN0602 Design Support Package](#)**DATA SHEETS AND EVALUATION BOARDS**[ADMT4000 Data Sheet](#)[LT3467 Data Sheet](#)[LT3467 Evaluation Board](#)**REVISION HISTORY****8/2025—Revision 0: Initial Version****ESD Caution**

ESD (electrostatic discharge) sensitive device. Charged devices and circuit boards can discharge without detection. Although this product features patented or proprietary protection circuitry, damage may occur on devices subjected to high energy ESD. Therefore, proper ESD precautions should be taken to avoid performance degradation or loss of functionality.

(Continued from first page) Circuits from the Lab circuits are intended only for use with Analog Devices products and are the intellectual property of Analog Devices or its licensors. While you may use the Circuits from the Lab circuits in the design of your product, no other license is granted by implication or otherwise under any patents or other intellectual property by application or use of the Circuits from the Lab circuits. Information furnished by Analog Devices is believed to be accurate and reliable. However, Circuits from the Lab circuits are supplied "as is" and without warranties of any kind, express, implied, or statutory including, but not limited to, any implied warranty of merchantability, noninfringement or fitness for a particular purpose and no responsibility is assumed by Analog Devices for their use, nor for any infringements of patents or other rights of third parties that may result from their use. Analog Devices reserves the right to change any Circuits from the Lab circuits at any time without notice but is under no obligation to do so. All Analog Devices products contained herein are subject to release and availability.

