

Introduction

The MAXREFDES1269 demonstrates how to build a DC-DC buck converter using the MAX20098 step-down controller for 5V DC output applications from a 6V to 36V input. This reference design delivers up to 20A at 5V output. The design uses a six-layer board. Table 1 shows an overview of the design specification.

The MAX20098 is a 3.5V to 36V synchronous, step-down DC-DC controller. It uses a current-mode control architecture and can operate in the pulse-width modulation (PWM) or skip-mode control schemes. The device can operate in dropout conditions at a 99% duty cycle. The external sync pin (FSYNC) logic input, under light-load applications, allows the device to operate either in the skip-mode or fixed-frequency forced-PWM (FPWM) mode to minimize electromagnetic interference (EMI). The output voltage is programmable from 1V to 10V with fixed 3.3V/5V options. The feedback (FB) regulation is accurate within $\pm 1\%$ over -40°C to $+125^{\circ}\text{C}$.

Hardware Specification

A small-size, high-efficiency, synchronous step-down converter using the MAX20098 is demonstrated for a 5V/20A application. Table 1 provides an overview of the design specification. Measured data and waveforms from the hardware setup are found in the test results.

Designed–Built–Tested

This document describes the hardware in Figure 1. It provides a detailed, systematic technical guide to design a buck converter using the MAX20098 for high voltage and smaller size. The small board in Figure 1 shows the actual solution size. Refer to the MAX20098 and MAX20098 EV kit data sheets for device operation details. The power supply was built and tested. The details follow later in this document.

Table 1. Design Specification

PARAMETER	SYMBOL	MIN	TYP	MAX
Input Voltage	V_{IN}	6V	14V	36V
Frequency	f_{SW}	400kHz		
Efficiency	η	> 85%		
Output Voltage	V_{OUT}	5V		
Load Step	I_{STEP}	10A to 20A		
Transient Deviation	ΔV_{OUT}	150mV		
Output Voltage Ripple	V_{PK-PK}	50mV		
Output Current	I_{OUT}	0A	—	20A
Output Power	P_{OUT}	100W		

 


Figure 1. MAXREFDES1269 hardware.

Quick Start

Required Equipment

- AC-DC power supply: Chroma Systems 62015L-60-6
- Electronic load: Keithley® 2380-120-60
- Oscilloscope: Teledyne® LeCroy® WaveSurfer® 3024z
- Multimeter: Keithley DMM6500

Procedure

The reference design is fully assembled and tested. Follow these steps to verify the board operation:

- 1) Connect the positive and negative terminals of the power supply to the input connector.
- 2) Set the power-supply voltage to 14V and current limit to 20A.
- 3) Turn on the power supply.
- 4) Verify that V_{OUT} is close to 5V using the DMM.
- 5) Verify that the switching frequency is close to 400kHz by monitoring the switching node voltage with the oscilloscope.

Design Procedure for a High-Efficiency Buck Converter

The design process is divided into the following stages:

- Calculating the switching frequency resistor
- Selecting the output voltage
- Selecting the current-sense resistor
- Selecting the inductor
- Selecting the input capacitor
- Selecting the output capacitor
- Selecting the external MOSFET
- Compensation network
- Selecting the BIAS capacitor
- PCB layout guidelines

This document complements the information in the MAX20098 data sheet.

The following design parameters are used throughout this document:

- V_{IN} = Input voltage
- V_{OUT} = Output voltage
- I_{OUT} = Output current
- f_{SW} = Switching frequency
- D = Duty cycle

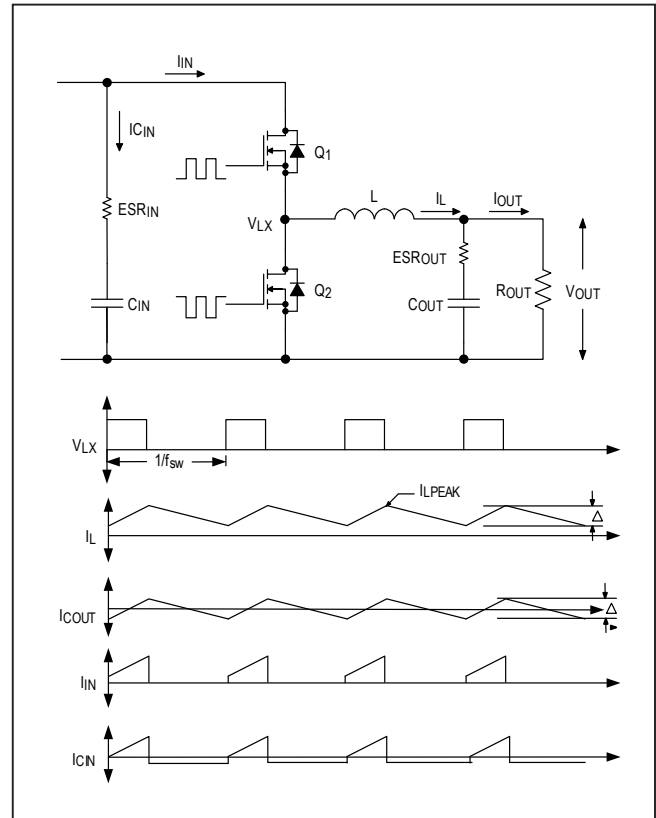


Figure 2. Synchronous buck waveforms.

Keithley is a registered trademark of Keithley Instruments, Inc.
LeCroy is a registered trademark of Teledyne LeCroy, Inc.
Teledyne is a registered trademark of Teledyne Technologies, Inc.
Fluke is a registered trademark of Fluke Electronics, Inc.

Step 1. Calculating the Switching Frequency Resistor

The switching frequency (f_{SW}) is set by a resistor (R1) connected from the FOSC pin to the AGND pin. The R1 value is:

$$R1 = \frac{400\text{kHz} \times 66\text{k}}{f_{SW}}$$

Set R1 = 66.5kΩ for a switching frequency of 400kHz.

Step 2. Selecting the Output Voltage

Set the output voltage using the R15 and R16 resistors. V_{FB} is the internal reference voltage and its typical value is 1V.

$$R15 = R16 \left(\frac{V_{OUT}}{V_{FB}} - 1 \right)$$

Setting $V_{OUT} = 5V$ and $V_{FB} = 1V$ (typ):

$$R15 = R16 \times 4$$

where R16 = 10kΩ, which gives R15 = 40.2kΩ.

Step 3. Selecting the Current-Sense Resistor

Use a ±1% tolerance current-sense resistor between the inductor and output for the best current-sense accuracy and overcurrent protection. This configuration constantly monitors the inductor current, allowing accurate current-limit protection. The overcurrent protection is enabled at 20% higher than the peak current of the inductor:

$$R11 = \frac{V_{LIMIT}}{1.15 \left(I_{OUT} + \frac{\Delta I_{P-P}}{2} \right)}$$

where V_{LIMIT} is 71mV, which is the minimum value of the current-limit threshold from the MAX20098 data sheet.

ΔI_{P-P} is considered as 4A. A margin of 15% is considered for the output current protection. R11 is calculated as 2.81mΩ. A Bourns CSS2H-2512K-3L00F 3mΩ metal element was chosen as the current-sense resistor.

An RC circuit is added across the sense resistor for noise filtering on the current-sense signal. RC is chosen for a 1/10 time constant compared to the switching time. R22 = 47Ω and C25 = 1nF.

Step 4. Selecting the Inductor

The inductor is selected based on the LIR and slope compensation. The LIR is the ratio of the peak-to-peak inductor current ripple to the average value of the inductor current. Typically, an inductor value is chosen to produce a current ripple (ΔI_L) equal to 30% of load current, giving a LIR of 0.3.

The inductance value required to meet the current ripple:

$$\begin{aligned} L1 &= \frac{(V_{IN} - V_{OUT}) \times D}{f_{SW} \times I_{OUT} \times LIR} \\ &= \frac{(36 - 5) \times 5}{36 \times 400 \times 10^3 \times 20 \times 0.3} \\ &= 1.79\mu\text{H} \end{aligned}$$

The inductance value required to meet the slope compensation:

$$L2 = \frac{V_{OUT} \times A_{VCS} \times R_{CS}}{2m}$$

where m is the internal slope compensation, A_{VCS} is the current-sense gain (13V/V), and R_{CS} is the current-sense resistor value.

$$\begin{aligned} L2 &= \frac{5 \times 13 \times 3 \times 10^{-3}}{2 \times 36 \times 10^3} \\ &= 2.71\mu\text{H} \end{aligned}$$

The inductance value to meet both the equations:

$$\begin{aligned} L &= \text{Max}(L1, L2) \\ &= 2.71\mu\text{H} \end{aligned}$$

The required value of inductance is 2.71μH.

Additionally, ensure the following relationships are satisfied:

$$I_{LSAT} > I_{PEAK} = I_{OUT} + \frac{\Delta I_L (P-P)}{2}$$

and

$$I_{LRMS} > I_{RMS} = \sqrt{I_{OUT}^2 + \frac{1}{12} \Delta I_L (P-P)^2}$$

where

$$\Delta I_L (P-P) = \frac{V_{OUT}}{f_{SW} \times L} \left(1 - \frac{V_{OUT}}{V_{IN}} \right)$$

and

$$I_{PEAK} = 22A$$

and

$$I_{RMS} = 20.075A$$

The Coilcraft® XAL1010-472ME with a 4.7μH inductance, and 25.4A I_{LSAT} and 24A I_{LRMS} saturation current is chosen.

Coilcraft is a registered trademark of Coilcraft, Incorporated.

Step 5. Selecting the Input Capacitor

The input capacitor RMS current requirement (I_{RMS}) is defined as:

$$I_{RMS} = I_{OUT(MAX)} \times \frac{\sqrt{V_{OUT}(V_{IN} - V_{OUT})}}{V_{IN}}$$

where $I_{OUT(MAX)}$ is the maximum load current. I_{RMS} has a maximum value when the input voltage equals twice the output voltage ($V_{IN} = 2 \times V_{OUT}$). So, $I_{RMS} = I_{OUT(MAX)}/2$. The required RMS current rating of the input capacitor is 10A.

The input-voltage ripple is composed of ΔV_Q (caused by the capacitor discharge) and ΔV_{ESR} (caused by the ESR of the input capacitor). The following equations show the ESR and capacitor requirement for a target voltage ripple at the input:

$$ESR_{IN} = \frac{\Delta V_{ESR}}{\left(I_{OUT} + \frac{\Delta I_{P-P}}{2}\right)}$$

$$C_{IN} = \frac{I_{OUT} \times \frac{V_{OUT}}{V_{IN}}}{\Delta V_Q \times f_{sw}}$$

I_{OUT} is the maximum output current in amps, ΔI_{P-P} is the peak-to-peak inductor current in amps, and f_{sw} is the switching frequency. The input capacitor is designed for an input voltage ripple of 3%. ΔV_{ESR} is the input voltage ripple due to ESR, which is 0.054V. ΔV_Q is the input voltage ripple caused by the capacitor discharge, which is 0.126V. Here, $ESR_{IN} = 2.2m\Omega$ and $C_{IN} = 99\mu F$. Some margin must be reserved due to the capacitor's DC bias and temperature characteristics. A combination of ceramic and electrolytic capacitors is used. Electrolytic capacitance = $3 \times 47\mu F$ and ceramic capacitance = $2 \times 4.7\mu F$ meet both the capacitance and RMS current requirements.

Step 6. Selecting the Output Capacitor

The required ESR and capacitance value due to load transient are:

$$ESR_{OUT} = \frac{\Delta V_{ESR}}{I_{STEP}}$$

$$C_{OUT} \geq I_{STEP}^2 \times \frac{L}{2 \times (V_{sup} - V_{OUT}) \times D_{MAX} \times \Delta V_Q}$$

$$+ I_{STEP} \times \frac{D_{MIN}}{2 \times \Delta V_Q \times f_{sw}}$$

I_{STEP} is the load step current in amps. The output capacitor is designed for an output voltage overshoot of 3% for a 50% load change. ΔV_{ESR} is the output voltage overshoot

due to ESR, which is 0.045V. ΔV_Q is the output voltage overshoot caused by the capacitor discharge, which is 0.105V. Here, $ESR_{OUT} = 4.5m\Omega$ and $C_{OUT} = 315\mu F$. Some margin must be reserved due to the capacitor's DC bias and temperature characteristics. A combination of ceramic and electrolytic capacitors is used. Electrolytic capacitance = $2 \times 220\mu F$ and ceramic capacitance = $5 \times 4.7\mu F + 100\mu F$. A higher value of capacitance is used at the output to create the point-of-load application.

The output voltage ripple due to the ESR and capacitance are:

$$\Delta V_{ESR} = ESR_{OUT} \times \Delta I_{PK-PK}$$

$$\Delta V_Q = \frac{\Delta I_{P-P}}{8 \times C_{OUT} \times f_{sw}}$$

where ΔI_{P-P} is the peak-to-peak inductor current in amps and f_{sw} is the switching frequency. ΔV_{ESR} is calculated as 1.5mV and ΔV_Q is 2mV. So, the total output voltage ripple is 3.5mV, which is within the specified limit of 50mV.

Step 7. Selecting the External MOSFET

Two external MOSFETs are required for the buck architecture supported by the MAX20098. The MOSFETs must be selected based on the critical parameters such as on-resistance, breakdown voltage, output capacitance, and input capacitance. A low $R_{DS(ON)}$ reduces the conduction losses in the MOSFET and a small gate/output capacitance reduces the switching losses.

Typically, a lower $R_{DS(ON)}$ MOSFET has higher gate charge for the same breakdown voltage. Hence, a compromise is made depending on the conditions to which the MOSFET is subjected. The Infineon® IAUC100N10S5L040 n-channel, 100V MOSFETs were selected here. This MOSFET has a very low $R_{DS(ON)}$ of 4m Ω and gate charge of 60nC to ensure higher efficiency for the converter.

Step 8. Compensation Network

The IC uses the current-mode control scheme for a buck controller. A series resistor (R_2) and a capacitor (C_5) are used for a stable, high-bandwidth loop in applications where ceramic capacitors are used for output filtering. The frequency of the zero created by the capacitance and ESR is lower than the desired closed-loop cross-over frequency for other types of capacitors due to the higher capacitance and ESR. Add another compensation capacitor (C_7) from COMP to AGND to cancel this zero to stabilize a non-ceramic output-capacitor loop.

$R_2 = 68k\Omega$, $C_5 = 2.7nF$, and $C_7 = 10pF$ were the chosen values. An additional RC circuit was added across the top feedback resistor to boost the phase margin. $R_{17} = 2.7k\Omega$ and $C_{24} = 330pF$ were the selected values.

Infineon is a registered trademark of Infineon Technologies AG.

Step 9. Selecting the BIAS capacitor

The internal circuitry of the IC requires a 5V bias supply. An internal 5V linear regulator (BIAS) generated this supply. The BIAS pin is bypassed with two 2.2 μ F ceramic capacitors in parallel to guarantee stability under full load.

Step 10. PCB Layout Guidelines

A good PCB layout is critical to achieve low switching power losses, and a clean, stable operation. Use a multilayer board for better noise immunity. Follow the guidelines for a good PCB layout:

- All the connections carrying pulsed currents must be very short and as wide as possible. The inductance of these connections must be kept to an absolute minimum due to the high di/dt of the currents. The inductance of a current-carrying loop is proportional to the area enclosed by the loop. The inductance is reduced if the loop area is made very small. Also, small current loop areas reduce the radiated EMI.
- A ceramic input filter capacitor must be placed close to the IC's V_{IN} pins. Also, its ground loop to the PGND must be short. This eliminates as much trace inductance effects as possible and gives the IC a cleaner voltage supply. A bypass capacitor for the V_{CC} pin also must be placed close to the pin to reduce the effects of trace impedance. Its ground loop to the PGND must be short.

- The analog small-signal ground and power ground for switching currents must be kept separate when routing circuitry around the IC. They must be connected where switching activity is minimal, typically the return terminal of the V_{CC} bypass capacitor. Doing so keeps the analog ground quiet. The ground plane must be kept continuous and unbroken as far as possible. No trace-carrying, high-switching current must be placed directly over any ground plane discontinuity.
- The PCB layout also affects the thermal performance of the design. A few thermal vias that connect to a large ground plane must be provided under the IC's exposed pad to dissipate heat efficiently. The PCB size, copper thickness, and board layer numbers affect the temperature dissipation capacity of the board. It can support a 10A load current with 1oz of copper, six layers, and an 88mm x 45mm board for this reference design.

Design Resources

Download the complete set of [Design Resources](#) including the schematics, bill of materials, PCB layout, and test files.

Revision History

REVISION NUMBER	REVISION DATE	DESCRIPTION	PAGES CHANGED
0	8/20	Initial release	—

Maxim Integrated
www.maximintegrated.com

Maxim Integrated cannot assume responsibility for use of any circuitry other than circuitry entirely embodied in a Maxim Integrated product. No circuit patent licenses are implied. Maxim Integrated reserves the right to change the circuitry and specifications without notice at any time. The parametric values (min and max limits) shown in the Electrical Characteristics table are guaranteed. Other parametric values quoted in this data sheet are provided for guidance.

© 2020 Maxim Integrated Products, Inc. All rights reserved. Maxim Integrated and the Maxim Integrated logo are trademarks of Maxim Integrated Products, Inc., in the United States and other jurisdictions throughout the world. All other marks are the property of their respective owners.