



MAX25614 Design

EE-Sim® OASIS Schematic Documentation




maxim
integrated™

Schematic

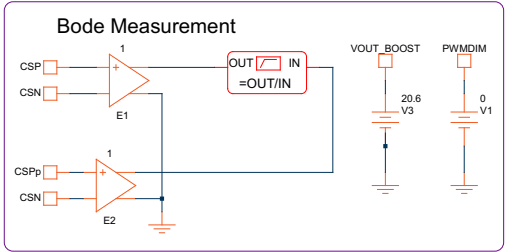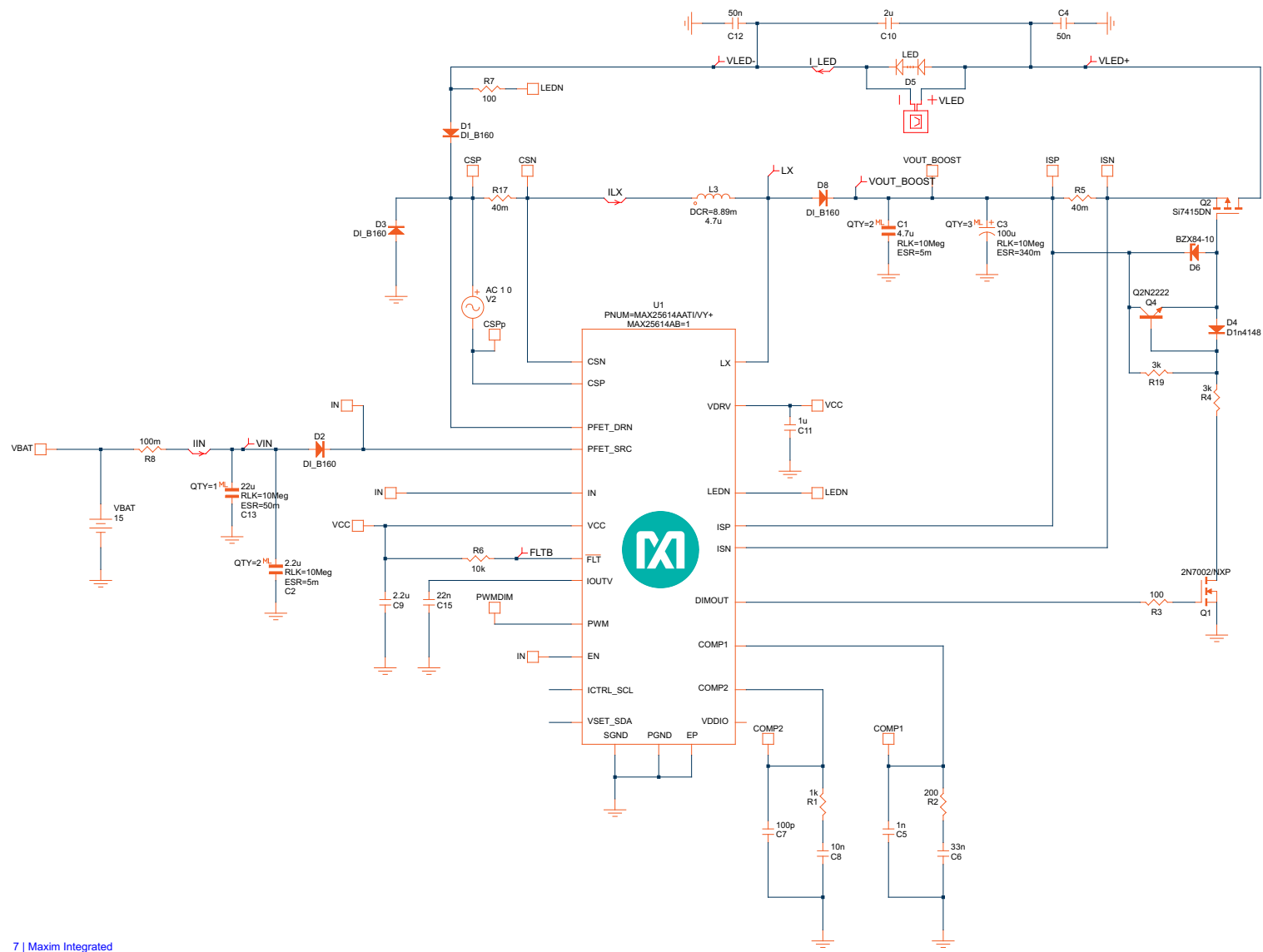


This schematic is used for AC analysis of the LED Driver in Boost mode

Gain and Phase plots for Boost Mode

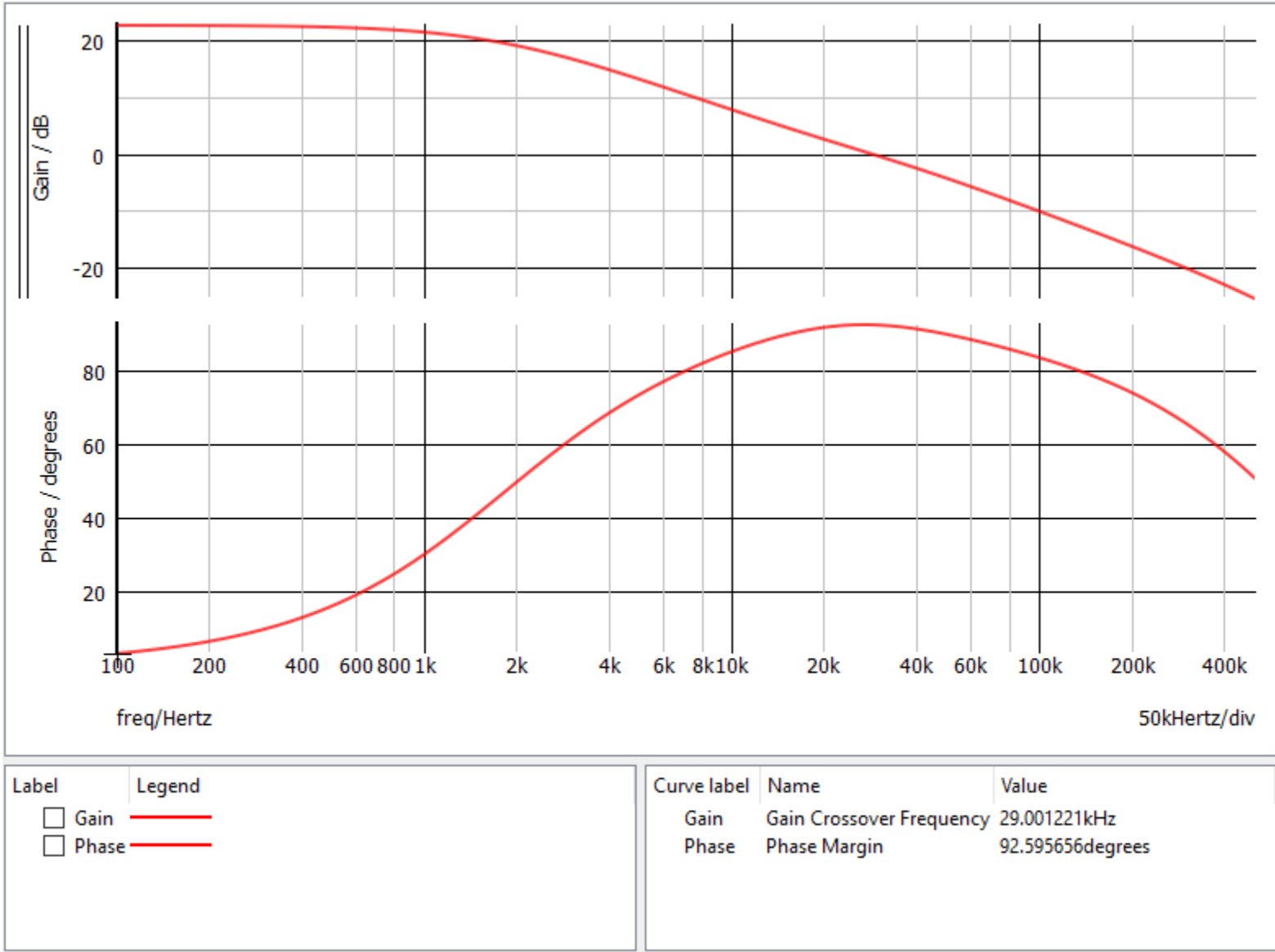


Schematic

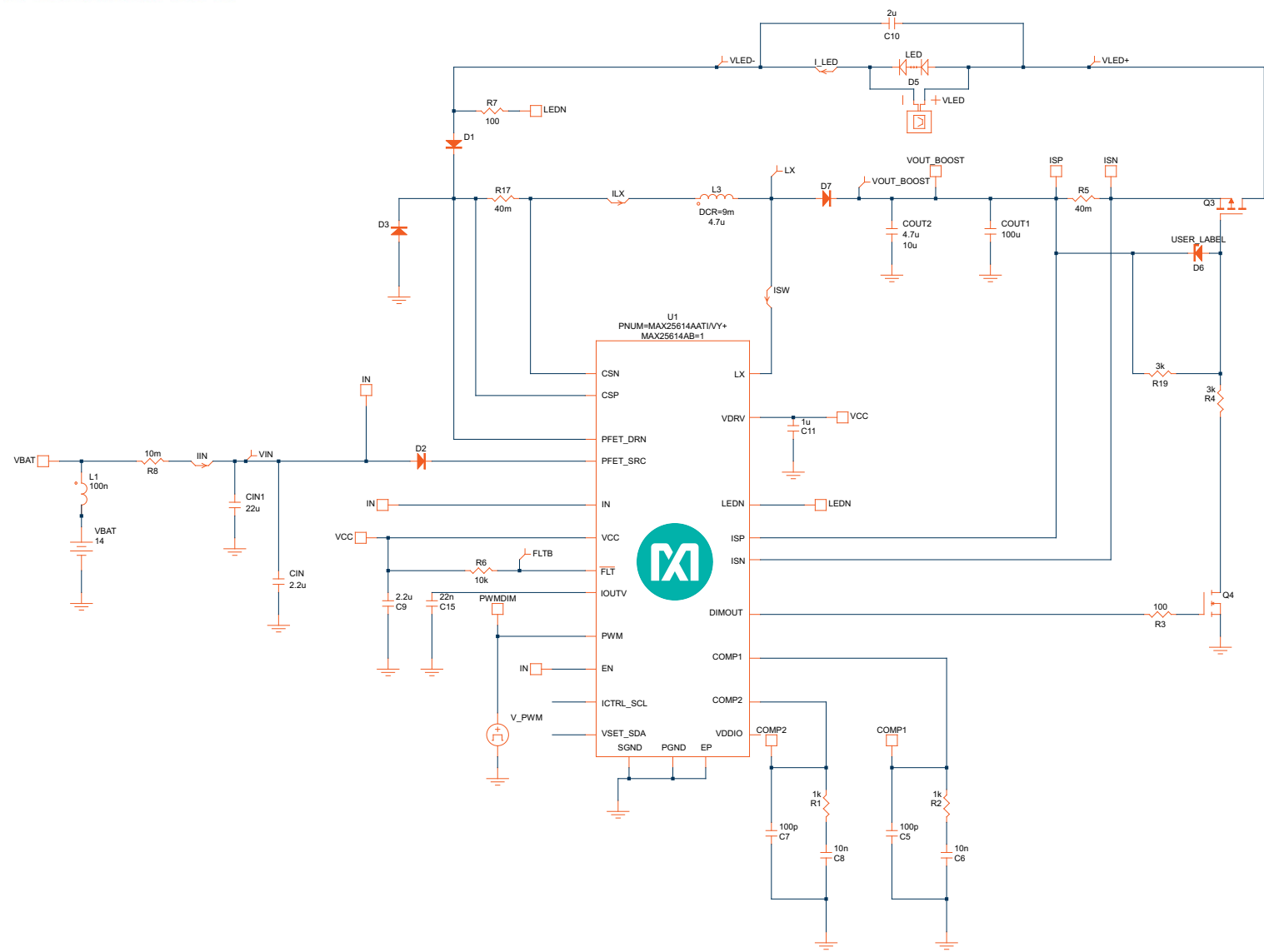


This schematic is used for transient response analysis.

Switching Waveforms

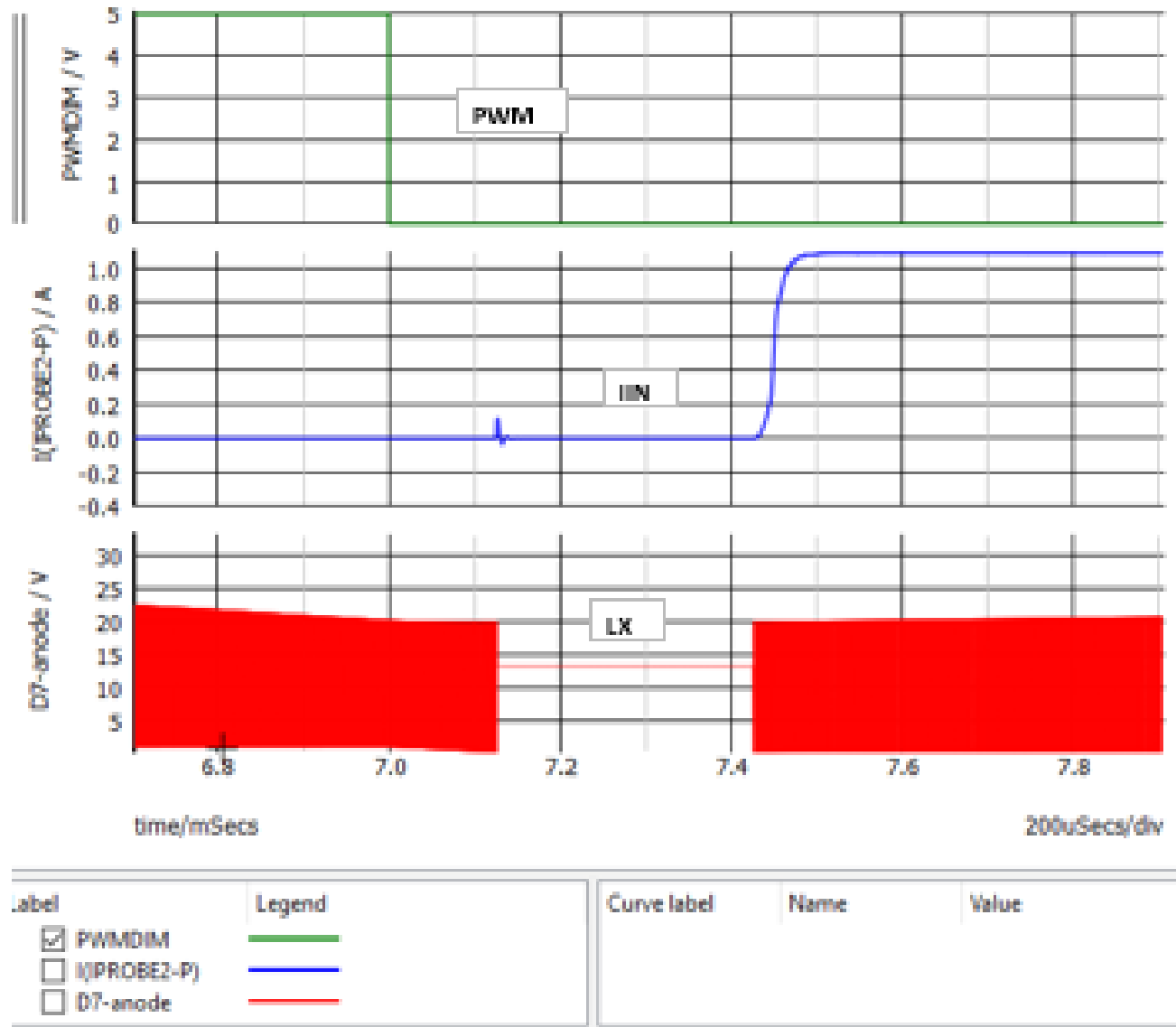

Transient Waveform

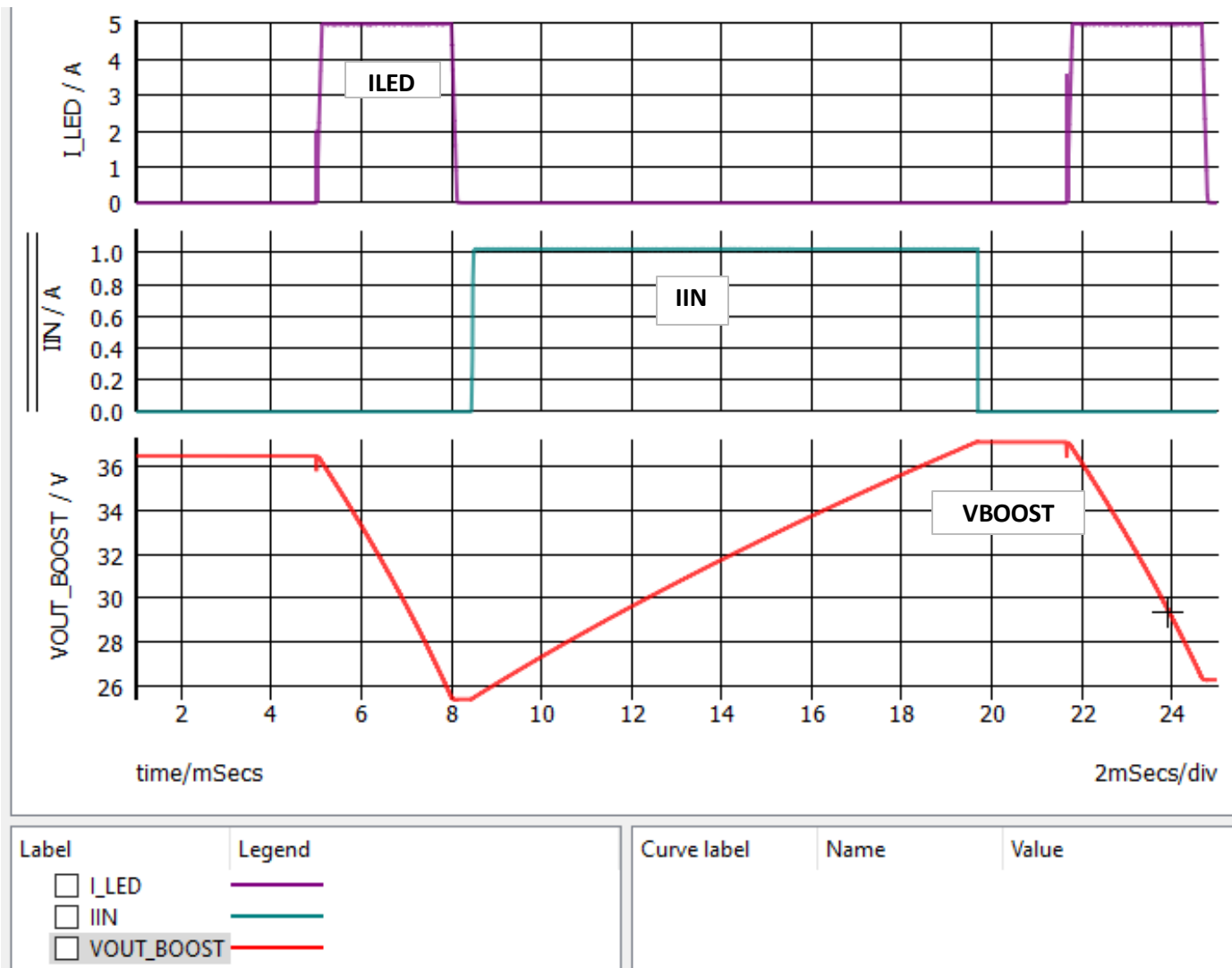

Start-Up Transient

