



ONE TECHNOLOGY WAY • P.O. BOX 9106 • NORWOOD, MASSACHUSETTS 02062-9106 • 617/329-4700

AN-132 APPLICATION NOTE

OP-470 SPICE Macro-Model

by Joe Buxton

INTRODUCTION

This application note describes the SPICE macro-model for the OP-470 very low noise quad operational amplifier. This model was tested with and is compatible with PSpice* and HSpice**. The schematic and net-list are included here so that the model can easily be used. This model can accommodate multiple frequency poles and zeros, which is an advanced concept that results in more accurate AC and transient responses. For example, 6 poles and 2 zeros are required to accurately model the OP-470, which this model can easily accommodate.

This macro-model represents one of the four amplifiers on one chip. To use the quad amplifiers, the simulation circuit needs only to call up the model four separate times and specify the same power supplies each time. Throughout the OP-470 macro-model RC networks produce multiple poles which simulate the amplifiers AC behavior. The stages, which each contain a single pole or a pole-zero pair, are separated from each other by voltage-controlled current sources so that it is easy to set individual pole locations. The only nonlinear elements in the entire model are two NPN transistors which comprise the input stage, and diodes for voltage clamping. Limiting the model to almost entirely ideal, linear circuit elements significantly reduces simulation time and simplifies model development.

MODEL DESCRIPTION

The schematic (Figure 1) and net-list (Figure 2) describe the complete OP-470 model. This model breaks up the OP-470 into many distinct stages as described below:

INPUT STAGE

To correctly model the OP-470's input behavior, the model uses a differential pair of NPN transistors biased with a 1mA current source (Figure 1a). To keep this stage as simple as possible, only the forward beta, β_F , is specified in the NPN-BJT model. This is chosen to give the correct input bias current, I_B . The voltage limiting network of the OP-470 input is added with the diodes in series with the voltage source across the inputs. A voltage source is used instead of another diode to save computer time.

As for nonideal behaviors of the input stage, such as V_{OS} , I_{OS} , and C_{IN} , these are modelled with external circuit elements. For example, no junction capacitance is specified for the NPN model, therefore a capacitor, C_{IN} , is added across the inputs. Furthermore, since the input NPNs in this model are perfectly matched, V_{OS} and I_{OS} error sources are added using an external voltage source and current source, respectively. Lastly, the collector resistors R_3 and R_4 are chosen to be $1/g_m$ of the NPN transistors to give a gain of unity in the input stage. C_2 is added to create one of the secondary poles in the model.

GAIN STAGES

The open-loop gain of the OP-470 is achieved entirely in the gain stage (Figure 1b), and all other stages have unity-gain. The gain is taken in two steps due to a limit for only one step based on the combination of the slow rate, dominant pole, and open-loop gain. The voltage-controlled current sources, G_1 and G_2 , have scaled transconductances that, when combined with R_7 and R_8 , give the gain in the first step at node 12. The gain in the second step is produced the same way, and together the two steps give the open loop gain of 1,000,000. The current sources G_1 and G_2 are controlled by the voltage drops across R_3 and R_4 in the input stage providing the differential to single ended voltage conversion. C_3 and C_4 create the dominant pole at 5.5Hz and model the amplifier's slow rate. Lastly, the diodes, D_5 and D_6 and voltage sources V_3 and V_4 , are necessary to clamp the voltage of node 15 below the power supplies. Because the next stage (Figure 1c) has unity-gain and its voltage is controlled by the voltage at node 15, then it too is clamped, at node 18, below the power supplies. The same is true for subsequent stages, including the output, such that the output voltage is clamped to within the specified voltage range.

POLE STAGES

In addition to the poles in the input stage and the gain stage additional poles are easily added with separate stages. The pole and pole-zero stages (Figure 1c-e, g) have unity-gain, which is result of the g_m of the voltage-controlled current sources being the reciprocal of the resistors. The pole and zero locations are determined by the resistor and capacitor or inductor values for each stage.

* PSpice is a registered trademark of MicroSim Corporation.
** HSpice is a trademark of Meta-Software, Inc.

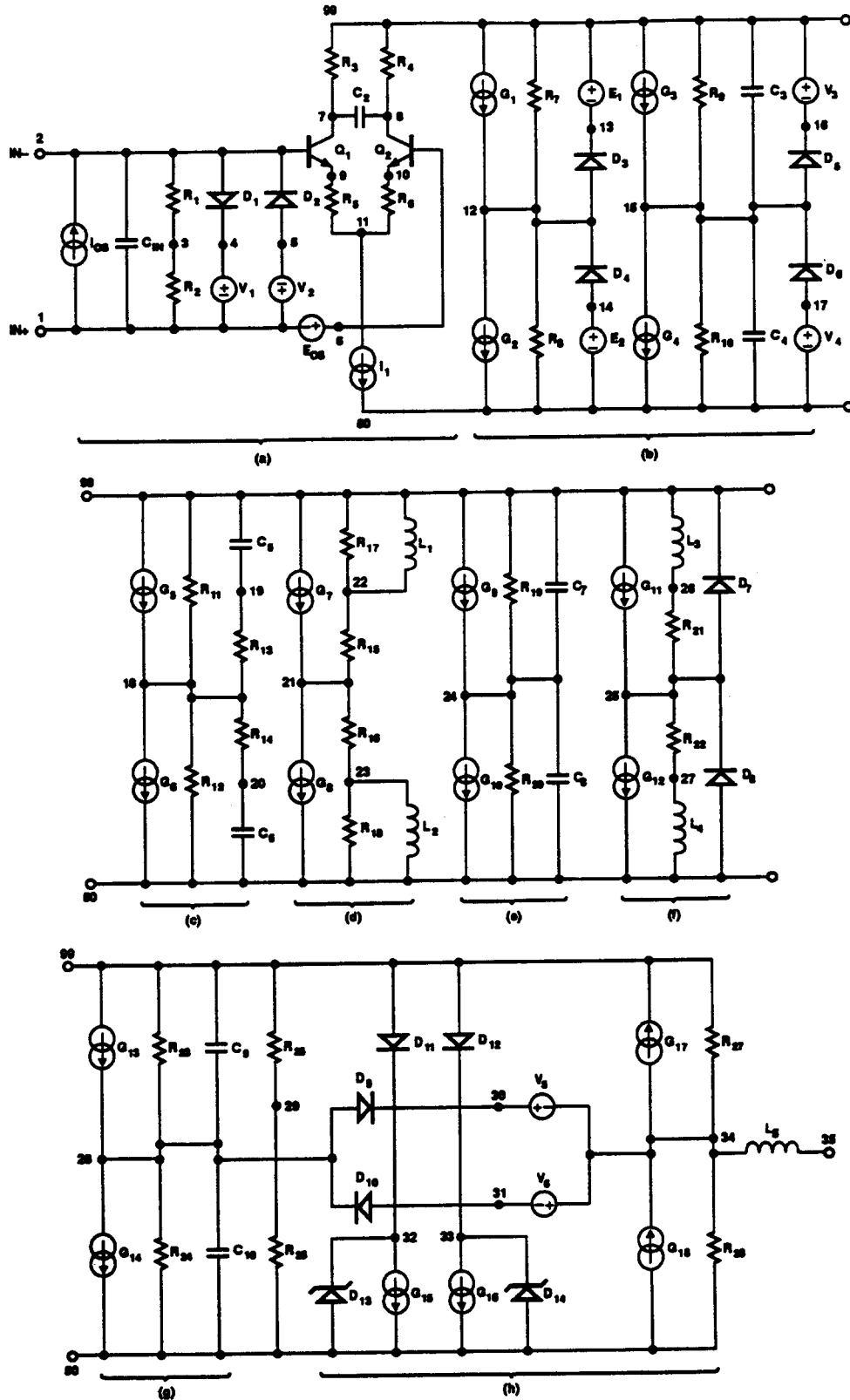


FIGURE 1: OP-470 SPICE Macro-Model Schematic and Node List

OP-470 MACRO-MODEL © ADI 1990

*SUBCKT OP-470 1 2 35 99 50

* INPUT STAGE & POLE AT 60 MHZ

```
R1 2 3 2E5
R2 1 3 2E5
R3 7 99 101.6
R4 8 99 101.6
CIN 1 2 2E-12
C2 7 8 13.05E-12
I1 11 50 1E-3
IOS 1 2 3E-9
EOS 6 1 POLY(1) 25 29 1E-4 1
Q1 7 2 9 QX
Q2 8 6 10 QX
R5 9 11 50
R6 10 11 50
D1 2 4 DX
V1 4 1 0.7
V2 1 5 0.7
D2 5 2 DX
```

* FIRST GAIN STAGE

```
R7 12 99 1E6
R8 12 50 1E6
G1 99 12 7 8 64.1E-6
G2 12 50 8 7 64.1E-6
D3 12 13 DX
D4 14 12 DX
E1 99 13 POLY(1) 99 29 -2.6 1
E2 14 50 POLY(1) 29 50 -2.6 1
```

* FIRST GAIN STAGE & DOMINANT POLE AT 6.8 HZ

```
R9 15 99 46.8E6
R10 15 50 46.8E6
C3 15 99 500E-12
C4 15 50 500E-12
G3 99 15 POLY(1) 12 29 380E-6 333.3E-6
G4 15 50 POLY(1) 29 12 380E-6 333.3E-6
V3 99 16 1.9
V4 17 50 1.9
D5 15 16 DX
D6 17 15 DX
```

* POLE AT ZERO AT 1.9 MHZ/3.5 MHZ

```
R11 18 99 1E6
R12 18 50 1E6
R13 18 19 1.19E6
R14 18 20 1.19E6
C5 19 99 38.21E-15
C6 20 50 38.21E-15
G5 99 18 15 29 1E-6
G6 18 50 29 15 1E-6
```

* ZERO-POLE AT 5 MHZ/10 MHZ

```
R15 21 22 1E6
R16 21 23 1E6
R17 99 22 1E6
R18 50 23 1E6
L1 99 22 15.92E-3
L2 50 23 15.92E-3
G7 99 21 18 29 1E-6
G8 21 50 29 18 1E-6
```

* POLE AT 10 MHZ

```
R19 24 99 1E6
R20 24 50 1E6
C7 24 99 15.9E-15
C8 24 50 15.9E-15
G9 99 24 21 29 1E-6
G10 24 50 29 21 1E-6
```

* COMMON-MODE GAIN NETWORK WITH ZERO AT 100 HZ

```
R21 25 26 1E6
R22 25 27 1E6
L3 26 99 1.592E3
L4 27 50 1.592E3
G11 99 25 3 29 1E-12
G12 25 50 29 3 1E-12
D7 25 99 DX
D8 50 25 DX
```

* POLE AT 50 MHZ

```
R23 28 99 1E6
R24 28 50 1E6
C9 28 99 3.18E-15
C10 28 50 3.18E-15
G13 99 28 24 29 1E-6
G14 28 50 29 24 1E-6
```

* OUTPUT STAGE

```
R25 29 99 20E3
R26 29 50 20E3
R27 34 99 300
R28 34 50 300
L5 34 35 1E-6
G15 32 50 28 34 3.33E-3
G16 33 50 34 28 3.33E-3
G17 34 99 99 28 3.33E-3
G18 50 34 28 50 3.33E-3
V5 30 34 1.3
V6 34 31 1.3
D9 28 30 DX
D10 31 28 DX
D11 99 32 DX
D12 99 33 DX
D13 50 32 DX
D14 50 33 DX
```

* MODEL USED

```
.MODEL QX NPN (BF = 166667)
.MODEL DX D (IS = 1E-15)
.MODEL DY D (IS = 1E-15 BV = 50)
.ENDS OP-470
```

FIGURE 2: OP-470 SPICE Net-List

COMMON-MODE STAGE

The common-mode error is based on the common-mode voltage of the input, which is created by the two input resistors, R_1 and R_2 . This voltage is referenced by G_{11} and G_{12} in the common-mode stage (Figure 1f). The transconductances of these two sources are scaled such that, in combination with R_{21} and R_{22} , the V_{CM} is attenuated by the CMRR of 120dB. This error voltage is then inserted back into the input stage as part of the offset voltage, which is done by the voltage controlled voltage source E_{OS} . The inductors, L_3 and L_4 , model the pole in the CMR versus frequency response of the OP-470.

OUTPUT STAGE

The output stage (Figure 1h) is modelled as an ideal output with an output resistance, R_{27} in parallel with R_{28} . An inductor, L_5 , is added to model the rising output impedance of the emitter-follower output stage with frequency. The voltage sources V_5 and V_6 , and diodes D_9 and D_{10} , combine to limit the voltage across the resistors, thus limiting the output current, I_{OUT} to 30mA.

PARAMETERS THAT ARE NOT MODELLED

To keep the OP-470 model as simple as possible and thus save computer and development time, not all features of the op amp were modelled as listed below:

- PSRR
- Crosstalk
- No Limits on Power Supply Voltages
- Maximum Input Voltage Range
- Temperature Effects (i.e., model parameters are assumed at 25°C)
- Input Noise Voltage and Current Sources
- Parameter Variations for Monte Carlo Analysis (i.e., all parameters are typical only)

These parameters are considered second-order effects and are not considered necessary for circuit simulation under normal

operating conditions. However, users can easily add these functions as needed.

MODEL PERFORMANCE

The graphs on these next two pages compare the actual responses of the OP-470 to the SPICE analysis under various load and gain conditions. To show the accuracy of the model's frequency response, it was tested with different gains. Shown below are the gain-phase plots for an open-loop gain (Figures 3 and 4) and a closed-loop gain of -1 (Figures 5 and 6). The actual responses (part "a" of each figure), which were measured using a network analyzer, show very close agreement to the SPICE simulations (part "b" of each figure). This agreement holds true for both the gain and phase curves, which demonstrates the accuracy of the model's frequency response.

The model can also accurately simulate the OP-470's transient response. The comparisons to actual results were done with the amplifier in a closed-loop gain of +1 with a 155pF capacitive load (260pF load for large signal) and a 2kΩ feedback resistor. The capacitive load was used to create the damped oscillations in the small and large-signal responses. Because of the multiple poles and zeros, the model's small-signal transient response (Figure 7b) shows close resemblance to the actual response (Figure 7a). The large-signal response (Figure 8) again shows good accuracy. Notice in the large-signal response that the slew rate is accurately modelled, and that the "bump" before the amplifier starts slewing is also modelled. As can be seen from the figures, the model agrees closely with the actual device's performance. This accurate transient response, along with the accurate AC response, makes the OP-470 macro-model a powerful tool in analyzing circuit stability and AC behavior under various gains and load conditions.

 


FIGURE 3: Gain Plots, Open-Loop Gain (a. Actual, b. Simulated)

 


FIGURE 4: Phase Plots, Open-Loop Gain (a. Actual, b. Simulated)

 


FIGURE 5: Gain Plots, Closed-Loop Gain of -1 (a. Actual, b. Simulated)

 


FIGURE 6: Phase Plots, Closed-Loop Gain of -1 (a. Actual, b. Simulated)

 


FIGURE 7: Small-Signal Transient Response, Gain = +1, 155pF Capacitive Load (a. Actual, b. Simulated)

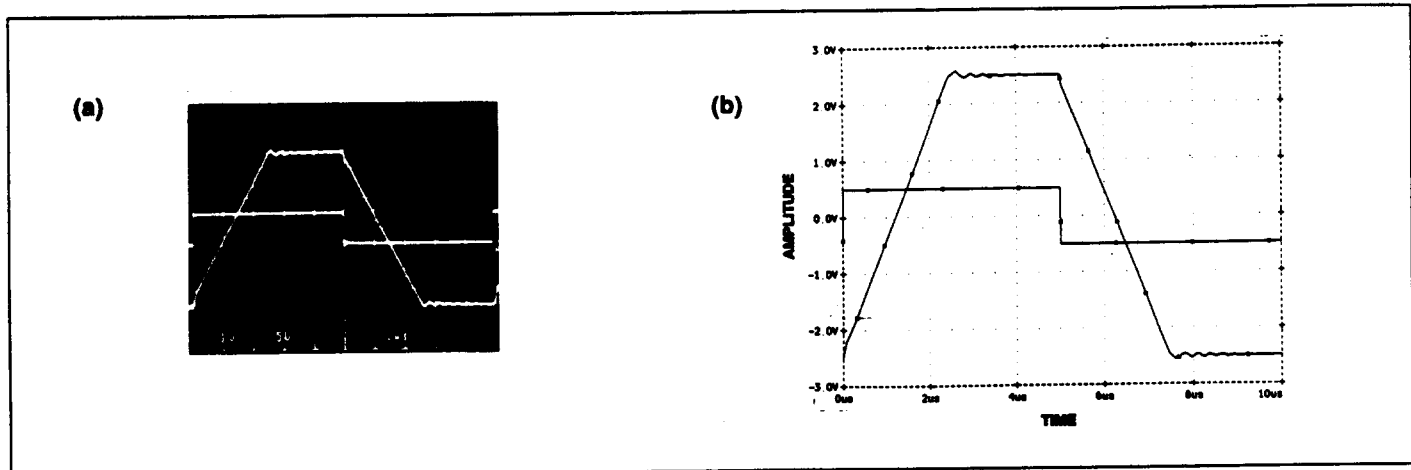


FIGURE 8: Large-Signal Transient Response, Gain = +1, 260pF Capacitive Load (a. Actual, b. Simulated)