

# design FAQs

Op-Amp  
Noise

Don Tuite  
Analog/Power Editor

## FREQUENTLY ASKED QUESTIONS

### Why the fresh emphasis on low-noise amplification?

Some of it is an issue of signal-to-noise ratio (SNR). Today, sensor voltages and device operating voltages are lower than they used to be, so noise is larger in relation to signal levels. Another factor is that the data converters being used have higher resolutions than in the past, so they need cleaner inputs.

### What kind of noise are we talking about?


This noise is intrinsic to the amplifier or generated by associated passive components and then amplified. External noise is a system-level issue.

### What are the sources of this noise?

Johnson (thermal) noise is generated by input and feedback resistors ( $e_{n,R2}$ ) and the amplifier's intrinsic voltage noise ( $e_n$ ) and current noise ( $i_n$ ) (Fig. 1). The equation for noise referred to in the circuit input (NoiseRTI) in Figure 1 shows the contributions of all the noise sources. The "k" factor in the expression's resistor noise is Boltzman's constant. T is absolute temperature (Kelvin), and R is resistance in ohms. As a rule of thumb, a 1-kΩ resistor generates a noise of 4 nV/√Hz at room temperature higher than some modern op amps.
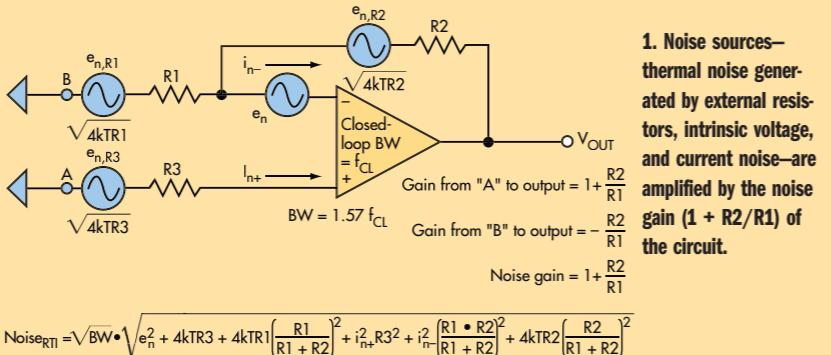
### How is noise expressed?

To allow all noise sources to be combined in a simple square root of the sum of the square's expres-



sion, baseband noise specs are given in terms of nV (or pA)/√Hz. That's possible as long as the noise sources are uncorrelated so the probability of any given amplitude across the frequency spectrum follows a normal (Gaussian) distribution.

### Noise isn't really constant across all frequencies, is it?

No. Both  $e_n$  and  $i_n$  have two components (Fig. 2a): low-frequency "1/f" noise, whose spectral density increases at 3 dB/octave as frequency decreases, and spectrally flat "white" noise at higher frequencies. For applications where 1/f noise is most critical, data sheets may also show the peak-to-peak noise across a limited bandwidth, e.g., 0.1 to 10 Hz (Fig. 2b).

### What is the "corner frequency," and why is it important?

The frequency at which the 1/f noise spectral density equals the white noise is known as the 1/f corner frequency ( $F_C$ ). It is obtained by extending the 1/f and white-noise portions of the noise plot and noting the point at

which the lines cross. It is important as a figure of merit. Also, the 1/f corner frequency isn't necessarily the same for voltage and current noise. Yet it often is only specified for voltage noise.



### How can I use this information in choosing a low-noise amplifier?

Consider the frequency band of interest and relate the rms noise within that bandwidth to your system requirements. Because noise is specified in terms of the square root of frequency, the various noise contributions can be evaluated as the square root of the sum of their squares. Thus, the total rms voltage noise,  $e_{n,\text{rms}}$ , in the bandwidth  $F_L$  to  $F_H$ , is simply:

$$e_{n,\text{rms}} = e_{n,w} \sqrt{F_C \cdot \ln \left( \frac{F_H}{F_L} \right) + (F_H - F_L)}$$

where  $e_{n,w}$  is the broadband white noise,  $F_C$  is the 1/f corner frequency, and  $F_L$  and  $F_H$  define the measurement bandwidth of interest.

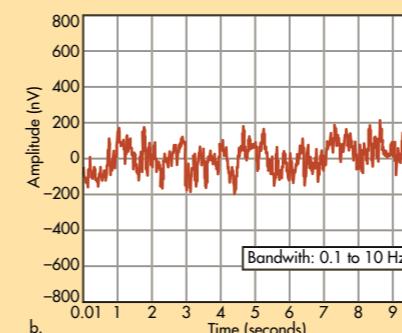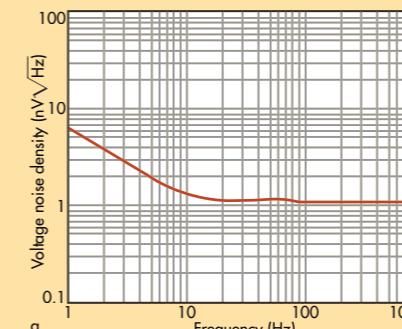Generally, any noise component that is four or five times higher than any of the others becomes dominant, and the rest can be disregarded. So at higher frequencies,



**2. Above the corner frequency, intrinsic noise has an essentially constant density. Between the corner frequency and 0 Hz, it rises at 3 dB/octave (a). Where 1/f noise is critical (b), data sheets may show actual peak-to-peak noise. Both of these plots come from the data sheet for Analog Devices' AD8599.**

$F_C \ln(F_H/F_L)$  becomes insignificant, and the total rms noise is simply the white noise times the square root of the frequency difference. In fact, if  $F_H$  is very much higher than  $F_L$ , the total rms noise is simply the white noise times the square root of  $F_H$ .

On the other hand, when you're operating in the 1/f region, the total rms noise is the noise level at the corner frequency (i.e., the white noise level) times the square root of the corner frequency times  $\ln(F_H/F_L)$ .

### What about current noise?

The fourth and fifth terms in the equation in Figure 1 show that when current noise flows through an impedance, it generates a noise voltage that adds to the other noise voltages in the square root of the sum of the squares. Also, while voltage noise is the first spec designers look at, if circuit impedance levels are above  $e_n/i_n$  (sometimes called the amplifier's "characteristic noise resistance"), current noise dominates.

ED ONLINE 17448


# product Q&As

## 36-V Dual Op Amp Offers 1 nV/√Hz and -105-dB THD @ 20 kHz

The AD8599 offers low noise of 1 nV/√Hz at 1 kHz and -105-dB low harmonic distortion, making it ideal for total dc to high-fidelity audio, medical, and precision instrumentation accuracy requirements. The AD8599 is unity-gain stable and has 60% lower voltage noise than the nearest competitor, while providing 110-dB PSRR

to achieve designs for low-noise preamps and gain staging. Each op amp delivers excellent dynamic response with a slew rate of 15 V/μs and 10-MHz unity-gain bandwidth. The AD8599 is designed using ADI's iPolar™ process technology, which combines the advantages of precision Bipolar and JFET and optimizes device size, performance, and power consumption.
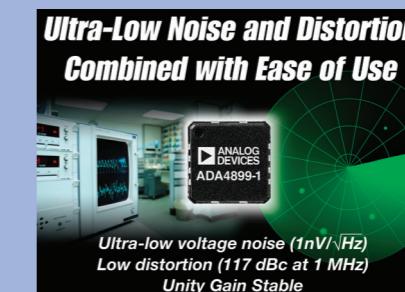
### 1-nV/√Hz, Unity-Gain Stable, Voltage Feedback Op Amp



High-resolution system design often requires performance tradeoffs between noise and distortion. The ADA4899-1 unity-gain stable op amp achieves 1-nV/√Hz voltage noise and 16- to 18-bit distortion levels at 1 MHz (117-dBc SFDR). It drives 100-Ω loads at breakthrough performance levels with only 15 mA of supply current. With the wide supply voltage range (4.5 to 12 V), low offset voltage (230 μV max), wide bandwidth (600 MHz), and slew rate (310 V/μs), the ADA4899-1 works in the most demanding applications.

Part Number	# Amps	V <sub>S</sub> (V)	BW (MHz)	Slew Rate (V/μs)	Noise (nV/√Hz)	V <sub>os</sub> max (mV)	I <sub>B</sub> max (mA)	I <sub>S</sub> /AMP typ (mA)	Package	Pricing (SUS/1K)
<b>High-Speed Op Amps</b>										
ADA4841-1/2	1/2	2.7 to 12	80	13	2.1	300 μV	5.3 μA	1.2	SOT-23/ MSOP/SOIC	\$1.59/ \$2.29
ADA4899-1	1	4.5 to 12	600	310	1	230 μV	1 μA	14.7	LFCSP/SOIC	\$1.89
AD8099	1	4.5 to 12	510	1350	0.95	0.5 mV	2 μA	15	LFCSP/SOIC	\$1.98
<b>Precision Op Amps</b>										
AD8599	2	9 to 36	10	15	1 @ 1 kHz	120 μV	180 nA	4.7	SOIC	\$3.20
ADA4004-4	4	10 to 36	12	2.7	1.8 @ 1 kHz	140 μV	85 nA	1.7	SOIC/LFCSP	\$3.06
AD8676	2	10 to 36	10	2.5	2.8 @ 1 kHz	50 μV	2 nA	2.7	SOIC/MSOP	\$1.64

Learn more about ADI's low-noise operational-amplifier portfolio at [www.analog.com/lownoiseamps-FAQ](http://www.analog.com/lownoiseamps-FAQ).

**EXPERIENCE THE DIGI·KEY DIFFERENCE**  
Visit us for all your Analog Devices products  
at [www.digikey.com/adi](http://www.digikey.com/adi) today!

