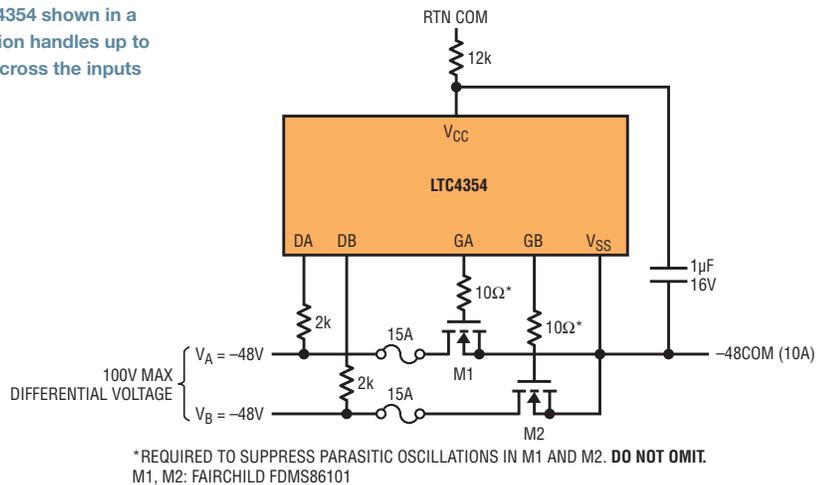


Negative Voltage Diode-OR Controller Tolerates Inputs to 300V and Beyond

Mitchell Lee

The LTC4354 negative voltage diode-OR controller is designed to operate with inputs of up to 100V. As shown in Figure 1, the maximum voltage between $-48V$, V_A and $-48V$, V_B is limited to 100V, and the voltage applied to either input is similarly limited to 100V relative to $-48COM$. A careful study of the LTC4354 data sheet reveals that the drain pins, DA and DB, which are the only pins exposed to high voltage, are limited to 80V. Nevertheless, with a 2k series limiting resistor, these pins can handle up to 100V.

Figure 1. The LTC4354 shown in a 10A, $-48V$ application handles up to 100V differential across the inputs




If it were possible to further increase the series resistance, even higher voltages could be tolerated by simply changing the 2k resistor. Unfortunately the drain pin input bias current sets a practical limit of 2k, so as to avoid interfering with the operation of the ideal diode function itself.

In systems where the inputs are subjected to spikes in excess of 100V, MOSFET breakdown clamps the maximum voltage, although admittedly bereft of characterization and guarantee.

If spikes in excess of 100V are an issue, the high voltage capability of the drain pins is easily extended beyond 100V by simply adding a Zener clamp, as shown in Figure 2. Input spikes above 75V are clamped by the Zener, with current limiting provided by the 2k resistor.

Figure 2. Zener clamps extend transient voltage capability to 150V and beyond

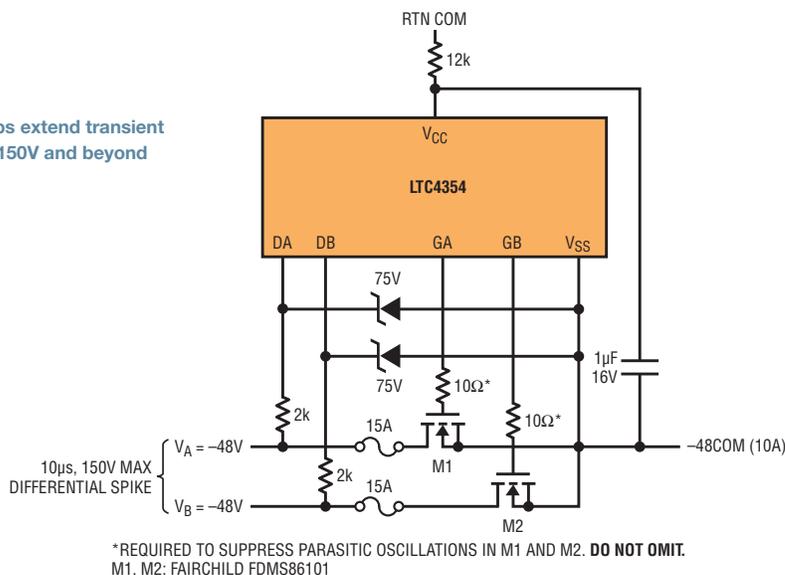

Zeners in the 250mW to 500mW range are capable of absorbing the peak current generated by a 150V, 10μs spike. Higher voltage and longer duration spikes may be accommodated by larger devices.

For sustained conditions, a simple Zener clamp is made untenable by the dissipation in both the resistor and Zener. The circuit shown in Figure 3 uses small, high voltage MOSFETs for limiting and can handle up to 400V. 11V gate

Zeners in the 250mW to 500mW range are capable of absorbing the peak current generated by a 150V, 10μs spike. Higher voltage and longer duration spikes may be accommodated by larger devices.

bias is conveniently obtained from the shunt-regulated V_{CC} pin without the need for any extra components, making this useful configuration a very simple modification of the basic circuit.

Under normal conditions, the $-48V$ inputs are at or near the V_{SS} potential, and the small MOSFETS M3 and M4 are driven fully on as their gates are biased to $\sim 11V$ with respect to V_{SS} by the V_{CC} pin. If one input rises with respect to V_{SS} , the small MOSFET remains on and the associated drain pin tracks the input. If the input continues to rise to the point where it is $\geq 10V$ with respect to V_{SS} , the small MOSFET turns into a source follower, safely limiting the drain pin to about $10V$ with respect to V_{SS} . MOSFETS

M1 and M2 can be expected to avalanche and clamp any positive-going spikes exceeding $300V$, to less than $400V$.

While the circuit in Figure 3 was designed for a $-48V$ system, changing R_{IN} to a $100k$, $1W$ unit allows the circuit to operate with inputs of $-200V$ to $-300V$ DC. Higher voltage standoff is possible with appropriate selection of MOSFETS. ■

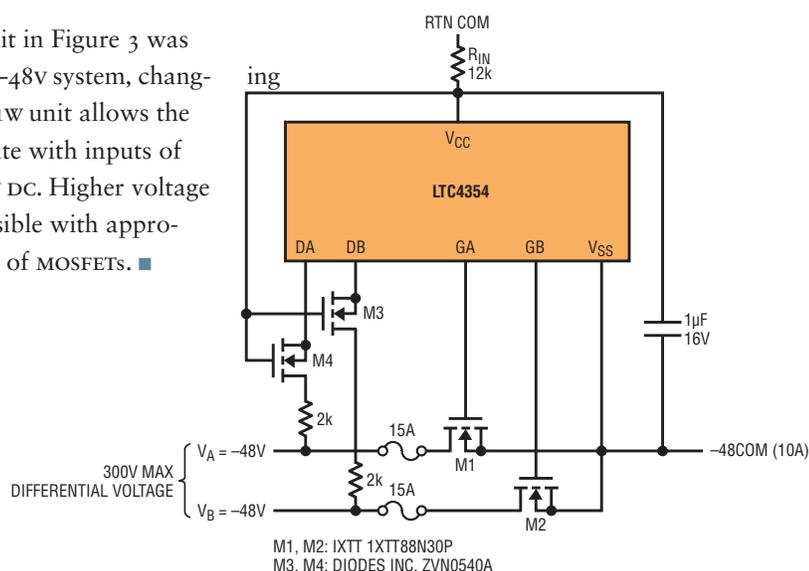


Figure 3. The LTC4354 shown in a 10A, $-48V$ application handles up to $300V$ differential across the inputs

supercap charger, continued from page 19 implies a boost regulator with a “blocking” output. This in turn necessitates the second ideal diode to allow the supercapacitor to power the buck regulator until the boost regulator engages. The boost regulator must operate to as low a voltage as possible to ensure that the maximum amount of energy is scavenged from the supercapacitor.

If the supercapacitor is initially charged to $5V$, then the energy in the supercapacitor is:

$$\frac{1}{2}CV^2 = \frac{1}{2} \cdot 0.55F \cdot 5^2 = 6.875J$$

The output power is $3.33V$ at $0.2A = 0.67W$, so the percentage of the energy stored in the supercap that is extracted with a buck-only circuit is:

$$\frac{\epsilon_{LOAD}}{\epsilon_{CAP}} = \frac{0.67 \cdot 4.68s}{6.875} = 45.1\%$$

The percentage of the energy stored in the supercap, extracted when the boost regulator is enabled, is:

$$\frac{\epsilon_{LOAD}}{\epsilon_{CAP}} = \frac{0.67 \cdot 7.92s}{6.875} = 77\%$$

The percentage of energy stored in the supercapacitor that is recovered increases from 45.1% to 77% . This allows use of a smaller, less expensive supercapacitor.

CONCLUSION

The power ride-through system shown here uses a $0.55F$ supercap to hold up power long enough for a microcontroller to complete some last gasp housekeeping tasks. One way to extend

the ride-through time for a given supercapacitor is to add a boost regulator to the system, which allows for energy scavenging. The run time of a given supercapacitor can be extended by $>30\%$ if energy scavenging is used. This is particularly relevant if the supercapacitor operating voltage is reduced to ensure high temperature reliability.

In addition, the shape of the output voltage is considerably improved as the input voltage to the output regulator is now square in shape. This results in a steady $3.3V$ output voltage with a sharp cutoff, instead of a ramped voltage drop as the supercap drains. ■