

The LTC3863 can produce a -0.4V to -150V negative output voltage from a positive input range of 3.5V to 60V . It uses a single-inductor topology with one active P-channel MOSFET switch and one diode. The high level of integration yields a simple, low parts count solution.

The LTC3863 can be programmed to enter either high efficiency Burst Mode operation or pulse-skipping mode at light loads. In Burst Mode operation, the controller directs fewer, higher current pulses and then enters a low current quiescent state for a period of time depending on load. In pulse-skipping mode, the LTC3863 skips pulses at light loads. In this mode, the modulation comparator may remain tripped for several cycles and force the external MOSFET to remain off, thereby skipping pulses. This mode offers the benefits of smaller output ripple, lower audible noise, and reduced RF interference, at the expense of lower efficiency when compared to Burst Mode operation. This circuit fits in about 0.5in^2 (3.2cm^2) with components on both sides of the board.

Figure 2 shows switch node voltage, inductor current, and ripple waveforms at 5V input and -12V output at 1A . The inductor is charged (current rises) when the PMOSFET is on, and discharges through the diode to the output when the PMOS turns off. Figure 3 shows the same waveforms at 30mA out in pulse-skipping mode. Notice how the switch node rings out around 0V when the inductor current reaches zero. The effective period stops when the current reaches zero. Figure 4 shows the same load condition with Burst Mode operation enabled. Power dissipation drops by 36% at this operating point, and efficiency increases from 72% to 80% . Figure 5 shows waveforms with the output shorted. The switching frequency is reduced to about 80kHz in this condition to prevent excessive current that could otherwise result.

HIGH EFFICIENCY

Figure 6 shows efficiency curves for both pulse-skipping and Burst Mode operation. Exceptional efficiency of 89.3% is achieved at 1A load and 12V input. Notice how Burst Mode operation dramatically improves efficiency at loads less than 0.1A . Pulse-skipping efficiency at light loads is still much higher than that obtained from synchronous operation.

CONCLUSION

The LTC3863 simplifies the design of converters producing a negative output from a positive source. It is elegant in its simplicity, high in efficiency, and requires only a small number of inexpensive external components to form a complete converter. ■

Figure 4. Switch node voltage, inductor current and ripple waveforms at 5V input and -12V output at 30mA in Burst Mode operation

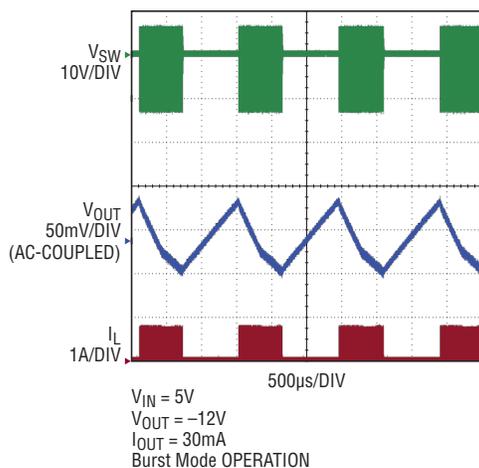


Figure 5. Switch node voltage, inductor current and ripple waveforms at 5V input with the output shorted

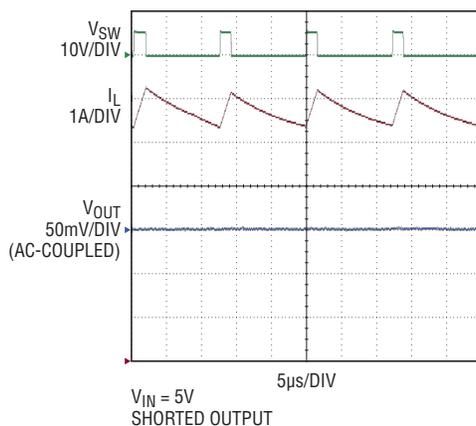


Figure 6. Efficiency in normal and Burst Mode operation

