

# Inverting DC/DC Controller Converts a Positive Input to a Negative Output with a Single Inductor

David Burgoon

There are a number of ways to produce a negative voltage from a positive voltage source, including using a transformer or two inductors and/or multiple switches, but none are as easy as using the LTC3863, which is elegant in its simplicity, has superior efficiency at light loads and reduces parts count when compared to these solutions.

## ADVANCED CONTROLLER CAPABILITIES

The LTC3863 can produce a  $-0.4\text{V}$  to  $-150\text{V}$  negative output voltage from a positive input range of  $3.5\text{V}$  to  $60\text{V}$ . It uses a single-inductor topology with one active P-channel MOSFET switch and one diode. The high level of integration yields a simple, low parts count solution.

The LTC3863 offers excellent light load efficiency, drawing only  $70\mu\text{A}$  quiescent current in user programmable Burst Mode<sup>®</sup> operation. Its peak current mode, constant frequency PWM architecture provides positive control of inductor current, easy loop compensation and top-notch loop dynamics. The switching frequency can be programmed from  $50\text{kHz}$  to  $850\text{kHz}$  with an external resistor and can be synchronized to an external clock from  $75\text{kHz}$  to  $750\text{kHz}$ . The LTC3863 offers programmable soft-start or output tracking. Safety features include over-voltage, overcurrent, and short-circuit protection including frequency foldback.

## -12V, 1A CONVERTER OPERATES FROM 4.5V-16V SOURCE

The circuit shown in Figure 1 produces a  $-12\text{V}$ ,  $1\text{A}$  output from a  $4.5\text{V}$ - $16\text{V}$  input. Operation is similar to a flyback converter, storing energy in the inductor when the switch is on and releasing it through the diode to the output when

the switch is off, except that with the LTC3863, no transformer is required. To prevent excessive current that can result from minimum on-time when the

output is short-circuited, the controller folds back the switching frequency when the output is below half of nominal.

Figure 1. Inverting converter produces  $-12\text{V}$  at  $1\text{A}$  from a  $4.5\text{V}$ - $16\text{V}$  source

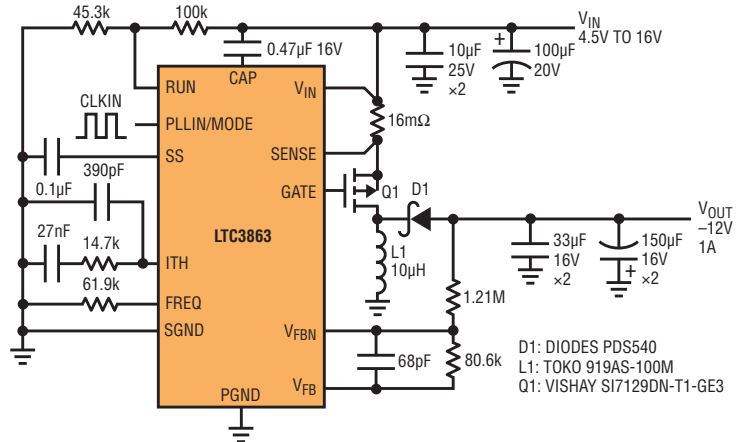


Figure 2. Switch node voltage, inductor current and ripple waveforms at  $5\text{V}$  input and  $-12\text{V}$  output at  $1\text{A}$


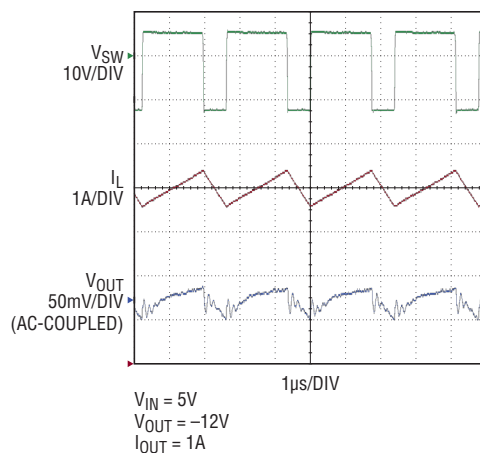


Figure 3. Switch node voltage, inductor current and ripple waveforms at  $5\text{V}$  input and  $-12\text{V}$  output at  $30\text{mA}$  in pulse-skipping mode

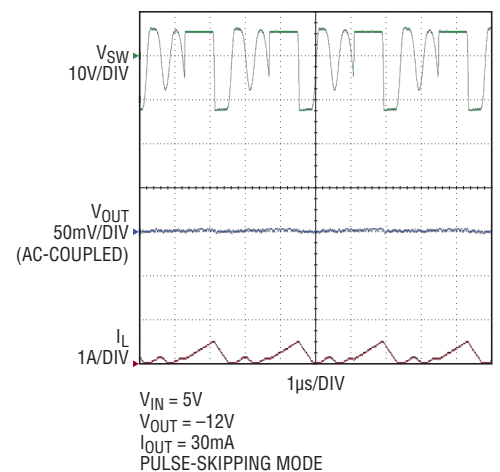

The LTC3863 can produce a  $-0.4\text{V}$  to  $-150\text{V}$  negative output voltage from a positive input range of  $3.5\text{V}$  to  $60\text{V}$ . It uses a single-inductor topology with one active P-channel MOSFET switch and one diode. The high level of integration yields a simple, low parts count solution.

The LTC3863 can be programmed to enter either high efficiency Burst Mode operation or pulse-skipping mode at light loads. In Burst Mode operation, the controller directs fewer, higher current pulses and then enters a low current quiescent state for a period of time depending on load. In pulse-skipping mode, the LTC3863 skips pulses at light loads. In this mode, the modulation comparator may remain tripped for several cycles and force the external MOSFET to remain off, thereby skipping pulses. This mode offers the benefits of smaller output ripple, lower audible noise, and reduced RF interference, at the expense of lower efficiency when compared to Burst Mode operation. This circuit fits in about  $0.5\text{in}^2$  ( $3.2\text{cm}^2$ ) with components on both sides of the board.

Figure 2 shows switch node voltage, inductor current, and ripple waveforms at  $5\text{V}$  input and  $-12\text{V}$  output at  $1\text{A}$ . The inductor is charged (current rises) when the PMOSFET is on, and discharges through the diode to the output when the PMOS turns off. Figure 3 shows the same waveforms at  $30\text{mA}$  out in pulse-skipping mode. Notice how the switch node rings out around  $0\text{V}$  when the inductor current reaches zero. The effective period stops when the current reaches zero. Figure 4 shows the same load condition with Burst Mode operation enabled. Power dissipation drops by  $36\%$  at this operating point, and efficiency increases from  $72\%$  to  $80\%$ . Figure 5 shows waveforms with the output shorted. The switching frequency is reduced to about  $80\text{kHz}$  in this condition to prevent excessive current that could otherwise result.

## HIGH EFFICIENCY

Figure 6 shows efficiency curves for both pulse-skipping and Burst Mode operation. Exceptional efficiency of  $89.3\%$  is achieved at  $1\text{A}$  load and  $12\text{V}$  input. Notice how Burst Mode operation dramatically improves efficiency at loads less than  $0.1\text{A}$ . Pulse-skipping efficiency at light loads is still much higher than that obtained from synchronous operation.

## CONCLUSION

The LTC3863 simplifies the design of converters producing a negative output from a positive source. It is elegant in its simplicity, high in efficiency, and requires only a small number of inexpensive external components to form a complete converter. ■

Figure 4. Switch node voltage, inductor current and ripple waveforms at  $5\text{V}$  input and  $-12\text{V}$  output at  $30\text{mA}$  in Burst Mode operation

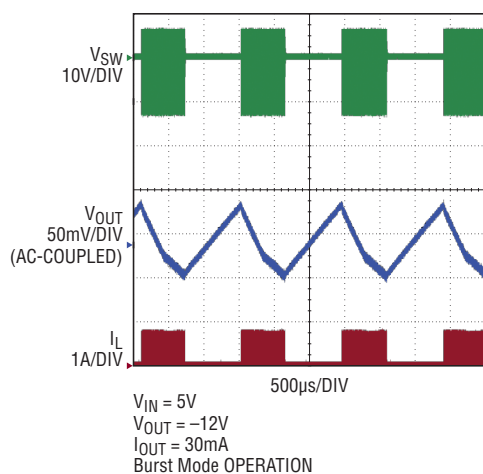


Figure 5. Switch node voltage, inductor current and ripple waveforms at  $5\text{V}$  input with the output shorted

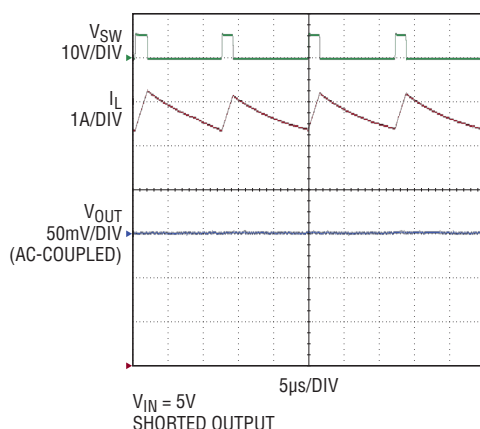


Figure 6. Efficiency in normal and Burst Mode operation

