

IN THIS ISSUE...

COVER ARTICLE

Reduce Charge Time for High Capacity Li-Ion Batteries with 2A Continuous Charging1
Tom Hack

Issue Highlights2
Linear Technology in the News.....2

DESIGN FEATURES

650MHz Selectable-Gain Amplifier/Differential ADC Driver Has Small Form but Many Functions6
Cheng-Wei Pei

Dual Step-Up Converter Drives White LEDs with 1000:1 PWM Dimming10
Keith Szolusha

Hot Swap™ Controller Monitors and Reports Power Supply Status12
Josh Simonson

Efficient Buck-Boost Converter Ideal for Power Saving Modes and Wide Input Voltage Ranges.....16
Kevin Ohlson

Dual/Triple Power Supply Monitor for Undervoltage and Overvoltage on Positive and Negative Supplies.....19
Andrew Thomas

High Speed Low Power RS485 Transceivers with Integrated Switchable Termination.....27
Ray Schuler and Steven Tanghe

1.5A VLDO™ Operates Down to 0.4V Output and Maintains 100mV Dropout30
Bill Walter

DESIGN IDEAS

.....33-46
(complete list on page 33)

New Device Cameos46

Design Tools.....47

Sales Offices48

Reduce Charge Time for High Capacity Li-Ion Batteries with 2A Continuous Charging

by Tom Hack

Introduction

The latest high capacity Li-Ion batteries meet the needs of power hungry portable devices, but they also increase the demands placed on battery chargers—demands that can be too much for a standard linear charger. For instance, a linear charger, operating at 1A charging current, charges a 1Ahr battery to 70% capacity within one hour, and fully charges it within three hours. Newer 2Ahr batteries need twice that current in order to be fully charged in the same amount of time. The problem is that a linear charger operating at 2A produces too much heat for continuous charging—it's just too inefficient. The LTC4001 solves this problem by incorporating a high

efficiency PWM charger to perform continuous 2A battery charging. It works with both standard and current-limited wall adapters—where the latter lowers battery charger dissipation and operating temperature.

Big Features; Small Footprint

A full-featured battery charger based on the LTC4001 requires an area not much larger than a dime (Figure 1). Fully programmable timer and charge rate terminations are included. Automatic battery “topping off” is also included. Filtering prevents accidental recharge from occurring in noisy environments (such as found in GPRS cellular phones). The LTC4001 works readily with NTC thermistors for battery temperature sensing. Remote battery sensing is included. Soft-start is fully programmable. The LTC4001 also drives charge status LEDs and provides logic signals for microprocessor-based designs.

The LTC4001 is tiny, fitting into a 4mm × 4mm package, but other factors also contribute to the charger's small footprint. High operating frequency (1.5MHz) reduces the size of the inductors and capacitors. Input short circuit blocking is built in so no external diode is required. Current

continued on page 3

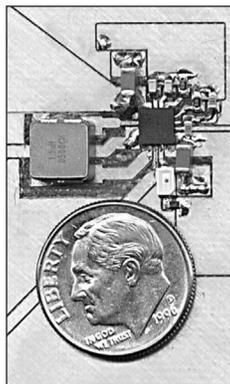


Figure 1. A typical LTC4001-based Li-Ion battery charger occupies minimal board real estate.

LTC4001, continued from page 1

sensing is internal, so there is no need for an expensive milliohm-sized current sense resistor.

Inside the LTC4001

The LTC4001 is the basis for a complete 2A Li-Ion battery charger (Figure 2). A 50mA linear charger provides cell conditioning while a synchronous buck charger provides constant-current/constant-voltage high rate charging (up to 2A). Protection and lockouts guard against a variety of events including: shorts at the battery and wall adapter inputs; improper programming of the charge current; open battery and/or over-voltage battery; defective battery; insufficient wall adapter voltage; chip over-temperature; battery over- or under- temperature.

A Bare Bones Charger

Figure 3 shows a bare bones 2A battery charger. With only five additional components, this charger offers a high efficiency, high power solution. This implementation leaves out status

indicator lights, battery temperature monitoring, and a timer (which may be provided by a microprocessor). In place of a timer, charge terminates when charge current drops below one-tenth the high rate charge current (an

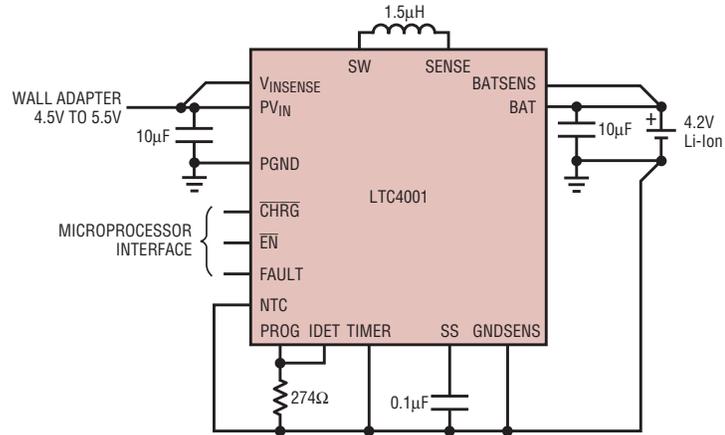


Figure 3. A bare bones battery charger

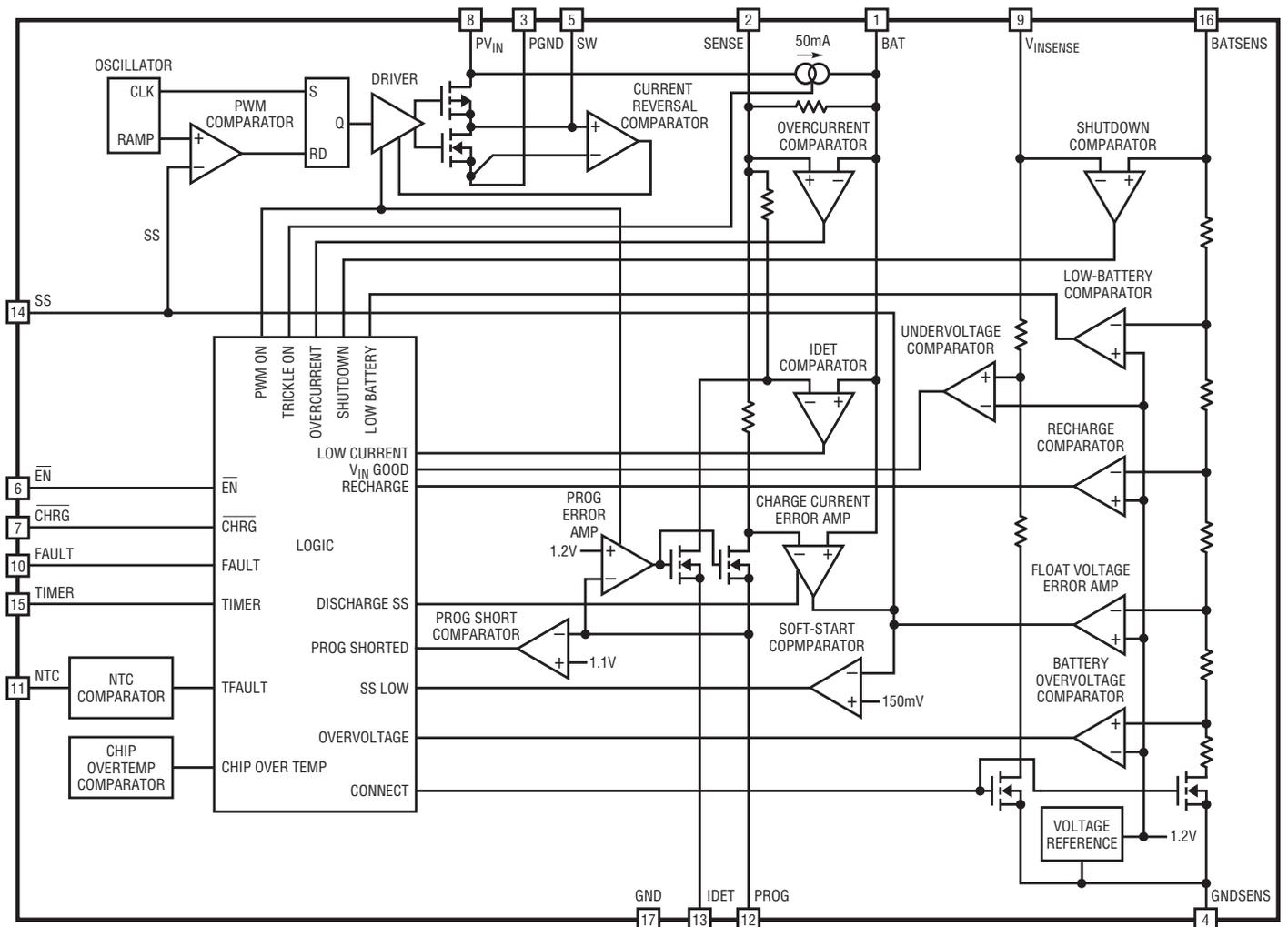


Figure 2. Simplified block diagram of the LTC4001 Li-Ion battery charger

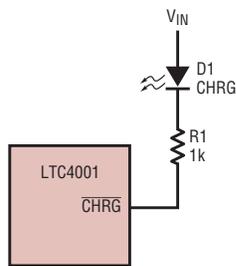


Figure 4. A simple status indicator

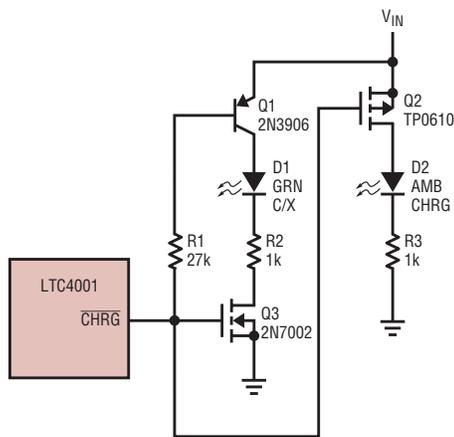


Figure 5. Full featured status indication

I_{DET} threshold equal to 200mA in this case). Internal charge termination may be completely defeated by connecting the timer pin to the I_{DET} pin instead of ground (allowing a microprocessor complete control of charge termination).

Adding Status Lights

The \overline{CHRG} pin indicates a variety of charger states (Table 1). Adding a resistor and LED in series with this pin to V_{IN} (Figure 4) indicates charger off (LED off), high rate charging or cell conditioning (LED on continuously at high brightness), and battery temperature out of range/NTC fault (LED blinking).

The LED also indicates when the battery is nearly full charged. As the battery approaches the float voltage and charge current drops below the I_{DET} threshold the LED is dimly lit. This is difficult to see, so a better approach uses two LEDs to indicate all charger states (Figure 5).

Interfacing with Microprocessors

The interface in Figure 6 can distinguish between all states available on the \overline{CHRG} pin. To detect cell conditioning or high rate charging, force the digital output pin, OUT, high and measure the voltage on the \overline{CHRG} pin. The N-channel mosfet pulls \overline{CHRG} low even with a 2k pull-up resistor. Near end of charge, the NMOS turns off, and \overline{CHRG} sinks only 30 μ A. The IN pin is pulled high by the 2k resistor connected to OUT. If OUT is placed into a high impedance state, the 30 μ A sink current from the \overline{CHRG} pin pulls IN low. When charging stops, \overline{CHRG} opens and OUT stays high, even with a 390k pull up resistor.

If a battery temperature fault occurs during high rate charging, the \overline{CHRG} pin blinks using a serrated pulse pattern. Nominal timing of this pattern is given in Figure 7. The extra edges provide rapid indication to a microprocessor and may be used to drive a microprocessor interrupt line for low processor overhead, but still provide for a visible fault indication when using LEDs.

Battery Temperature Sensing

By adding one resistor and one thermistor, battery temperature sensing may be included. The LTC4001 is designed for Vishay Dale's "R-T Curve 2" therm-

istors, but any thermistor with an R_{COLD} -to- R_{HOT} ratio of about 7 will also work. If battery sensing is not needed, the NTC pin is grounded.

Operation with Conventional and Current Limited Wall Adapters

Wall adapters with or without current limiting may be used with the LTC4001, but the lowest power dissipation battery charging occurs with a current limited wall adapter. To use this feature, program the LTC4001 above the wall adapter current limit. For example, if the wall adapter current limit is 2A, set the LTC4001 charge current slightly higher than 2A (allowing for tolerances).

To understand operation with a current limited wall adapter, assume battery voltage V_{BAT} is initially below V_{TRIKL} , the trickle charge threshold (Figure 8). Battery charging begins at approximately 50mA, well below the wall adapter current limit so the voltage into the LTC4001 (V_{IN}) is the wall adapter's rated output voltage ($V_{ADAPTER}$). Battery voltage rises eventually reaching V_{TRIKL} . The linear charger shuts off and the PWM (high rate) charger turns on using soft start. Battery charging current rises during the soft-start cycle causing a corresponding increase in wall adapter load current. When the wall adapter reaches current limit, the wall adapter output voltage collapses, and

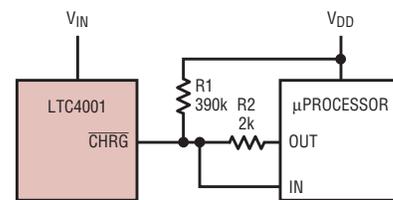


Figure 6. A microprocessor interface

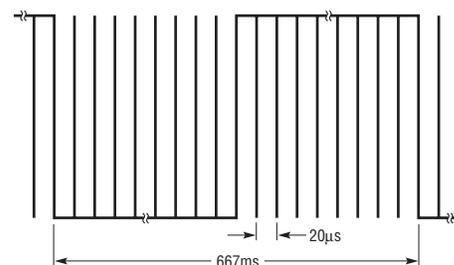


Figure 7. \overline{CHRG} temperature fault waveform

Table 1. \overline{CHRG} Behavior

Charger State	\overline{CHRG} Behavior
Not charging	Open
High rate Charging and $I_{BAT} > I_{DET}$ Or cell conditioning	NMOS turned on pulling pin low
High Rate Charging and $I_{BAT} < I_{DET}$	30 μ A pull down current
NTC temperature fault while charging at $I_{BAT} > I_{DET}$	Blink

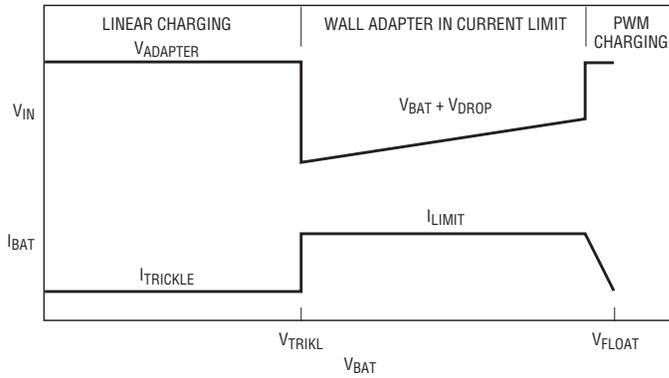


Figure 8. Idealized charging behavior

So how does LTC4001 dissipation stack up against a 2A linear charger? Most of a linear charger's dissipation occurs in the series pass element so the dissipation is approximately equal to the voltage drop in the pass element times the charge current. Worst case dissipation occurs at the lowest battery voltage where high rate charging occurs (to make a valid comparison to the LTC4001 this would be 2.85V). For a 5.0V input, this translates into a dissipation of 4.3W! Higher input voltage makes the situation even worse.

A Charger with All the Bells and Whistles

A full featured battery charger is shown in Figure 10. It includes a three hour timer, battery temperature monitoring, programmable charge and I_{DET} currents, remote sensing, and status lights. A fault light has been included that indicates when a shorted battery is detected or when the battery is out of normal temperature range.

Conclusion

The LTC4001 sets a new standard for small, low parts count, full-featured, high efficiency Li-Ion battery chargers. Low power dissipation makes continuous 2A battery charging practical, cutting dissipation to approximately one fifth the dissipation of a straight linear charger. 

the LTC4001 PWM charger duty cycle ramps up to 100% (the top-side PMOS switch in the LTC4001 buck regulator stays on continuously.) As the battery voltage approaches V_{FLOAT}, the float voltage error amplifier commands the PWM charger to deliver less than I_{LIMIT}. The wall adapter exits current limit and V_{IN} jumps back up to V_{ADAPTER}. Battery charging current continues to drop as V_{BAT} rises, dropping to zero at V_{FLOAT}.

Because the voltage drop in the LTC4001 is very low when charge current is highest, power dissipation is also very low.

Low Dissipation

Trickle charging uses a linear charger but low charge current produces low power dissipation, typically 256mW (V_{IN} = 5V, V_{BAT} = 0). High rate charging uses a high efficiency buck switcher

and total charger dissipation is approximately 1.2W at 2A (Figure 9). High rate charging with a current limited wall adapter produces even lower charger dissipation (537mW at V_{BAT} = 4.2V with a 2A current limited wall adapter) because there is very little voltage drop for the battery charging path inside the LTC4001.

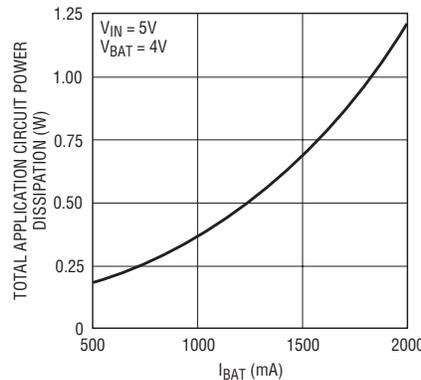


Figure 9. High rate charger power dissipation

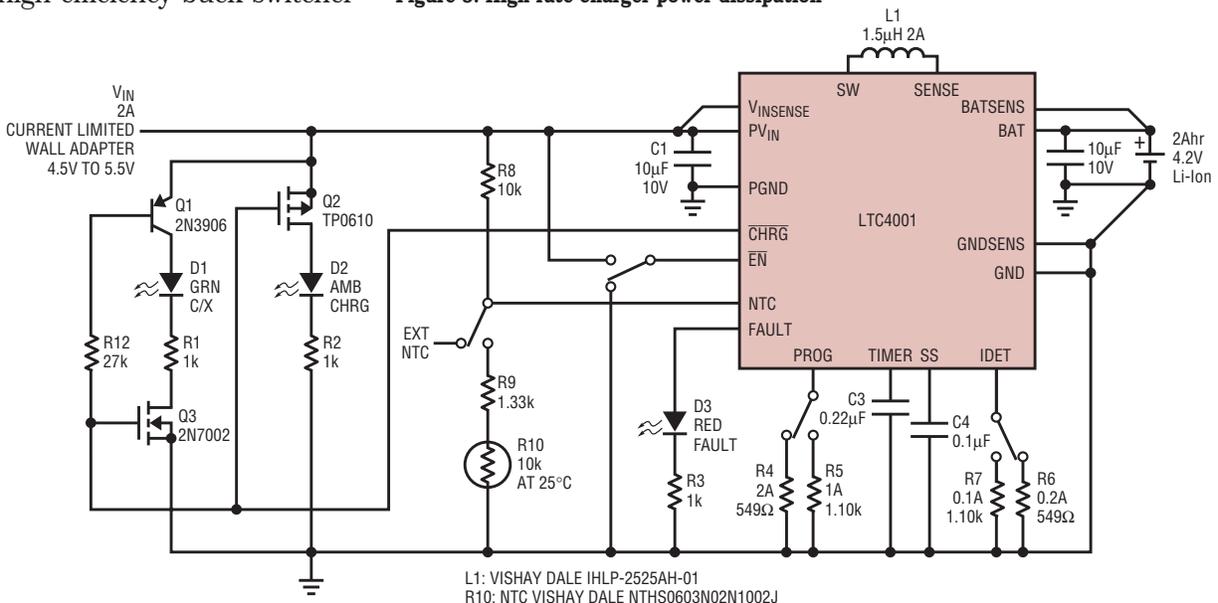


Figure 10. A full featured battery charger