

0V to 18V Ideal Diode Controller Saves Watts and Space over Schottky

by Pinkesh Sachdev

Introduction

Schottky diodes are used in a variety of ways to implement multisource power systems. For instance, high availability electronic systems, such as network and storage servers, use power Schottky diode-OR circuits to realize a redundant power system. Diode-ORing is also used in systems that have alternate power sources, such as an AC wall adapter and a backup battery feed. Power diodes can be combined with capacitors to hold up a load voltage during an input brownout. In this case, the power diodes are placed in series with the input voltage, with the capacitors on the load side of the diode. While the capacitors provide power, the reverse-biased diode isolates the load from the sagging input.

Schottky diodes suffice for these applications when currents are below a few amperes, but for higher currents, the excess power dissipated in the diode due to its forward voltage drop demands a better solution. For instance, 5A flowing through a diode with a 0.5V drop wastes 2.5W within the diode. This heat must be dissipated with dedicated copper area on the PCB or heat sinks bolted to the diode, both of which take significant space. The diode's forward drop also makes

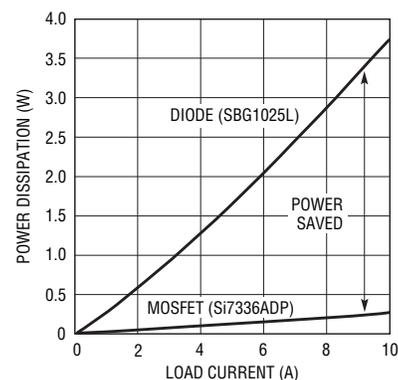


Figure 2. As load current increases, so do the power savings gained from using an ideal diode (LTC4352 + Si7336ADP) instead of a power Schottky diode (SBG1025L).

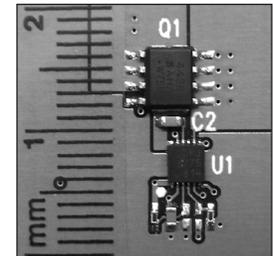
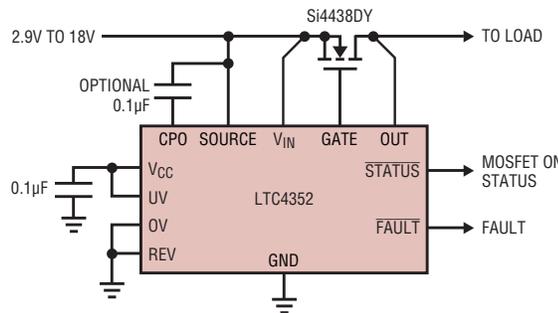


Figure 1. The LTC4352 controlling an N-Channel MOSFET replaces a power diode and associated heat sink to save power, PCB area, and voltage drop. Also shown: the small PCB footprint of the ideal diode circuit using a 3mm x 3mm DFN-12 packaged LTC4352 and SO-8 size MOSFET.

it impractical for low voltage applications. This problem calls out for an ideal diode with a zero forward voltage drop to save power and space.

The LTC4352 ideal diode controller in tandem with an N-channel MOSFET creates a near-ideal diode for use with 0V to 18V input supplies. Figure 1 illustrates the simplicity of this solution. This ideal diode circuit can replace a

power Schottky diode to create a highly efficient power ORing or supply holdup application. Figure 2 shows the power savings of the ideal diode circuit over a Schottky diode. 3.5W is saved at 10A, and the saving increases with load current. With its fast dynamic response, the controller excels in low voltage diode-OR applications which are more sensitive to voltage droop.

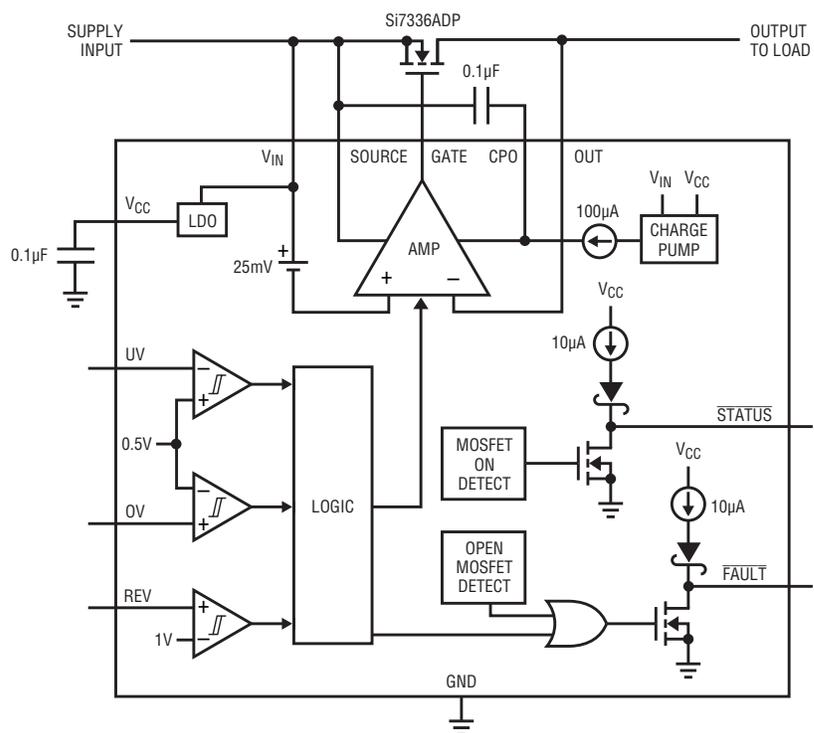


Figure 3. Simplified internals of the LTC4352

What Makes It Ideal?

The LTC4352 monitors the differential voltage across the MOSFET source (the “anode”) and drain (the “cathode”) terminals. The MOSFET has an intrinsic source-to-drain body diode which conducts the load current at initial power-up. When the input voltage is higher than the output, the MOSFET is turned on, resulting in a forward voltage drop of $I_{LOAD} \cdot R_{DS(ON)}$. The $R_{DS(ON)}$ can be suitably chosen to provide an easy 10x reduction over a Schottky diode’s voltage drop. When the input drops below the output, the MOSFET is turned off, thus emulating the behavior of a reverse biased diode.

An inferior ideal diode control technique monitors the voltage across the MOSFET with a hysteretic comparator. For example, the MOSFET could be turned on whenever the input to output voltage exceeds 25mV. However, choosing the lower turn-off threshold can be tricky. Setting it to a positive forward voltage drop, say 5mV, causes the MOSFET to be turned off and on repeatedly at light load currents. Setting it to a negative value, such as -5mV, allows DC reverse current.

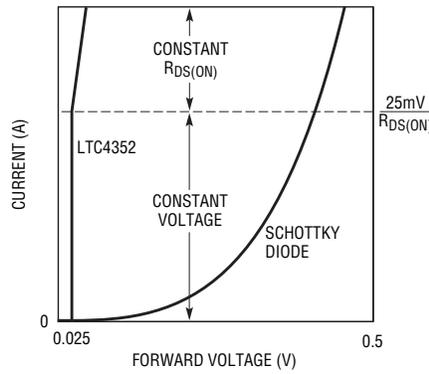


Figure 4. The forward I-V characteristic of the LTC4352 ideal diode vs a Schottky diode.

The LTC4352 implements a linear control method to avoid the problems of the comparator-based technique. It serves the gate of the MOSFET to maintain the forward voltage drop across the MOSFET at 25mV (AMP of Figure 3). At light load currents, the gate of the MOSFET is slightly above its threshold voltage to create a resistance of $25mV/I_{LOAD}$. As the load current increases, the gate voltage rises to reduce the MOSFET resistance. Ultimately, at large load currents, the MOSFET gate is driven fully on, and the forward voltage drop


rises linearly with load current as $I_{LOAD} \cdot R_{DS(ON)}$. Figure 4 shows the resulting ideal diode I-V characteristic.

In a reverse voltage condition, the gate is servoed low to completely turn off the MOSFET, thus avoiding DC reverse current. The linear method also provides a smooth switchover of currents for slowly crossing input supplies in diode-OR applications. In fact, depending on MOSFET and trace impedances, the input supplies share the load current when their voltages are nearly equal.



Fast Switch Control

Most ideal diode circuits suffer slower transient response compared to conventional diodes. The LTC4352, on the other hand, responds quickly to changes in the input to output voltage. A powerful driver turns off the MOSFET to protect the input supply and board traces from large reverse currents. Similarly, the driver turns on the switch rapidly to limit voltage droop during supply switchover in diode-OR applications.

Figure 5 shows a fast switchover event occurring in a 3.3V ideal diode-

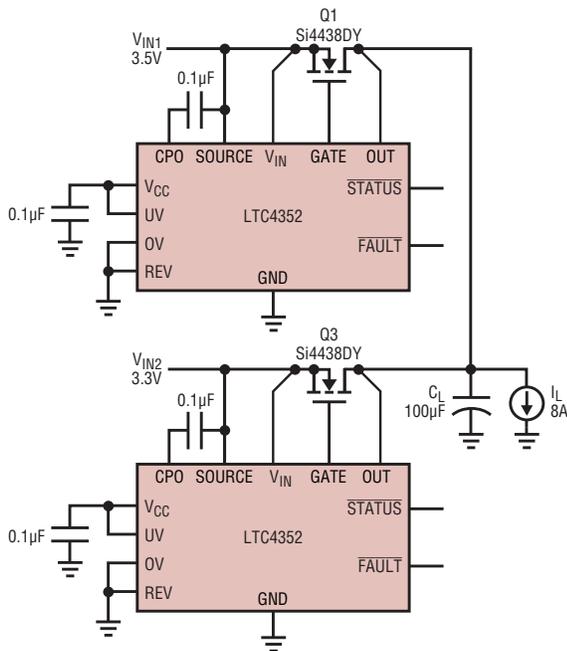

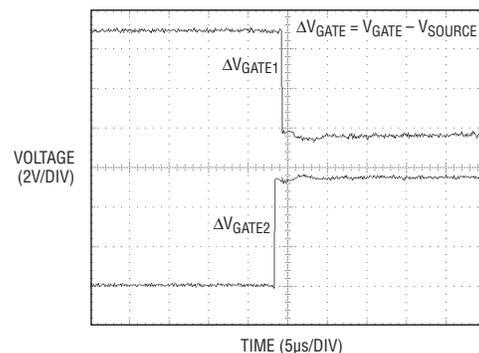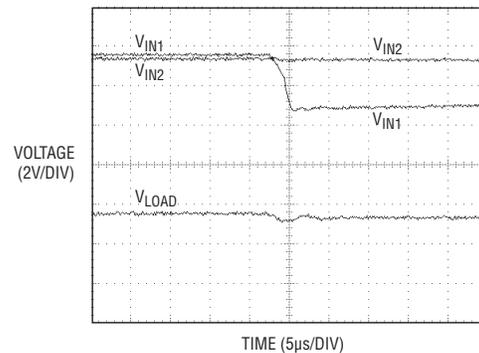a. Ideal diode-OR of 3.5V and 3.3V input supply.



b. Supply switchover from V_{IN1} to V_{IN2} due to short-circuit on V_{IN1} shows minimal disturbance on load voltage.

Figure 5. Ideal diode-OR fast switchover

OR circuit. Initially V_{IN1} supplies the entire load current since it is higher than V_{IN2} . In this state, MOSFET Q1 is on and Q3 is off. A short circuit causes V_{IN1} to collapse below V_{IN2} . The LTC4352's fast response shuts off Q1 and turns on Q3 so that the load current can now be supplied by V_{IN2} . This fast switchover minimizes disturbance on the load voltage so that downstream circuits can continue to operate smoothly.

To achieve fast switch turn-on, the LTC4352 uses an internal charge pump with an external reservoir capacitor. This capacitor is connected between the CPO and SOURCE pins. CPO is the output of a charge pump that can deliver up to 100 μ A of pull-up current. The reservoir capacitor accumulates and stores charge, which can be called upon to produce 1.5A of transient GATE pull-up current during a fast turn-on event. The reservoir capacitor voltage drops after the fast turn-on since it charge-shares with the input gate capacitance (C_{ISS}) of the MOSFET. For an acceptable drop, the reservoir capacitor value should be around 10 times the C_{ISS} of the MOSFET.

It is easy to disable fast turn-on. Omitting the reservoir capacitor slows down the gate rise time as determined by the CPO pull-up current charging C_{ISS} . Slow gate turn-on may cause the load to droop roughly a volt below the input as current flows through the MOSFET body diode until the channel is enhanced. This may be acceptable

Table 1. Operating state of the LTC4352 ideal diode as indicated by the STATUS and FAULT lights

LED State		Ideal Diode Operating State	
STATUS Green LED	FAULT Red LED	MOSFET	UV/OV
○	○	OFF	NO
●	○	ON	NO
○	●	OFF	YES
●	●	OPEN	NO

at higher input voltage applications, such as 12V.

Do What No Diode Has Done Before

The LTC4352 goes above and beyond the functionality of a diode by incorporating input undervoltage and overvoltage protection, outputs to report status and fault information, open MOSFET detection, and the ability to allow reverse current.

Figure 6 shows the LTC4352 in a 5V ideal diode circuit with undervoltage and overvoltage protection. The UV and OV pins have comparators with a 0.5V trip threshold and 5mV hysteresis (Figure 3). The resistive dividers from the input supply to these pins set up an input voltage window, typically 4.36V to 5.78V, where the ideal diode function operates. The STATUS pin pulls low to light up a green LED whenever the gate is high and power is flowing through the external MOSFET. For V_{IN}

outside the input voltage window, the gate is held off and the FAULT pin pulls low to signal a fault condition. A red LED, D2, provides visual indication. Back-to-back MOSFETs are needed to block conduction through their intrinsic source-to-drain body diodes in the gate low condition. A single MOSFET, Q1, could be used in the case where only a V_{IN} out-of-range indication is sufficient. But care should be taken that the load current flowing through Q1's body diode, when its gate is low, does not cause excessive heat dissipation in the MOSFET.

The MOSFET switch could fail open circuit or its $R_{DS(ON)}$ may degrade over years of operation, increasing the voltage drop across the switch. A large drop also results when excessive current flows through the MOSFET, possibly due to an output short circuit. The LTC4352 detects such failures and flags it through its FAULT pin. The open MOSFET detection circuit trips whenever it senses more than 250mV of forward voltage drop across the MOSFET—even with the gate turned on. Note that this condition only causes the FAULT pin to pull low, but no action is taken to turn off the switch. Table 1 translates STATUS and FAULT LED status to the operating state of the LTC4352.

The input at the REV pin configures the LTC4352's behavior for reverse current. It is tied low for normal diode operation, which blocks reverse current from flowing through the external MOSFET. Driving REV above 1V turns the gate completely on to its limit, even during reverse current conditions.



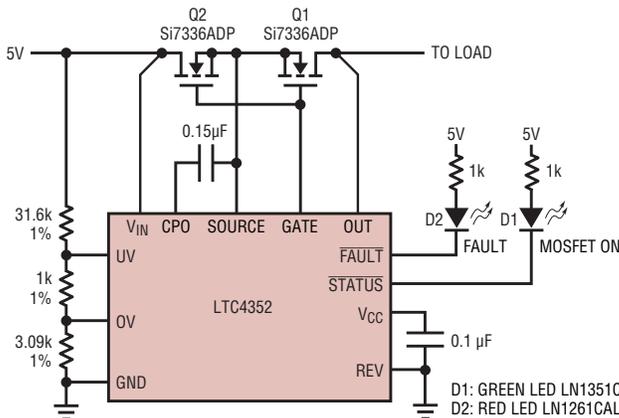


Figure 6. A 5V ideal diode circuit with input undervoltage and overvoltage protection. Ideal diode function operates for $4.36V < V_{IN} < 5.78V$, else GATE is low.

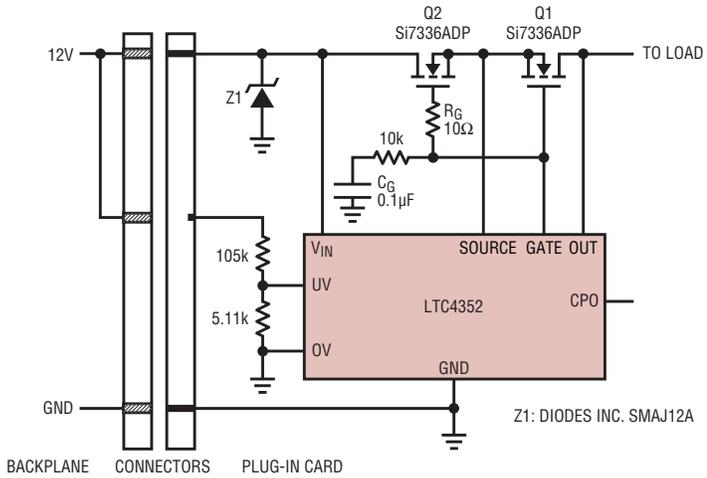

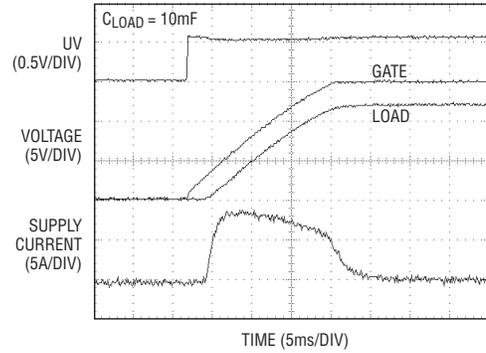a. Omitting the CPO capacitor and adding an RC network on the gate allows inrush current control on a Hot Swap board.



b. After short pin makes contact and UV is above 0.5V, GATE starts ramping up. Once it crosses the MOSFET threshold voltage, LOAD follows with the same dV/dt . Here, inrush is limited to 8.3A peak for a 10mF C_{LOAD} .

Figure 7. Controlling inrush current

Only undervoltage, overvoltage, and V_{CC} undervoltage lockout can override this to turn-off the gate. This feature is handy either in power path control applications which allow reverse current flow to occur, or for testing purposes.

Inrush Control on a Hot Swap Board

When the diode power input flows across a connector on a hot swap board, the LTC4352 can do double-duty to control the inrush current. Again, back-to-back MOSFETs are required for this application to block conduction through the MOSFET body diodes. The inrush current is limited by slowing the rise rate of the load voltage. This is done by limiting dV/dt on the MOSFET gate and operating it in a source-follower configuration.

Figure 7 illustrates an application where the LTC4352 is used for inrush control. Since the goal is to limit dV/dt on the gate, the fast turn-on characteristic of the ideal diode is disabled by omitting the CPO reservoir capacitor. The gate current is now limited to the CPO pull-up current of $100\mu A$. To further reduce dV/dt , an RC network is added on the gate. The resistor decouples the capacitor during fast turn-off due to reverse current or overvoltage faults.

Resistor R_G prevents high frequency oscillations in Q2.

When the board is hot-plugged, the long power pins make contact first. The LTC4352 powers up, but holds the gate off since UV is low. After a few milliseconds of board insertion delay, the short UV pin makes contact. If V_{IN} is above 10.8V, the MOSFET gate starts ramping up. The MOSFET turns on as the gate reaches the threshold voltage, and current starts charging the output. Q2 operates in the source follower mode and suffers the most power dissipation. Its V_{DS} starts off at V_{IN} and decreases to $25mV/2$. Care should be taken that the power dissipated during inrush falls within the safe operating area (SOA) of the MOSFET.

Down to Earth Operation

The V_{IN} operating range extends all the way down to 0V. However, when operating with inputs below 2.9V, an external supply is needed on the V_{CC} pin. This supply should be in the range 2.9V to 6V. For a 2.9V to 4.7V subset of this range, V_{IN} should always be lower than V_{CC} . A $0.1\mu F$ bypass capacitor is also needed between the V_{CC} and GND pins. Figure 8 shows an ideal diode circuit, where a 5V supply powers up the V_{CC} pin. In this case, V_{IN} can operate all the way down to 0V and up to 18V.

For input supplies from 2.9V to 18V, the external supply at the V_{CC} pin is not needed. Instead, an internal low dropout regulator (LDO in Figure 3)

continued on page 31

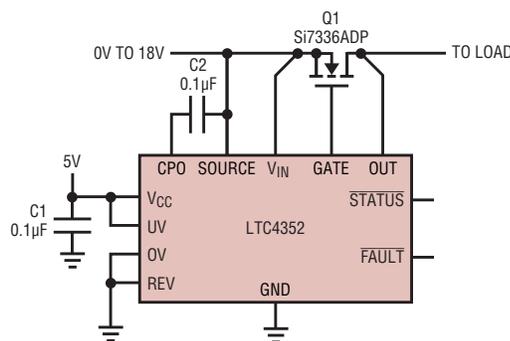


Figure 8. A 0V to 18V ideal diode circuit. By powering the V_{CC} pin with an external supply in the 4.7V to 6V range (here 5V), V_{IN} can operate down to 0V and up to 18V.

bias supply. Another boost converter and an inverter generate V_{ON} and V_{OFF} , which also use the 5V supply as input.

When power is first applied to the input, the RUN-SS1 capacitor starts charging. When its voltage reaches 0.8V, Switcher 1 is enabled. The capacitor at the RUN-SS1 pin controls the ramp rate for the Switcher 1 output, V_{LOGIC} and inrush current in L1. Switchers 2, 3 and 4 are controlled by the BIAS pin, which is usually connected to V_{LOGIC} . When the BIAS pin is higher than 2.8V, the capacitors at the RUNSS-2 and RUN-SS3/4 pin begin charging to enable Switchers 2, 3 and 4. When AV_{DD} reaches 90% of its programmed voltage, the PGOOD pin is pulled low. When AV_{DD} , V_{OFF} and E3 all reach 90% or their programmed voltages, the C_T timer is enabled and a 20 μ A current source begins to charge C_T . When the C_T pin reaches 1.1V, the output PNP turns on, connecting E3 to V_{ON} . Figure 2 shows the start up sequence of the circuit in Figure 1.

If one of the regulated voltages, V_{LOGIC} , AV_{DD} , V_{OFF} or E3 dips more than 10%, the internal PNP turns off to shut down V_{ON} . This action protects the panels, as V_{ON} must be present to turn on the TFT display. The PGOOD

pin can drive an optional PMOS device at the output of the boost regulator to disconnect the load at AV_{DD} from the input during shutdown. The converter uses all ceramic capacitors. X5R and X7R types are recommended, as these materials maintain capacitance over a wide temperature range.

All four switchers employ a constant frequency, current mode control scheme. Switching regulator 1 uses a feedback scheme that senses inductor current, while the other switching regulators monitor switch current. The inductor current sensing method avoids minimum on-time issues and maintains the switch current limit at any input-to-output voltage ratio. The other three regulators have frequency foldback scheme, which reduces the switching frequency when its FB pin is below 0.75V. This feature reduces the average inductor current during start up and overload conditions, minimizing the power dissipation in the power switches and external components.

Layout Considerations

Proper PC board layout is important to achieve the best operating performance. Paths that carry high switching current should be short and wide to

minimize parasitic inductance. In a buck regulator, this loop includes the input capacitor, internal power switch and Schottky diode. In a boost regulator, this loop includes the output capacitor, internal power switch and Schottky diode. Keep all the loop compensation components and feedback resistors away from the high switching current paths. The LT3513 pin out was designed to facilitate PCB layout. Keep the traces from the center of the feedback resistors to the corresponding FB pins as short as possible. LT3513 has an exposed ground pad on the backside of the IC to reduce thermal resistance. A ground plane with multiple vias into ground layers should be placed underneath the part to conduct heat away from the IC.

Conclusion

The LT3513 is a comprehensive, but compact, power supply solution for TFT-LCD panels. Its wide input range and low power dissipation allow it to be used in a wide variety of applications. All four of the integrated switching regulators have a 2MHz switching frequency and allow the exclusive use of the ceramic capacitors to minimize circuit size, cost and output ripple. 

LTM4604, LTM4608, continued from page 29
than 5% at full load. Excellent current sharing results in well balanced thermal stresses on the paralleled LTM4608s, which in turn makes for a more reliable system. Figure 7 demonstrates the small temperature difference between these two paral-

leled LTM4608 boards supplying 16A output current.

Conclusion

The LTM4604 and LTM4608 15mm \times 9mm μ Module regulators are complete power supply solutions for low input voltage and high output cur-

rent applications. They significantly simplify circuit and layout designs by effortlessly fitting into the tightest spaces, including the bottom of the PCB. Despite their compact form, these μ Modules are rich in features, and they can be easily paralleled when more output current is needed. 

LTC4352, continued from page 27

generates a 4.1V supply at the V_{CC} pin. For V_{IN} below 4.1V, V_{CC} follows approximately 50mV below V_{IN} . The 0.1 μ F V_{CC} capacitor is still needed for bypassing and LDO stability.

Conclusion

An ever-present theme in electronic system design has been to pack more computation in smaller form factors and tighter power budgets. Another

trend has been to lower the voltage of distributed power, which increases the current to maintain power levels. Given these constraints, board designers must scrutinize each diode in a high current power path for its power and area consumption.

The LTC4352 MOSFET controller provides the same functionality as a diode but at higher efficiencies and cooler temperatures, especially as currents increase. It also incorporates

useful features such as fast switch control, 0V operation, undervoltage and overvoltage protection, open MOSFET detection, ability to allow reverse current, Hot Swap capability, and fault and status outputs. All of this functionality comes wrapped in space-saving 12-pin DFN (3mm \times 3mm) and MSOP packages, making it possible to produce an ideal diode solution in a smaller footprint than conventional diodes. 