

IN THIS ISSUE...

COVER ARTICLE

2-Phase, Non-Synchronous Boost Controller Simplifies Design of High Voltage, High Current Supplies1
Muthu Subramanian and Tick Houk

Linear in the News.....2

DESIGN FEATURES

Reliable Precision Voltage Reference with 5ppm/°C Drift is Factory Trimmed and Tested at -40°C, 25°C and 125°C7
Michael B. Anderson and Brendan Whelan

Ultralow Noise 15mm×15mm×2.8mm μ Module™ Step-Down Regulators Meet the Class B of CISPR 22 and Yield High Efficiency at up to 36V_{IN}10
Judy Sun, Jian Yin, Sam Young and Henry Zhang

Dual Hot Swap™ Controller Brings Digital Monitoring to AdvancedTCA, μ TCA and AMC Applications.....15
Josh Simonson

±32V Triple-Output Supply for LCDs, CCDs and LEDs Includes Fault Protection in a 3mm × 3mm QFN20
Eko T Lisuwandi

PD Interface for PoE+ Includes 25.5W Classification and Protection Features in a Low Profile 4mm × 3mm DFN26
Kirk Su

DESIGN IDEAS

.....30-42
(complete list on page 30)

Design Tools.....43

Sales Offices44

2-Phase, Non-Synchronous Boost Controller Simplifies Design of High Voltage, High Current Supplies

by Muthu Subramanian and Tick Houk

Introduction

Due to an increasing need for high power step-up power supplies in automotive and industrial applications, Linear Technology has recently introduced the LTC3862 family of 2-phase, single output non-synchronous boost DC/DC controllers. The LTC3862 provides a flexible, high performance step-up controller in three convenient package options: GN24, 5mm × 5mm 24-pin exposed pad QFN and 24-pin exposed pad TSSOP. The LTC3862 is optimized for power MOSFETs that require 5V gate drive, whereas the LTC3862-1 is designed for 10V gate drive MOSFETs.

The LTC3862 utilizes a fixed frequency, peak current mode control topology to drive ground-referenced power MOSFETs, each with a current sense resistor in its source. The use of a precision transconductance (g_m) error amplifier allows for easy loop compensation and facilitates the parallel connection of several ICs in multiphase applications. The operating frequency can be programmed from 75kHz to 500kHz using a single resistor, and a phase lock loop allows the switching frequency to be synchronized to an external clock over a 50kHz to 650kHz range.

The LTC3862 is a versatile control IC optimized for a wide variety of step-up DC/DC converter applications. This makes it easy to optimize efficiency, size and weight of the power supply, while keeping component and manufacturing costs low.

A 24V, 5A Car Audio Power Supply

Today's high end car audio systems require significant power to drive upwards of seven speakers inside the passenger compartment. High frequency speakers such as tweeters are generally very efficient, but low frequency drivers such as subwoofers require substantial power to achieve high volume. In addition to the need for high power, the car audio system should be immune to changes in the battery voltage. These requirements can be met through the use of a step-up converter for the power

continued on page 3


LT, LTC, LTM, Burst Mode, OPTI-LOOP, Over-The-Top and PolyPhase are registered trademarks of Linear Technology Corporation. Adaptive Power, Bat-Track, BodeCAD, C-Load, DirectSense, Easy Drive, FilterCAD, Hot Swap, LinearView, μ Module, Micropower SwitcherCAD, Multimode Dimming, No Latency $\Delta\epsilon$, No Latency Delta-Sigma, No R_{SENSE}, Operational Filter, PanelProtect, PowerPath, PowerSOT, SmartStart, SoftSpan, Stage Shedding, SwitcherCAD, ThinSOT, TimerBlox, True Color PWM, UltraFast and VLDO are trademarks of Linear Technology Corporation. Other product names may be trademarks of the companies that manufacture the products.



Linear in the News...

Linear Unveils Battery Stack Monitor for Hybrid/Electric Vehicles

In September, Linear announced an innovative new product focused on the challenge of monitoring a stack of batteries for applications such as hybrid/electric vehicles and battery backup systems. The company announced the product in a series of press meetings in North America, Europe and Asia, including press conferences in Munich and Beijing, as well as meetings in Silicon Valley, London, Paris, Stockholm, Seoul and Tokyo. Linear has already seen significant customer interest in the device for a broad range of applications.

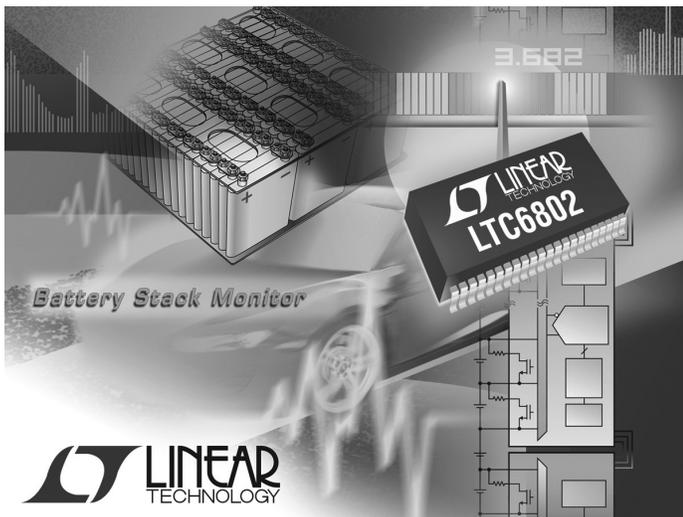

The anticipated migration to zero emission vehicles awaits the development of viable high performance battery systems. Lithium batteries offer the promise of high energy density, but improving reliability, prolonging lifetime and meeting cost targets require sophisticated battery management electronics. Battery management electronics must accurately monitor and balance each individual battery cell in long, high voltage battery strings—the type required for high power applications. This is a significant electronics challenge, combining automotive demands with the task of extracting small differential voltages from 0V to more than 1000V of common mode voltage. To address this need, Linear Technology developed the LTC6802.

A single LTC6802 multicell battery monitoring IC is capable of precisely measuring the voltages of up to 12 series-connected battery cells. For longer battery strings, multiple LTC6802s can be placed in series to monitor large numbers of battery stacks. The LTC6802's novel stacking technique allows multiple LTC6802s to be placed in series without optocouplers or isolators. Stacked LTC6802s can precisely measure all battery cell voltages, independent of battery string size, within 13ms.

The LTC6802's maximum measurement error is less than 0.25%, which allows cells to operate over their full charge and discharge limits, thus maximizing lifetime and useful battery capacity. The LTC6802 monitors each cell for undervoltage and overvoltage conditions, communicating to a host controller via a 1MHz serial interface. To address overcharge conditions, each of the LTC6802's inputs supports a MOSFET switch for quick individual cell discharge.

The LTC6802 incorporates a number of other features in its 8mm × 12mm surface mount package, including temperature sensor inputs, GPIO lines and a pin-accessible precision voltage reference.

The LTC6802 is fully specified for operation from -40°C to 85°C and offers diagnostics and fault detection. The combined robustness, exceptional precision and tiny package directly address the critical requirements of high powered, high performance battery systems.

EDN Debuts Jim Williams Article Archive

EDN magazine has launched an archive of articles on their website, entitled, "How-to articles and Design Ideas from EDN's most revered contributor, Jim Williams." Thus far, EDN has posted Jim Williams' in-depth applications articles from the present, going back to 1994—42 articles so far. The magazine has plans to continue building the archive, eventually posting articles as far back as 1980.

This work is a tribute to the significant contributions made to the electronics design community by Jim Williams and the yeoman efforts of EDN's analog editor, Paul Rako to make these technical articles available to a wide range of readers worldwide. You can access the articles and watch the archive as it grows at www.edn.com/jimwilliams.

Linear Technology at IIC China Conference

Linear will have a booth at three IIC Conference locations in the coming months: February 26–27 in Shenzhen, March 2–3 in Xian, and March 5–6 in Beijing.

At the conference, Linear will focus on products for the industrial and automotive markets. China continues to be a significant growth market for Linear in a number of key product areas, including:

- Data converters for industrial applications
- Power products and signal conditioning products for industrial applications
- Power μ Module™ DC/DC regulators
- Products for automotive applications, including:
 - Multicell battery stack monitors
 - Current sense amplifiers
 - LED drivers 

LTC3862, continued from page 1

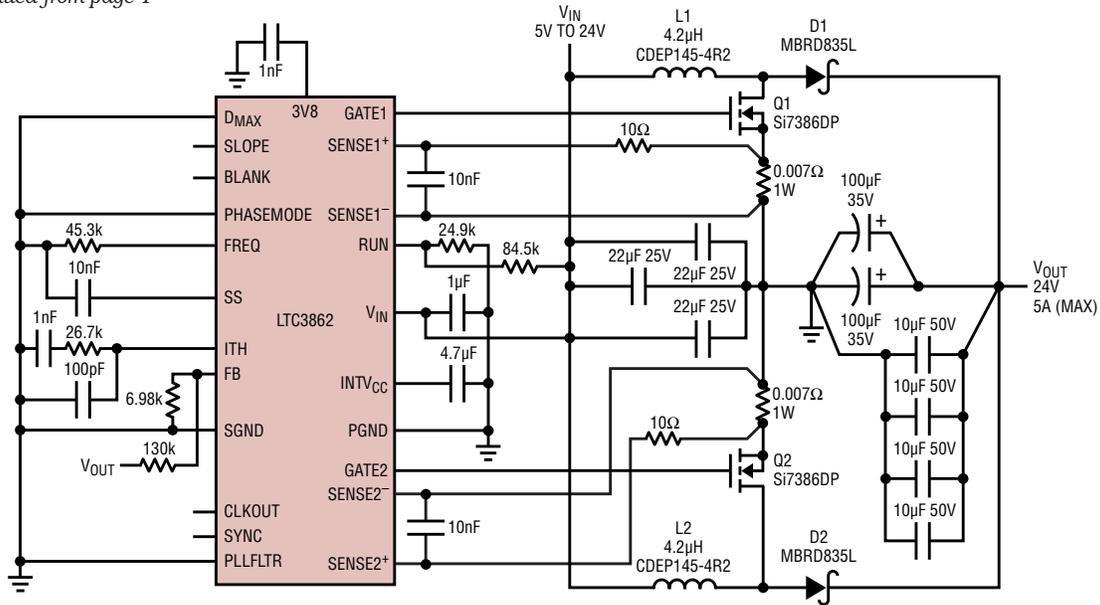


Figure 1. A 120W 2-phase, 24V/5A output car audio power supply

amplifiers. Figure 1 shows a 2-phase, 24V/5A output audio power supply that operates from a car battery, and Figure 2 shows the efficiency curve for this converter.

A 2-phase design with an operating frequency of 300kHz allows the use of significantly smaller output capacitors and inductors than a single-phase design. To keep the output ripple voltage below 60mV peak-to-peak and satisfy the RMS ripple current demand, a combination of two 100µF, 35V aluminum electrolytic capacitors are connected in parallel with four 10µF, 50V ceramic capacitors. The 4.2µH, 10.6A inductor (CDEP145-4R2) from Sumida Inductors is chosen for its high

A 2-phase design with an operating frequency of 300kHz allows the use of significantly smaller output capacitors and inductors than a single-phase design.

Also, the output current of this converter can easily be scaled by adding additional power stages and controllers, without modifying the basic design.

saturation current rating and surface mount package design.

The MOSFET is a Vishay Si7386DP, which has a maximum $R_{DS(ON)}$ of 7mΩ at $V_{GS} = 10V$ and 9.5mΩ at $V_{GS} = 4.5V$. The 35V, 8A Schottky from On Semiconductor (MBRD835L) offers surface mount capability and small size. It should be noted that the output current of a converter such as this can easily be scaled by adding additional power stages and controllers, without modifying the basic design.

Excellent Channel-to-Channel Current Matching Ensures a Balanced Thermal Design

In order to provide the best channel-to-channel inductor current matching, the LTC3862 is designed to make the transfer function from the output of the error amplifier (the ITH pin) to the current comparator inputs (SENSE+ and SENSE- pins) as accurate as possible. The specification for the maximum current sense threshold is 75mV, and the channel-to-channel ($V_{SENSE1} - V_{SENSE2}$) mismatch specification is $\pm 10mV$, over the $-40^{\circ}C$ to $150^{\circ}C$ temperature range. This excellent matching ensures balanced inductor currents and a thermally stable design, even with multiple regulators daisy-chained together. Figure 3 shows how

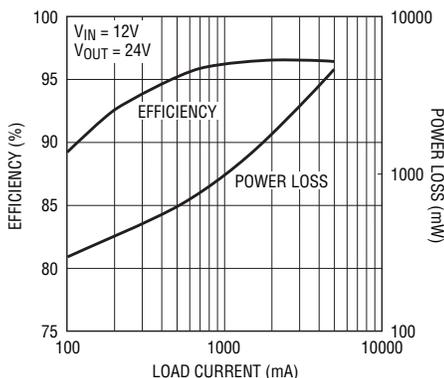


Figure 2. Efficiency and power loss vs load current for the 120W car audio power supply

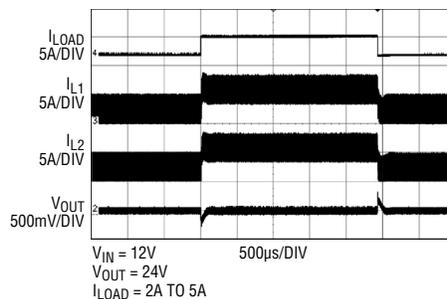


Figure 3. Inductor current waveforms in load step show accurate current matching between load sharing channels

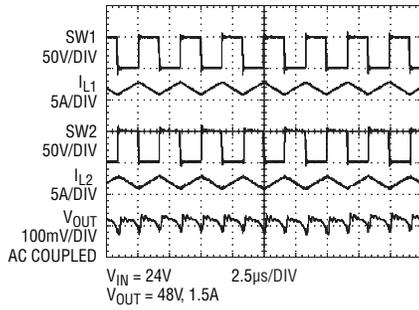


Figure 4. Inductor current and switch node voltage waveforms at heavy load, continuous conduction mode (CCM)

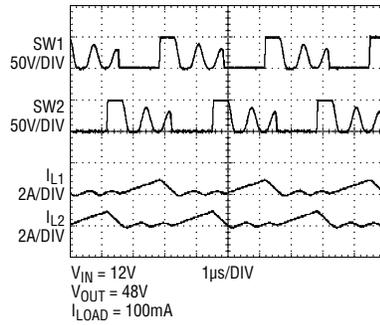


Figure 5. Inductor and switch node voltage waveforms at light load, discontinuous conduction mode (DCM)

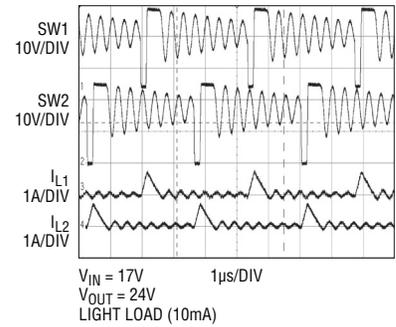


Figure 6. Inductor and switch node voltage waveforms at light load (pulse-skipping)

well matched the inductor currents are for the car audio power supply during a load step.

Constant Frequency Operation over a Wide Load Current Range

Constant frequency operation eases the task of input and output filter design, and prevents a power supply from becoming audible at light load. At heavy load, the inductor currents are generally continuous (CCM), as shown in Figure 4. At light load, the inductor current will go discontinuous (DCM), as shown in Figure 5. When the load current drops below what can be supported by the minimum on-time of the converter (approximately 180ns), the controller will begin to skip cycles in order to maintain output regulation,

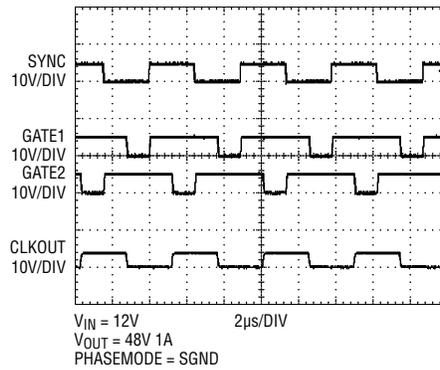


Figure 7. Synchronizing the LTC3862 to an external clock using the phase lock loop

the better, since constant frequency operation is maintained down to this threshold. In Figure 6 the onset of pulse-skipping occurs at a relatively low 0.2% of the maximum load current.

For systems where synchronization to an external clock is required, the LTC3862 contains a phase lock loop (PLL). Figure 7 illustrates the switching waveforms with an external sync signal applied to the SYNC pin.

Strong Gate Drivers and a High Current Internal LDO Complete the Package

In high output voltage systems, switching losses in the power MOSFETs can sometimes exceed the conduction losses. In order to reduce switching losses as much as possible, the LTC3862 incorporates strong gate drivers. The PMOS pull-up transistor has a typical $R_{DS(ON)}$ of 2.1Ω, and the NMOS pull-down transistor has a typical $R_{DS(ON)}$ of 0.7Ω. In addition to reducing switching losses, these strong gate drivers allow two power MOSFETs to be connected in paral-

as shown in Figure 6. This is a normal operating condition that doesn't cause any problems in the system, as long as the peak inductor current is low.

In general, the lower the load current at the onset of pulse-skipping,

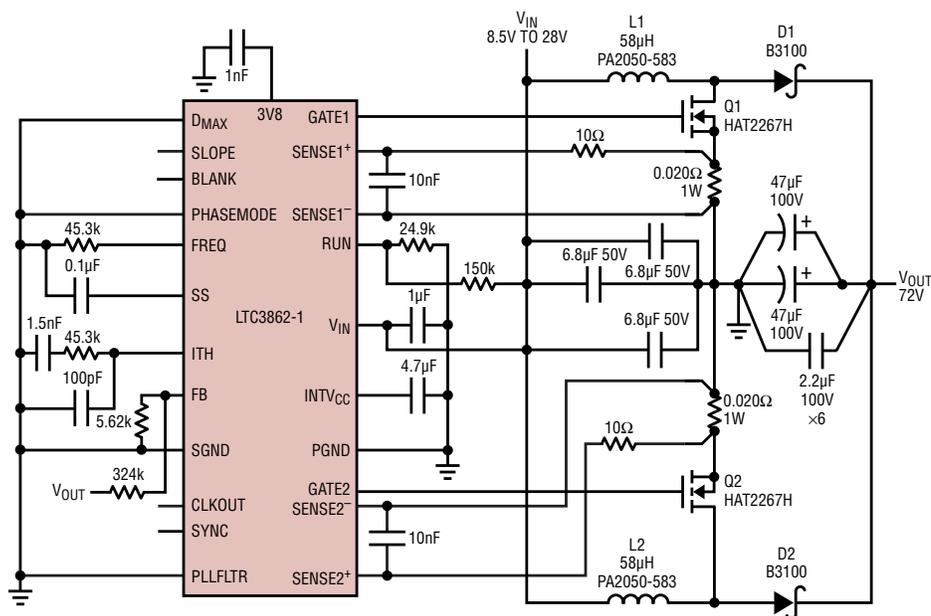


Figure 8. An 8.5V-28V input, 72V/1.5A output low emissions diesel fuel injector actuator supply

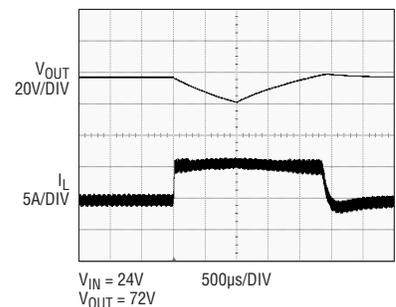


Figure 9. Load step waveforms for diesel fuel injector actuator supply

lel for each channel in high current applications.

In order to simplify operation in single-supply systems, the LTC3862 includes a 5V low dropout regulator (LDO) that can support output currents up to 50mA. The use of a PMOS output transistor ensures that the full supply voltage is available for driving the power MOSFETs under low supply conditions, such as during automotive cold cranking. An undervoltage lockout circuit detects when the LDO output voltage falls below 3.3V and shuts off the gate drivers, thereby

protecting the power MOSFETs from switching at low V_{GS} .

The LTC3862 is capable of operation over a 4V to 36V input voltage range, making it suitable for a wide variety of boost applications.

Lower Emissions Diesel Fuel Injection: A 8.5V–28V Input, 72V, 1.5A Output Boost

Tomorrow’s low emissions diesel fuel injection systems require more precise and faster actuation of the fuel injectors than do their gasoline counterparts. Stepping up the voltage

of the system is an easy way to achieve fast actuation by increasing di/dt in the actuator, since the energy stored on a capacitor is $CV^2/2$. Boosting the car battery voltage from 13V to 72V significantly increases the di/dt , enabling faster actuation. The actuation of the injector typically discharges the supply capacitor by 10V–20V, after which the boost converter recharges the output cap to 72V. Figure 8 illustrates this 8.5V to 28V input, 72V/1.5A output 2-phase boost converter. Figure 9 illustrates the load step for a simulated injector.

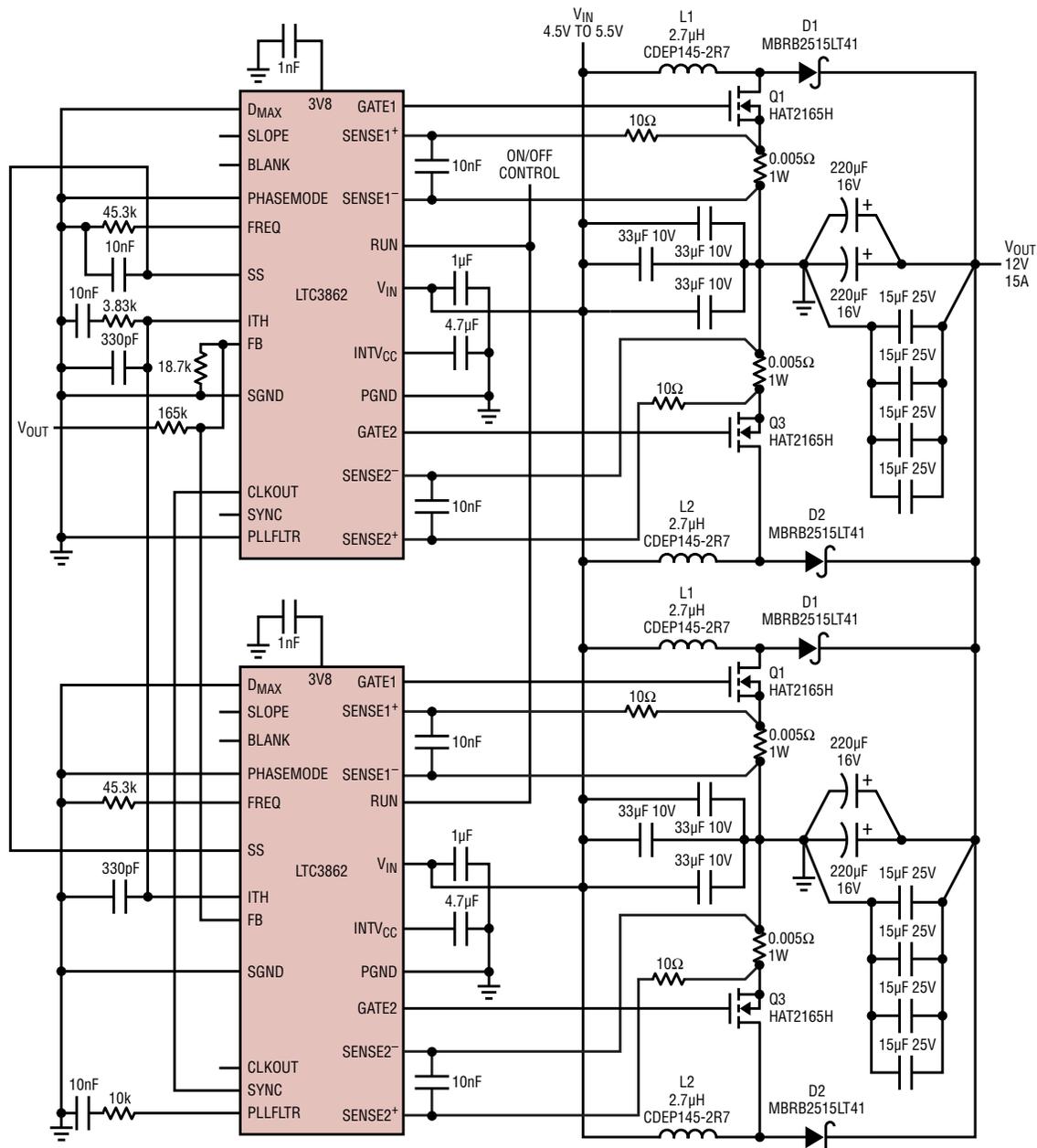


Figure 10. A 4-phase, 12V/15A industrial power supply that operates from a 5V input

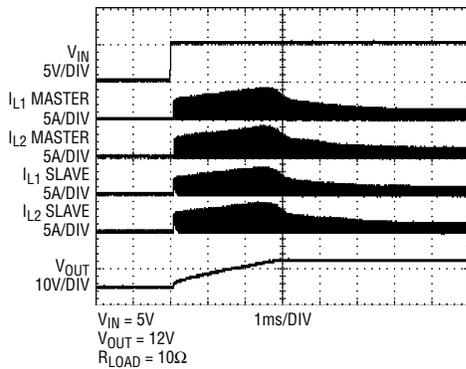


Figure 11. Power supply start-up waveforms for 4-phase, 12V/15A industrial power supply

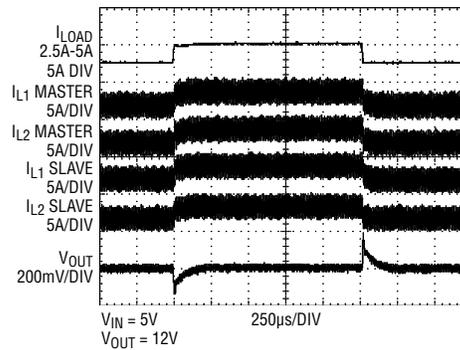


Figure 12. Load step waveforms for 4-phase, 12V/15A industrial power supply

This power supply operates at a switching frequency of 300kHz in order to reduce switching losses and uses a 57.8μH, 5A inductor (PA2050-583). An 80V Renesas HAT2267H MOSFET was chosen for this application, in order to provide sufficient guardband above the 72V output. The MOSFET has a maximum $R_{DS(ON)}$ of 13mΩ at $V_{GS} = 10V$. The Diodes Inc surface mount diode (B3100) was chosen for the 3A output current level. A combination of a two 47μF, 100V electrolytic and six 2.2μF, 100V low ESR ceramic capacitors are used to reduce the output ripple to below 100mV peak-to-peak and satisfy the RMS ripple current requirement.

A 4-Phase, 5V Input, 12V/15A Output, Industrial Power Supply

Figure 10 illustrates an industrial power supply that converts a 5V input to a 12V output at up to 15A of load current. The use of four phases greatly eases the task of choosing the power components, and reduces output ripple significantly. Figure 11

In high output voltage systems, switching losses in the power MOSFETs can sometimes exceed the conduction losses. In order to reduce switching losses as much as possible, the LTC3862 incorporates strong gate drivers. The PMOS pull-up transistor has a typical $R_{DS(ON)}$ of 2.1Ω, and the NMOS pull-down transistor has a typical $R_{DS(ON)}$ of 0.7Ω. In addition to reducing switching losses, these strong gate drivers allow two power MOSFETs to be connected in parallel for high current applications.

shows the start-up waveforms for this converter. Figure 12 shows the load step waveforms.

Multiphase operation is made possible using the PHASEMODE, SYNC and CLKOUT pins. The PHASEMODE pin controls the phase relationship between GATE 1 and GATE 2, as well as between GATE 1 and CLKOUT. The CLKOUT pin of a master controller is connected to the SYNC pin of a slave, where the phase lock loop ensures proper synchronization. The PHASEMODE pin can be used to program 2-, 3-, 4-, 6- and 12-phase operation.

48V/5A Demo Circuit

The DC1286A demonstration circuit board is designed for high power applications, providing a 48V/5A output using the GN24 package option of the LTC3862 or LTC3862-1. The 6-layer PCB design ensures proper routing of the SENSE lines, and exhibits minimal jitter even at 50% duty cycle. Jumpers are provided to easily change the BLANK time, PHASE, maximum duty, and SLOPE compensation. There is an optional onboard 12V V_{IN} supply to power the IC, and the component footprint provides flexibility to use various inductors, MOSFET's and diodes.

Conclusion

The LTC3862 is a versatile control IC optimized for a wide variety of step-up DC/DC converter applications. Its flexible, high performance operation and three convenient package options make it possible to optimize efficiency, size and weight of the power supply, while keeping the total component and manufacturing costs low.

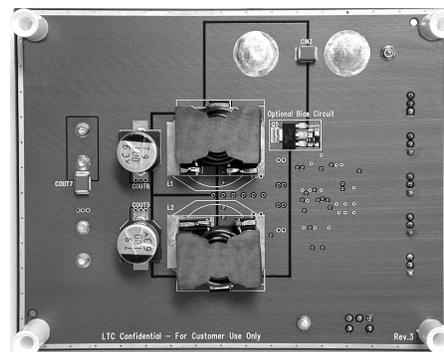
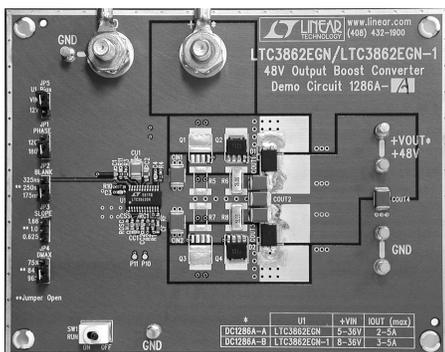


Figure 13. 48V/5A output, high power demonstration circuit

Reliable Precision Voltage Reference with 5ppm/°C Drift is Factory Trimmed and Tested at -40°C, 25°C and 125°C

by Michael B. Anderson and Brendan Whelan

Introduction

High precision requirements are no longer limited to the most exotic and expensive measurement equipment. Designers of industrial monitors and automotive monitor and control circuits are using precision circuits to maximize the performance and uninterrupted operating times of their products. Improved precision allows for more accurate assessment of sensor outputs that measure ambient conditions, equipment position, battery condition, component wear and many other system indicators. Precise and consistent measurements are the key to managing system elements that change very little over their operating lives. Recognizing these slight changes can allow estimation of the remaining lifetime of lamps, motors, and other components, or allow control of battery charge and discharge to maximize operating life. These applications not only require high accuracy, low drift and low noise, but also a wide operating temperature range and reasonable cost.

Factory Calibration Means Dependable Precision

The LTC6652 reference is a precision low drift voltage reference that includes advanced curvature compensation circuitry and post-package trim. To guarantee reliable performance, these parts are tested at -40°C, 25°C and 125°C to verify they meet specification across the entire temperature range. This comprehensive testing ensures that the LTC6652 can be used with confidence in demanding applications. One result of this testing is demonstrated in Figure 1. The output voltage versus temperature for several randomly chosen parts shows a drift characteristic that is consistent from part to part. This is a result of a propri-

etary curvature compensation circuit that tracks the operating conditions and the manufacturing process, yielding consistent results. Figure 2 shows a typical temperature drift distribution of randomly selected production tested LTC6652s, illustrating how well the design and testing methodology works. Finally, the initial accuracy distribution is tightly controlled, as shown in Figure 3.

Compare the Real Specs: Is the Temperature Range Operating or Functional?

When comparing voltage references for use in demanding environments, it is important to know, with confidence, how the voltage reference performs at the extremes. When it is important for the reference to provide precision (not just survive) in a harsh environment, the LTC6655 leaves most competing voltage references behind.

For example, many applications requiring a precision reference are designed to work over the industrial temperature range (-40°C to 85°C). If the ambient temperature reaches 85°C, the interior of the enclosure and the temperature of the reference will

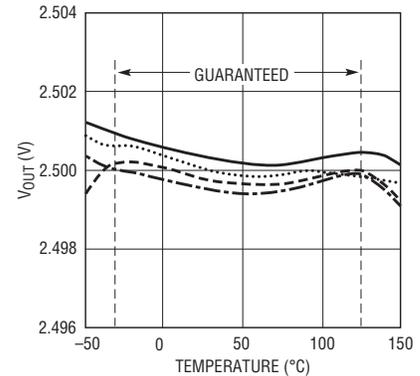


Figure 1. Typical drift characteristics of production trimmed and tested parts

likely exceed 85°C. It is not uncommon in this case for the interior of a circuit enclosure to climb above 100°C due to the thermal dissipation of its components. In addition, any comparable voltage reference fully loaded at 5mA with a 13.2V input voltage would self-heat an additional 18°C, raising its own internal junction temperature to 118°C. This temperature is well outside the useful range of most voltage references. The LTC6652, however, maintains exceptional performance in these conditions, despite the extreme environment. By comparison, the drift of a reference specified only to 85°C will

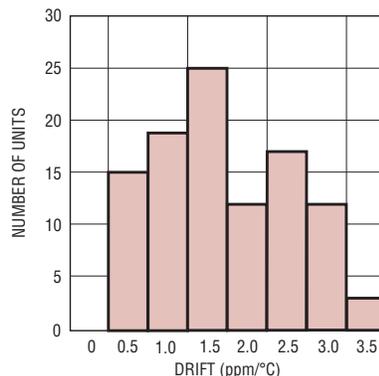


Figure 2. Drift distribution (-40°C to 125°C)

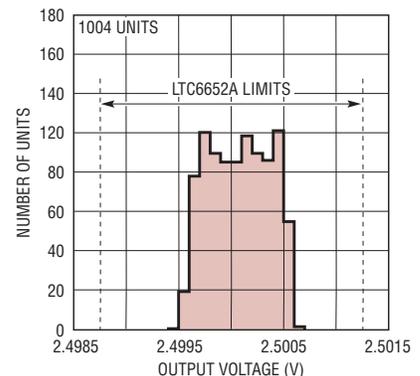


Figure 3. Typical V_{OUT} distribution for LTC6652-2.5

likely exhibit substantial additional error, or it may even fail to operate. Other references that claim similar performance to the LTC6652 often are only “functional”, meaning they don’t fail, but they don’t meet specification either at temperatures exceeding 85°C or below 0°C. These competing parts are rarely tested across their entire specified temperature range. The reality of industrial circuit design is that in many cases, component specifications over “industrial” temperatures are woefully inadequate.

In contrast, every LTC6652 is fully tested at 25°C, -40°C and again at 125°C for every device, not just a small sample. This extensive testing proves the consistently high quality of the LTC6652 over its entire wide temperature range.

Further, the LTC6652 was designed from the ground up to accommodate a wide temperature range. Figure 1 clearly illustrates its consistent performance over the entire range. There is no need to question or derate the performance of a system that uses the LTC6652 at its temperature extremes. The consistent, guaranteed performance makes it easy to design, specify and calibrate a high performance system. This is not the case with some competing products.

Eliminate Field Calibration

After any precision reference is soldered onto a printed circuit board, thermal hysteresis will likely shift the output from its factory trimmed value. Further temperature cycling will also contribute to a shift in the output voltage. Over time, the output will tend to drift slightly as well due to aging of the circuit. The circuit design, fabrication process and mechanical design of the LTC6652 is optimized for low thermal hysteresis and excellent long-term stability, reducing the need for field calibration. Thermal hysteresis is caused by differing rates of expansion and contraction of materials within a packaged semiconductor device as the device experiences temperature changes. As the package material and the semiconductor die expand and contract at different rates, mechani-

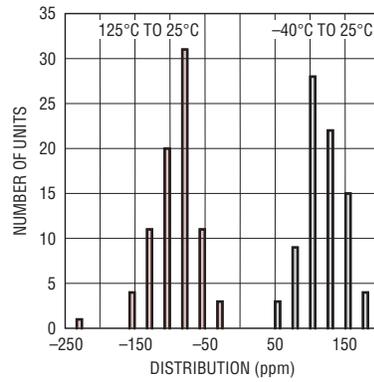


Figure 4. Hysteresis plot (-40°C to 125°C)

cal force changes device parameters (ever so slightly) and cause the output voltage to change. This change is measured in parts per million (ppm) and is shown in Figure 4.

The LTC6652 boasts a typical thermal hysteresis value of 105ppm over its full temperature range. What this means is that when a device goes

The LTC6652 reference family is designed and factory trimmed to yield exceptional drift and accuracy performance. The entire family is guaranteed and production tested at -40°C, 25°C and 125°C to ensure dependable performance in demanding applications. Low thermal hysteresis and low long-term drift reduce or eliminate the need for field calibration.

from room temperature to 125° and back again to room temperature, the output will typically shift 105ppm. For a 2.5V voltage option, the output would shift -260µV. A cold excursion would shift the most recent room temperature measurement +260µ. Typical hysteresis of 105ppm is equivalent to 0.0105%; just a small fraction of the initial accuracy.

It may be convenient to compare typical values for thermal hysteresis when choosing a voltage reference. It is important to remember that these numbers do not tell the whole story. It is the distribution of expected hysteresis that must be used to determine the expected error caused by temperature cycling. Referring to Figure 4, some parts will have better or worse hysteresis. This chart helps to estimate a realistic error budget. This is something our competitors don’t always include, yet is critically important when specifying precision systems.

Over time a reference is likely to shift on its own even if it’s kept at a constant temperature. This is known as long-term drift. Long-term drift is measured in ppm/√khr and has a logarithmic characteristic where the change in output voltage decays as time passes. Figure 5 shows the long-term drift of the LTC6652. Note that most of the drift occurs within the first 1,000 or 2,000 hours as the PCB and package settle. Afterward the drift tends to settle, and the slope is reduced over time as a function of √khr. Direct measurement on soldered down parts is the only way to determine

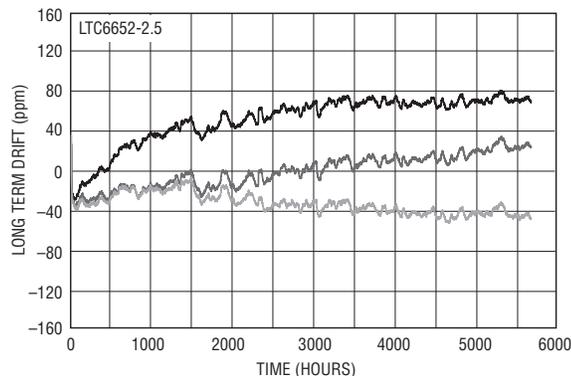


Figure 5. Example of long-term drift

long-term drift. Accelerated testing does not work. Some users burn in their boards, which helps eliminate this initial slope, further reducing the effect of long-term drift.

The three curves shown in Figure 5 give a general indication of how much long-term drift to expect. The typical specification is $60\text{ppm}/\sqrt{\text{kHz}}$, which translates into $150\mu\text{V}$ drift. Combining the typical thermal hysteresis and long-term drift numbers yields 165ppm . To put this in perspective, the LTC6652 temperature coefficient is typically $2\text{ppm}/^\circ\text{C}$ over 165°C temperature range, which yields 330ppm due to drift alone. The combined thermal hysteresis and long-term drift is half this number (or just 20% of the maximum drift specification). The superior thermal hysteresis and long-term drift performance of the LTC6652 ensures accuracy and reliability over the product lifetime, virtually eliminating the need for field calibration.

Small Footprint and Output Capacitor Optional

The performance of the LTC6652 is often only found in larger packages such as an SOIC. However, the LTC6652 is packaged in a small 8-lead MSOP and does not require an input or output capacitor. This minimizes required board space, thus simplifying the design of applications with tight PCB constraints such as small sensor enclosure applications. Another advantage of not using capacitors is eliminating energy storage devices tied to sensitive circuits. This

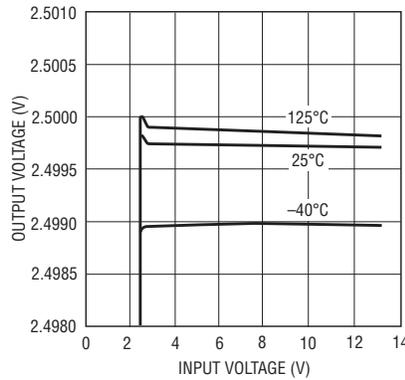


Figure 6. Line regulation

The LTC6652 reference family has seven output voltage options, making it suitable for a variety of today's demanding applications. These options are 1.25V, 2.048V, 2.5V, 3V, 3.3V, 4.096V, and 5V.

is a useful feature in safety critical systems, where energy storage must be minimized. If, however, low noise is a priority, an input capacitor may be added to suppress high frequency transients on the supply line, while an output capacitor will reduce wideband noise and improve AC PSRR. Either way, the LTC6652 offers stable operation. Small size and a range of useful input and output capacitors allows the LTC6652 to satisfy the requirements of many different applications. This includes everything from small,

tight-fitting portable applications to high precision, low noise measurement applications.

Output Can Source and Sink Current

The LTC6652 is a series voltage reference that can source current, but it can also sink current like a shunt reference. Some series voltage references can only source output current and rely on a resistor divider for feedback and to sink a small amount of current. These types of devices can experience long settling times, especially when charge is kicked back from a switched capacitor circuit causing the output voltage to rise. The sink (overvoltage) settling time on a source only reference is dominated by the RC time constant of the output capacitor and the resistive divider. For example, a $2.2\mu\text{F}$ output capacitor and a $125\text{k}\Omega$ resistive divider will have a 275ms time constant. Depending on the size of the perturbation and the system precision, a source only reference may not settle in a timely fashion. The LTC6652 current sink capacity is 5mA and will dynamically respond for faster settling.

Shunt references are two terminal devices that maintain the output voltage by sinking more or less current. The sinking ability of the LTC6652 allows it to operate in a similar, but more efficient manner. In fact, for voltage options of 3V or higher, the V_{IN} pin can actually go below the V_{OUT} pin while sinking currents of $100\mu\text{A}$ and higher and still maintain good regulation.

Wide Input Range, Low Dropout, and Seven Voltage Options

The LTC6652 reference family has seven output voltage options to choose from, making it suitable for a variety of today's demanding applications. These options are 1.25V , 2.048V , 2.5V , 3V , 3.3V , 4.096V , and 5V . For low input voltage requirements, the 1.25V and 2.048V options work with input voltages down to 2.7V . The other five options require only 300mV input-to-

continued on page 14

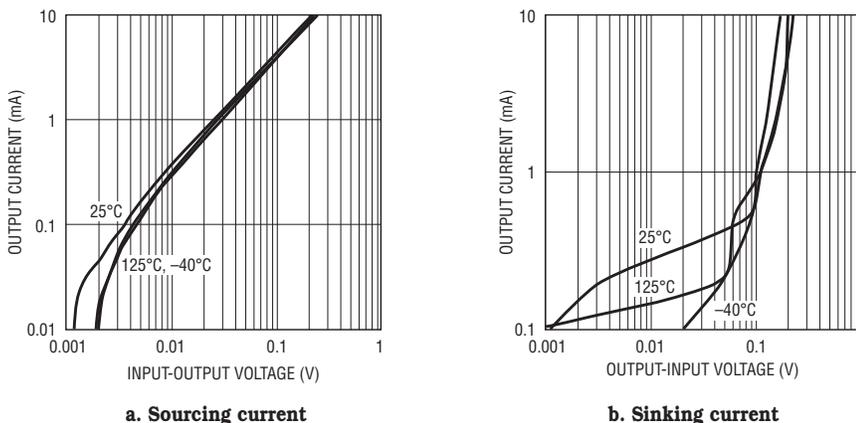


Figure 7. Dropout voltage sourcing and sinking current

Ultralow Noise 15mm×15mm×2.8mm μ Module Step-Down Regulators Meet the Class B of CISPR 22 and Yield High Efficiency at up to 36V_{IN}

by Judy Sun, Jian Yin, Sam Young and Henry Zhang

Introduction

Power supply designers face many tradeoffs. Need high efficiency, large conversion ratios, high power and good thermal performance? Choose a switching regulator. Need low noise? Choose a linear regulator. Need it all? Compromise. One compromise is to follow a switcher with a linear regulator (or regulators). Although this cleans up the output noise relative to a switcher-only solution, a good portion of the conducted and radiated EMI remains—even if ferrite beads, π filters, and LC filters are used. The problem can always be traced back to the switcher, where fast di/dt transitions and high switching frequencies

These μ Module step-down regulators are designed to achieve both high power density and meet EMC (electromagnetic compatibility) standards. The integrated ultralow noise feature allows both devices to pass the Class B of CISPR 22 radiated emission limit, thus eliminating expensive EMI design and lab testing.

lead to high frequency EMI, but some applications, especially those with large conversion ratios, require a switcher.

Fortunately, the LTM4606 and LTM4612 μ Module regulators offer the advantages of a switching regulator while maintaining ultralow conducted and radiated noise. These μ Module step-down regulators are designed to achieve both high power density and meet EMC (electromagnetic compatibility) standards. The integrated ultralow noise feature allows both devices to pass the Class B of CISPR 22 radiated emission limit, thus eliminating expensive EMI design and

Table 1. Feature comparison of ultralow noise μ Module regulators

Feature	LTM4606	LTM4612
V _{IN}	4.5V to 28V	5V to 36V
V _{OUT}	0.6V to 5V	3.3V to 15V
I _{OUT}	6A DC Typical, 8A Peak	5A DC Typical, 7A Peak
CISPR 22 Class B Compliant		
Output Voltage Tracking and Margining		
PLL Frequency Synchronization		
±1.5% Total DC Error		
Power Good Output		
Current Foldback Protection		
Parallel/Current Sharing		
Low Input and Output Referred Noise		
Ultrafast Transient Response		
Current Mode Control		
Programmable Soft-Start		
Output Overvoltage Protection		
Package	15mm × 15mm × 2.8mm	15mm × 15mm × 2.8mm

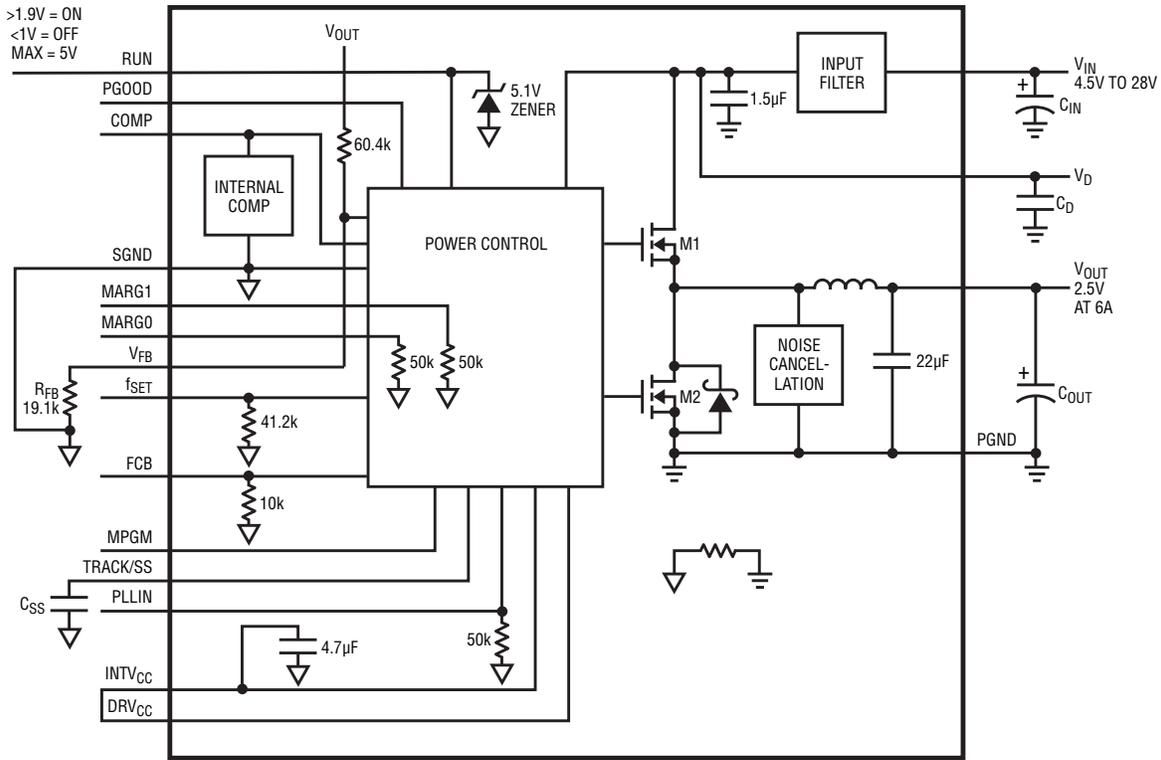


Figure 1. Simplified block diagram of the LTM4606 (LTM4612 is similar). Only a few capacitors and resistors are required to build a complete wide-input-range regulator.

lab testing. See Table 1 for a feature comparison of these two parts.

Both μ Module regulators are offered in space saving, low profile and thermally enhanced 15mm \times 15mm \times 2.8mm LGA packages, so they can be placed on the otherwise unused space at the bottom of PC boards for high-accuracy point-of-load regulation. This is not possible with linear regulators that require a bulky cooling system. Almost all support components are integrated into the μ Module package, so layout design is relatively simple,

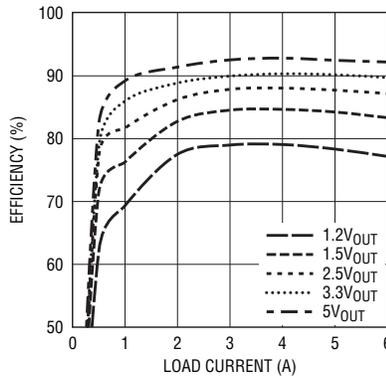


Figure 2. Efficiency of the LTM4606 with a 12V input.

requiring only a few input and output capacitors.

For more output power, both parts can be easily paralleled, where output currents are automatically shared due to the current mode control structure.

Easy Power Supply Design with Ultralow Noise μ Module Regulators

With a few external input and output capacitors, the LTM4612 can deliver 4.5A of DC output current

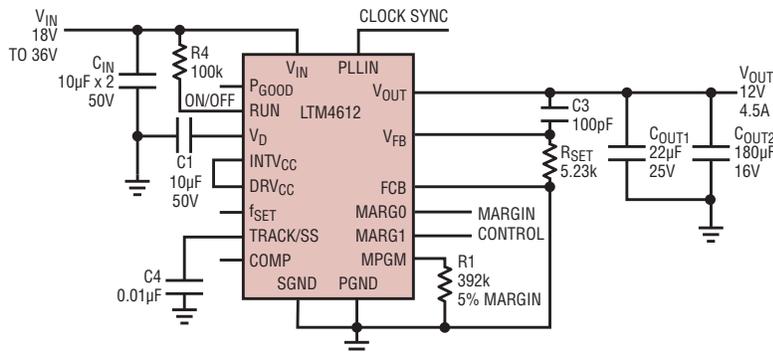


Figure 3. A few capacitors and resistors complete an 18V-36V input, 12V/4.5A output design.

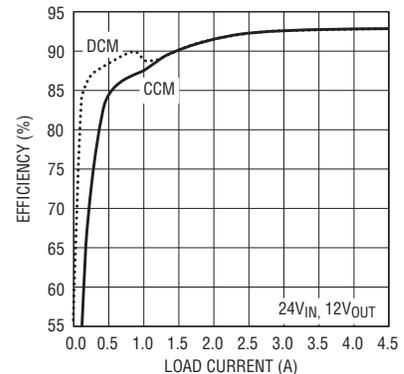


Figure 4. Efficiency for the circuit in Figure 3.

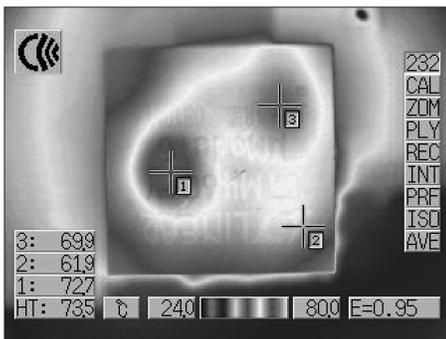


Figure 5. Thermal image of an LTM4606 with 24V input and 3.3V output at 6A

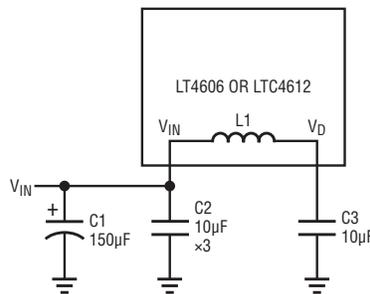


Figure 6. Input π filter reduces high frequency input noise.

Figure 3 shows a complete 18V–36V V_{IN} , 12V/4.5A V_{OUT} design with the LTM4612. Figure 4 shows the efficiency.

Both parts offer good thermal performance with a large output load current. Figure 5 shows the LTM4606 thermal image with 24V input and 3.3V output at 6A load current. The maximum case temperature is only 73.5°C with the 20W output power.

Both include a number of built-in features, such as controllable soft-start, RUN pin control, output voltage tracking and margining, PGOOD indicator, frequency adjustment and external clock synchronization. Efficiency can be further improved by applying an external gate driver voltage to the DRV_{CC} pin, especially in high V_{IN} applications. Discontinuous mode operation can be enabled to increase the light load efficiency.

Reduce Conducted EMI

Conducted input and output noise of switching regulators (aka ripple) is usually a problem when the regulator operates at high frequency, which is common in space-constrained applications. The LTM4606 and LTM4612 reduce peak-to-peak ripple at the input by integrating a high frequency inductor as shown in Figure 6. The external input capacitors at the V_D and V_{IN} pins form a high frequency input π filter. This effectively reduces conductive EMI coupling between the module and the main input bus.

Since most input RMS current flows into capacitor C3 at the V_D pin, C3 should have enough capacity to handle the RMS current. A 10 μ F ceramic capacitor is recommended. To effectively attenuate EMI, place C3 as close as possible to the V_D pin. The ceramic capacitors C2 mainly determine the ripple noise attenuation, so the capacitor value can be varied to meet the different input ripple requirements. C1 is only needed if the input source impedance is compromised by long inductive leads or traces.

Since these μ Module regulators are used in a buck circuit topology, the lowpass filter formed by the output inductor L and capacitor C_{OUT}

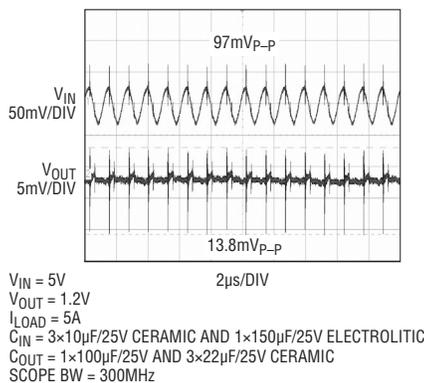


Figure 7. Input and output noise of comparable μ Module regulator without low noise feature

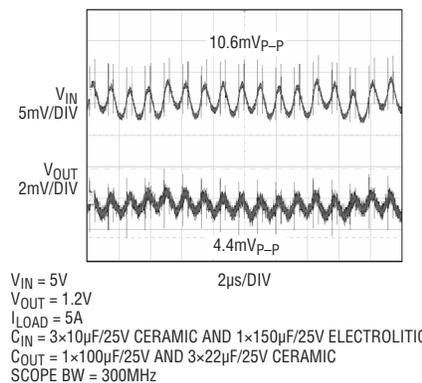


Figure 8. Input and output noise of LTM4606 μ Module regulator is significantly lower than the regulator in Figure 7.

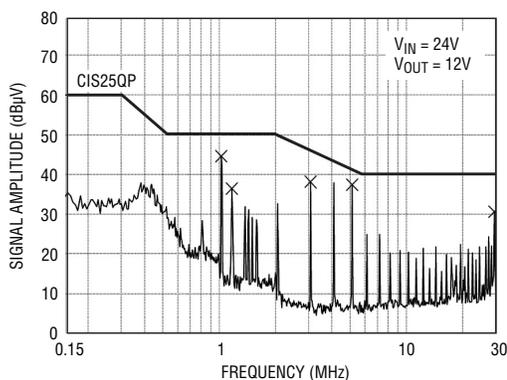


Figure 9. The conducted EMI test of the LTM4612 passes EMI standard CISPR 25 level 5.

and the LTM4606 can deliver 6A. The LTM4612’s programmable output can be precisely regulated in a 3.3V-to-15V range from a 4.5V-to-36V input; the LTM4606 can produce 0.6V to 5V from a 4.5V-to-28V range. With current mode control and optimized internal compensations, both offer stable output even in the face of significant load transients.

Figure 1 shows the simplified block diagram of the LTM4606 with an input from 4.5V to 28V and 2.5V/6A output. Figure 2 shows the efficiency test curves with 12V input voltage under CCM mode. About 92% efficiency is achieved at full load with LTM4606, running at 900kHz switching frequency.

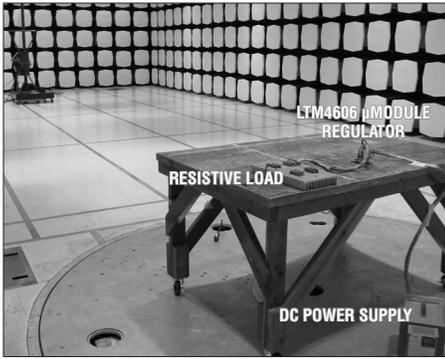


Figure 10. Setup of the radiated emission scan

can similarly reduce the conducted output EMI.

To show the relative noise attenuation of these μ Module regulators, a similar module without the low noise feature is compared to the LTM4606 for input and output noise, as shown in Figure 7 and Figure 8. Both modules are tested from 5V input to 1.2V output at 5A with resistive loads. The same board layout and I/O capacitors are used in the comparison. The results show that the LTM4606 produces much lower input and output noise, with a nearly 10 \times reduction of the peak-to-peak input noise and better than 3 \times reduction of the output noise compared to the similar module in Figure 7.

Figure 9 shows the conducted EMI testing results for the LTM4612 with a 24V V_{IN} , 12V/5A V_{OUT} , which accommodates the EMI standard CISPR 25 level 5. The input capacitance for this test comes from 4 \times 10 μ F/50V ceramics plus a single 150 μ F/50V electrolytic.

Reduce Radiated EMI

Switching regulators also produce radiated EMI, caused by the high dI/dt signals inherent in high efficiency regulators. The input π filter helps to limit radiated EMI caused by high dI/dt loops in the immediate module area, but to further attenuate radiated EMI, the LTM4606 and LTM4612 include an optimized gate driver for the MOSFET and a noise cancellation network.

To test radiated EMI, several setups are tested in a 10-meter shielded chamber as shown in Figure 10. To ensure a low baseline radiated noise,

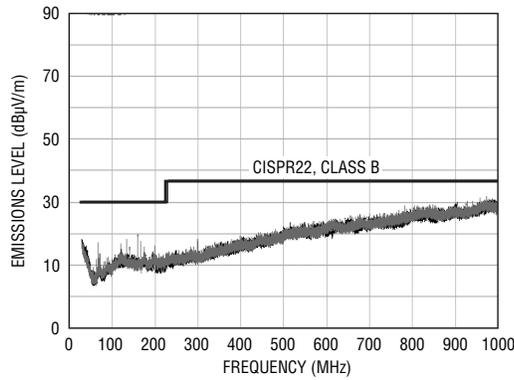


Figure 11. Radiated emission scan of baseline noise (no switching regulator module)

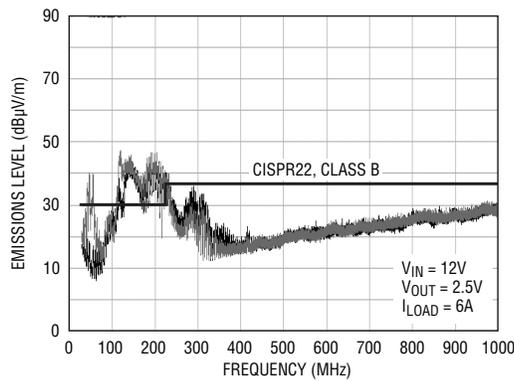


Figure 12. Radiated emission peak scan of a typical module without the low noise features.

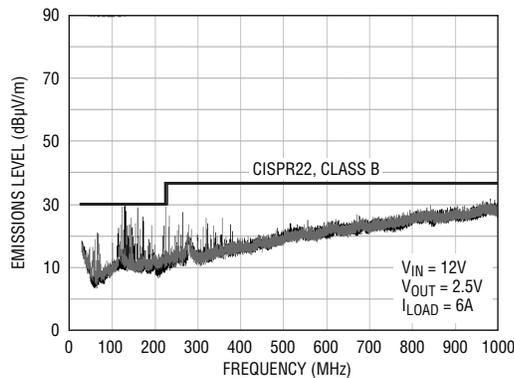


Figure 13. The radiated EMI test of the LTM4606 passes EMI standard CISPR 22 Class B.

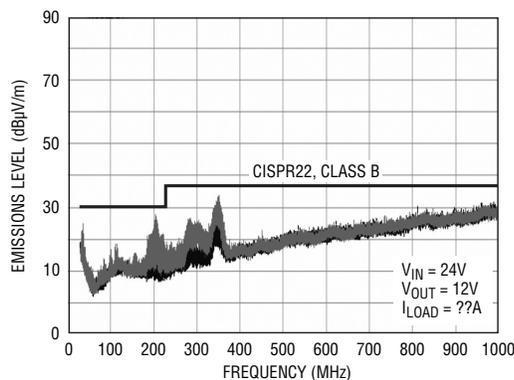


Figure 14. The radiated EMI test of the LTM4612 passes EMI standard CISPR 22 Class B.

Table 2. Noise margins are good for radiated emission results shown in Figure 13

Frequency (MHz)	Antenna Polarization	EUT Azimuth (Degrees)	Antenna Height (cm)	Uncorrected Amplitude (dB μ V)	ACF (dB/m)	Pre-Amp Gain (dB)	CBL (dB)	DCF (dB)	Corrected Amplitude (dB μ V)	Limit (dB μ V)	Margin (dB)
134.31	H	354	364	1.3	11.428	0	1.532	0	14.26	30	15.74
119.96	V	184	110	3.5	12.694	0	1.456	0	17.65	30	12.35
160.02	H	0	354	0.5	10.499	0	1.793	0	12.792	30	17.208
174.37	H	0	100	1.2	9.638	0	1.944	0	12.782	30	17.218
224.28	V	0	100	-1.87	10.586	0	2.044	0	10.76	30	19.24
263.63	H	0	371	-4.72	12.6	0	2.385	0	10.265	37	26.735

a linear DC power supply is used for the input, and a resistive load is employed on the output. The baseline noise is checked with the power supply providing a DC current directly to the resistive load. The baseline emission scan results are shown in Figure 11. There are two traces in the plot, one for the vertical and horizontal orientations of the receiver antenna.

Figure 12 shows the peak scan results of a μ Module buck regulator—not the LTM4606 or LTM4612—without the integrated low noise feature. The scan results show that the noise below 350MHz is produced by the μ Module switching regulator, when compared to the baseline noise level. Radiated EMI here does not meet the Class B of CISPR 22 (quasi-peak) radiated emission limit.

In contrast, Figure 13 shows the peak scan results of the low noise LTM4606 module. To ensure enough margin to the quasi-peak limit for different operation conditions, the six highest noise points are checked as shown in the table of Figure 13 using the quasi-peak measurement. The results show that it has more than 12dB μ V margin below the Class B of CISPR 22(quasi-peak) radiated emission limit.

Figure 14 shows the results for the LTM4612 meeting the Class B of CISPR 22 radiated emission limit at 24V V_{IN} , 12V/5A V_{OUT} .

Conclusion

The LTM4606 and LTM4612 μ Module regulators offer all of the high performance benefits of switching regulators minus the noise issues. The ultralow

noise optimized design produces radiated EMI performance with enough margin below the Class B of CISPR 22 limit to simplify application in noise-sensitive environments.

Design is further simplified by exceptional thermal performance, which allows them to achieve high efficiency and a compact form factor. A low profile 15mm \times 15mm \times 2.8mm package contains almost all of the support components—only a few input and output capacitors are required to complete a design. Several μ Module regulators can be easily run in parallel for more output power. The versatility of these parts is rounded out by optional features such as soft-start, RUN pin control, output voltage tracking and margining, PGOOD indicator, frequency adjustment and external clock synchronization. 

LTC6652, continued from page 9

output headroom while fully loaded, and they require less headroom with a reduced load or while sinking current. Popular application requirements, such as a 2.5V reference operating on a 3V supply, or a 4.096V reference operating on a 5V supply, are easily accommodated. For high input voltage requirements, all voltage options work up to 13.2V. Regardless of input voltage the LTC6652 maintains its excellent accuracy as shown in the line regulation plot in Figure 6. A plot of the dropout voltage for both sourcing and sinking current is shown in Figures 7a and 7b, respectively.

Superior Performance

While many references share some features of the LTC6652, it's difficult to find any that include all the features at the same level of performance and reliability. Additional features include low noise, good AC PSRR, and excellent load regulation (both sourcing and sinking current). Low power consumption and a shutdown mode round out the feature list.

Conclusion

The LTC6652 reference family is designed and factory trimmed to

yield exceptional drift and accuracy performance. The entire family is guaranteed and production tested at -40°C, 25°C and 125°C to ensure dependable performance in demanding applications. Low thermal hysteresis and low long-term drift reduce or eliminate the need for field calibration. The small 8-lead MSOP package and sparse capacitor requirements minimize required board space. The wide input range from 2.7V to 13.2V and seven output voltage options will tackle the needs of most precision reference users. 

Dual Hot Swap Controller Brings Digital Monitoring to AdvancedTCA, μ TCA and AMC Applications

by Josh Simonson

Introduction

Recently ratified plug-in card bus standards, such as AdvancedTCA, μ TCA and AMC, reduce the number of power supplies that are routed across the connector when compared to earlier standards, such as CompactPCI. Bulk power is limited to one fairly high voltage supply, making for an efficient distribution channel. For instance, distributed 12V power is locally converted to lower voltages to minimize distribution currents and related losses in connectors and power handling circuitry. Some cards also have a lower voltage (3.3V) maintenance power supply that provides low current

Even with the simplification that new plug-in standards bring, there remain rigorous power, heat dissipation and reliability requirements for Hot Swap, monitoring and control. The LTC4222 satisfies these requirements with integrated dual Hot Swap controllers and voltage and current monitoring via an onboard ADC.

housekeeping functionality to a card even when the bulk supply is off.

Even with the obvious simplification that these standards bring, there remain rigorous power, heat dissipation and reliability requirements, which demand advanced Hot Swap, monitoring and control capability. The LTC4222 satisfies these requirements with dual Hot Swap controllers and integrated voltage and current monitoring via an onboard ADC.

Hot swapping requires a power switch to initially isolate the board, and a controller to slowly turn on the switch to minimize backplane distur-

Table 1. A few of the LTC4222's many features

Feature	Benefits
Wide Input Voltage Range: Operates from inputs of 2.9V to 29V, with 35V absolute maximum	<ul style="list-style-type: none"> <input type="checkbox"/> Suitable for 3.3V, 5V, 12V and 24V systems <input type="checkbox"/> Simplifies design because part functions on a semi-regulated supply <input type="checkbox"/> Large overvoltage transient range eases design tolerances for transient protection
10-Bit ADC: Monitors current, output voltage and external pin voltage	<ul style="list-style-type: none"> <input type="checkbox"/> Increases reliability <input type="checkbox"/> Board power information provides an early warning of board failure <input type="checkbox"/> Verify board is staying within its allotted power <input type="checkbox"/> Allows integrity check of redundant supply paths <input type="checkbox"/> Allows active power management to safely maximize power utilization within the chassis cooling constraints
I²C/SMBus: Communicates as a read-write slave device using a 2-wire serial interface	<ul style="list-style-type: none"> <input type="checkbox"/> Improves integration with the host system. Interface allows the host to configure the part, determine which faults are present or have occurred, and read back ADC measurements
Optionally Coupled Faults: The config pin allows channels to function independently or couples faults to shut down both channel if either generates a fault	<ul style="list-style-type: none"> <input type="checkbox"/> Provides flexibility for different architectures <input type="checkbox"/> Allows the part to power two independent sockets or sequence the application of power <input type="checkbox"/> Enables both channels to shut down on a fault, isolating a faulty board
Fast short Circuit Response: Fast (<1 μ s) current limit response to shorts	<ul style="list-style-type: none"> <input type="checkbox"/> Protects connector from overcurrent <input type="checkbox"/> Limits the disturbance to the input supply from a short circuit
Alert Host After Faults: When configured (using I ² C), faults activate an active pull-down on the ALERT pin	<ul style="list-style-type: none"> <input type="checkbox"/> Interrupting the host for immediate fault servicing limits system damage <input type="checkbox"/> Reduces the bus traffic for polling

bances. Since the Hot Swap controller monitors card voltage and current, it is a natural place to integrate higher level monitoring with a data converter. This provides detailed information about the health of the power path and the power consumption of down-stream circuits. Such information can be used to monitor performance over time and identify boards that are drifting towards failure or out of spec.

The LTC4222 works in applications from 24V (with transients to 35V) down to 3.3V where the operating input voltage could drop to 2.9V. Functionally, the LTC4222 is very similar to a pair of LTC4215s or LTC4260s. Table 2 compares features of the LTC4222, LTC4215 and LTC4260. Since all three parts may be used for 12V systems, Table 2 may be used to select the part(s) with the optimal set of features for a specific 12V application.

AMC Application

The LTC4222 combines a robust Hot Swap circuit with a data converter and I²C interface to allow power monitoring in addition to hot plug functionality and fault isolation. In a typical application, see Figure 1, the LTC4222 uses external N-channel pass transistors to isolate the hot swapped board from the backplane when it is first inserted. After a debounce time the controller can begin to apply power to the board or wait for a turn-on command from a host processor. Power is gradually ramped up to minimize any backplane disturbance. After the power-up process is complete, the LTC4222 continues to monitor for faults in the power path. The CONFIG pin controls whether the two channels start-up and turn-off at the same time or independently. Some of the major features of the LTC4222 are listed in Table 1.

An N-channel pass transistor, Q1, controls the application of power to V_{OUT1} on the board as in Figure 1. A series sense resistor, R_{SENSE1}, allows the LTC4222 to measure the current in the power-path with the ADC and provides the current sense input to the current limit and circuit breaker. Resistor R5 suppresses self-oscilla-

Table 2. Feature comparison of the LTC4222, LTC4215 and LTC4260

Feature	LTC4222	LTC4215	LTC4260
Channels	2	1	1
V _{DD} Abs Max	35V	24V	100V
V _{DD} Min	2.9V	2.9V	8.5V
Current Limit/Circuit Breaker	50mV	25mV	50mV
Circuit Breaker Precision	5%	10%	10%
Built in Overvoltage Threshold		15.6V	
Optional Coupled Faults			
ADC Direct Address/Alert			
ADC Resolution	10-bit	8-bit	8-bit
ADC SOURCE LSB	31.25mV	60mV	400mV
ADC V _{SENSE} LSB	62.5μV	151μV	300μV
ADC ADIN LSB	1.25mV	4.85mV	10mV
Internally Generated V _{CC}	3.3V	3.1V	5.5V
Package	5mm x 5mm QFN	4mm x 5mm QFN	5mm x 5mm QFN

tions in Q1. Resistors R1–R3 set the undervoltage (UV) and overvoltage (OV) fault thresholds. Capacitor C_F filters the power signal to prevent faults from noise or transient events. R7 and R8 select the power good threshold and set the foldback current limit level, which dramatically improves safe operating

area (SOA) requirements for Q1. Capacitor C_{SS} sets a maximum inrush current slew rate to avoid transient glitches on the backplane and C_{TIMER} is used to set the start-up time limit, which protects Q1 by turning it off if the system attempts to start-up into an excessive load. C3 is used to bypass

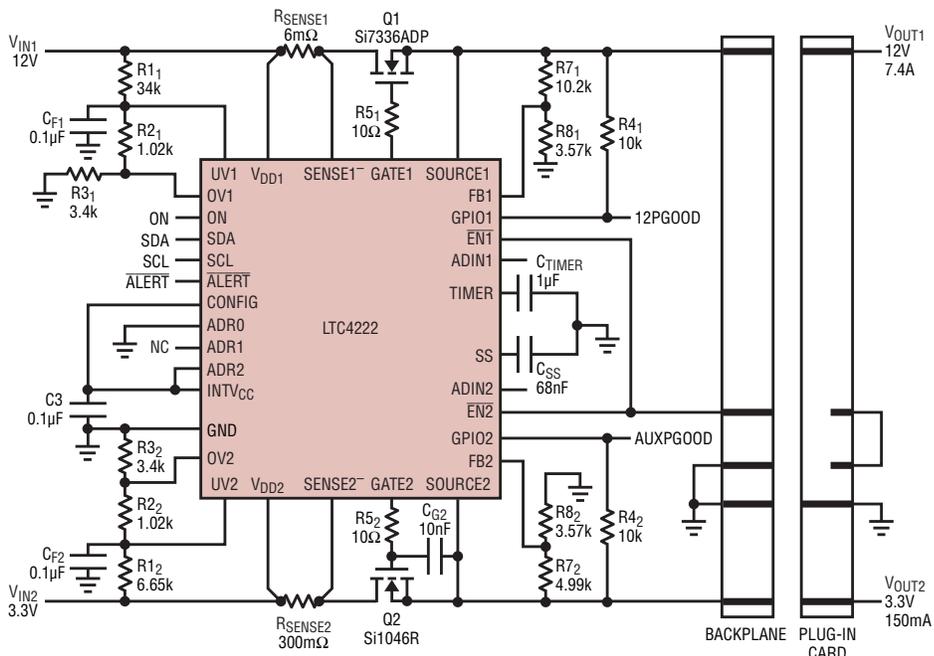


Figure 1. Typical AMC application

the internal 3.3V core voltage on the INTV_{CC} pin and prevent the LTC4222 from resetting on input supply glitches. The INTV_{CC} pin may also be used to power external loads, such as an I²C bus buffer, up to 10mA. The behavior of channel 2 is identical to channel 1.

Typically, the pins on the connector are staggered so that bulk power is applied first with the longest pins, followed by communication lines on medium length pins, and finally, Hot Swap control lines such as the supply for the UV, OV, or \overline{EN} pins. The UV, OV, and \overline{EN} pins must be in the correct state for a period of 100ms before Q1 is allowed to turn on to allow any connector signal bouncing to subside before starting up. At this point the ON pin turns the part on immediately if it is high, or holds the part off if it is low. The ON pin can be overridden and Q1 turned on or off through the I²C bus by writing to the ON bit in the control register.

If the CONFIG pin is low, these conditions must be met for both channels to initiate start-up, and both channels will start up at the same time, as shown in Figure 2. A fault on either channel when the CONFIG pin is low results in both channels turning off,

as shown in Figure 3, at which point they latch off or auto-retry together as configured in the control registers. This allows a faulting board to be entirely disconnected.

When the CONFIG pin is tied high, the two channels can start-up independently as long as both V_{DD} voltages are above their UVLO levels. If one channel is enabled during the 100ms debounce time of the other channel, the 100ms debounce is restarted and both channels will start together, however if one channel is enabled while the other channel is starting up or going through an overcurrent cool-down cycle, the channel attempting to start must wait for the other channel to finish before it is allowed to start.

With CONFIG tied high, the two channels can easily be sequenced by tying the power good output on the GPIO pin of one channel to the UV pin of the other channel. The GPIO pin pulls down the UV pin and holds the other channel off until the first channel starts up and the FB pin detects that power is good, at which point the GPIO pin releases the UV pin and the second channel starts up, as shown in Figure 4.

If one channel experiences a fault when the CONFIG pin is tied high, the other channel remains on, as shown in Figure 5. This allows the LTC4222 to supply two slots on a backplane-based application where non-failing slots are supposed to remain on when adjacent slots fail, such as providing 12V payload power switching for two μ TCA slots as shown in Figure 6.

Measure Board Power with Integrated ADC

Monitoring the supply voltage and current is a useful way of tracking the health of the power path. New data can be compared with historical data for the same card to detect changes in power consumption that could indicate that the card is behaving abnormally. An abnormal card can be shut down and flagged for service, perhaps before a more severe fault or system malfunction occurs. The LTC4222 includes a 10-bit data converter that continuously monitors six voltages: two ADIN pins, two SOURCE pins and two current sense voltages between the SENSE⁺ and SENSE⁻ pins. The ADIN pins are uncommitted ADC inputs that allow the user to monitor any available voltage. The ADIN pins are monitored with a 1.28V full scale and are connected directly to the data converter input without any signal scaling. The SOURCE pins use a 1:24 divider at the input, which gives a 32V full scale. The SENSE voltage amplifiers have a voltage gain of 20, which results in a 64mV full scale. The converter uses an over-sampling and offset cancellation method that preserves the full 10-bit dynamic range on the SENSE channels.

If the data converter reads more than 2mV on a V_{DD}-SENSE channel while the external switch is turned off, the LTC4222 generates a FET-SHORT fault to indicate that the switch may be damaged. The presence of this condition is indicated in the STATUS register bit C5 for the originating channel and logged to FAULT register bit D5. The LTC4222 takes no action in this condition other than logging the fault and generating an alert if configured to do so.

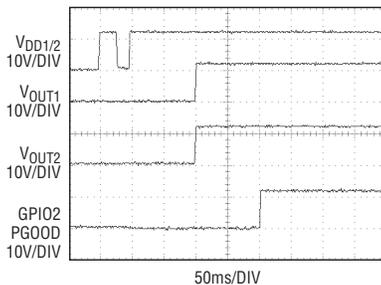


Figure 2. Start-up waveform with coupled turn-on

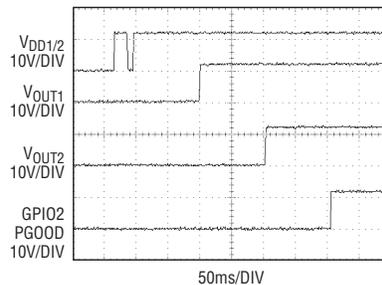


Figure 4. Start-up waveform with sequencing

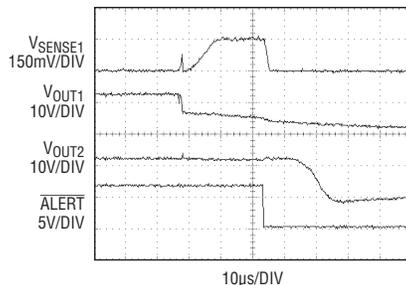


Figure 3. Fault-off waveform with coupled faults

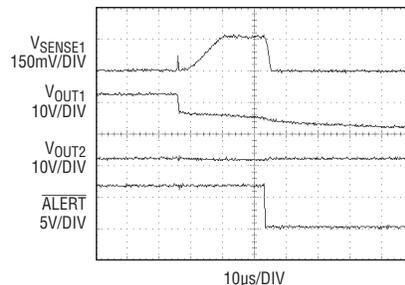


Figure 5. Fault-off waveform with independent faults

The results from each conversion are stored in 12 ADC registers. The default behavior of the data converter is a free-running mode in which it sequentially measures all six channels continuously and updates the output registers 15 times per second. The data converter can be stopped by setting ADC_CONTROL register bit 0 (HALT)—subsequent writes to the ADC_CONTROL register with the HALT bit set initiate a single conversion on the data converter channel selected by ADC_CONTROL register bits 1–3. An optional alert can be generated on the $\overline{\text{ALERT}}$ pin to indicate a conversion has finished by setting ADC_CONTROL register bit 4, or alternately the ADC_BUSY bit (ADC_CONTROL bit 5) can be polled until it indicates that the data converter has completed the conversion. Note that the ADC_BUSY bit is always set when the data converter is in its free-running mode. When the data converter is halted, the data converter registers may be written to and read from for software testing.

Versatile Inrush Current Control

As described above, the LTC4222 waits to turn on each channel's external switch until the channel's input has met the UV and OV thresholds and an internal 100ms debounce timer has expired. The start-up time is determined by the capacitor on the TIMER pin, or 100ms if the TIMER pin is tied to INTV_{CC}. During this time the circuit breaker is disabled to prevent an overcurrent fault from occurring, the power good signal from the corresponding GPIO pin is also disabled to prevent turning on a load before the current limit has reached the full value via the SS (soft-start) and FB (foldback) pins. The inrush current slew rate (dI/dt) is limited via the SS pin. The inrush current is also folded back from 50mV to 17mV via the FB pin. An optional RC network on the external MOSFET gate can be used to set the inrush current below the foldback level by setting the maximum slope of the output voltage. When both channels are starting up at the same

time, the current sense voltages are both regulated to the lowest value commanded by the two FB pins and the SS pin.

At the end of the start-up period the current limit circuit is checked. If the current limit is still regulating the current, the LTC4222 determines that the output failed to come up and generates an overcurrent fault. If the current limit circuit is not active then the current limit threshold is moved to 150mV, the power good signal to the GPIO pin is enabled and the 50mV circuit breaker is armed.

The SS pin sets the current slew rate limit at start-up. It starts at ground, which corresponds to a negative voltage on the sense resistor and results in the MOSFET being turned off. A current into the soft-start capacitor produces a ramp that corresponds to increasing V_{DD}-SENSE voltage. When either channel's current limit circuit releases the gate (when the commanding V_{DD}-SENSE voltage becomes positive) the current from the SS pin is stopped to wait for that GATE pin to rise and start to turn on the MOSFET.

Once the current limit circuit begins to regulate the V_{DD}-SENSE voltage, the current from the SS pin is resumed and the ramp continues until it reaches the foldback level. It is important that the SS pin stop the ramp while the GATE pins are slewing because the ramp would otherwise continue and result in an uncontrolled step in current once the MOSFET threshold is reached. An uncontrolled step may violate inrush specifications and cause supply glitches on the backplane. Due to offset differences between the current limit circuits, the soft-start ramp may pause twice as each gate slews at a different time when both channels turn on in the same start-up cycle.

If the soft-start ramp reaches one of the the foldback current limit levels, the soft-start circuit stops the ramp. The ramp is allowed to continue as the voltage at the lowest FB pin rises and increases the foldback current limit, still limited in slope and limited in magnitude by foldback as well. The FB pin for a channel that is either on

or off while the other is starting up is ignored and does not affect the start-up current limit.

If an RC network is placed on a GATE pin to manually set the inrush current to a value below the foldback level, the current limit circuit leaves regulation and begins slewing when it is unable to achieve the V_{DD}-SENSE voltage commanded by the SS and FB pins. If the start-up timer expires in the meantime, an overcurrent fault is not generated because the current limit is not active. The power good output for the GPIO pin relays the state of the FB pin, and the circuit breaker is armed. Either the output voltage finishes rising and a power good is asserted when the FB pin crosses its 1.235V threshold, or the current rises to the circuit breaker threshold and the part generates an overcurrent fault.

In the event there is an overcurrent condition after start-up, the current limit circuit limits the V_{DD}-SENSE voltage to 150mV while the circuit breaker waits for a 20 μ s timeout before producing an overcurrent fault. After any overcurrent fault, the part waits for a cool-down period of 50 times the start-up time before allowing either channel to start or restart via auto-retry, or cycling the $\overline{\text{EN}}$, UV or OV pins. The ON pins or the ON bits in the control registers can be cycled to bypass the cool-down time.

Controlled Turn-Off

When the LTC4215 is turned off by a fault or I²C transaction, the GATE pin is pulled down with a 1mA current source. Once the GATE pin is below the SOURCE pin, a diode from SOURCE to GATE turns on and the voltage at the SOURCE pin is discharged by the same 1mA current.

If there is a short that causes the sense voltage to exceed 150mV, a 450mA pull-down current from GATE to SOURCE removes the gate charge of the switch. Once the sense voltage falls to 150mV, the current limit regulates there for 20 μ s before turning the gate off with the 1mA current source.

If there is a significant inductance between V_{DD} (SENSE+) and upstream bulk capacitance, across a connec-

tor for instance, it is possible that a short circuit at the output with a very fast discharge time could cause the V_{DD} input voltage to collapse while the current through this inductance slews. In this case, after $2\mu\text{s}$, the V_{DD} undervoltage lockout circuit turns on and discharges the GATE pin with the 450mA pull-down to the SOURCE pin to quickly turn the switch off.

Save Power with Precise 50mV Circuit Breaker

In systems where a circuit breaker has only 20% accuracy, the designer must be able to safely provide 50% more power than the card actually consumes to ensure that the application doesn't suffer from heat and supply limitations on the high side or produce a fault in normal operation on the low side. For instance, in a system that requires 10A, a 20% accurate hot swap must have a nominal circuit breaker threshold of 12.5A. Since the threshold could be as high as 15A, the power supply needs to be able to supply 15A. In the case of a 5% threshold, the nominal threshold is 10.5A and the maximum possible current is 11A. Using the part with a 5% circuit breaker over the part with

the 20% circuit breaker frees 4A for use elsewhere, or allows the use of a 30% smaller, and less expensive, power supply.

High Voltage Rating for 12V Applications

The LTC4222 has a maximum input voltage rating of 35V, which is higher

than the breakdown voltage of the external MOSFET for most 12V applications, and also allows the LTC4222 to be used in 24V applications. If the breakdown voltage of the external MOSFET is less than the 35V abs-max of the LTC4222, there is no need for a transorb at the input in a card-resident application because voltage surges are safely absorbed by the MOSFET. If a transorb is still required, the high voltage rating of the LTC4222 makes it easy to select a transorb above the maximum operating range of the application, and below the 35V maximum for the part.

Conclusion

The LTC4222 is a smart power gateway for boards with two or more hot-swappable supplies. It provides fault isolation, closely monitors the health of the power paths and provides versatile means of controlling the inrush current profile. It logs faults, provides real-time status information, and can interrupt the host if necessary. Meanwhile, an internal 10-bit ADC continuously monitors board current and voltages. These features make the LTC4222 an ideal power gateway for high availability systems. 

The LTC4222 is a smart power gateway for boards with two or more hot-swappable supplies. It provides fault isolation, closely monitors the health of the power paths and provides a versatile means of controlling the inrush current profile. It logs faults, provides real-time status information, and can interrupt the host if necessary. Meanwhile, an internal 10-bit ADC continuously monitors board current and voltages.

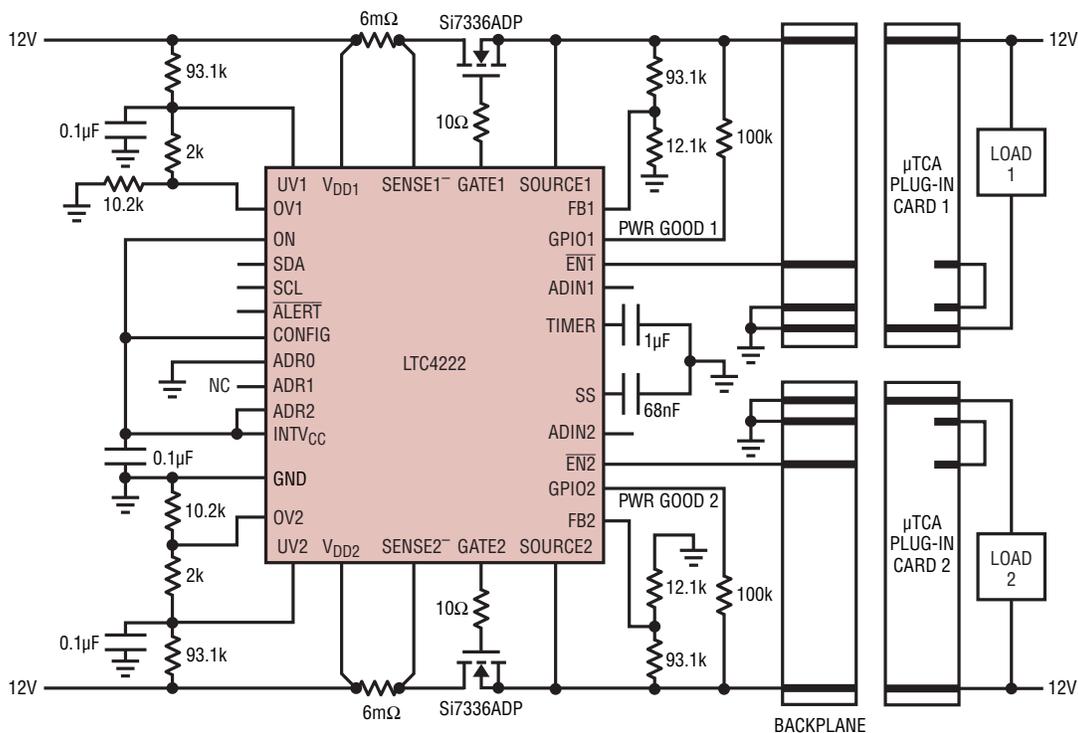


Figure 6. μTCA application supplying 12V payload power to two μTCA slots

±32V Triple-Output Supply for LCDs, CCDs and LEDs Includes Fault Protection in a 3mm × 3mm QFN

by Eko T. Lisuwandi

Introduction

The task of designing a battery powered system with multiple high voltage supplies is a daunting one. In such systems board space is at a premium and high efficiency is required to extend battery life. Supplies must be sequenced in start-up and shut-down, and multiple supplies must be able to maintain regulation without interaction across supplies.

The LT3587 is a 1-chip solution that combines three switching regulators and three internal high voltage switches to produce two high voltage boost converters and a single high voltage inverter. The LT3587 is designed to run from inputs ranging from 2.5V to 6V, making it ideal for battery powered systems. Small package size and low

component count produces a small, efficient solution. Typical applications include digital still and video cameras, high performance portable scanners and display systems, PDAs, cellular phones and handheld computers that have high voltage peripherals such as CCD sensors, LED backlights, LCD displays or OLED displays.

Features

To keep the component count low, the LT3587 integrates three high voltage power switches capable of switching 0.5A, 1A and 1.1A at up to 32V in a 3mm × 3mm QFN package. Each of the positive channels includes an output disconnect to prevent a direct DC path from input to output when

the switches are disabled. The LT3587 also includes a bidirectional fault pin (\overline{FLT}), which can be used for fault indication (output) or for emergency shutdown (input).


The LT3587 offers a wide output range, up to 32V for the positive channels (channels 1 and 3) and -32V for the inverter (channel 2). Channel 3 is configurable as either a voltage or current regulator. When configured as a current regulator, channel 3 uses a 1-wire output that requires no current sense or high current ground return lines, easing board layout. A single resistor programs each of the three channels output voltage levels and/or the channel 3 output current level.

Intelligent soft-start allows for sequential soft-start of channel 1 followed by the inverter negative output using a single capacitor. Internal sequencing circuitry disables the inverter until channel 1 output has reached 87% of its final value.

Triple-Output Supply for CCD Imager and LED Backlight

Figure 1 shows a typical application providing a positive and negative voltage bias for a CCD imager and a 20mA current bias for an LED backlight. All three channels of the LT3587 use a constant frequency, current mode control scheme to provide voltage and/or current regulation at the output.

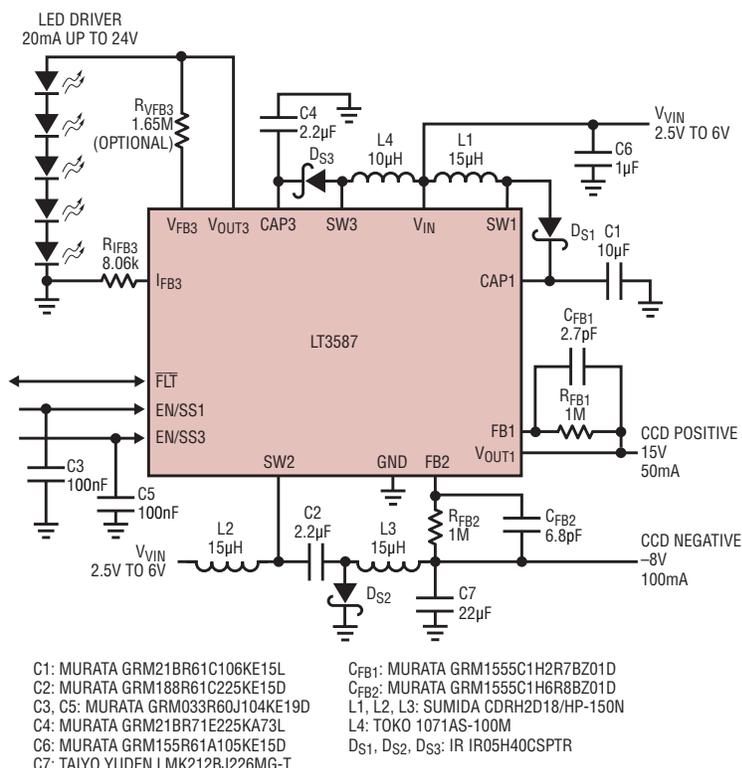The positive CCD bias is configured as a simple non-synchronous boost converter. Its output voltage is set to 15V via the feedback resistor R_{FB1} . The 15 μ H inductor (L1) is sized for a maximum load of 50mA. The negative CCD bias is configured as a non-synchronous Cuk converter. Its output voltage is set at -8V using the feedback resistor R_{FB2} . The two 15 μ H



- C1: MURATA GRM21BR61C106KE15L
- C2: MURATA GRM188R61C225KE15D
- C3, C5: MURATA GRM033R60J104KE19D
- C4: MURATA GRM21BR71E225KA73L
- C6: MURATA GRM155R61A105KE15D
- C7: TAIYO YUDEN LMK212BJ226MG-T
- C_FB1: MURATA GRM1555C1H2R7BZ01D
- C_FB2: MURATA GRM1555C1H6R8BZ01D
- L1, L2, L3: SUMIDA CDRH2D18/HP-150N
- L4: TOKO 1071AS-100M
- D_S1, D_S2, D_S3: IR IR05H40CSPTR

Figure 1. Solution for a Li-Ion powered camera provides positive and negative supplies for biasing a CCD imager and an LED driver for a 5-LED backlight

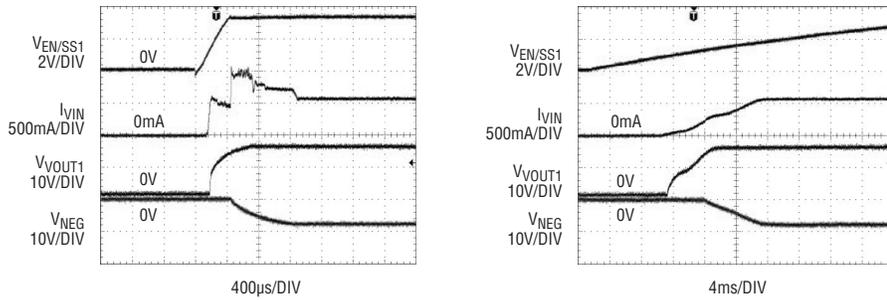


Figure 2. Start-up waveforms with no soft-start capacitor, and with a 10nF soft-start capacitor

(L2 and L3) inductors are sized for a maximum load of 100mA.

The LED backlight driver is configured as an output-current-regulated boost converter. Its output current is set at 20mA using the current programming resistor R_{IFB3} . The 10µH inductor (L4) is sized for a typical load of 20mA at up to 24V. Note the optional voltage feedback resistor, R_{VFB3} , on the LED driver. This resistor acts as a voltage clamp on the LED driver output, so that if one of the LED fails open, the voltage on the LED driver output is clamped to 24V.

Soft-Start

All channels feature soft-start (a slow voltage ramp from zero to regulation) to prevent potentially damaging large inrush currents at start-up. Soft-start is implemented via two separate soft-start control pins: EN/SS1 and EN/SS3. The EN/SS1 pin controls the soft-start for channel 1 and the inverter, while the EN/SS3 pin controls the soft-start for channel 3. Both of these soft-start pins are pulled up with a 1µA internal current source.

A capacitor from the EN/SS1 pin to ground (C3 in Figure 1) programs a soft-start ramp for channel 1 and channel 2 (the inverter). As the 1µA current source charges up the capacitor, the regulation loops for channel 1 and channel 2 are enabled when the EN/SS1 pin voltage rises above 200mV. During start-up, the peak switch current for channel 1 proportionally rises with the soft-start voltage ramp at the EN/SS1 pin. The inverter switch current also follows the voltage ramp at the EN/SS1 pin, but its switch current ramp does not start until the

voltage on the EN/SS1 pin is at least 600mV. This ensures that channel 2 starts up after channel 1. Channel 1 and channel 2 regulation loops are free running with full inductor current when the voltage at the EN/SS1 pin is above 2.5V.

In a similar fashion, a capacitor from the EN/SS3 pin to ground (C5 in Figure 1) sets up a soft-start ramp for channel 3. When the voltage at the EN/SS3 pins goes above 200mV, regulation loop for channel 3 is enabled. When the voltage at the EN/SS3 pin is above 2V, the regulation loop for channel 3 is free running with full inductor current.

Start-Up Sequencing

The LT3587 also includes internal sequencing circuitry that inhibits the channel 2 from operating until the feedback voltage of channel 1 (at the FB1 pin) reaches about 1.1V (about

87% of the final voltage). The size of the soft-start capacitor controls channel 2 start-up behavior.

If there is no soft-start capacitor, or a very small capacitor, then the negative channel starts up immediately with full inductor current when the positive output reaches 87% of its final value. If a large soft-start capacitor is used, then the EN/SS1 voltage controls the inverter channel past the point of regulation of the positive channel. Figure 2 shows the start-up sequencing without soft-start and with a 10nF soft-start capacitor.

Output Disconnect

Both of the positive channels (channels 1 and 3) have an output disconnect between their respective CAP and V_{OUT} pins. This disconnect feature prevents a DC path from forming between V_{IN} and V_{OUT} through the inductors when switching is disabled (Figure 1).

For channel 1, this output disconnect feature is implemented using a PMOS (M1) as shown in the partial block diagram in Figure 3. When turned on, M1 normally provides a low resistance, low power dissipation path for delivering output current between the CAP1 pin and the V_{OUT1} pin. M1 is on as long as the voltage difference between CAP1 and V_{IN} is greater than 2.5V. This allows the positive bias to stay high as long as possible while the negative bias discharges during turn off.

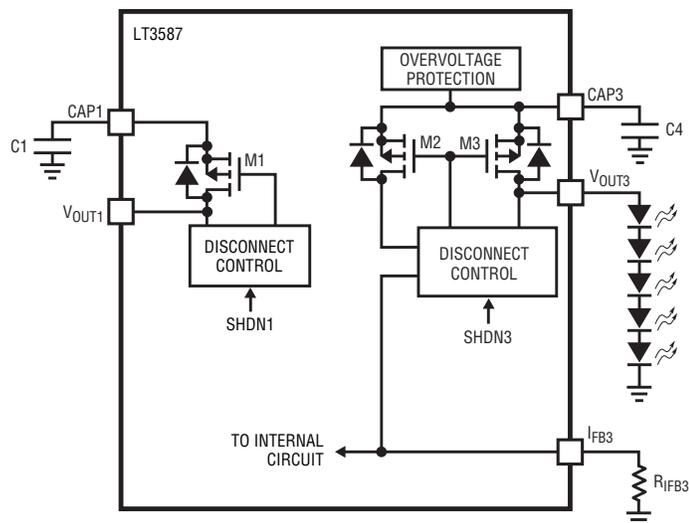


Figure 3. Partial block diagram of the LT3587 showing the disconnect PMOS for channels 1 and 3

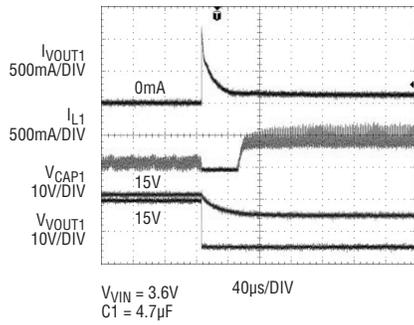


Figure 4. Channel 1 short circuit event

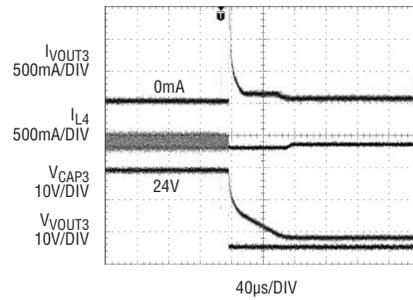


Figure 5. Channel 3 short circuit condition with and without 20mA current limit

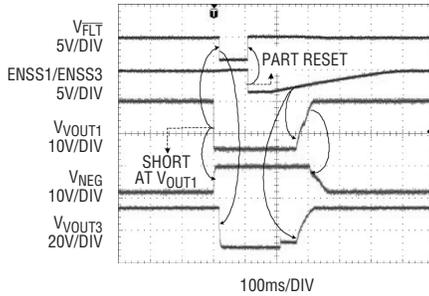


Figure 6. Fault detection of a short circuit event

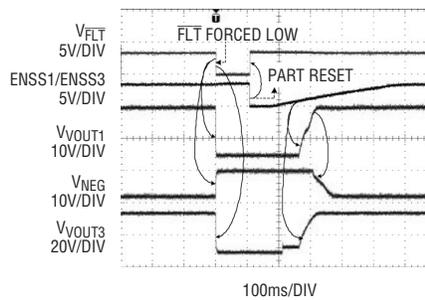


Figure 7. Waveforms for when the $\overline{\text{FLT}}$ pin is externally forced low

The disconnect transistor M1 is current limited to provide a maximum output current of 155mA. There is also a protection circuit for M1 that limits the voltage drop across CAP1 and V_{OUT1} to about 10V. When the voltage at CAP1 is greater than 10V, such as during an output overload or short circuit to ground, then M1 is set fully on, without any current limit, to allow for the voltage on CAP1 to discharge as fast as possible. When the voltage across CAP1 and V_{OUT1} reduces to less than 10V, the output current is then again limited to 155mA. Figure 4 shows the output voltage and current during an overload event with V_{CAP1} initially at 15V.

The output disconnect feature on channel 3 is implemented similarly using M3 (Figure 3). However, in this case M3 is only turned off when the EN/SS3 pin voltage is less than 200mV and the regulation loop for channel 3 is disabled.

The disconnect transistor M3 is also current limited, providing a maximum output current at V_{OUT3} of 100mA. M3 also has a similar protection circuit as M1 that limits the voltage drop across CAP3 and V_{OUT3} to about 10V. Figure 5

The LT3587 is a versatile, highly integrated device that provides a compact solution for devices such as cameras, handheld computers and terminals requiring multiple high voltage supplies. A low part count and a 3mm × 3mm package keep the solution size small. High efficiency conversion makes it suitable for battery powered applications. Adjustable output voltage and wide output range of up to 32V for the positive boosts, and -32V for the inverter, make it a flexible solution for systems that require high voltage supplies.

shows the output voltage and current during an overload event with V_{CAP3} initially at 24V.

Fault Detection and Indicator

The LT3587 features fault detection on all outputs and a fault indicator pin, $\overline{\text{FLT}}$. The fault detection circuitry is enabled only when at least one of the channels has completed the soft-start process and is free running with full inductor current. Once fault detection is enabled, if any of the enabled channel feedback voltages (V_{FB1} , V_{FB2} or the greater of V_{VFB3} and V_{IFB3}) falls below its regulation value for more than 16ms, the $\overline{\text{FLT}}$ pin pulls low.

One particularly important case is an overload or short circuit condition on any of the outputs. In this case, if the corresponding loop is unable to bring the output back into regulation within 16ms, a fault is detected and the $\overline{\text{FLT}}$ pin pulls low.

Note that the fault condition is latched—once activated all three channels are disabled. Enabling any of the channels requires resetting the part by shutting it down (forcing both the EN/SS1 and EN/SS3 pins low below 200mV) and then on again. Figure 6 shows the waveforms when a short circuit condition occurs at channel 1 for more than 16ms and the subsequent resetting of the part.

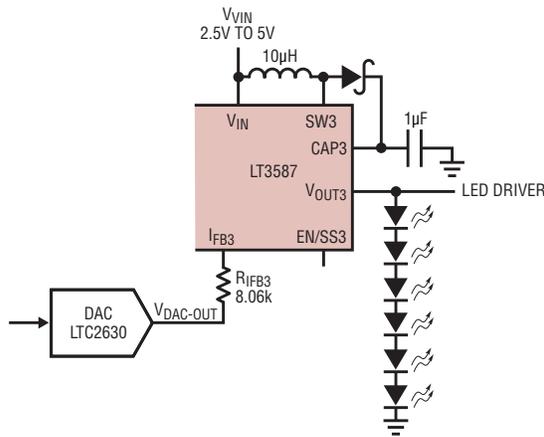


Figure 8. Analog dimming using a DAC and a resistor

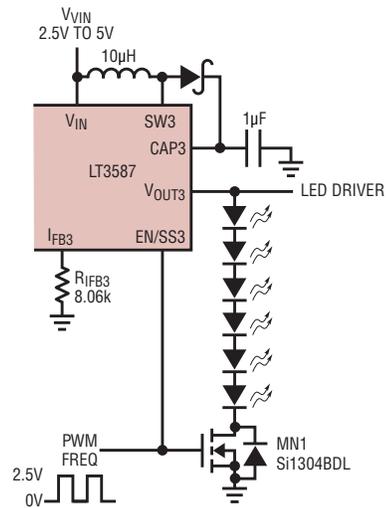


Figure 9. Driver for six LEDs with PWM dimming

Besides acting as a fault output indicator, the $\overline{\text{FLT}}$ pin is also an input pin. If this pin is externally forced below 400mV, the LT3587 behaves as if a fault event has occurred and all the channels turn off. In order to turn the part back on, remove the external voltage that forces the pin low and reset the part. Figure 7 shows the waveforms when the $\overline{\text{FLT}}$ pin is externally forced low and the subsequent resetting of the part.

Dimming Control for Channel 3 as a Current-Regulated LED Driver

As shown in Figure 1, one of the most common applications for the channel 3 is as a current regulator for a backlight LED driver. In many high end display applications requiring an LED backlight, the ability to dim the display brightness is crucial for implementing a power saving mode or to maintain contrast in different ambient lighting conditions.

There are two different ways to implement a dimming control of the LED string. LED current can be adjusted by either using a digital to analog converter (DAC) and a resistor R_{IFB3} or by using a PWM signal.

Analog Dimming Using a DAC and a Resistor

For some applications, the preferred method of brightness control is using a DAC and a resistor. This method

is more commonly known as analog dimming. This method is shown in Figure 8.

Since the programmed V_{OUT3} current is proportional to the current through R_{IFB3} , the LED current can be adjusted by changing the DAC output voltage. A higher DAC output voltage level results in lower LED current and hence lower overall brightness. For accurate dimming control, keep the DAC output impedance low enough to sink approximately 1/200 of the desired maximum LED current. Note the maximum possible output current is limited by the output disconnect current limit to 100mA.

PWM Dimming

One problem with analog dimming as described above is that changing the forward current flowing in the LEDs not only changes the brightness intensity of the LEDs, it also changes the color. This is a problem for applications

that cannot tolerate any shift in the LED chromaticity.

Controlling the LED intensity with a direct PWM signal allows dimming of the LEDs without changing the color. A PWM frequency of ~80Hz or higher guarantees that there is no visible flicker. The amount of on-time in the PWM signal is proportional to the intensity of the LEDs. The color of the LEDs remains unchanged in this scheme since the LED current value is either zero or a constant value ($I_{\text{VOUT3}} = 160\text{V}/R_{\text{IFB3}}$).

Figure 9 shows an LED driver for six white LEDs. If the voltage at the CAP3 pin is higher than 10V when the LED is on, direct PWM dimming method requires an external NMOS. This external NMOS is tied between the cathode of the lowest LED in the string and ground.

The output disconnect feature and the external NMOS ensure that the LEDs quickly turn off without discharging the output capacitor. This allows the LEDs to turn on faster. Figure 10 shows the PWM dimming waveforms for the circuit in Figure 9.

The time it takes for the LED current to reach its programmed value sets the achievable dimming range for a given PWM frequency. At extreme lower end of the duty cycle, the linear relation between the average LED current and the PWM duty cycle is no longer preserved. The minimum on time is

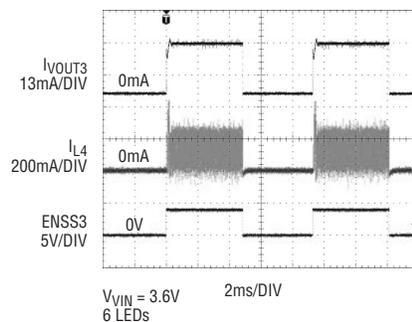


Figure 10. PWM dimming waveforms

chosen based on how much linearity is required for the average LED current. For example for the circuit in Figure 9, to produce approximately 10% deviation from linearity at the lower duty cycle, the minimum on time of the LED current is approximately 320 μ s (3.2% duty cycle) for a 3.6V input voltage and a 100Hz PWM frequency. The achievable dimming range for this application is then 30 to 1 (approximately the reciprocal of the minimum duty cycle).

The dimming range can be significantly extended by combining PWM dimming with analog dimming. The color of the LEDs no longer remains constant because the forward current of the LED changes with the output voltage of the DAC. For the six LED application described above, the LEDs can be dimmed first by modulating the duty cycle of the PWM signal with the DAC output at 0V. Once the minimum duty cycle is reached, the value of the DAC output voltage can be increased to further dim the LEDs. The use of both techniques together allows the average LED current for the six LED application to be varied from 20mA down to less than 1 μ A (a 20000:1 dimming ratio).

Channel 3 Overvoltage and Overcurrent Protection

Channel 3 can be configured either as a voltage regulated boost converter or as a current regulated boost converter. The regulation loop of channel 3 uses the greater of the two voltages at V_{FB3} and I_{FB3} as feedback to set the peak current of its power switch. This architecture allows for a programmable current limit on voltage regulation or voltage limit on current regulation.

When configured as a boost voltage regulator, a feedback resistor from the output pin V_{OUT3} to the V_{FB3} pin sets the voltage level at V_{OUT3} at a fixed level. In this case, the I_{FB3} pin can either be grounded if no current limiting is desired or be connected to ground with a resistor to set an output current limit value (I_{LIMIT}). As briefly noted before, the pull up current on the I_{FB3} pin is controlled to be typically 1/200 of the output load current at

Channel 3 can be configured either as a voltage-regulated boost converter or as a current-regulated boost converter. The regulation loop of channel 3 uses the greater of the two voltages at V_{FB3} and I_{FB3} as feedback to set the peak current of its power switch. This architecture allows for a programmable current limit on voltage regulation or a voltage limit on current regulation.

the V_{OUT3} pin. In this case, when the load current is less than I_{LIMIT} , channel 3 regulates the voltage at the V_{FB3} pin to 0.8V. If there is an increase in load current beyond I_{LIMIT} , the voltage at V_{FB3} starts to drop and the voltage at I_{FB3} rises above 0.8V. The channel 3 loop then regulates the voltage at the I_{FB3} pin to 0.8V, limiting the output

current at V_{OUT3} to I_{LIMIT} . Figure 11 compares the transient responses with and without current limit when a current overload occurs.

The channel 3 CAP3 pin has over voltage protection. When the voltage at CAP3 is driven above 29V, the channel 3 loop is disabled and SW3 pin stops switching. When configured as a boost current regulator, a feedback resistor from the I_{FB3} pin to ground sets the output current at V_{OUT3} at a fixed level. In this case, if the V_{FB3} pin is grounded then the over voltage protection defaults to 29V.

On the other hand a resistor can be connected from the V_{OUT3} pin to the V_{FB3} pin to set an output voltage clamp (V_{CLAMP}) level lower than 29V. In this case, when the voltage level is less than V_{CLAMP} , the channel 3 loop regulates the voltage at the I_{FB3} pin to 0.8V. On the other hand, when the output load fails open circuit or disconnected, the voltage at I_{FB3} drops to reflect the lower output current and the voltage at V_{FB3} starts to rise. When the voltage at V_{OUT3} rises beyond V_{CLAMP} , the voltage at the V_{FB3} pin goes

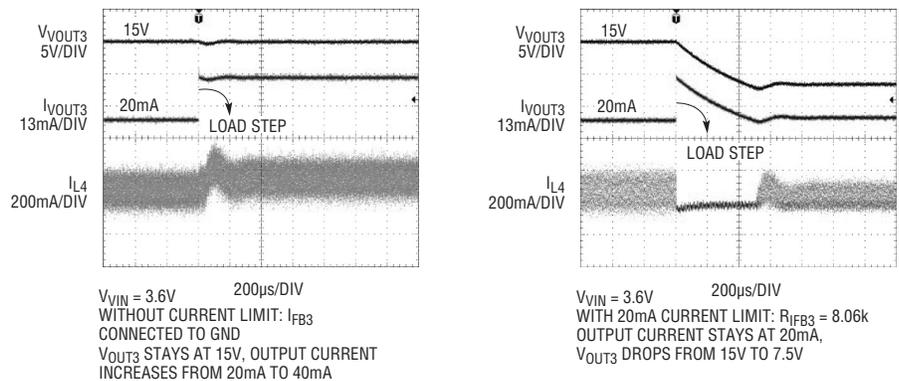


Figure 11. Channel 3 in an output current overload event with and without output current limit

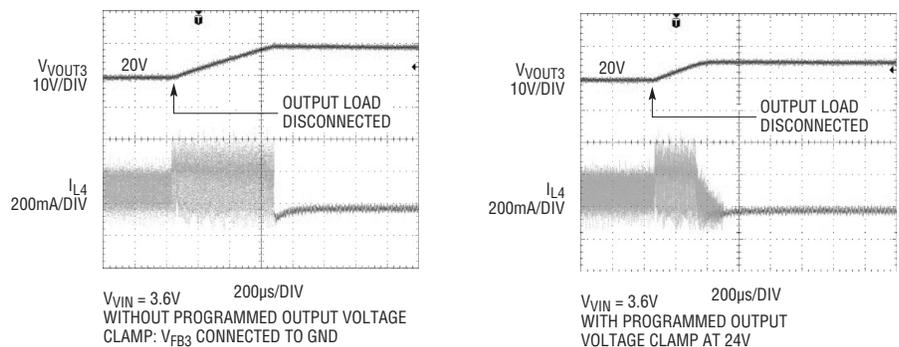


Figure 12. Channel 3 in an output open circuit with and without programmed output voltage clamp

above 0.8V. The channel 3 loop then regulates the voltage at the V_{FB3} pin to 0.8V, limiting the voltage level at V_{OUT3} to V_{CLAMP} . Figure 12 contrasts the transient responses with and without programmed V_{CLAMP} when the output load is disconnected.

Low Input Voltage

While the LT3587's V_{IN} supply voltage range is 2.5V to 6.0V, the inductors can run off a lower voltage. Most portable devices and systems have a separate 3.3V logic supply voltage, which can be used to power the LT3587. This allows the outputs to be powered straight from the lower voltage power source such as two alkaline cells. This configuration results in higher efficiency. Figure 13 shows a typical digital still camera application powered this way. It has positive and negative CCD supplies and an LED backlight supply.

Replace Inductor with Schottky for Smaller Footprint

If higher current ripple is tolerable at the output of the inverter (channel 2), replace inductor L3 with a Schottky diode D3 as shown in Figure 14. Since the Schottky diode footprint is usually smaller than the inductor footprint, this alternate topology is recommended for space constrained applications. This topology is only viable if the absolute value of the inverter output is greater than V_{IN} . This Schottky diode is configured with the anode connected to the output of the inverter and the cathode to the output end of the flying capacitor C2 as shown in Figure 14.

Conclusion

The LT3587 is a versatile, highly integrated device that provides a simple solution to devices such as cameras, handheld computers and terminals requiring multiple high voltage supplies. A low part count and a compact 3mm x 3mm package keep the solution size small. High efficiency conversion makes it suitable for battery powered applications.

Adjustable output voltage and wide output range of up to 32V for the positive boosts, and -32V for the inverter, make it a flexible solution for systems that require high voltage supplies. Channel 3's ability to work as a voltage regulator or as a true 1-wire current

regulator give the LT3587 status as a true all-in-one power supply.

Additional features, such as soft-start, supply sequencing, output disconnect and fault handling also add to the versatility of this part and further simplify power supply design. 

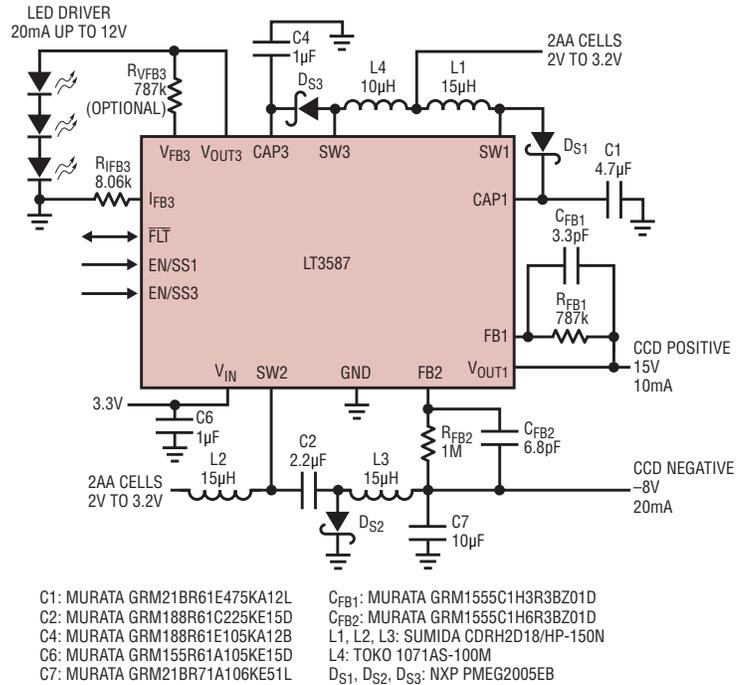


Figure 13. Two AA cells produce CCD positive and negative supplies and a driver for a 3-LED backlight.

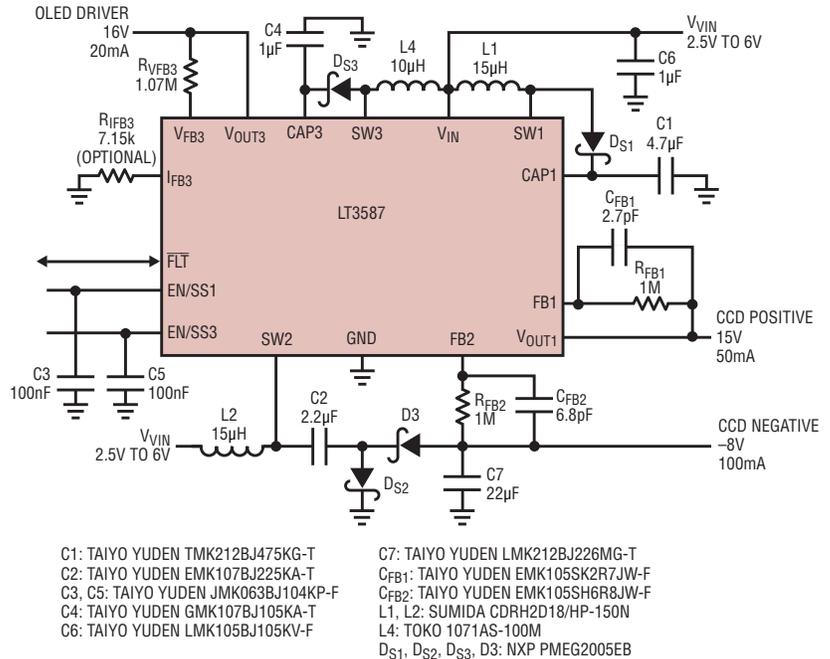


Figure 14. Li-ion driver for an OLED panel and a CCD imager with a Schottky diode replacing the inverter's output inductor

PD Interface for PoE+ Includes 25.5W Classification and Protection Features in a Low Profile 4mm × 3mm DFN

by Kirk Su

Introduction

The third generation Power over Ethernet standard increases the power available to PDs to 25.5W, up from the earlier standard's 12.95W (see sidebar). In the new standard, a Type-2 (high power) PD must communicate via handshake with Type-2 power sourcing equipment (PSE) to determine that the PSE is capable of providing high power. Type-2 PSEs are backwards compatible to the old standard.

The LTC4265 is a PoE PD interface that can identify 2-event classification (see sidebar) protocol and present an active signal as required for operation in an IEEE 802.3at-compliant PD. In addition, the LTC4265 may be configured for a variety of auxiliary power options with the aid of the shutdown and signature corrupt features.

The LTC4265 is highly integrated and easy to apply, requiring only one classification programming resistor.

The LTC4265 is a PoE PD interface that can identify 2-event classification protocol and present an active signal as required for operation in an IEEE 802.3at-compliant PD. In addition, the LTC4265 may be configured for a variety of auxiliary power options with the aid of the shutdown and signature corrupt features.

No additional external components are required to program the LTC4265 since all features (signature resistance, UVLO, OVLO, inrush current, and thermal protection) are built in and programmed into the LTC4265

to guarantee a smooth power-up transition and PD operation with any Power Sourcing Equipment (PSE). This eliminates additional component costs and cumbersome calculations that

Overview of the Third Generation Power over Ethernet System (PoE+)

The Power over Ethernet (PoE) standard specifies how DC power can be distributed alongside high speed data through a single RJ45 connector. The second generation standard (IEEE 802.3af) allows Powered Devices (PDs) to draw 12.95W from Power Sourcing Equipment (PSEs). The popularity of the standard has PD equipment vendors running up against the 12.95W power limit. To answer the call for more power, the newer IEEE 802.3at standard (also called PoE+) establishes a high power allocation while maintaining compatibility with the existing IEEE 802.3af systems.

In the new standard, PSEs and PDs are distinguished as Type-1 if they comply with the IEEE 802.3af power levels, or Type-2 if they comply with the IEEE 802.3at power levels. The maximum available power to a Type-2 PD is 25.5W.

The IEEE 802.3at standard also establishes a new method for Type-2 equipment to mutually identify each other while maintaining compatibility with the existing PoE systems. A Type-2 PSE has the option of declaring the presence of high power by performing 2-event classification (Layer 1) or by communicating with the PD over the data line (Layer 2). In turn, a Type-2 PD must recognize both layers of communications and identify a Type-2 PSE before beginning 25.5W operations. 

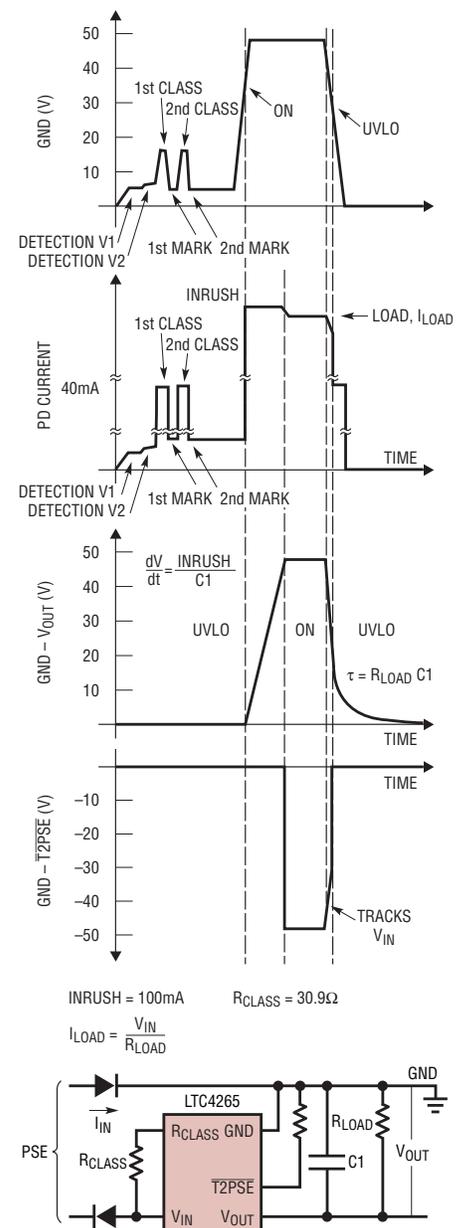


Figure 1. Example of 2-event classification waveform

are required in other power interface products to set thresholds, signature resistance, and current limits. The LTC4265 comes in a low profile, thermally enhanced, 4mm × 3mm DFN package.

What is 2-Event Classification?

The IEEE 802.3at establishes two ways to communicate the presence of a Type-2 PSE. The Layer 1 approach requires a PSE to perform 2-event classification, where classification probing is performed twice. The Layer 2 approach requires the PSE to communicate over the high speed data line. A Type-2 PD is required to recognize a Type-2 PSE using either layer of communication. Layer 1 communication using 2-event classification is included in the IEEE 802.3at standard for the benefit of PSEs/power injectors which do not have access to the high speed data line.

Since Layer 2 communications takes place directly between the PSE and the LTC4265 load, the LTC4265 concerns itself only with recognizing 2-event classification. Figure 1 shows an example of a 2-event classification. The 1st classification event occurs when the PSE presents an input voltage between 14.5V to 20.5V and the LTC4265 presents a class 4 load current. A Type-2 PSE then drops the

input voltage into the Mark voltage range of 6.9V to 10V, signaling the 1st Mark event. The PD in the Mark voltage range presents a load current between 0.25mA to 4mA. A Type-2 PSE repeats this sequence, signaling

the 2nd Classification and 2nd Mark event occurrence.

The Type-2 PSE then applies power to the PD and the LTC4265 charges up the reservoir capacitor C1 with a controlled inrush current. When C1 is fully charged, and the LTC4265

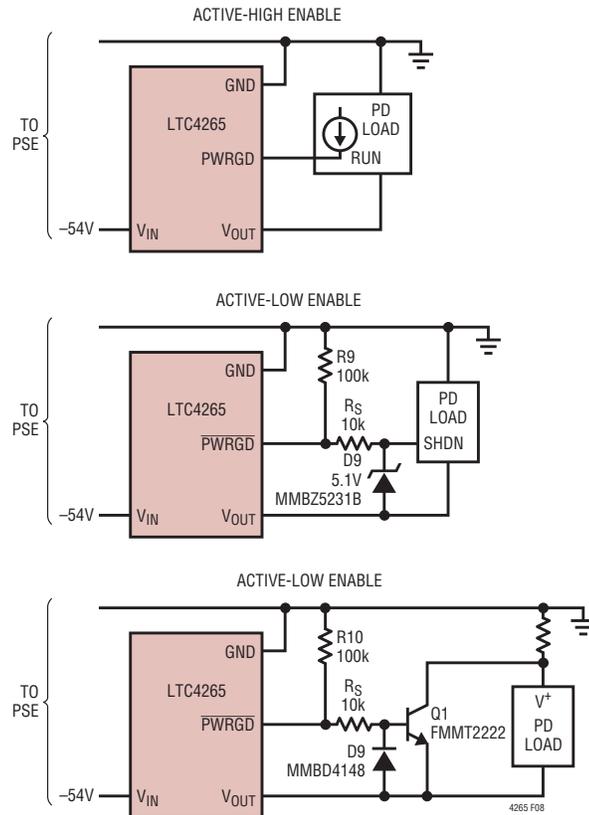


Figure 3. Examples of enabling/disabling the PD load via the complementary power good pins

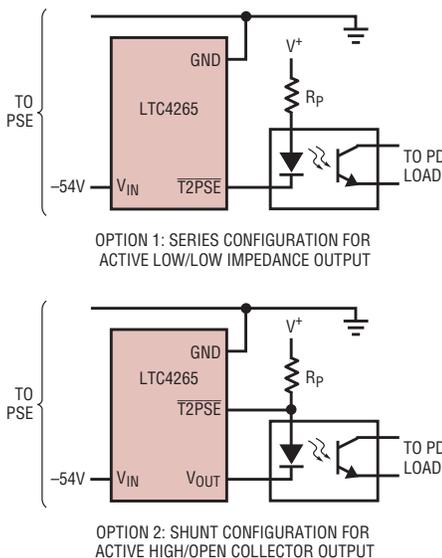


Figure 2. Interfacing with the Type-2 PSE via the T2PSE pin

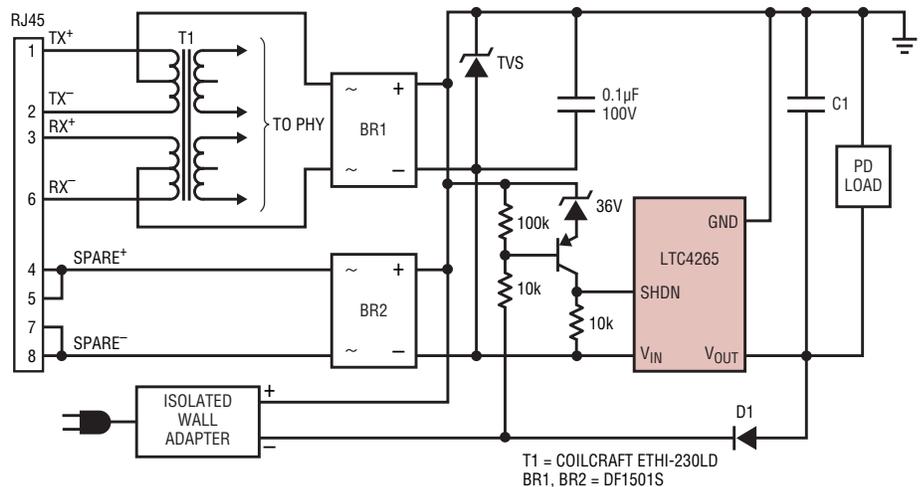


Figure 4. Auxiliary power supply. Auxiliary power takes precedence over PoE power (using the SHDN pin).

Primary-Side Sensing Takes Complexity out of Isolated Flyback Converter Design

by Tiger Zhou

Introduction

Flyback converters are widely used in isolated DC/DC applications, but they are not necessarily a designer's first choice. Power supply designers grudgingly choose a flyback out of necessity for electronic isolation; certainly not because they are an easy to design. A flyback converter requires that significant design time be devoted to transformer design, a task further complicated by limited off-the-shelf transformer selection and the necessity for customized magnetics. Moreover, the flyback converter has stability issues due to the well-known right-half-plane (RHP) zero in the control loop, which is further complicated by the propagation delay of an optocoupler.

The LT3573 isolated monolithic flyback converter solves many of the design difficulties commonly associ-

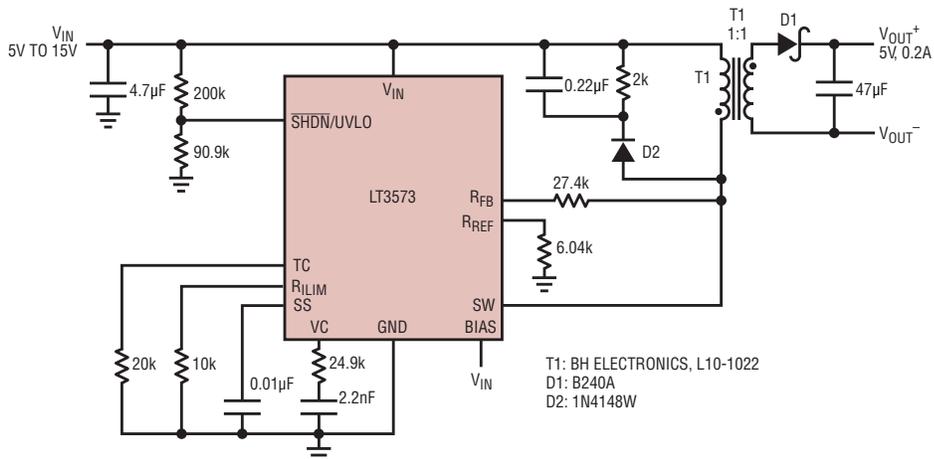


Figure 1. Amazingly simple flyback converter takes advantage of the primary side sensing scheme of the LT3573. Note the absence of an optocoupler. Also note the tiny coupling inductor available from many magnetics vendors.

ated with flyback converters by using a primary-side sensing scheme that is capable of detecting the output voltage through the flyback switching node waveform. During the switch off-period, the diode delivers the current to the output, and the output voltage is thus reflected to the primary-side of the flyback transformer (or the switch node). The magnitude of the switch node voltage is the summation of the input voltage and reflected output voltage. The flyback converter is able to reconstruct the output voltage from the measurement of the switching node voltage during the off period. This scheme has previously proven itself in Linear Technology's family of photoflash capacitor charger ICs. Design is simplified by getting rid of the optocoupler while maintaining the galvanic isolation between the primary-side and secondary-side of the transformer.

The LT3573's utilization of boundary mode operation further reduces converter size and simplifies system design. The flyback converter turns on the 1.25A, 60V internal switch right after the secondary diode current reduces to zero, while it turns

off when the switch current reaches the pre-defined current limit. Thus it always operates at the transition of continuous conduction mode (CCM) and discontinuous conduction mode (DCM), which is called boundary mode. Boundary mode operation also offers a superior load regulation.

Other features, such as soft-start, adjustable current limit, undervoltage lockout and temperature compensation further facilitate the flyback converter design. Figure 1 shows a simple flyback converter using LT3573.

Primary-Side Sensing Needs No Optocoupler

An optocoupler is essential for a traditional flyback converter. It transmits the output voltage feedback signal through an optical link while maintaining an isolation barrier. However, the optocoupler current transfer ratio (CTR) often changes with temperature, degrading accuracy. Also, the optocoupler causes a propagation delay, which impacts the dynamic response of the control loop.

The LT3573 eliminates the need for an optocoupler by sensing the output

DESIGN IDEAS

Primary-Side Sensing Takes Complexity out of Isolated Flyback Converter Design.....30
Tiger Zhou

Easy Automotive Power Supplies: Compact Regulator Produces Dual Outputs as Low as 0.8V from 3.6V-36V and is Unfazed by 60V Transients.....32
Peter J. Andrews

High Power 2-Phase Synchronous Boost Replaces Hot Diodes with Cool FETs—No Heat Sinks Required35
Narayan Raja, Tuan Nguyen and Theo Phillips

100V Controller in 3mm x 3mm QFN or MSE Drives High Power LED Strings from Just About Any Input37
Keith Szolusha

Parallel Buck-Boost µModule Regulators to Produce High Current in Sub-2.8mm Height Applications40
Judy Sun, Sam Young and Henry Zhang

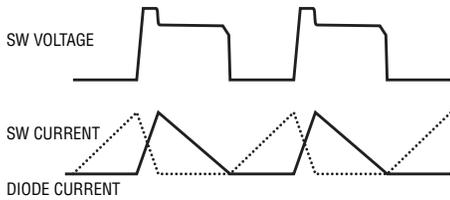


Figure 2. LT3573 flyback converter in boundary mode.

voltage on the primary-side. The output voltage is accurately measured at the primary-side switching node waveform during the off period. In addition to the obvious simplification and cost savings of this design, this scheme improves dynamic performance during load transients, which further simplifies the control loop design.

Boundary Mode Operation Reduces Converter Size and Simplifies System Design

Since the flyback converter operates in boundary mode, the switch is always turned on at zero current and the diode has no reverse recovery loss. Reducing power losses allows the flyback converter to operate at a relatively high switching frequency, which in turn reduces the transformer size when compared to lower frequency operation. Figure 1 shows an isolated flyback using a small coupling inductor with 19µH primary inductance.

Another benefit of boundary mode operation is a simplified control loop.

The LT3573 simplifies the design of flyback converters by using a primary-side sensing scheme that detects the output voltage through the flyback switching node waveform.

Figure 2 shows the LT3573 flyback converter voltage and current waveform in boundary mode. Assuming a 1:1 transformer is used; the control-to-output transfer function is:

$$G_{VC} = \frac{1-D}{2} \cdot \frac{R \left(R_C + \frac{1}{s \cdot C} \right)}{R + R_C + \frac{1}{s \cdot C}}$$

Where R is the load resistor, C is the output capacitor, R_C is the ESR of the output capacitor and D is the duty cycle. From this, a load pole at

$$s_p = \frac{1}{RC}$$

and ESR zero at

$$s_z = \frac{1}{R_C C}$$

are observed. This reduced-order transfer function can be easily compensated by an external V_C network.

The simplified control loop network also eases transformer design. The control-to-output transfer function has no inductance component, which means the flyback converter easily tolerates transformer variations. The transformer inductance only affects the converter switching frequency; it does not affect the converter output capability and stability. The data sheet includes a detailed design example, which outlines converter design guidelines.

Boundary Mode Operation for Superior Load Regulation

Since the diode voltage drop is included in the reflected output voltage, it can affect load regulation in primary-side sensing flyback converters that operate in CCM. The reason is the diode has nonlinear I-V characteristics. Other methods such as load regulation compensation must be used if a tight load regulation is required. However, the load regulation is much improved in boundary mode operation because the reflected output voltage is always sampled at the diode current zero-crossing. The LT3573 flyback converter has a typical 1% load regulation.

Figure 3 shows a 5V, 1A flyback converter that accepts a 9V to 30V input. The BIAS winding is used to improve the system efficiency. The T_C resistor compensates the output voltage at all temperatures, the UVLO resistors set the intended input range, and the current limit resistor programs the output current.

Conclusion

The LT3573 simplifies the design of isolated flyback converters with a primary-side sensing scheme and boundary mode operation. Its wide 3V to 40V input range, and its ability to deliver 7W output power make it suitable for industrial, automotive and medical applications. It also includes undervoltage lockout, soft-start, temperature compensation, adjustable current limit and external compensation. 

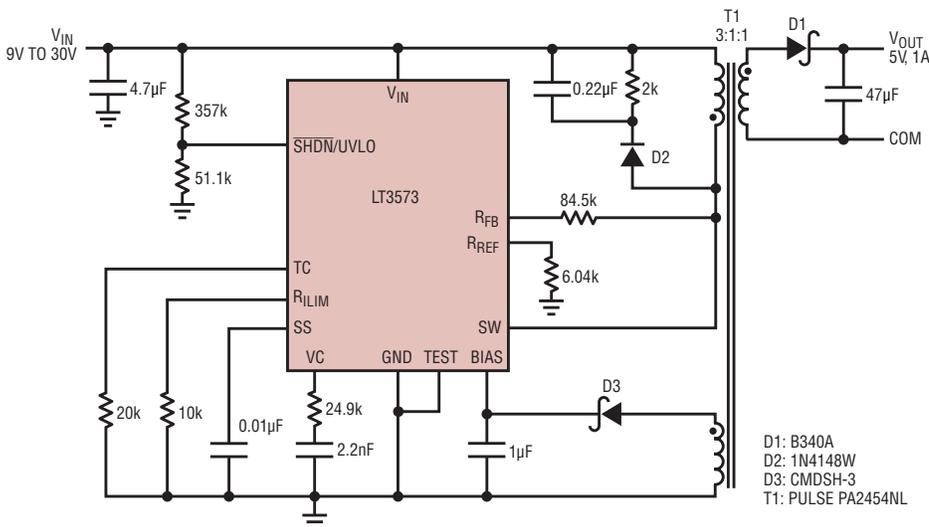


Figure 3. A 9V-30V input, 5V/1A flyback converter with a BIAS winding to maximize the system efficiency.

Easy Automotive Power Supplies: Compact Regulator Produces Dual Outputs as Low as 0.8V from 3.6V–36V and is Unfazed by 60V Transients

by Peter J. Andrews

Introduction

The LT3509 dual channel step-down regulator operates over an impressively vast supply range of 3.6V to more than 36V, but its real distinguishing feature is its ability to handily protect both itself and downstream components from transient input voltages up to 60V. It accomplishes this by entering a safe shutdown mode when the supply exceeds 38V, such as load dump events in automotive electrical systems.

In a vehicle electrical system, overvoltage transients can occur when heavy loads are switched because the rapid change in current across the wiring inductance induces a high voltage. These transients are usually short in duration, from several microseconds to several milliseconds. Longer duration voltage surges can happen when the battery is disconnected and the alternator and its regulator must respond to reduce the energizing field in the rotor. This can take several hundred milliseconds, enough time to damage electronic components and subsystems.

The LT3509 protects itself and downstream systems from transient overvoltage events by shutting down for the duration of the event. For non-critical systems, that is all the protection that is needed, as long as power is restored relatively quickly. For critical systems that require full functionality during a transient event, a supercapacitor ride-through circuit can continue to provide hold-up power (see Linear Technology Design Note 450 or the cover article from

the September 2008 issue of *Linear Technology* magazine). This article shows a circuit that allows powered systems to ride-through transients without requiring a reset.

A Little About the LT3509

The LT3509 integrates popular high voltage features into a compact dual supply solution for a wide range of applications. Each of two channels can produce up to 0.7A at an output voltage as low as 0.8V to within a

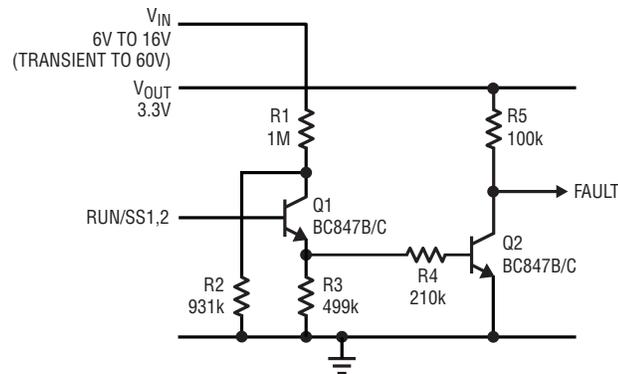


Figure 1. LT3509 RUN/SS to FAULT signal interface

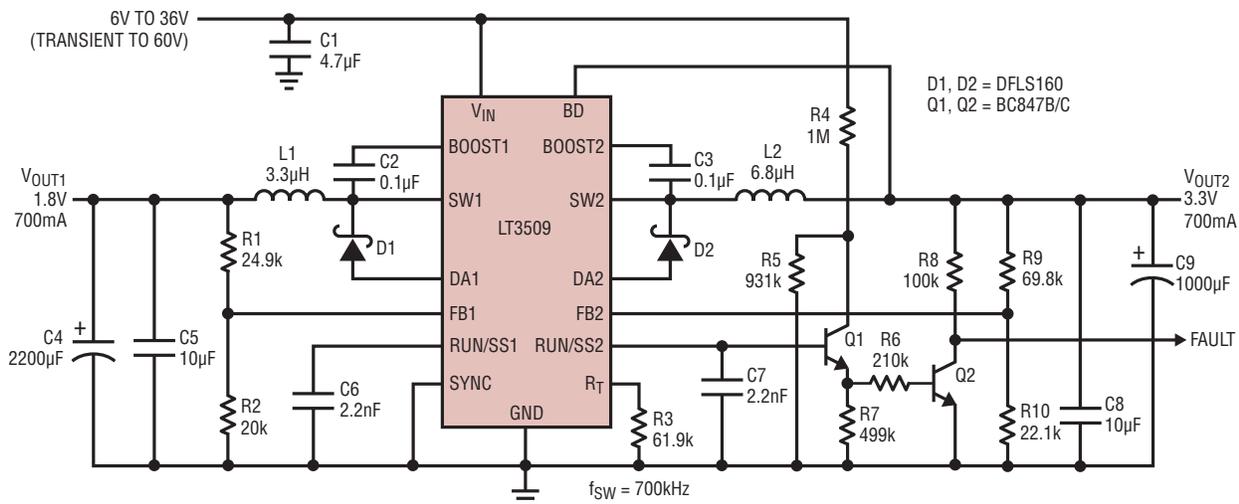


Figure 2. 12V auto battery to 3.3V and 1.8V with hold-up capacitors and FAULT indicator

half a volt of the input supply. It has integrated BOOST diodes and internal compensation to minimize the component count and the required board area. Robust short-circuit protection is also provided using catch diode current sensing. The ride-through feature is particularly useful in automotive applications, as is the wide operating frequency range of 300kHz to 2.2MHz and the ability to synchronize to an external reference clock. The switching frequency can be chosen or externally driven to meet stringent EMI requirements.

Riding Through Supply Transients

One way to reduce the ride-through energy storage requirements is to provide a FAULT signal to the powered systems so that they can enter a low power state for the duration of the event. For example a microcontroller could enter a HALT state, digital circuitry could stop or reduce the clock frequency, displays could be blanked and audio circuits muted. This reduces the power draw to a minimum so that the output voltages can be maintained with relatively small electrolytic capacitors.

The LT3509 itself does not provide a dedicated logic signal to indicate that an overvoltage event has occurred but it is possible to detect the event by monitoring the RUN/SS pins. These pins are pulled low by an internal device whenever an overvoltage condition exists, but as they were not intended to drive logic directly a small interface circuit is required as shown in Figure 1. The RUN/SS

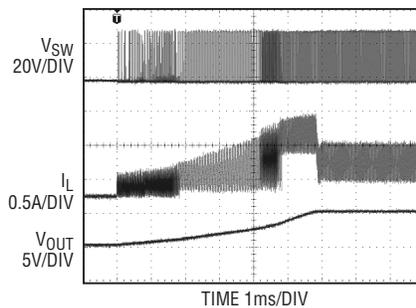


Figure 3. Soft-start waveforms

pins are pulled up to approximately 3.0V by an internal 1 μ A pull-up in normal operation and are pulled to about 0.6V during a fault condition. This circuit has a switching threshold of around 1.4V and draws very little input current. The circuit operates at a very low current and the transistors were carefully selected—generic types may not give satisfactory performance. Q1's collector must be supplied from V_{IN} with a resistor divider as shown. If connected to V_{OUT}, the collector base junction will be forward biased at power-up and thus preventing the LT3509 from starting up. The resistor divider keeps the collector-emitter voltage of Q1 below its breakdown voltage.

Automotive Accessory Supply 3.3V and 1.8V with Ride-Through Capability

The schematic in Figure 2 shows a typical application for a dual supply system requiring 3.3V and 1.8V rails, such as a radio or satellite navigation system. The goal is to maintain support for a ride-through capability described in the introduction where the output voltage is maintained just

long enough for the powered circuitry to enter a low current state. The key features are that it includes the fault indication circuit of Figure 1 and the standard 10 μ F ceramic output capacitors C5 and C8 are augmented with 1000 μ F electrolytic capacitors C4 and C9. The ceramic capacitors should still be used to control high frequency ripple as they have much lower ESR than the electrolytic types.

The operating frequency is kept low to ensure that the 1.8V channel operates in fixed frequency mode at the normal operating voltage. The output capacitors have to support the output voltage while the regulator shuts off due to an overvoltage ride-through event. They must also supply the full load current for the time taken from the start of the overvoltage event until the load is put in a powered down state. The delay time from the overvoltage condition until the fault signal is asserted is dependent on the capacitor value on the RUN/SS pin. With the component values in the example circuit this is approximately 40 μ s. To this must be added any time for the powered circuit to shut down. The voltage droop during this time can be calculated from $\Delta V = I \cdot t / C$. So for 700mA, 40 μ s and 1000 μ F gives $\Delta V = 0.7A \cdot 40\mu s / 1000\mu F = 28mV$.

Once the powered circuits have shut down, the droop rate depends on the residual current draw and the duration of the transient event. In an ideal case the system power should reduce to a few μ A in which case the dominant current draw will be from the feedback divider, which in the example circuit takes around 37 μ A. Using the same equation, for a 400ms event, the droop during the transient is: $\Delta V = 40\mu A \cdot 0.4s / 1000\mu F = 16mV$. Clearly the biggest droop occurs during the initial loss of power.

One last thing to consider is what happens when the transient is finished and normal operation resumes. The FAULT signal de-asserts as soon as the RUN/SS pin rises above the threshold, but the regulator is not able to deliver full current until the RUN/SS pin reaches approximately 2V. It may be necessary to create a small delay,

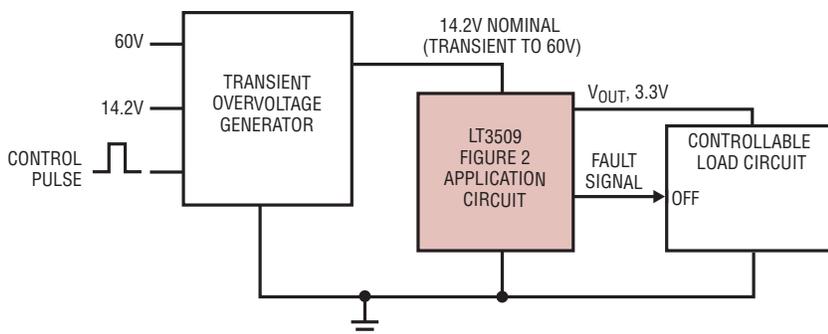


Figure 4. Test and demonstration set-up

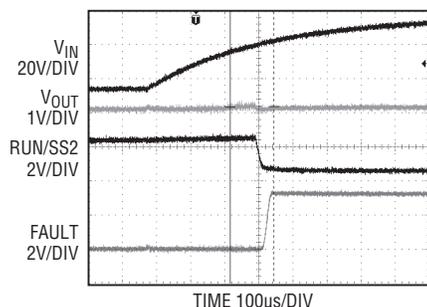


Figure 5. Transition to ride-through mode

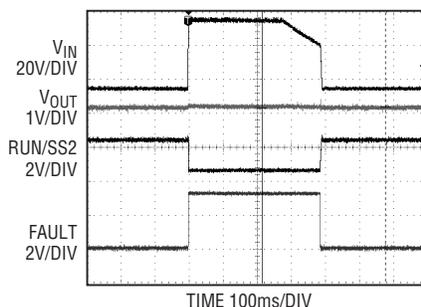


Figure 6. Complete ride-through event

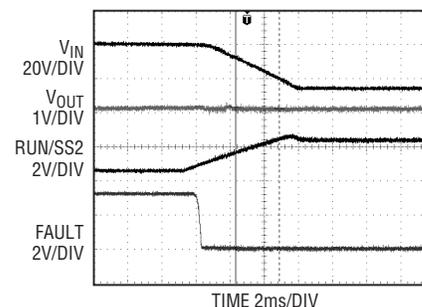


Figure 7. End of ride-through event

by software perhaps, from the time FAULT goes away until full current is demanded.

The LT3509 prevents inrush currents at start-up with a current limiting soft-start feature, which allows the available output current to ramp up slowly. Both the peak current limit and the valley current limit (the one sensed through the catch diodes) are controlled by the voltage on the RUN/SS pins, so as capacitors C6 and C7 charge up, the output current slowly increases to its normal maximum value. An example of the soft-start characteristic is shown in Figure 3.

Demonstration and Test Results

The ride-through performance the application of Figure 1 is tested using the setup shown in Figure 4. A switched supply produces either a normal input or an overvoltage transient. The output is connected to an active load circuit with ON/OFF controlled by the FAULT signal. Figure 5 shows the start of the overvoltage event on a fast time base to show the step that occurs as the regulator shuts off, but before the load is reduced. Figure 6 shows the entire 400ms transient and the droop that happens when there is no output but also very little load. Figure 7 shows

the end of the event on an expanded timescale.

Conclusion

Overvoltage transients are a fact of life in automobile and industrial power systems. The LT3509, combined with a small, low cost capacitor, can be used to both protect components from overvoltage transients and allow the downstream systems to ride through the event without having to completely reset. It is possible to ride through an overvoltage transient of even several hundred milliseconds, provided a brief interruption of service can be tolerated. 

LTC4265, continued from page 29

is applied. That is, the DC/DC converter continues to operate through the power transition. But the transition from auxiliary power to PoE power (when the auxiliary is removed) is not seamless since a PSE must redetect the PD before applying power.

Guidelines for Pairing the LTC4265 with a DC/DC Converter

The LTC4265 can be paired with just about any DC/DC converter, but two are particularly well suited to Type-2 Power over Ethernet Applications: the LT3825 flyback controller and LT1952 forward controller. Forward and flyback converters satisfy the electronic isolation requirement in the IEEE 802.3af and IEEE 802.3at specifications. In addition to the topology requirements, the LT3825 and LT1952 controllers are selected based on their ability to tolerate the wide PoE line voltage range, which varies from 36V to 57V.

As PoE power levels increase, the Schottky diode typically placed at the output of the secondary winding becomes an efficiency drain as it dissipates more power with increased output current. In addition, the output diode requires a considerably large heat sink and board area to displace the heat.

For these reasons, many power-hungry PDs are better served by synchronous DC/DC topologies, where the output diode is replaced with an active switch synchronized to the operation of the controller. Both the LT3825 and LT1952 include built-in synchronous drivers, enabling the use of an active switch.

Figure 5 shows the LTC4265 paired with an LT1952 in a self-driven synchronous forward power supply configuration. Figure 6 shows the LTC4265 paired with a LT3825. This is a synchronous flyback power supply configuration with no optoisolator

feedback. The LT3825 may also be configured for a forward topology.

These are not the only DC/DC converter solutions that work well with the LTC4265. The LTC4265 can be easily applied in applications that already have a DC/DC converter.

Conclusion

The LTC4265 PD interface provides the features required in a PD interface to operate under the IEEE 802.3at standard with minimum component count. Since all of the features (signature resistance, UVLO, OVLO, inrush current, and thermal protection) are built in, little is needed around its low profile 4mm x 3mm DFN package to create a complete PoE Type-2 interface. Simply pair it with a PoE-ready DC/DC converter by hooking up the Type-2 and power good indicator pins, and a high power PD is ready to go. Add to this the ability to handle auxiliary power, and the LTC4265 proves a versatile PoE+ tool. 

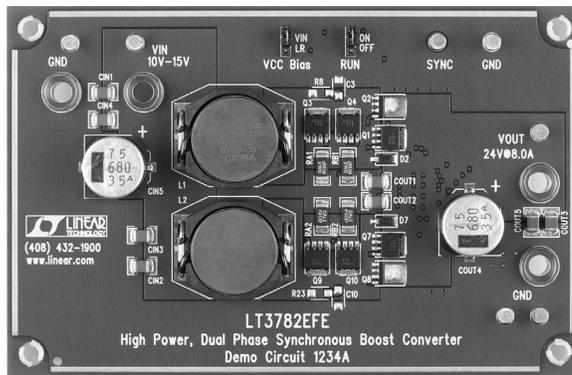


Figure 2. Layout of the circuit in Figure 1. Note that no heat sinks are needed, even at the high power levels produced by this relatively compact circuit.

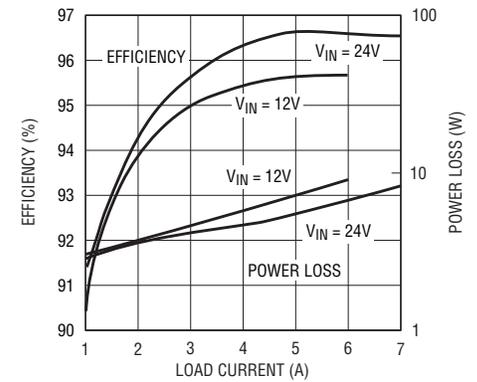


Figure 3. Efficiency and power loss of the circuit in Figure 1 compared to the efficiency of the circuit when the synchronous FETs are replaced with non-synchronous boost diodes.

Multiphase Operation Reduces Application Size

There are a number of good reasons to choose a multiphase/multi-channel DC/DC converter over an equivalent single-phase solution, including reduced EMI and improved thermal performance, but the biggest advantage can be a significant reduction in application size. Although a 2-phase solution requires more components, two inductors and two MOSFETs instead of one, it offers a net reduction in space and cost. This is because the inductors and MOSFETs are more than proportionally smaller than those required in the single-phase solution. Moreover, because the switching signals are mutually anti-phase, their output ripples tend to cancel each


continued on page 39

strong bottom switch drivers for high gate charge high voltage MOSFETs and uses a constant frequency, peak current mode architecture to produce high output voltages from 6V to 40V inputs. Its 2-phase architecture keeps external components small and low profile.


Synchronous Operation

At high current levels, a boost diode dissipates a significant amount of power, while a synchronous switch can burn far less. It all comes down to the forward voltage drop. The power dissipated in the boost diode is $I_{IN} \cdot V_D$, while the power dissipated by the synchronous switch is $I_{IN}^2 \cdot R_{DS(ON)}$ (or $I_{IN} \cdot V_{DS(ON)}$). A typical sub-10mΩ MOSFET running 10A dissipates 1W, while the 0.5V drop of a typical

Schottky diode burns a whopping 5W. Because the forward drop of a synchronous MOSFET is proportional to the current flowing through it, FETs can be paralleled to share current and drastically reduce power dissipation. On the other hand, paralleling boost diodes does little to reduce power dissipation as the forward drop through the diodes holds fairly constant. The non-synchronous boost diode topology is more than just inefficient relative to a synchronous solution—the extra heat generated in a boost diode must go somewhere, necessitating a larger package footprint and heat sinking. At high power levels, a non-synchronous boost application becomes larger in size and higher in cost over a synchronous solution.

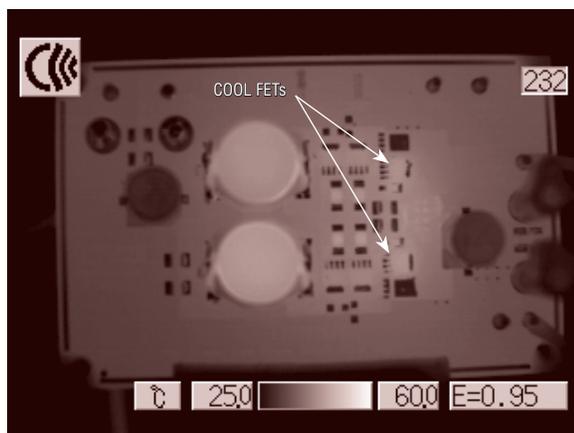

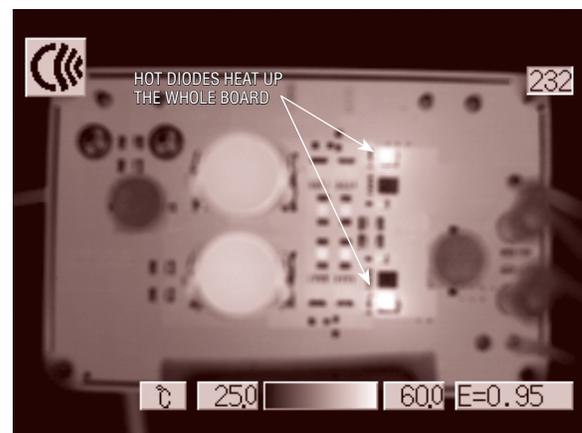a. Thermal image of the board in Figure 2 built up with synchronous FETs



b. Thermal image of the board in Figure 2 built up with boost diodes

Figure 4. The board in Figure 2 runs fairly cool (a), but when the synchronous FETs are replaced with boost diodes, the entire board heats up considerably with the diodes running significantly hotter than the FETs (b). ($V_{IN} = 12V$, $I_{LOAD} = 6A$, two minutes after power up.)

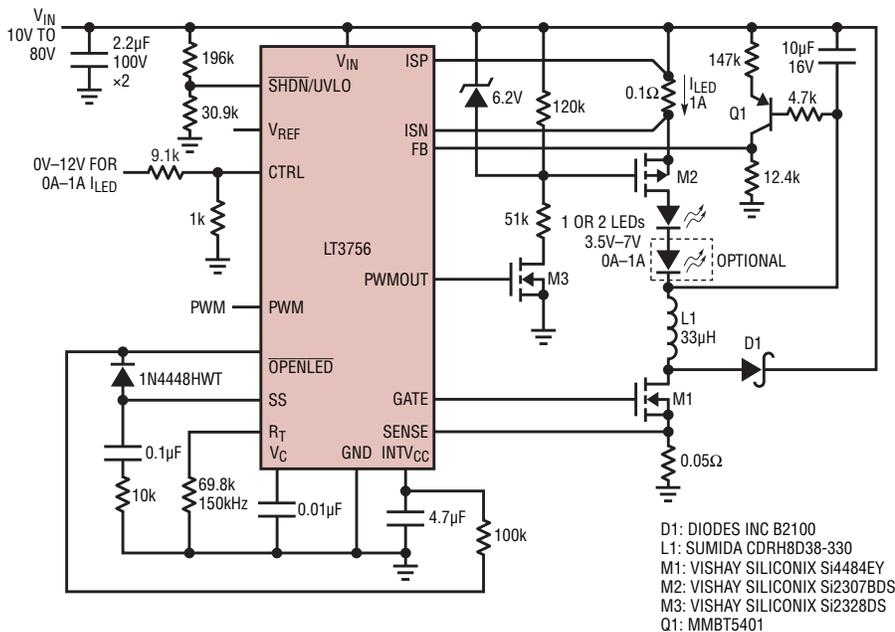


Figure 2. An 80V_{IN} buck mode LED driver with PWM dimming for single or double LEDs

50°C discrete component temperature rise—far more manageable than the potential heat produced by the 83V string of 1.5A LEDs.

Even if PWM dimming is not required, the PWMOUT dimming MOSFET is useful for LED disconnect during shutdown. This prevents current from running through the string of ground-connected LEDs—possible under certain input conditions.

If an LED fails open or if the LED string is removed from the high power driver, the FB constant voltage loop takes over and regulates the output at 95V until a proper string is attached between LED⁺ and LED⁻. Without overvoltage protection, the LED sense resistor would see zero LED current and the control loop would work hard to increase its output. Eventually, the output capacitor voltage would go over 100V, exceeding the maximum rating of several components. While in OVP the OPENLED status flag goes low.

High Voltage Buck Mode LED Driver with High PWM Dimming Ratio

When the input voltage is higher than the LED string voltage, the LT3756 can serve equally well as a constant current buck mode converter. For example, an automotive battery's voltage can present a wildly moving target,

from drooping voltages to dizzyingly high voltage spikes. The buck mode LED driver in Figure 2 is perfect for such harsh environments. It operates with a wide 10V-to-80V input range to drive one or two 3.5V LEDs (7V) at 1A. In this case, both the V_{IN} pin and ISP and ISN current sense inputs can go as high as 80V.

PWM dimming requires a level-shift from the PWMOUT pin to the high side LED string as shown in Figure 2. The maximum PWM dimming ratio increases with higher switching frequency, lower PWM dimming frequency, higher input voltage and lower LED power. In this case, a 100:1 dimming ratio is possible with a 100Hz dimming frequency, a 48V input, a 3.5V or 7V LED at 1A, and a 150kHz switching frequency. Although higher switching frequency is possible with the LT3756, the duty cycle eventually has its limits. Generous minimum on-time and minimum off-time restrictions require a frequency on the lower end of its range (150kHz) to meet both the harsh high-V_{IN}-to-low-V_{LED} (80V_{IN} to one 3.5V LED) and low-V_{IN}-dropout requirements (10V_{IN} to 7V_{LED}) of this particular converter.

The overvoltage protection of the buck mode LED driver has a level shift as well. Q1, a npn transistor, helps regulate the maximum allowable

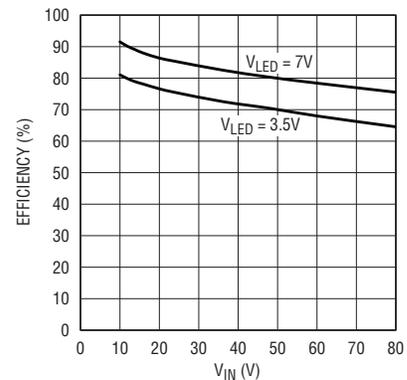


Figure 3. Efficiency for the buck mode converter in Figure 2

output capacitor voltage to a level just beyond that of the LED string. Without the level-shifted OVP network tied to FB, an open LED string would result in the output capacitor charging up to the input voltage. Although the buck mode components will survive this scenario, the LEDs may not survive being plugged back into a potential equal to the input voltage. That is, a single 3.5V LED might not survive being connected directly to 80V.

Single Inductor Buck-Boost Mode LED Driver

One increasingly common LED driver requirement is that the ranges of both the LED string voltage and the input voltage are wide and overlapping. In fact, some designers prefer to use the same LED driver circuit for several different battery sources and several different LED string types. Such a versatile configuration trades some efficiency, component cost, and board space for design simplicity, but the tradeoffs are usually mitigated by the significantly reduced time-to-market by producing an essentially off-the-shelf multipurpose LED driver.

The buck-boost mode topology shown in Figure 4 uses a single inductor and can both step-up and step-down the input voltage to the LED string voltage. It accepts inputs from 6V to 36V to drive 10V–50V LED strings at up to 400mA. The PWM dimming and OVP are level-shifted in a manner similar to the buck mode for optimal performance of these features.

The inductor current is the sum of the input current and the LED string

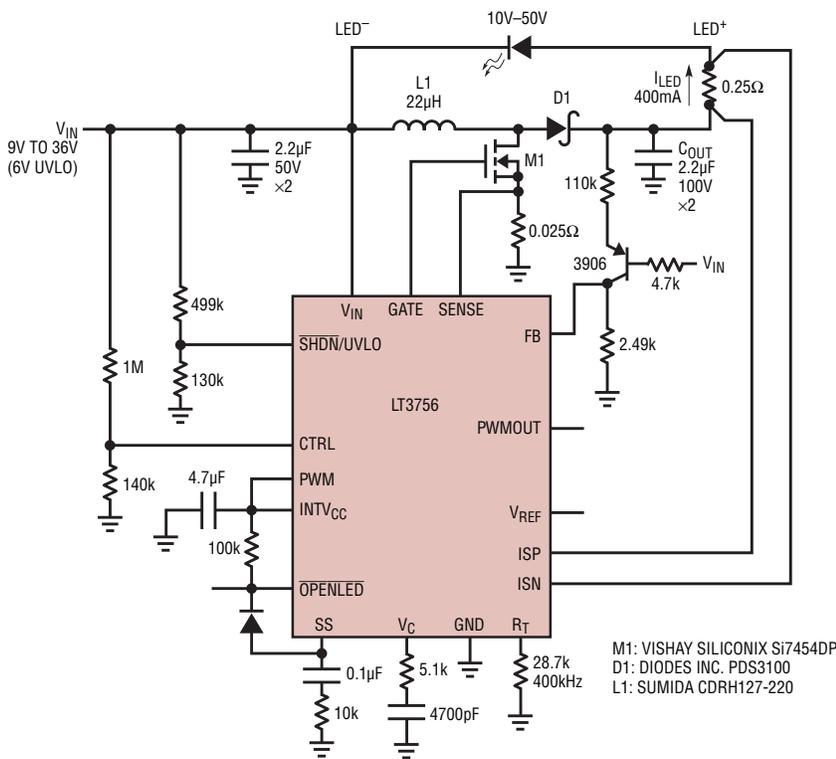


Figure 4. A buck-boost mode LED driver with wide-ranging V_{IN} and V_{LED}

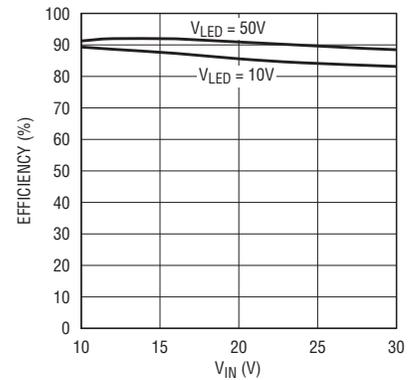


Figure 5. Efficiency for the buck-boost mode converter in Figure 4

current; the peak inductor current is also equal to the peak switching current—higher than either a buck mode or boost topology LED driver with similar specs due to the nature of the hookup. The 4A peak switch current and inductor rating reflects the worst-case 9V input to 50V LED string at 400mA.

Below 9V input, the CTRL analog dimming input pin is used to scale back

the LED current to keep the inductor current under control if the battery voltage drops too low. The LEDs turn off below 6V input due to undervoltage lockout and will not turn back on until the input rises above 7V, to prevent flickering. In buck-boost mode, the output voltage is the sum of the input voltage and the LED string voltage. The output capacitor, the catch diode, and

the power MOSFET can see voltages as high as 90V for this design.

Conclusion

The 100V LT3756 controller is ostensibly a high power LED driver, but its architecture is so versatile, it can be used in any number of high voltage input applications. Of course, it has all the features required for large (and small) strings of high power LEDs. It can be used in boost, buck-boost mode, buck mode, SEPIC and flyback topologies. Its high voltage rating, optimized LED driver architecture, high performance PWM dimming, host of protection features and accurate high side current sensing make the LT3756 a single-IC choice for a variety of high voltage input and high power lighting systems. 

LT3782A, continued from page 36

other out, thus reducing the total output ripple by 50%, which in turn reduces output capacitance requirements. The input current ripple is also halved, which reduces the required input capacitance and reduces EMI. Finally, the power dissipated as heat is spread out over two phases, reducing the size of heat sinks or eliminating them altogether.

24V at 8A from a 10V-15V Input

Figure 1 shows a high power boost application that efficiently produces a 24V/8A output from a 10V-15V input. The LTC4440 high side driver is used

to level shift the SGATE signals and drive the synchronous MOSFETs. The 250kHz switching frequency optimizes efficiency and component size/board area. Figure 2 shows the layout. Proper routing and filtering of the sense pins, placement of the power components and isolation using ground and supply planes ensure an almost jitter free operation, even at 50% duty cycle.

Figure 3 shows the efficiency of the circuit in Figure 1 with synchronous MOSFETs (measured to 8A) and the efficiency of an equivalent non-synchronous circuit using boost diodes (measured to 6A). The 1% improvement in peak efficiency may not seem significant, but take a look at the difference

in heat dissipation shown in Figure 4, which shows thermal images of both circuits under equivalent operating conditions. The thermal advantages of using synchronous switches are clear.

Conclusion

The 2-phase synchronous boost topology possible with the LT3782A offers several advantages over a non-synchronous or a single-phase boost topology. Its combination of high efficiency, small footprint, heat sink-free thermal characteristics and low input/output capacitance requirements make it an easy fit in automotive and industrial applications. 

Parallel Buck-Boost μ Module Regulators to Produce High Current in Sub-2.8mm Height Applications

by Judy Sun, Sam Young and Henry Zhang

Introduction

For applications requiring DC/DC converters to regulate an output voltage that is somewhere in the middle of an input voltage range, circuit designers are always troubled by the complexity and/or low efficiency of available converter topologies, such as SEPIC, flyback or forward converters. As an alternative, Linear Technology offers a number of 4-switch synchronous buck-boost regulator/controller ICs that significantly improve efficiency and save space over other buck-boost topologies—even as they simplify design and produce higher power densities. Linear Technology μ Modules further simplify design by integrating

A big advantage of μ Module regulators is that they can be easily paralleled to increase output power capability. The current mode control scheme ensures balanced current sharing among the paralleled μ Module regulators at both steady state and transient conditions, whether running in buck, boost, or buck-boost mode.

most of the discrete components into a single package. For instance, the LTM4605 and LTM4607 buck-boost μ Modules fit almost all required components into a 15mm \times 15mm \times 2.8mm surface mount package, requiring only an external inductor, a current sensing resistor, a voltage setting resistor and a few input and output capacitors. μ Module solutions also offer exceptional thermal performance, further simplifying already simple layout.

Another big advantage of μ Module regulators is that they can be easily paralleled to increase output power capability. The current mode

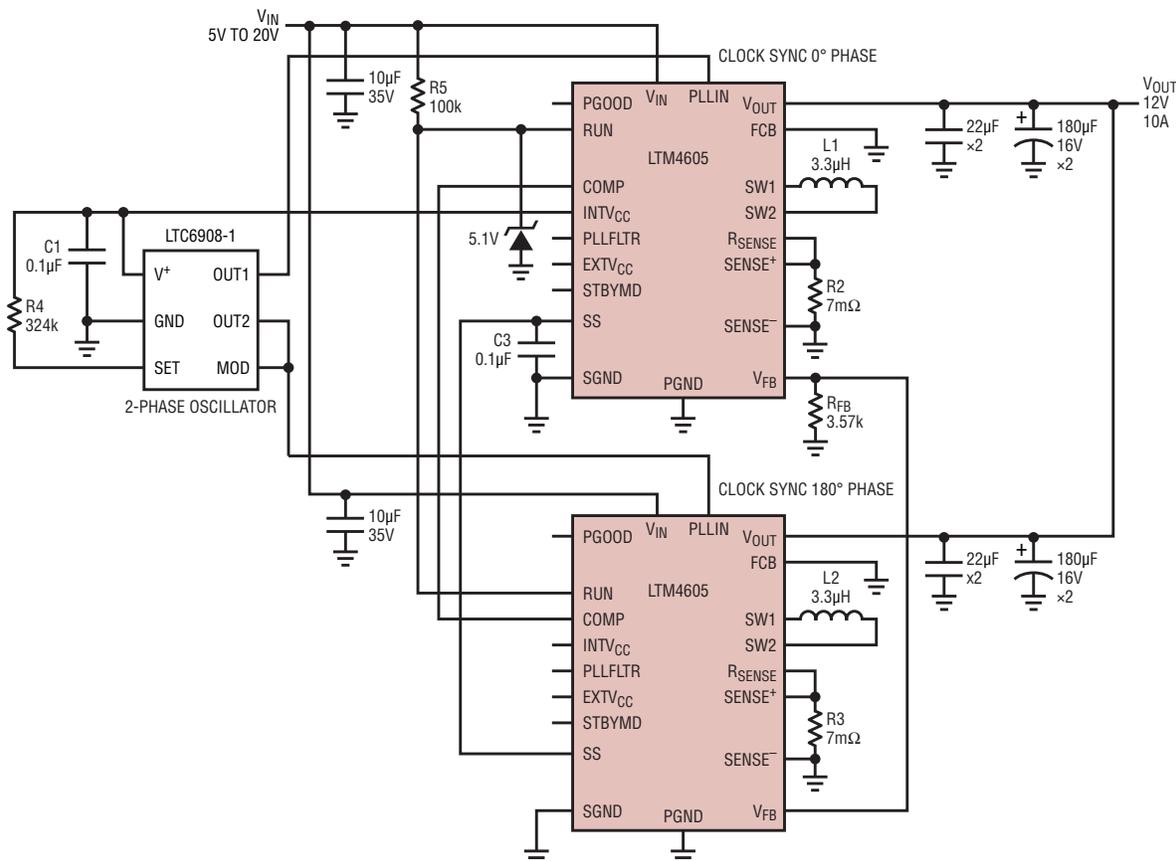


Figure 1. Paralleling two LTM4605s for high output current

control scheme ensures balanced current sharing among the paralleled μ Modules at both steady state and transient conditions, whether running in buck, boost, or buck-boost mode.

Parallel Two LTM4605 μ Module Regulators for 12V at 10A in Boost Mode, 20A in Buck Mode

Paralleling the μ Module buck-boost regulators is simple: just tie their V_{IN} , V_{OUT} , COMP, V_{FB} , RUN and SS pins together, as shown in Figure 1. The LTC6908-1 oscillator synchronizes the two paralleled modules so that they operate with a 180° phase difference. Interleaving the power output in this way effectively cancels input and output ripple, thus minimizing required input and output capacitance.

This circuit in Figure 1 accepts a 5V to 20V input, and generates a 12V output. The rated output current is 10A for boost mode and 20A for buck mode. Figure 2 shows the efficiency curves at a 300kHz switch-

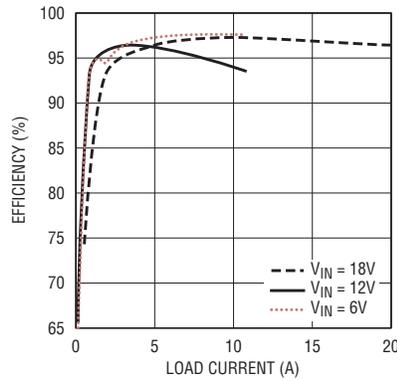


Figure 2. High efficiency from the parallel LTM4605s in Figure 1 (CCM mode)

ing frequency. The paralleled modules achieve about 95% efficiency in boost mode and more than 97% efficiency in buck-boost and buck mode, over a wide load range.

Because the inductor currents are sensed and controlled by the same COMP pin voltage, the current sharing is naturally guaranteed among paralleled μ Modules. It does not matter if the system is running in buck mode, buck-boost mode or boost

mode, DC current sharing is excellent throughout. Figure 3 demonstrates well-balanced inductor currents for the two paralleled LTM4605s in all three operation modes.

Thanks to the high efficiencies and well-balanced output currents, the thermal stress is evenly distributed between the two LTM4605s and two inductors, ensuring high system reliability. Figure 4 shows thermal pictures of the two paralleled LTM4605s, where the inductors are mounted above the LTM4605 μ Modules. The temperature rises of the two LTM4605s and two inductors are very similar in all three cases with V_{IN} at 18V, 12V and 6V. Even without forced air flow, the maximum temperature rise is only 45°C .

Parallel Four for 12V at 20A in Boost Mode, 40A in Buck Mode

Need more output current than two LTM4605s can handle? In that case, just parallel more μ Module regulators.

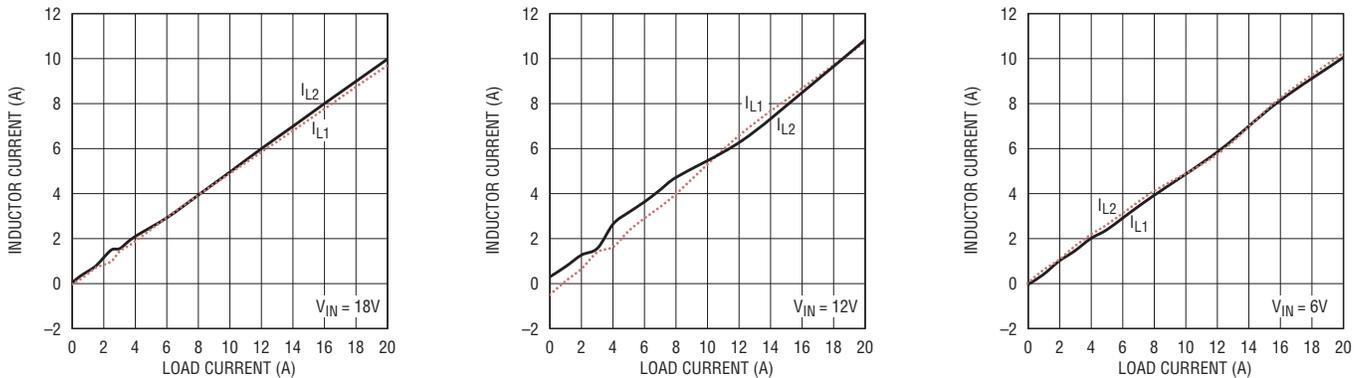


Figure 3. Balanced inductor currents for two paralleled LTM4605s in different operating modes

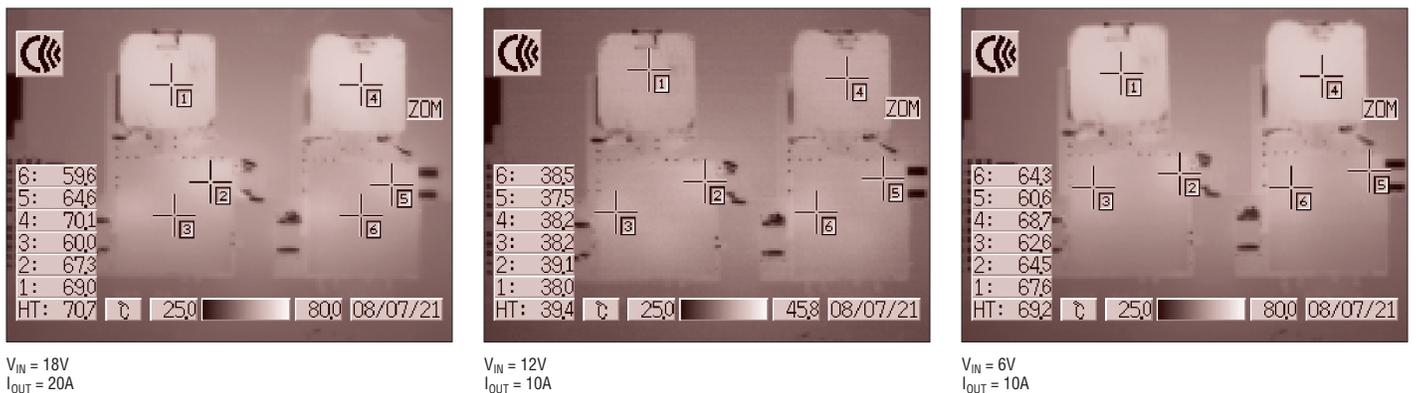


Figure 4. Thermal stress is evenly distributed between the two LTM4605s and two inductors for the circuit in Figure 1 (shown here with no air flow or heat sink).

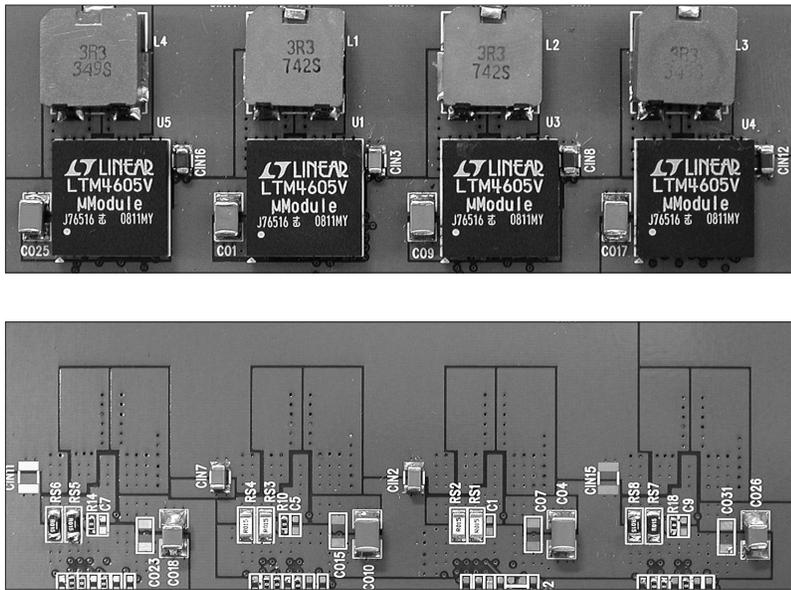


Figure 5. Simple layout of four LTM4605 μModule regulators in parallel: top and bottom sides of the board (additional input and output bulk caps are placed on the top and bottom).

For example, simply connect the V_{IN} , V_{OUT} , COMP, V_{FB} , RUN and SS pins of four LTM4605s in parallel to produce 20A in boost mode and more in buck mode. The LTM4605 or LTM4607 μModule is internally compensated so that it is stable in any parallel system.

Figure 5 shows the layout of four paralleled LTM4605s. This simple design delivers 240W of output power with a high power density and low profile. The input range is 5V to 20V, producing a 12V output. It is capable of supporting 20A loads in boost mode and up to 40A in buck mode. A 4-phase oscillator synchronizes the μModule regulators with 90° phase interleaving. This effectively cancels input and

The LTM4605 and LTM4607 buck-boost μModule regulators are ideal for the applications where the output voltage is within the input voltage range.

output ripple. Figure 6 shows that efficiency is better than 95% in boost mode and up to 97% in buck mode, over a wide output current range.

Figure 7 shows the thermal performance for the four paralleled LTM4605s running at full load at three different input voltages. Load current, and thus power dissipation,


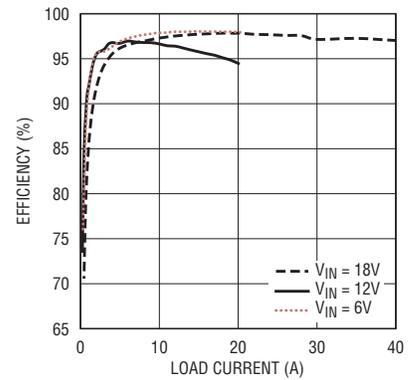


Figure 6. The tested efficiency for the four LTM4605s paralleled in Figure 5 (CCM mode)


is equally shared among the four inductors because of the internal current mode control scheme. High efficiency and well-balanced currents lead to excellent thermal performance, which allows this 240W system to fit tight spaces.

Conclusion


The LTM4605 and LTM4607 buck-boost μModule regulators are ideal for the applications where the output voltage is within the input voltage range. In addition, these integrated μModules can be easily paralleled to provide more power. Outstanding current sharing performance is ensured by the internal current mode control scheme, whether the μModules are running in buck, buck-boost or boost mode. With minimum circuit and PCB layout design effort, the paralleled LTM4605 and LTM4607 μModules provide high output power, high efficiency, and high reliability in an extraordinarily compact form factor. 

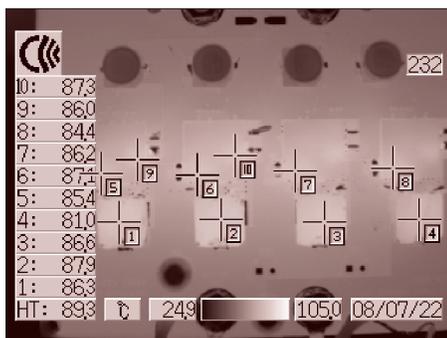

$V_{IN} = 18V$
 $I_{OUT} = 40A$

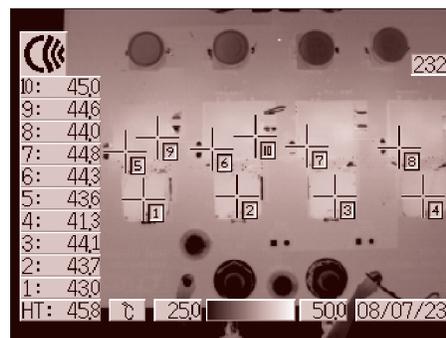

$V_{IN} = 12V$
 $I_{OUT} = 20A$

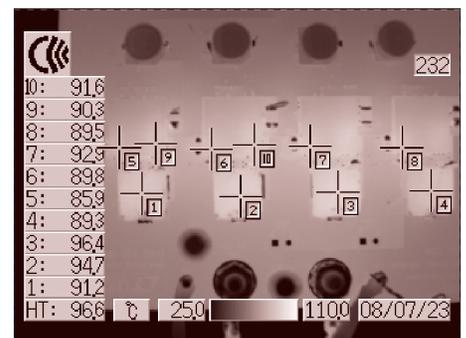

$V_{IN} = 6V$
 $I_{OUT} = 20A$

Figure 7. Thermal performance of the four LTM4605s paralleled in Figure 5 at 240W with no air flow or heat sink

www.linear.com

MyLinear

(www.linear.com/mylinear)

MyLinear is a customizable home page to store your favorite LTC products, categories, product tables, contact information, preferences and more. Creating a MyLinear account allows you to...

- Store and update your contact information. No more reentering your address every time you request a sample!
- Edit your subscriptions to *Linear Insider* email newsletter and *Linear Technology Magazine*.
- Store your favorite products and categories for future reference.
- Store your favorite parametric table. Customize a table by editing columns, filters and sort criteria and store your settings for future use.
- View your sample history and delivery status.

Using your MyLinear account is easy. Just visit www.linear.com/mylinear to create your account.

Purchase Products

(www.linear.com/purchase)

Purchase products directly from Linear Technology either through the methods below or contact your local LTC sales representative or licensed distributor.

Credit Card Purchase — Your Linear Technology parts can be shipped almost anywhere in the world with your credit card purchase. Orders up to 500 pieces per item are accepted. You can call (408) 433-5723 or email orders@linear.com with questions regarding your order.

Linear Express — Purchase online with credit terms. Linear Express is your new choice for purchasing any quantity of Linear Technology parts. Credit terms are available for qualifying accounts. Minimum order is only \$250.00. Call 1-866-546-3271 or email us at express@linear.com.

Product and Applications Information

At www.linear.com you will find our complete collection of product and applications information available for download. Resources include:

Data Sheets — Complete product specifications, applications information and design tips

Application Notes — In depth collection of solutions, theory and design tips for a general application area

Design Notes — Solution-specific design ideas and circuit tips

LT Chronicle — A monthly look at LTC products for specific end-markets

Product Press Releases — New products are announced constantly

Solutions Brochures — Complete solutions for automotive electronics, high speed ADCs, LED drivers, wireless infrastructure, industrial signal chain, handheld, battery charging, and communications and industrial DC/DC conversion applications.

Product Selection

The focus of Linear Technology's website is simple—to get you the information you need quickly and easily. With that goal in mind, we offer several methods of finding the product and applications information you need.

Part Number and Keyword Search — Search Linear Technology's entire library of data sheets, Application Notes and Design Notes for a specific part number or keyword.

Sortable Parametric Tables — Any of Linear Technology's product families can be viewed in table form, allowing the parts to be sorted and filtered by one or many functional parameters.

Applications Solutions — View block diagrams for a wide variety of automotive, communications, industrial and military applications. Click on a functional block to generate a complete list of Linear Technology's product offerings for that function.

Design Support

Packaging (www.linear.com/packaging) — Visit our packaging page to view complete information for all of Linear Technology's package types. Resources include package dimensions and footprints, package cross reference, top markings, material declarations, assembly procedures and more.

Quality and Reliability (www.linear.com/quality) — The cornerstone of Linear Technology's Quality, Reliability & Service (QRS) Program is to achieve 100% customer satisfaction by producing the most technically advanced product with the best quality, on-time delivery and service. Visit our quality and reliability page to view complete reliability data for all of LTC's products and processes. Also available is complete documentation on assembly and manufacturing flows, quality and environmental certifications, test standards and documentation and failure analysis policies and procedures.

Lead Free (www.linear.com/leadfree) — A complete resource for Linear Technology's Lead (Pb) Free Program and RoHS compliance information.

Simulation and Software

Linear Technology offers several powerful simulation tools to aid engineers in designing, testing and troubleshooting their high performance analog designs.

LTspice/SwitcherCAD™ III (www.linear.com/swcad) — LTspice / SwitcherCAD III is a powerful SPICE simulator and schematic capture tool specifically designed to speed up and simplify the simulation of switching regulators. LTspice / SwitcherCAD III includes:

- Powerful general purpose Spice simulator with schematic capture, waveform viewing, and speed enhancements for switching regulators.
- Complete and easy to use schematic capture and waveform viewer.
- Macromodels for most of Linear Technology's switching regulators as well as models for many of LTC's high performance linear regulators, op amps, comparators, filters and more.
- Ready to use demonstration circuits for over one hundred of Linear Technology's most popular products.

FilterCAD — FilterCAD 3.0 is a computer-aided design program for creating filters with Linear Technology's filter ICs.

Noise Program — This program allows the user to calculate circuit noise using LTC op amps and determine the best LTC op amp for a low noise application.

SPICE Macromodel Library — A library includes LTC op amp SPICE macromodels for use with any SPICE simulation package.

Subscribe!

Subscribe to
Linear Technology magazine at
www.linear.com/mylinear

SALES OFFICES

NORTH AMERICA

NORTHERN CALIFORNIA / NEVADA

Bay Area

720 Sycamore Dr
Milpitas, CA 95035
Tel: (408) 428-2050
Fax: (408) 432-6331

Sacramento / Nevada

2260 Douglas Blvd., Ste. 280
Roseville, CA 95661
Tel: (916) 787-5210
Fax: (916) 787-0110

PACIFIC NORTHWEST

Denver

7007 Winchester Cir., Ste. 130
Boulder, CO 80301
Tel: (303) 926-0002
Fax: (303) 530-1477

Portland

5005 SW Meadows Rd., Ste. 410
Lake Oswego, OR 97035
Tel: (503) 520-9930
Fax: (503) 520-9929

Salt Lake City

Tel: (801) 731-8008

Seattle

2018 156th Ave. NE, Ste. 100
Bellevue, WA 98007
Tel: (425) 748-5010
Fax: (425) 748-5009

SOUTHWEST

Los Angeles

21243 Ventura Blvd., Ste. 238
Woodland Hills, CA 91364
Tel: (818) 703-0835
Fax: (818) 703-0517

Orange County

15375 Barranca Pkwy., Ste. A-213
Irvine, CA 92618
Tel: (949) 453-4650
Fax: (949) 453-4765

Phoenix

2085 E. Technology Cir., Ste. 101
Tempe, AZ 85284
Tel: (480) 777-1600
Fax: (480) 838-1104

San Diego

5090 Shoreham Place, Ste. 110
San Diego, CA 92122
Tel: (858) 638-7131
Fax: (858) 638-7231

CENTRAL

Chicago

2040 E. Algonquin Rd., Ste. 512
Schaumburg, IL 60173
Tel: (847) 925-0860
Fax: (847) 925-0878

Cleveland

7550 Lucerne Dr., Ste. 106
Middleburg Heights, OH 44130
Tel: (440) 239-0817
Fax: (440) 239-1466

Columbus

Tel: (614) 488-4466

Detroit

39111 West Six Mile Road
Livonia, MI 48152
Tel: (734) 779-1657
Fax: (734) 779-1658

Indiana

Tel: (317) 581-9055

Iowa

Tel: (319) 393-5763

Kansas

Tel: (913) 829-8844

Minneapolis

7805 Telegraph Rd., Ste. 225
Bloomington, MN 55438
Tel: (952) 903-0605
Fax: (952) 903-0640

Wisconsin

Tel: (262) 859-1900

NORTHEAST

Boston

15 Research Place
North Chelmsford, MA 01863
Tel: (978) 656-4750
Fax: (978) 656-4760

Connecticut

Tel: (860) 228-4104

Philadelphia

3220 Tillman Dr., Ste. 120
Bensalem, PA 19020
Tel: (215) 638-9667
Fax: (215) 638-9764

SOUTHEAST

Atlanta

Tel: (770) 888-8137

Austin

8500 N. Mopac, Ste. 603
Austin, TX 78759
Tel: (512) 795-8000
Fax: (512) 795-0491

Dallas

17000 Dallas Pkwy., Ste. 200
Dallas, TX 75248
Tel: (972) 733-3071
Fax: (972) 380-5138

Fort Lauderdale

Tel: (954) 473-1212

Houston

1080 W. Sam Houston Pkwy.,
Ste. 225
Houston, TX 77043
Tel: (713) 463-5001
Fax: (713) 463-5009

Huntsville

Tel: (256) 881-9850

Orlando

Tel: (407) 688-7616

Raleigh

15100 Weston Pkwy., Ste. 202
Cary, NC 27513
Tel: (919) 677-0066
Fax: (919) 678-0041

Tampa

Tel: (813) 634-9434

CANADA

Calgary, AB

Tel: (403) 455-3577

Montreal, QC

Tel: (450) 689-2660

Ottawa, ON

Tel: (613) 421-3090

Toronto, ON

Tel: (416) 239-0817

Vancouver, BC

Tel: (604) 729-1204

ASIA

AUSTRALIA / NEW ZEALAND

Linear Technology Corporation

133 Alexander Street
Crowns Nest NSW 2065
Australia
Tel: +61 (0)2 9432 7803
Fax: +61 (0)2 9439 2738

CHINA

Linear Technology Corp. Ltd.

Units 1503-04, Metroplaza
Tower 2
223 Hing Fong Road
Kwai Fong, N.T., Hong Kong
Tel: +852 2428-0303
Fax: +852 2348-0885

Linear Technology Corp. Ltd.

Room 2701, City Gateway
No. 398 Cao Xi North Road
Shanghai, 200030, PRC
Tel: +86 (21) 6375-9478
Fax: +86 (21) 5465-5918

Linear Technology Corp. Ltd.

Room 816, 8/F
China Electronics Plaza B
No. 3 Dan Ling Rd., Hai Dian
District
Beijing, 100080, PRC
Tel: +86 (10) 6801-1080
Fax: +86 (10) 6805-4030

Linear Technology Corp. Ltd.

Room 2604, 26/F
Excellence Times Square Building
4068 YiTian Road, Futian District
Shenzhen, 518048, PRC
Tel: +86 755-8236-6088
Fax: +86 755-8236-6008

JAPAN

Linear Technology KK

8F Shuwa Kioicho Park Bldg.
3-6 Kioicho Chiyoda-ku
Tokyo, 102-0094, Japan
Tel: +81 (3) 5226-7291
Fax: +81 (3) 5226-0268

Linear Technology KK

6F Kearny Place Honmachi Bldg.
1-6-13 Awaza, Nishi-ku
Osaka-shi, 550-0011, Japan
Tel: +81 (6) 6533-5880
Fax: +81 (6) 6543-2588

Linear Technology KK

7F Sakuradori Ohtsu KT Bldg.
3-20-22 Marunouchi, Naka-ku
Nagoya-shi, 460-0002, Japan
Tel: +81 (52) 955-0056
Fax: +81 (52) 955-0058

KOREA

Linear Technology Korea Co., Ltd.

Yundang Building, #1002
Samsung-Dong 144-23
Kangnam-Ku, Seoul 135-090
Korea
Tel: +82 (2) 792-1617
Fax: +82 (2) 792-1619

SINGAPORE

Linear Technology Pte. Ltd.

507 Yishun Industrial Park A
Singapore 768734
Tel: +65 6753-2692
Fax: +65 6752-0108

TAIWAN

Linear Technology Corporation

8F-1, 77, Nanking E. Rd., Sec. 3
Taipei, Taiwan
Tel: +886 (2) 2505-2622
Fax: +886 (2) 2516-0702

EUROPE

FINLAND

Linear Technology AB

Teknobulevardi 3-5
P.O. Box 35
FIN-01531 Vantaa
Finland
Tel: +358 (0)9 2517 8200
Fax: +358 (0)9 2517 8201

FRANCE

Linear Technology S.A.R.L.

Parc Tertiaire Silic
2 Rue de la Couture, BP10217
94518 Rungis Cedex
France
Tel: +33 (1) 56 70 19 90
Fax: +33 (1) 56 70 19 94

GERMANY

Linear Technology GmbH

Osterfeldstrasse 84, Haus C
D-85737 Ismaning
Germany
Tel: +49 (89) 962455-0
Fax: +49 (89) 963147

Linear Technology GmbH

Haselburger Damm 4
D-59387 Ascheberg
Germany
Tel: +49 (2593) 9516-0
Fax: +49 (2593) 951679

Linear Technology GmbH

Jesinger Strasse 65
D-73230 Kirchheim/Teck
Germany
Tel: +49 (0)7021 80770
Fax: +49 (0)7021 807720

ITALY

Linear Technology Italy Srl

Orione 3, C.D. Colleoni
Via Colleoni, 17
I-20041 Agrate Brianza (MI)
Italy
Tel: +39 039 596 5080
Fax: +39 039 596 5090

SWEDEN

Linear Technology AB

Electrum 204
Isafjordsgatan 22
SE-164 40 Kista
Sweden
Tel: +46 (8) 623 16 00
Fax: +46 (8) 623 16 50

UNITED KINGDOM

Linear Technology (UK) Ltd.

3 The Listons, Liston Road
Marlow, Buckinghamshire
SL7 1FD
United Kingdom
Tel: +44 (1628) 477066
Fax: +44 (1628) 478153



Linear Technology Corporation

1630 McCarthy Blvd.
Milpitas, CA 95035-7417
1-800-4-LINEAR • 408-432-1900 • 408-434-0507 (fax)
www.linear.com

To subscribe to *Linear Technology* magazine, visit www.linear.com/mylinear