

Power Consumption: a Primary Consideration in Smart Transmitter Design

by Tracey Johnson, applications engineer, and Michal Brychta, applications engineer, Analog Devices, Inc.

Designing loop-powered field instruments with a 4 mA to 20 mA analog output and a HART® (highway addressable remote transducer) interface within the required power budget can be challenging. Modern field instruments, otherwise known as smart transmitters, are intelligent, microprocessor-based devices that monitor process control variables. Such field devices are becoming increasingly intelligent as more and more processing capabilities are being distributed into the field domain. The incorporation of such additional intelligence, as well as increased functionality and diagnostic capabilities heightens the challenge involved in developing a system that can operate effectively within the limited power available from the 4 mA to 20 mA loop. This article explores the power consumption challenge faced by system designers and provides insights into how a sample solution developed by Analog Devices and registered with the HART Communication Foundation tackles this challenge, both at the overall system level and within the fundamental signal chain elements of the smart transmitter design.

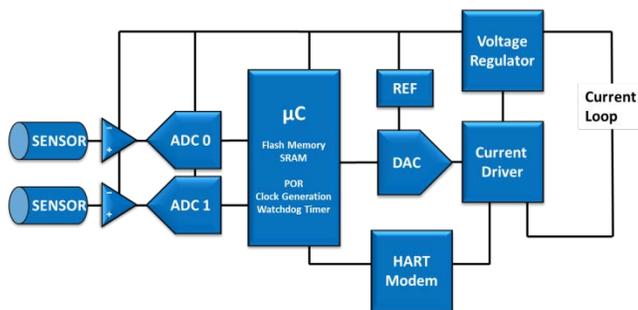


Figure 1. Smart Transmitter Signal Chain

The most important element of any transmitter is the primary sensor and its optimum operation to deliver the most accurate representation of the environmental parameter being measured. The primary variable is often dependent on a secondary variable (for example, the temperature compensation of a pressure sensor). In the example shown in Figure 2, the sensor is a resistive bridge

with 5 kΩ impedance, and the chosen mode of operation is a continuous 3.3 V voltage excitation. This results in the sensor consuming 660 µA of the overall system power budget.

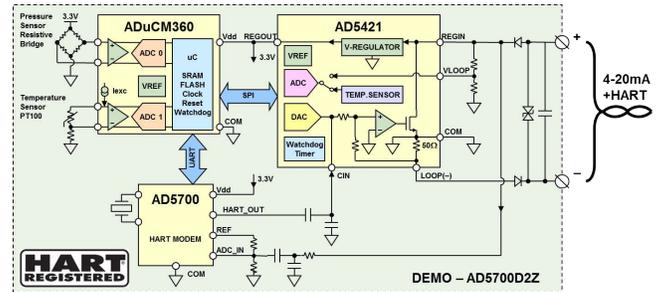


Figure 2. HART Enabled Field Instrument Demo Block Diagram

The ADuCM360 precision analog microcontroller integrates two low noise precision instrumentation amplifiers with programmable gain. The amplifiers are optimized for the lowest possible power and their stages are switched on only when needed for the required gain. This allows the best trade-off to be made between the circuit's performance and power requirements. In the sample circuit described here, the primary sensor could be used with only half the excitation voltage, resulting in half the signal level, and optimizing the signal chain performance by programmatically doubling the amplifier gain from 16 to 32. This would mean a saving of 330 µA in sensor excitation current and an increase of 60 µA in the amplifier supply current—giving a net saving of 270 µA. When considering such trade-offs, there are indeed other aspects to consider; for example, the sensor signal-to-noise ratio during external electromagnetic disturbance. The fully integrated programmable solution can help to make evaluation of these options easier for the designer.

Two 24-bit analog-to-digital converters (ADCs) sample the amplified primary and secondary sensor signals and translate them to the digital domain. In Figure 2, the ADCs are integrated on the ADuCM360 and again optimized for the lowest power needed for the required performance. The Σ-Δ architecture offers inherent high resolution, linearity and precision, and the digital filter, which is always included in the Σ-Δ ADC, allows programmable trade-offs between the required signal bandwidth and the input noise, the latter having a direct impact on the achievable resolution. Often a resolution higher than 16 bits is needed on the field instrument input in order to deliver 16-bit resolution on its output.

Table 1. Demo Circuit Power Calculations

	Circuit Block	Supply Current (mA)	% of Total Current
Sensor	Primary sensor (resistive bridge, 5 kΩ at 3.3 V)	0.660	
	Secondary sensor (RTD, 200 μA excitation)	0.200	
	Sensor Total	0.860	28%
ADuCM360	Instrumentation amplifier 1 (gain = 8)	0.130	
	Instrumentation amplifier 2 (gain = 16)	0.130	
	24-bit ADC 1, including input buffer	0.140	
	24-bit ADC 2, including input buffer	0.140	
	Voltage reference, RTD current source reference	0.135	
	ADuCM360 Analog Circuitry Total	0.675	22%
	Microcontroller core (@ 2 MHz) and memory	0.790	
	SPI, UART, timers, watchdog, other circuitry	0.085	
	Clock generator	0.170	
	ADuCM360 Digital Circuitry Total	1.045	34%
AD5421	16-bit DAC	0.050	
	V-to-I driver	0.060	
	Voltage reference	0.050	
	Power management, voltage regulators	0.055	
	SPI, watchdog, other circuitry	0.010	
	AD5421 Total	0.225	7%
AD5700	Modulator/demodulator (worst case, transmitting)	0.124	
	Clock generator (with external crystal)	0.033	
	AD5700 Total	0.157	5%
	Other circuitry on board, dynamic currents	0.138	4%
	Combined Total	3.100	100%

In conclusion, not only does this solution deliver on low power, but it is also a high performance solution, with minimum area overhead, not to mention HART compliance. It has been compliance tested, verified and registered as an approved HART solution with the HART Communication Foundation. This successful registration instills confidence in circuit designers when using the components outlined in the circuit. The high level of integration in the ADuCM360 enables a high level of flexibility, and shifts the focus from traditional discrete component designs to the optimum use of each integrated block within the chip. The system designer can explore the previously described trade-offs, even at late stages of a design, by simply changing the circuit setup in the software. This allows for short design cycles, ease of circuit modifications, and tuning of circuit performance, without the need to go through costly and time consuming PCB revisions. This integrated and fully programmable CN0267 solution is fully documented, with hardware available to order online.



Figure 4. HART Registered Field Instrument Demo Board

REFERENCES

HART Communication Foundation, www.hartmcomm.org.

RESOURCES

Share this article on



