

# Index

---

## A

AC CMR vs. frequency, table, 5-20

AC input coupling, 5-2

AD620:

closed-loop gain vs. frequency, 3-4

CMR vs. frequency, 3-4

for EKG monitor transducer, 6-23

gain nonlinearity, 3-5

for Hall effect magnetic transducer, 6-23

industry standard, 3-2, 3-3

input circuit, 5-6

for load cell transducer, 6-23

low power in-amp, 6-20

monolithic in-amp, 5-10

for photodiode sensor transducer, 6-23

pin configuration, 3-3

for RTD transducer, 6-23

simplified schematic, 3-4

small signal pulse response, 3-5

for thermistor transducer, 6-23

for thermocouple transducer, 6-23

AD620 series:

input circuit diagram, 5-6

RFI circuit, 5-15

AD621:

closed-loop gain vs. frequency, 3-7

CMR vs. frequency, 3-7

for EKG monitor transducer, 6-23

gain nonlinearity, 3-7

greater accuracy than AD620, 3-6

for Hall effect magnetic transducer, 6-23

for load cell transducer, 6-23

monolithic in-amp, 5-11

for photodiode sensor transducer, 6-23

for RTD transducer, 6-23

simplified schematic, 3-6

small signal pulse response, 3-7

for thermistor transducer, 6-23

for thermocouple transducer, 6-23

AD622:

for Hall effect magnetic transducer, 6-23

low cost:

closed-loop gain vs. frequency,  
3-5, 3-6

CMR vs. frequency, 3-5

gain nonlinearity, 3-5

for photodiode sensor transducer, 6-23

AD623:

3-op amp circuit basis, 3-17

closed-loop gain vs. frequency, 3-18

CMR vs. frequency, 3-18

composite:

circuits, 6-4, 5

CMR, 6-4

driving ADC, circuit, 6-5

for EKG monitor transducer, 6-23

gain nonlinearity, 3-18

for Hall effect magnetic transducer, 6-23

input architecture, 5-6

input circuit, 5-6

for photodiode sensor transducer, 6-23

rail-to-rail, 5-1

RFI filter, 5-16

RFI suppression circuit, 5-16

for RTD transducer, 6-23

simplified schematic, 3-17

single-supply data circuit, 6-20

small signal pulse response, 3-18

for thermistor transducer, 6-23

for thermocouple transducer, 6-23

AD626:

for current sense (shunt) transducer, 6-23

differential amplifier:

single- or dual-supply, 4-7, 4-8

CMR ratio, 4-8

gains, 4-8

signal pulse response, 4-8

simplified schematic, 4-8

for level sensor transducer, 6-23

AD627:

classic bridge circuit, 6-19

closed-loop gain vs. frequency, 3-20

CMR vs. frequency, 2-6, 3-19

for EKG monitor transducer, 6-23

feedback loops, 3-19

gain, equation, 3-19

gain nonlinearity, 3-20

for Hall effect magnetic transducer, 6-23

input circuit, 5-6

low power, 6-25, 6-26

monolithic 2-op amp in-amp, 2-5, 2-6

for photodiode sensor transducer, 6-23

RFI suppression circuit, 5-15

for RTD transducer, 6-23

simplified schematic, 3-19

small signal pulse response, 3-20

for thermistor transducer, 6-23

for thermocouple transducer, 6-23

AD628:

bandwidth gain block, 6-11

block diagram, 1-5

for current sense (shunt) transducer, 6-23

difference amplifier, 6-13

differential scaling amplifier, 6-6, 6-7

high common-mode voltage difference amplifier,  
4-6, 4-7

circuit connections, 4-6

CMRR vs. frequency, 4-7

gain adjustment, 4-6, 4-7

large signal frequency response, 4-7

- simplified schematic, 4-6
- small signal frequency response, 4-7
- for level sensor transducer, 6-23
- low gain, circuit, 6-7
- precision gain block:
  - circuit, 6-6
  - gain of -10, circuit, 6-10
  - gain of +1, circuit, 6-11
  - gain of +10, circuit, 6-9
  - gain of +11, circuit, 6-10
  - high CMR, 6-6
  - no external components, 6-9
- AD629:
  - for current sense (shunt) transducer, 6-23
  - difference amplifier, 1-5, 1-8, 6-16
    - high common-mode range, 6-12
    - high common-mode voltage, 6-17
  - high voltage measurement, 6-2
    - circuit, 6-2
  - for level sensor transducer, 6-23
  - monolithic difference amplifier, 2-1
  - for thermistor transducer, 6-23
  - unity-gain difference amplifier, 4-8
    - CMR vs. frequency, 4-9
    - connection diagram, 4-9
- AD822, unity-gain inverter, 6-20
- AD8130:
  - high frequency differential receiver/amplifier:
    - block diagram, 4-9
    - CMR vs. frequency, 4-9, 4-10
    - frequency response vs. supply voltage, 4-10
  - summing circuit:
    - frequency response, 6-16
    - performance photo, 6-16
- AD8200 family, current sensing difference amplifier, 4-2
- AD8202:
  - for current sense (shunt) transducer, 6-23
  - current sensing difference amplifier:
    - connection diagram, 4-2
    - simplified schematic, 4-2
    - two-stage system architecture, 4-3
  - high-side current measurement, 6-18
- AD8203:
  - current sensing difference amplifier:
    - gain of 14, 4-2
    - two-stage system architecture, 4-3
- AD8205:
  - for current sense (shunt) transducer, 6-23
  - current sensing difference amplifier, gain of 50, 4-2
  - difference amplifier:
    - single-supply, 4-3, 4-4
      - CMRR, 4-3
      - simplified schematic, 4-3
- AD8206, difference amplifier, gain and power consumption, 4-4
- AD8210:
  - current shunt amplifier, high common-mode input, 4-1
- difference amplifier:
  - CMRR vs. frequency and temperature, 4-5
  - current shunt monitor IC, block diagram, 4-4
  - motor control application, 6-19
- AD8220:
  - CMRR vs. frequency, 3-8
  - connection diagram, 3-8
  - for EKG monitor transducer, 6-23
  - FET input, gain-programmable, 3-8
  - JFET in-amp, input circuit, 5-7
  - JFET input circuit, 5-7
  - for photodiode sensor transducer, 6-23
- AD8221:
  - bridge circuit, 1-1
  - characteristics, 3-2 to 3-3
  - closed-loop gain vs. frequency, 3-3
  - CMRR, A-1
  - CMR vs. frequency, 3-3, A-3
  - CMRR specification, 3-3
  - dynamic response, A-2
  - for EKG monitor transducer, 6-23
  - filter circuits, 5-13, 5-16, 5-19
  - gain, A-2
  - gain bandwidth, 3-2
  - gain equation, A-5
  - for Hall effect magnetic transducer, 6-23
  - input, A-2
  - input circuit, 5-5
  - input current, A-1
  - for load cell transducer, 6-23
  - low noise device, 5-5
  - noise, A-1
  - output, A-2
  - for photodiode sensor transducer, 6-23
  - pinout, 3-3
  - power supply, A-2
  - reference input, A-2
  - for RTD transducer, 6-23
  - simplified schematic, 3-2
  - specifications, A-1
    - table, A-1 to A-2
  - in strain gage, high CMRR, 6-5
  - temperature range, A-2
  - for thermistor transducer, 6-23
  - for thermocouple transducer, 6-23
  - voltage offset, A-1
- AD8222:
  - dual in-amp:
    - connection diagram, 3-3
    - differential output performance, 3-3
  - for EKG monitor transducer, 6-23
  - for Hall effect magnetic transducer, 6-23
  - input circuit, 5-5
  - for load cell transducer, 6-23
  - for photodiode sensor transducer, 6-23
  - for thermocouple transducer, 6-23
  - true differential output in-amp, 6-1

- AD8225:
    - for EKG monitor transducer, 6-23
    - input circuit, 5-5
    - for level sensor transducer, 6-23
    - for load cell transducer, 6-23
    - monolithic, 3-16, 5-11
      - CMR vs. frequency, 3-16
      - gain nonlinearity, 3-16
      - simplified schematic, 3-16
    - RFI filter circuit, 5-16
    - for RTD transducer, 6-23
    - for thermistor transducer, 6-23
  - AD8230:
    - auto-zeroing, 3-8 to 3-12
      - CMR, 3-12
      - connection diagram, 3-8
      - gain setting, 3-12
      - gain vs. frequency, 3-12
      - internal workings, 3-9 to 3-12
      - signal sampling rate, 3-9
    - for Hall effect magnetic transducer, 6-23
    - input circuit, 5-6
    - for load cell transducer, 6-23
    - for RTD transducer, 6-23
    - for thermocouple transducer, 6-23
    - zero-drift, input circuitry, 5-6
  - AD8250:
    - gain-programmable, 3-20
      - data acquisition, 3-20
      - medical applications, 3-20
      - schematic, 3-20
    - for Hall effect magnetic transducer, 6-23
    - input circuit, 5-7
    - for RTD transducer, 6-23
  - AD8251:
    - gain-programmable, 3-20
      - data acquisition, 3-20
      - medical applications, 3-20
      - schematic, 3-20
    - for Hall effect magnetic transducer, 6-23
    - for RTD transducer, 6-23
  - AD8553:
    - auto-zeroing:
      - connection diagram, 3-13
      - current-mode, 3-12, 3-13
      - schematic, 3-13
    - chopper, 3-13
    - for EKG monitor transducer, 6-23
    - for level sensor transducer, 6-23
    - precision current source:
      - circuit, 6-3
      - integrator, 6-3
      - low frequency differential output, 6-3
    - zero-drift, input circuit, 5-7
  - AD8555:
    - auto-zeroing/chopper, 3-13
      - closed-loop gain vs. frequency, 3-15
      - CMRR vs. frequency, 3-15
      - schematic, 3-14
    - for load cell transducer, 6-23
    - for photodiode sensor transducer, 6-23
    - for RTD transducer, 6-23
    - RFI filter circuit, 5-17
    - sensor amplifier, 5-17
    - zero-drift:
      - input circuit, 5-8
      - sensor applications, 5-8
    - zero-drift, sensor signal amplifier, 3-13 to 3-15
      - connection diagram, 3-13
  - AD8556:
    - for load cell transducer, 6-23
    - on-chip EMI/RFI filter:
      - block diagram, 5-17
      - common-mode RFI/EMI, test circuit, 5-18
      - dc input offset values, 5-18
      - dc offset shift, 5-18
      - differential-mode EMI/RFI, test circuit, 5-18
    - for RTD transducer, 6-23
    - input circuit, 5-8
    - sensor applications, 5-8
    - zero-drift sensor signal amplifier, 3-13
      - block diagram, 3-15
      - EMI/RFI filters, 3-15
  - ADC:
    - high level interface, 6-13, 6-14
    - interface circuit:
      - single-supply, 6-13-6-14
        - common-mode input, 6-14
        - SNR, 6-14
    - matching in-amp circuits, 7-1 to 7-8
    - recommended for use with in-amps, tables, 7-2 to 7-6
    - requirements, calculation, 7-1
    - system resolution vs. converter resolution and preamp gain, table, 7-1
  - ADuC812, 12-bit ADC, embedded microcontroller, 6-26
  - AMP03:
    - differential amplifier, 7-8
    - monolithic unity-gain difference amplifier:
      - closed-loop gain vs. frequency, 4-5
      - CMRR vs. frequency, 4-5
      - functional block diagram, 4-5
      - high CMRR vs. frequency and temperature, 4-5
      - small signal pulse response, 4-6
  - Auto-zeroing in-amp, 3-8 to 3-15
- B**
- Bandwidth, 1-8, 1-9
  - Bessel filter, values, 5-22
  - Bipolar bridge, low dropout, driver, 6-20
  - Bridge:
    - applications, 6-19, 6-20
    - using ac excitation, 6-5
  - Bridge circuit, 5-13
  - Butterworth filter, values, 5-22

## C

- Cable, shielded, 6-24
- Cable termination, 5-5
- CCD imaging, 7-7
  - imaging equipment, 1-6
- Chebyshev filter, values, 5-22
- Chopper in-amp, 3-13
- Circuit:
  - bridge:
    - 3-op amp CMR, 1-4
    - 3-op amp in-amp, CMR, 1-4
  - bridge preamp, 1-1
- Classic bridge circuit, 6-19
- CMR, 1-1 to 1-5, 1-7, A-3
  - AC, A-3
    - in-amp, A-3
  - common-mode voltage, 1-2
  - dc values, 1-3
  - in-amp, 1-7, A-3
  - op amp vs. in-amp, 1-3, 1-4
  - signal amplification, 1-1 to 1-3
  - trimming, 5-23
- CMRR, A-3
  - circuit, degradation, 2-1
  - definition, 1-2
  - equation, 1-2
  - in-amp, A-3
  - increase proportional to gain, 2-3
- CMV, 1-2
- Common-mode filter:
  - conventional, 5-19
  - with X2Y capacitor, 5-19
- Common-mode gain, 1-2
- Common-mode rejection, see CMR
- Common-mode rejection ratio, see CMRR
- Common-mode RF choke, for in-amp RFI filter, 5-20
- Common-mode voltage, 1-1, 1-2
  - in op amp circuit, 1-3
- Composite in-amp:
  - circuit, 6-4
    - CMR, 6-4
    - CMR at gain of 2, 6-4
    - CMR at gain of 100, 6-4
- Composite in-amp circuit:
  - high frequency CMR, 6-3 to 6-5
  - at various gains, circuits, 6-4
- Controlling, 1-6
  - in-amp, 1-6
- Conversion, differential to single-ended, 1-9
- Current sense transducer, characteristics, table, 6-23
- Current sensor interface, 6-24, 6-25
- Current transmitter, circuit, 6-12

## D

- Data acquisition, 1-5
- DC return path, diagrams, 5-2
- Decoupling, 5-1
- Difference amp:

- high voltage measurement, 6-1 to 6-5
- monolithic, 4-1 to 4-10
- table, 4-1

- Difference amplifier, 6-16
  - applications circuit, 6-1 to 6-26
  - block diagram, 1-5
  - circuit, 1-5
  - IC, 1-5
  - nonlinearity vs. voltage, 6-17
  - selection table, B-1
  - use, 1-5, 1-6

- Differential input circuit:
  - single-pole low-pass filter, 6-6
  - 2-pole low-pass filter, 6-8

- Differential output, circuit, 6-1

- Differential signal voltage, 1-1

- Digi-Key part # PS1H102GND, 5-14

- Diode, leakage, 5-9

## E

- ECG:
  - monitor transducer, characteristics, table, 6-23
  - schematic, 6-22

- EKG, see ECG

- Electrostatic discharge, see ESD

- Error, calculations, 5-12

- ESD:

- input protection, 5-5

- overload protection, 5-7

- External CMR, performance, 5-23

- External gain resistor, thermal gradient, error source, 5-11

- External protection diodes, 5-8

## F

- Fast Schottky barrier rectifier, 5-9

- Filter:

- common-mode, using X2Y capacitors, 5-19

- common-mode bandwidth, 5-14

- component values, corner frequencies, tables, 6-9

- differential:

- bandwidths, 5-13, 5-14

- basic circuit, 5-13

- low-pass, to improve SNR, 5-21, 5-22

- RFI, 5-13, 5-16 to 5-18

- 2-pole low-pass, frequency response, 6-8

- Float sensor transducer, characteristics, table, 6-23

## G

- Gain, 1-8

- buffered subtractor circuit, 2-2

- Gain drift, minimizing, 5-9

- Gain error, A-5, A-6

- input signal level differences, 5-10

- Gain range, A-5

- Gain resistor:

- error source, 5-11

- required value, table, 3-18

- Gain vs. temperature, A-6

## H

Hall effect magnetic transducer, characteristics, table, 6-23

High frequency differential receiver/amplifier, 4-9, 4-10

High-side current sense, 6-19

High speed data acquisition, 7-7

High speed signal conditioning, 1-6

High voltage:

measurement:

methods, circuits, 6-1

new system:

circuit, 6-2

cross plot, 6-2

nonlinearity error, 6-2

performance, 6-2

High voltage monitor, circuit, 6-16

## I

Impedance, high input, 1-8

In-amp:

2-op amp, 2-4 to 2-6

3-op amp, 2-2 to 2-4

CMR trim circuit, 5-23

feedback resistors, design, 5-10

3-op amp bridge circuit, CMR, 1-4

ac-coupled circuit, 5-2

ac input coupling, recommended component values,  
table, 5-4

advantages, 1-7

application, 5-1 to 5-23

applications circuit, 6-1 to 6-26

auto-zeroing, 3-8 to 3-15

basics, 1-1 to 1-9

bipolar input stages, higher CMR, 2-3

buffers ADC, dc correction, 7-7

characteristics, 1-7 to 1-9

circuit:

CMR, 6-4

matched to ADCs, 7-1 to 7-8

CMR, 1-7

composite, circuit, 6-4

dc accuracy, design issues, 5-9, 5-10

definition, 1-1

differential output circuit, 6-1

differential vs. common-mode input signals,  
circuit, 1-6

dual-supply operation, 5-1

external protection diodes, 5-9

external resistor, 1-7

fixed gain, dc performance, 5-11

functional block diagram, 1-6

high performance, 3-2 to 3-5

high quality, definition, 1-7 to 1-9

high speed, high performance circuit, 7-8

input characteristics, 1-2

input ground return, 5-2, 5-3

input protection basics, 5-5 to 5-9

internal characteristics, 2-1 to 2-6

low noise, 1-8

low power, single-supply, 3-19, 3-20

low power, output buffering, 6-25

micropower, RFI circuit, 5-15

monolithic, 3-1 to 3-20

advantages, 3-1

design, 3-2 to 3-8

for single-supply operation, 3-17, 3-18

monolithic difference, 4-1 to 4-10

multiplexed, 7-7

operating gains, table, 2-4

output, 1-7

buffer, for low impedance, 5-3

power supply bypassing, diagram, 5-1

rail-to-rail output swing, diagram, 5-1

reference input:

CMR error, 5-4

driving, 5-4

RFI rejection measurement, circuit, 5-21

selection table, B-1, B-2

series protection resistor values, table, 5-8

single-supply:

input and output swing, 5-1

key specifications, A-6

single-supply operation, 5-1

specifications, A-1 to A-6

stability, 5-1

summary, table, 3-1

transducer interface application, 6-21

uses, 1-5, 1-6

vs. op amp, 3-1

differences, 1-1 to 1-4

Wheatstone bridge, 6-19

In-amp circuit, input buffers, CMR, 1-4

Input and output voltage swing, A-6

Input bias, 1-8, A-4

Input noise, 5-12

International rectifier SD101 series, 5-9

## J

J-type thermocouple, 6-26

Johanson Dielectrics, X2Y capacitor, 5-19

Johnson noise, 5-5

## L

Level sensor transducer, characteristics, table, 6-23

Linearity, best straight line method, A-6

Load cell transducer, characteristics, table, 6-23

Low-pass filter:

4-pole:

recommended component values, table, 5-22  
values, 5-22

## M

Medical ECG monitor circuit, 6-22

Medical instrumentation, 1-6

Micropower in-amp, RFI circuit, 5-15

Monitoring, 1-6

Monolithic difference in-amp, 4-1 to 4-10  
applications, 4-1

## N

- Noise, 1-9
  - ground, 6-12, 6-13
  - low, 1-8
- Noise error, 5-12
- Nonlinearity, A-6
  - low, 1-8
- Nyquist criteria, 7-8

## O

- Offset current, A-4
- Offset current error, 1-8
- Offset error, 5-12
- Op amp:
  - CMR, 1-3
  - in-amp difference amplifier circuit, block diagram, 2-1
  - subtractor, as in-amp, 2-1
  - vs. in-amp, 1-1 to 1-5
- OP27, transfer function, 6-13
- OP177, integrator, 6-16
- Operating voltage range, A-4
- Output buffer, for low power in-amp, 6-25
- Output swing, 1-9
- Overload:
  - steady state, 5-5
  - transient, 5-5

## P

- Photodiode sensor transducer, characteristics, table, 6-23
- PID loop, integrator, 6-3
- Power, 1-9
- Power controlling, 1-6
- Power supply bypassing, 5-1
- Power supply decoupling, 5-1
- Power vs. bandwidth, 1-9
- Precision 48 V bus monitor:
  - circuit, 6-17
  - output vs. input linearity, 6-18
  - remote voltage measurement, circuit, 6-17
  - temperature drift, 6-18
- Precision voltage-to-current converter, 6-24, 6-25
- Proportional integral differential, see: PID
- Pulse Engineering, common-mode choke, 5-20

## Q

- Quiescent supply current, A-4, A-5

## R

- Rail-to-rail input, 1-9
- RC coupling component, selecting and matching, 5-3, 5-4
- Receiver circuit, 6-26
- Referred to input, see RTI
- Referred to output, see RTO
- Remote load sensing, circuit, 6-24
- Resistance temperature detector transducer,
  - characteristics, table, 6-23

## Resistor values:

- for in-amps, table, 5-8
- for various gains, table, 4-7

## RFI:

- circuit, diagram, 5-13
- input filter component values, selection, 5-14
- rectification error, reducing, 5-12 to 5-20

## RFI attenuation, X2Y vs. conventional common-mode filter, 5-19

- RFI filter, 5-16 to 5-18
  - bandwidths, 5-13
  - design, 5-12 to 5-20
  - for in-amp, 5-17

## RFI rectification:

- error prevention, filter circuit, 5-13
- error reduction, in-amp circuit, 5-12

## RFI suppression, using common-mode RF choke, 5-20

- RFI testing, 5-21
- RTI, in-amp, A-4
- RTI error, 5-11, 5-12
- RTO, in-amp, A-4
- RTO error, 5-11, 5-12

## S

- Schottky diode, 5-8, 5-9
- Settling time, 5-23
  - in-amp, A-5
- Signal-to-noise ratio, see SNR
- Signal voltage, in op amp circuit, 1-3
- Silicon diode, 5-8
- Single-supply bridge configuration transducer,
  - characteristics, table, 6-23
- Single-supply receiver, circuit, 6-26
- Slew rate, in-amp, 1-9
- Software programming, in-amp, 1-6
- Specifications, in-amp, A-3
- SSM2019, audio preamplifier, 6-26
- SSM2141, differential line receiver, 6-26
- SSM2143, differential line receiver, 6-26
- Strain gage, measurement, with AC excitation, 6-5
- Strain gage bridge transducer, characteristics, table, 6-23
- Subtractor amp, 4-1 to 4-10
- Subtractor circuit:
  - buffered, diagram, 2-2
  - input buffering, diagram, 2-1
- Summing amplifier:
  - circuit, 6-15
  - high input impedance, 6-15
  - high speed noninverting, 6-15 to 6-17
- Switch:
  - high-side, 6-19
  - low-side, 6-18

## **T**

- Thermal EMF, 5-10
- Thermal gradient, error source, 5-11
- Thermal sensor transducer, characteristics, table, 6-23
- Thermistor transducer, characteristics, table, 6-23
- Thermocouple amplifier, single-supply in-amp, 6-26
- Thermocouple effect, 5-10
- Thermocouple transducer, characteristics, table, 6-23
- 3-op amp in-amp, 2-2, 2-3
  - circuit, 2-2
  - CMR trim circuit, 5-23
  - design considerations, 2-3, 2-4
  - feedback resistors, gain error, circuit, 5-10
  - reduced CMV range, circuit, 2-3
- Total error, A-4
- Total noise, 5-12
- Total offset error, A-4
- Transducer, characteristics, table, 6-23
- Transfer function, nonlinearity, A-6
- Transformer-coupled input, dc return path, diagram, 5-2
- Transient, overload protection, 5-9
- 2-op amp in-amp:
  - architecture, 2-5
  - circuit, 2-4
  - common-mode design, 2-5, 2-6
  - limitations:
    - high CMR, 2-6
    - output swing, 2-5
  - transfer function, 2-4

## **V**

- Video applications, 1-6
- Voltage:
  - common mode, 1-1
  - differential signal, 1-1
  - offset, 1-7
- Voltage drift, lowest offset, design, 5-9, 5-10
- Voltage offset, A-3, A-4
- Voltage-to-current converter, 6-25

## **W**

- Weight measurement transducer, characteristics, table, 6-23

## **X**

- X2Y capacitor, 5-19
  - electrostatic model, 5-19

## **Z**

- Zener diode, 6-17
- Zero-drift in-amp, 7-5, 7-6