
In-Amp Input RFI Protection

PROTECTING IN-AMPS AGAINST RFI

Real-world applications must deal with an ever increasing amount of radio frequency interference (RFI). Of particular concern are situations in which signal transmission lines are long and signal strength is low. This is the classic application for an in-amp, since its inherent common-mode rejection allows the device to extract weak differential signals riding on strong common-mode noise and interference. One potential problem that is frequently overlooked, however, is that of *radio frequency rectification* inside the in-amp. When strong RF interference is present, it may become rectified by the internal junctions of the IC and then appear as a dc output offset error.

Common-mode signals present at an in-amp's input are normally greatly reduced by the amplifier's common-mode rejection. Unfortunately, RF rectification occurs because even the best in-amps have virtually no common-mode rejection at frequencies above 20 kHz. A strong RF signal may become rectified by the amplifier's input stage and then appear as a dc offset error. Once rectified, no amount of low-pass filtering at the in-amp output will remove the error. If the RF interference is of an intermittent nature, this can lead to measurement errors that go undetected.

COMMON-MODE (CM) AND DIFFERENTIAL-MODE (DM) RC INPUT FILTERS

A general-purpose approach to proper filtering for device level application of in-amps is shown in Figure 1. In this circuit the in-amp could be any one of a number of devices. The relatively complex balanced RC filter preceding the in-amp performs all of the high frequency filtering. The in-amp would be programmed for the gain required in the application, via its gain-set resistance (not shown).

Within the filter, note that fully balanced filtering is provided for both CM (R1-C1 and R2-C2) as well as differential mode (DM) signals (R1+R2, and C3 || the series connection of C1-C2). If R1-R2 and C1-C2 aren't well matched, some of the input common-mode signal at V_{IN} will be converted to a differential mode signal at the in-amp inputs. For this reason, C1 and C2 should be matched to within at least 5% of each other. Also, R1 and R2 should be 1% metal film resistors, so as to aid this matching.

It is assumed that the source resistances seen at the V_{IN} terminals are low with respect to R1-R2, and matched. In this type of filter, C3 should be chosen at least ten times larger than C1 or C2 ($C3 \geq 10C1, 10C2$), in order to suppress spurious differential signals due to CM-to-DM conversion resulting from mismatch of the R1-C1 and R2-C2 time constants.

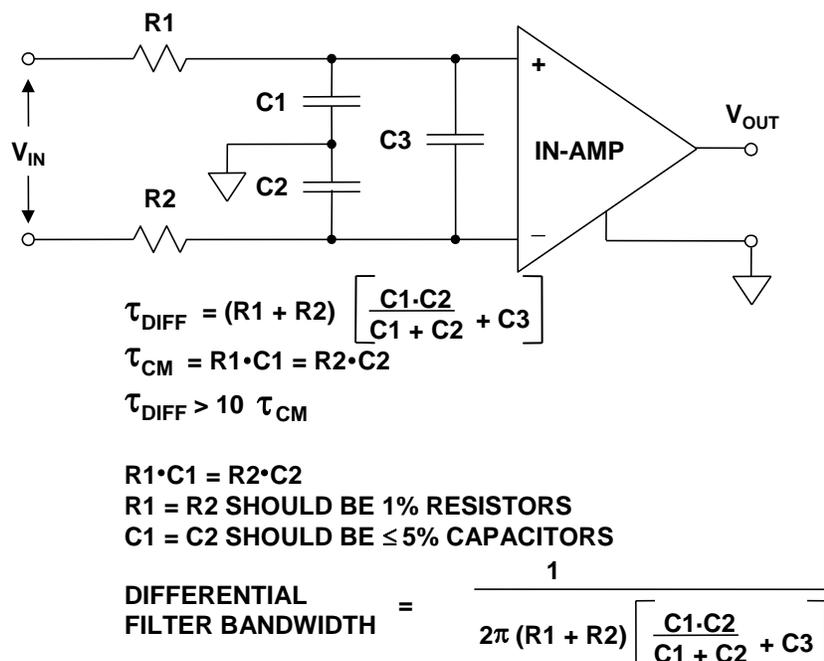


Figure 1: A General-Purpose Common-Mode/Differential-Mode RC EMI/RFI Filter for In-Amps

The resulting CM filter bandwidth is $1/2\pi R1 \cdot C1$, and the DM filter bandwidth is approximately $1/4\pi R1 \cdot C3$, assuming that $C3 \gg C1$.

The overall DM filter bandwidth should be at least 100 times the input signal bandwidth. Physically, the filter components should be symmetrically mounted on a PC board with a large area ground plane and placed close to the in-amp inputs for optimum performance.

Figure 2 shows a family of these filters, as suited to a range of different in-amps. The RC components should be tailored to the different in-amp devices, as per the table. These filter components are selected for a reasonable balance of low EMI/RFI sensitivity and a low increase in noise (vis-à-vis that of the related in-amp, without the filter).

To test the EMI/RFI sensitivity of the configuration, a 1 V p-p CM signal can be applied to the input resistors, as noted. With a typically used in-amp such as the [AD620](#) working at a gain of 1000, the maximum RTI input offset voltage shift observed was 1.5 μ V over the 20 MHz range. In the AD620 filter example, the differential bandwidth is about 400 Hz.

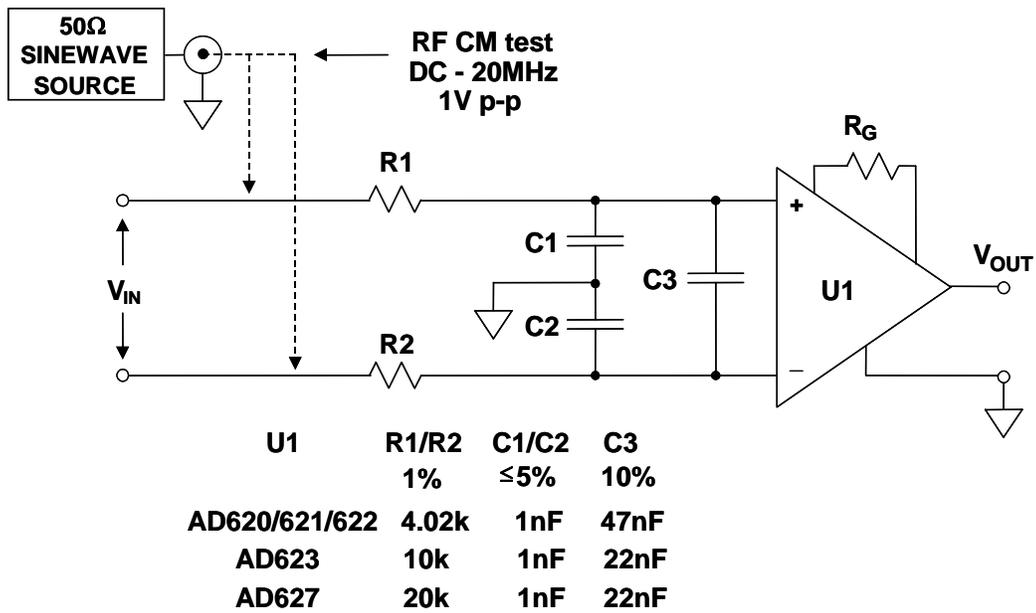


Figure 2: Flexible Common-Mode and Differential-Mode RC EMI/RFI Filters are useful with the [AD620](#) Series, the [AD623](#), [AD627](#), and other In-Amps


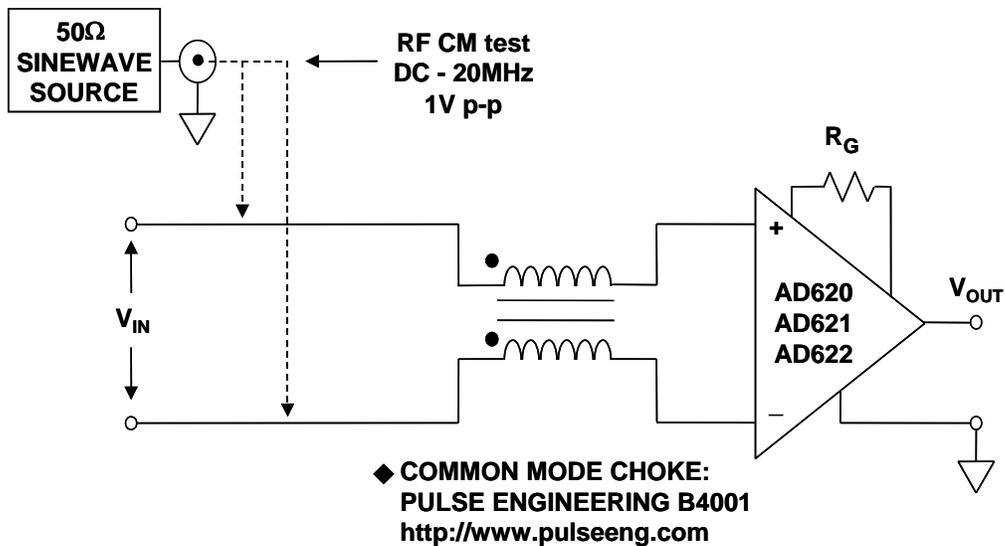


Figure 3: For Simplicity as well as Lowest Noise EMI/RFI Filter Operation, a Common-Mode Choke is useful with the AD620 Series In-Amp Devices

In addition to being a low component count approach, choke-based filters offer low noise, by dispensing with the resistances. Selecting the proper common-mode choke is critical, however. The choke used in the circuit of Figure 3 above is a [Pulse Engineering](#) B4001. The maximum RTI offset shift measured from dc to 20 MHz at $G = 1000$ was $4.5 \mu\text{V}$. Either an off-the-shelf choke such as the B4001 can be used for this filter, or, alternately one can be constructed. Since balance of the windings is important, bifilar wire is suggested. The core material must of course operate over the expected frequency band. Note that, unlike the Figure 1 family of RC filters, a choke-only filter offers no differential filtration. Differential mode filtering can be optionally added, with a second stage following the choke, by adding the R1-C3-R2 connections of Figure 1.

COMMON-MODE FILTERS USING X2Y® CAPACITORS

Figure 4 shows the connection diagram for an [X2Y](#) capacitor. These are very small, three terminal devices with four external connections—A, B, G1, and G2.

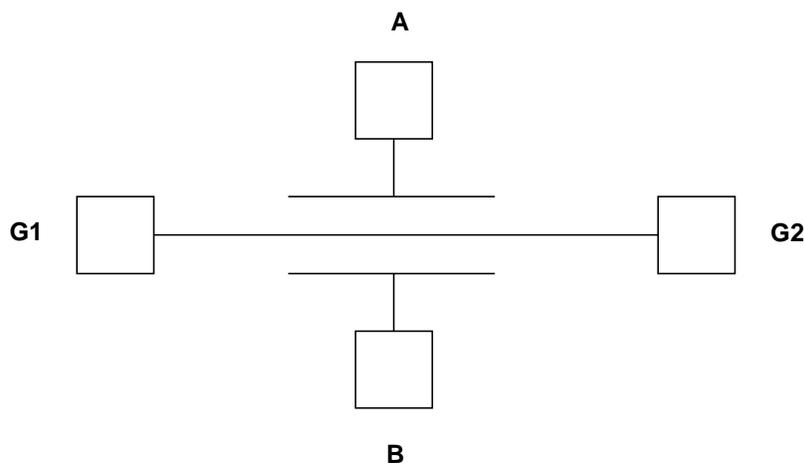

See www.x2y.com for manufactures of x2y capacitors

Figure 4: X2Y® Capacitor Electrostatic Model

The G1 and G2 terminals connect internally within the device. The internal plate structure of the X2Y capacitor forms an integrated circuit with very interesting properties. Electrostatically, the three electrical nodes form two capacitors that share the G1 and G2 terminals. The manufacturing process automatically matches both capacitors very closely. In addition, the X2Y structure includes an effective autotransformer/common-mode choke. As a result, when these devices are used for common-mode filters, they provide greater attenuation of common-mode signals above the filter's corner frequency than a comparable RC filter. This usually allows the omission of the capacitor C3, with subsequent savings in cost and board space.

Figure 5A illustrates a conventional RC common-mode filter, while Figure 5B shows a common-mode filter circuit using an X2Y device. Figure 6 is a graph contrasting the RF attenuation provided by these two filters.

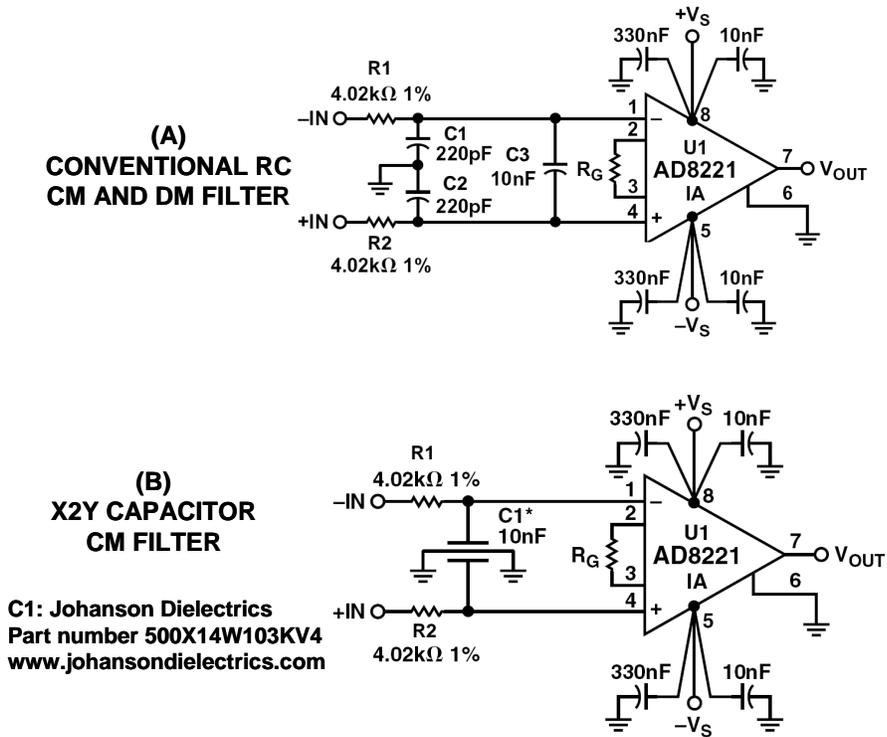


Figure 5: Conventional RC and X2Y CM Filters

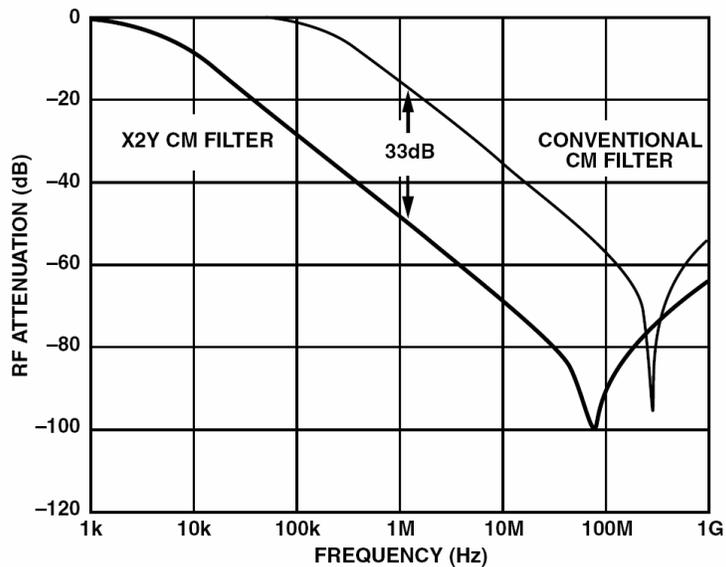


Figure 6: RF Attenuation for X2Y vs. Conventional RC Common-Mode Filter

REFERENCES

1. Hank Zumbahlen, *Basic Linear Design*, Analog Devices, 2006, ISBN: 0-915550-28-1. Also available as [*Linear Circuit Design Handbook*](#), Elsevier-Newnes, 2008, ISBN-10: 0750687037, ISBN-13: 978-0750687034. Chapter 2.
2. Walter G. Jung, [*Op Amp Applications*](#), Analog Devices, 2002, ISBN 0-916550-26-5, Also available as [*Op Amp Applications Handbook*](#), Elsevier/Newnes, 2005, ISBN 0-7506-7844-5. Chapter 2.
3. Charles Kitchin and Lew Counts, [*A Designer's Guide to Instrumentation Amplifiers, 3rd Edition*](#), Analog Devices, 2006.

Copyright 2009, Analog Devices, Inc. All rights reserved. Analog Devices assumes no responsibility for customer product design or the use or application of customers' products or for any infringements of patents or rights of others which may result from Analog Devices assistance. All trademarks and logos are property of their respective holders. Information furnished by Analog Devices applications and development tools engineers is believed to be accurate and reliable, however no responsibility is assumed by Analog Devices regarding technical accuracy and topicality of the content provided in Analog Devices Tutorials.