

Digitally Programmed State Variable Filter

by Hank Zumbahlen,
Analog Devices, Inc.

IN THIS TUTORIAL

The parameters of digitally programmed state variable filters can be adjusted individually. These filters are one of a set of discrete circuits described in a series of mini tutorials.

One of the attractive features of the state variable filter is that the parameters (gain, cutoff frequency, and Q) can be individually adjusted. This attribute can be exploited to allow digital control of these parameters.

To start, the state variable filter is reconfigured slightly. The resistor divider that determines Q is changed to an inverting configuration. The new filter schematic is shown in Figure 1. Then the resistors R1, R2, R3 & R4 (of Figure 1) are replaced by

CMOS multiplying DACs. Note that R5 is implemented as the feedback resistor implemented in the DAC. The schematic of this circuit is shown in Figure 2.

This example uses the AD7528 and the AD825. The AD7528 is an 8-bit dual multiplying digital-to-analog converter (MDAC). The AD825 is a high speed FET input op amp. Using these components, the frequency range can be varied from around 550 Hz to around 150 kHz (see Figure 3). The Q can be varied from approximately 0.5 to over 12.5 (see Figure 4). The gain of circuit can be varied from 0 dB to -48 dB (see Figure 5).

The operation of the DACs in controlling the parameters can be best thought of as the DACs changing the effective resistance of the resistors. This relationship is

$$DAC \text{ Equivalent Resistance} = \frac{256 \times DAC}{Resistance} \quad (1)$$

This, in effect, varies the resistance from 11 kΩ to 2.8 MΩ for the AD7528.

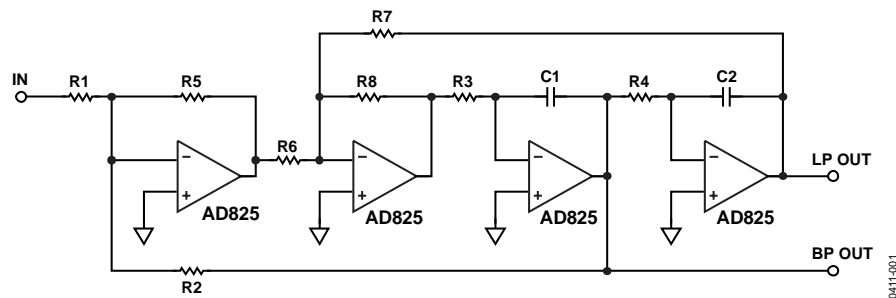


Figure 1. Redrawn State Variable Filter

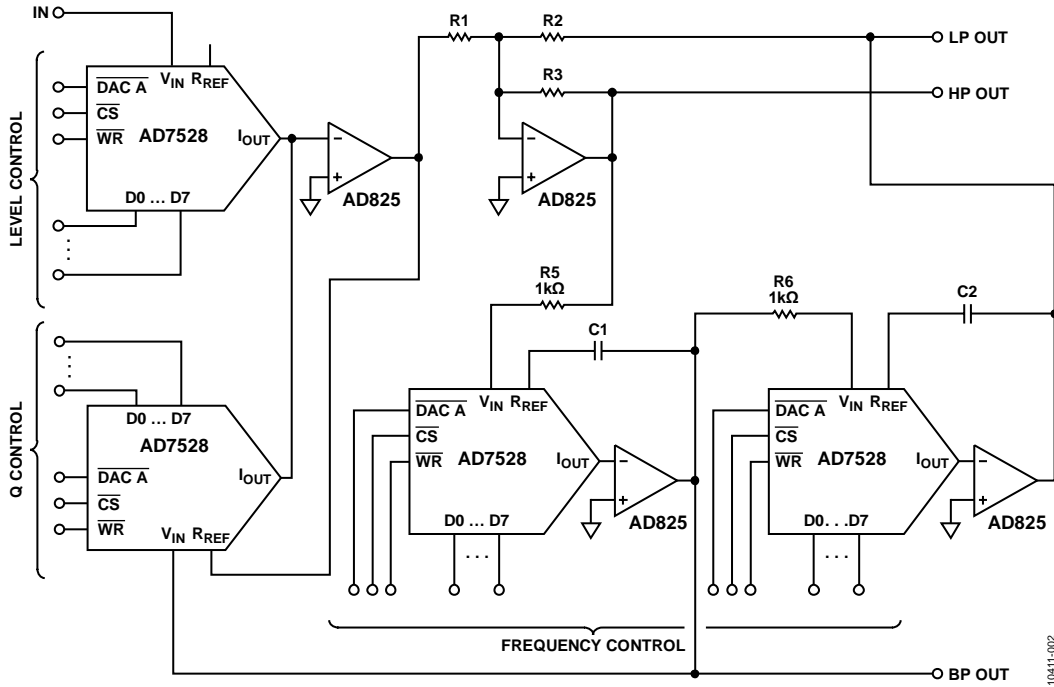


Figure 2. Digitally Controlled State Variable Filter

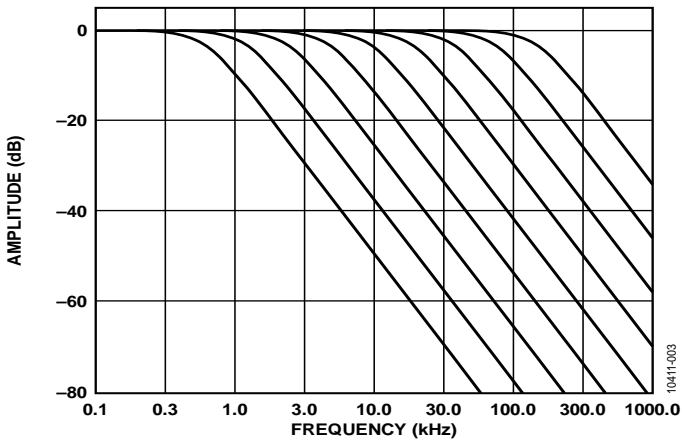


Figure 3. Frequency Response vs. DAC Control Word

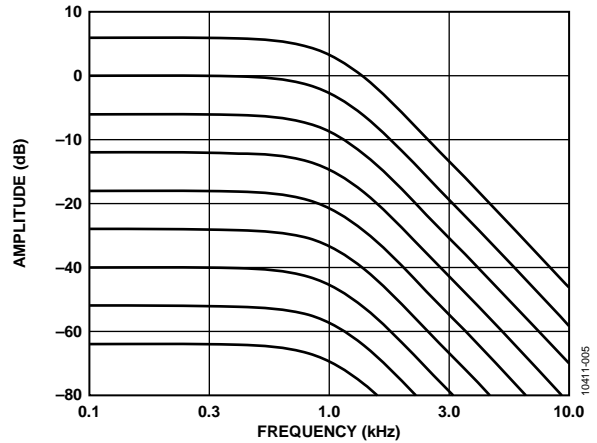


Figure 5. Gain Variation vs. DAC Control Word

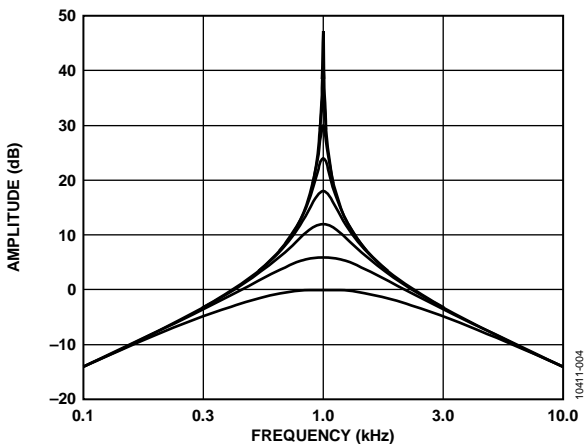


Figure 4. Q Variation vs. DAC Control Word

One limitation of this design is that the frequency is dependent on the ladder resistance of the DAC. This particular parameter is not controlled. DACs are trimmed so that the ratios of the resistors, not their absolute values, are controlled. In the case of the AD7528, the typical value is 11 kΩ. It is specified as 8 kΩ minimum and 15 kΩ maximum. A simple modification of the circuit can eliminate this issue. The cost is two more op amps (see Figure 6). In this case, the effective resistor value is set by the fixed resistors rather than the DAC's resistance. Since there are two integrators, the extra inversions caused by the added op amps cancel.

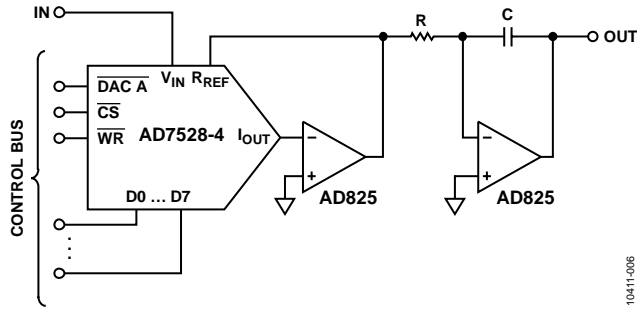


Figure 6. Improved Digitally Variable Integrator

Note that multiplying DACs could be replaced by analog multipliers. In this case, the control would obviously be an analog rather than a digital signal. One could just as easily have

used a digital pot in place of the MDACs. The difference is that instead of increasing the effective resistance, the value of the pot would be the maximum resistance.

REFERENCES

Zumbahlen, Hank. *Linear Circuit Design Handbook*. Elsevier. 2008. ISBN: 978-7506-8703-4.

REVISION HISTORY

4/12—Revision 0: Initial Version