

### Devices Connected/Referenced

AD7192	4.8 kHz, Ultralow Noise 24-Bit $\Sigma$ - $\Delta$ ADC with PGA
ADP3303	5 V Low Dropout Linear Regulator
ADP3303	3.3 V Low Dropout Linear Regulator


## Precision Weigh Scale Design Using the AD7192 24-Bit Sigma-Delta ADC with Internal PGA

### CIRCUIT FUNCTION AND BENEFITS

This circuit is a weigh scale system that uses the AD7192. The AD7192 is an ultralow noise, low drift, 24-bit  $\Sigma$ - $\Delta$  converter that includes a PGA. Therefore, the device simplifies the weigh scale design because most of the system building blocks are included on chip. Since the part operates with an output data rate from 4.7 Hz to 4.8 kHz and maintains good performance over the complete output data rate range, this allows the part to be used in weigh scale systems that operate at low speeds along with higher speed weigh scale systems, such as hopper scales.
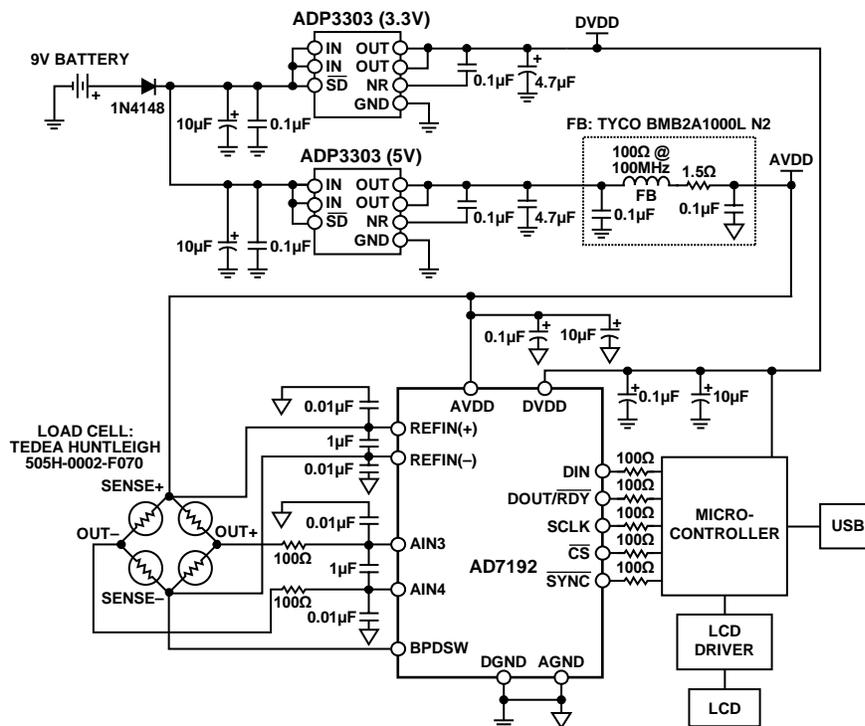
### CIRCUIT DESCRIPTION

Since the AD7192 provides an integrated solution for weigh scales, it interfaces directly to the load cell. The only external components required are some filters on the analog inputs and capacitors on the reference pins for EMC purposes. The low level signal from the load cell is amplified by the AD7192's PGA. The PGA is programmed to operate with a gain of 128. The conversions from the AD7192 are then sent to the microcontroller where the digital information is converted to weight and displayed on the LCD.



Rev. A

"Circuits from the Lab" from Analog Devices have been designed and built by Analog Devices engineers. Standard engineering practices have been employed in the design and construction of each circuit, and their function and performance have been tested and verified in a lab environment at room temperature. However, you are solely responsible for testing the circuit and determining its suitability and applicability for your use and application. Accordingly, in no event shall Analog Devices be liable for direct, indirect, special, incidental, consequential or punitive damages due to any cause whatsoever connected to the use of any "Circuit from the Lab". (Continued on last page)

Figure 1. Weigh Scale System Using the AD7192 (Simplified Schematic: All Connections Not Shown)

Figure 2 shows the actual test setup. A 6-wire load cell is used, as this gives the optimum system performance. A 6-wire load cell has two sense pins, in addition to the excitation, ground, and two output connections. These sense pins are connected to the high side and low side of the Wheatstone bridge. The voltage developed across the bridge can, therefore, be accurately measured. In addition, the AD7192 has differential analog inputs, and it accepts a differential reference. Connection of the load cell differential SENSE lines to the AD7192 reference inputs creates a ratiometric configuration that is immune to low frequency changes in the power supply excitation voltage. With a 4-wire load cell, the sense pins are not present, and the ADC reference pins are connected to the excitation voltage and ground. With this arrangement, the system is not completely ratiometric because there will be a voltage drop between the excitation voltage and SENSE+ due to wire resistance. There will also be a voltage drop due to wire resistance on the low side.

The AD7192 has separate analog and digital power supplies. The digital power supply is independent of the analog power supply and can equal any voltage between 2.7 V and 5.25 V. The microcontroller uses a 3.3 V power supply. Therefore, DVDD is also powered from 3.3 V. This simplifies the interface between the ADC and the microcontroller because no external level shifting is required.

There are several methods to power the weigh scale system. It can be powered from the mains power supply or battery powered (as shown in Figure 1). A 5 V low noise regulator is used to ensure that the AD7192 and the load cell receive a low

Figure 2. Weigh Scale System Using the AD7192

noise supply. An ADP3303 (5 V) low noise regulator is used to generate the 5 V supply. The filter network shown inside the dotted box ensures a low noise AVDD for the system. In addition, noise reduction capacitors are placed on the regulator output as recommended in the ADP3303 (5 V) data sheet. To optimize the EMC performance, the regulator output is filtered before being supplied to the AD7192 and the load cell. The 3.3 V digital supply is generated using the ADP3303 (3.3 V). It is essential that low noise regulators are used to generate all the power supply voltages to the AD7192 and the load cell, as any noise on the power supply or ground planes will introduce noise into the system and degrade the circuit performance.

If a 2 kg load cell with a sensitivity of 2 mV/V is used, the full-scale signal from the load cell is 10 mV when the excitation voltage is 5 V. A load cell has an offset or TARE associated with it. This TARE can have a magnitude that is up to 50% of the load cell's full-scale output signal. The load cell also has a gain error, which can be up to ±20% of full scale. Some customers use a DAC to remove or null the TARE. When the AD7192 uses a 5 V reference, its analog input range is equal to ±40 mV when the gain is set to 128 and the part is configured for bipolar operation. The wide analog input range of the AD7192 relative to the load cell's full-scale signal (10 mV) is beneficial as it ensures that the offset and gain error of the load cell do not overload the ADC's front end.

The AD7192 has an rms noise of 11 nV when the output data rate is 4.7 Hz. The number of noise-free counts is equal to

$$\frac{10 \text{ mV}}{6.6 \times 11 \text{ nV}} = 137,740 \quad (1)$$

where the factor of 6.6 converts the rms voltage into a peak-to-peak voltage.

The resolution in grams is

$$\frac{2 \text{ kg}}{137,740} = 0.015 \text{ g} \quad (2)$$

The noise-free code resolution is equal to

$$\log_2(137,740) = \frac{\log_{10}(137,740)}{\log_{10}(2)} = 17 \text{ bits} \quad (3)$$

In practice, the load cell itself will introduce some noise. There will also be some drift due to time and temperature of the load cell along with the AD7192's drift. To determine the accuracy of the complete system, the weigh scale can be connected to the PC via the USB connector. Using LabView software, the performance of the weigh scale system can be evaluated. Figure 4 shows the measured output performance when a 1 kg weight is placed on the load cell and 500



conversions are gathered. The noise of the system is calculated by the software to be 14 nV and is 98 nV peak-to-peak. This equates to 102,000 noise-free counts or 16.6 bits of noise-free code resolution.

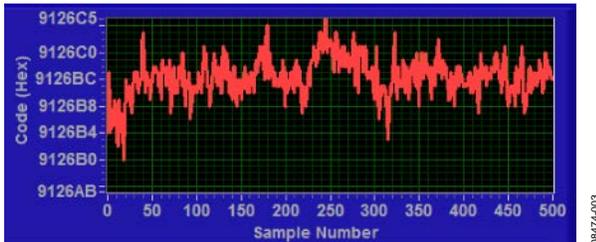


Figure 3. Measured Output Code for 500 Samples Showing the Effects of Noise

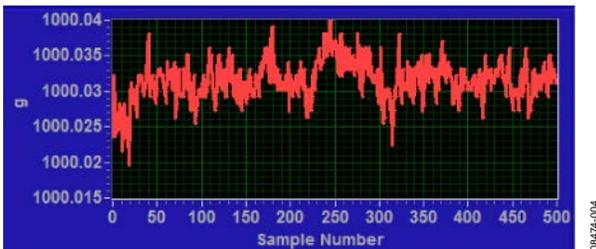


Figure 4. Measured Output Code for 500 Samples Showing the Effects of Noise

Figure 4 shows the performance in terms of weight. The variation in output is 0.02 grams over the 500 codes. So, the weigh scale system achieves an accuracy of 0.02 grams.

The plots show the actual conversions being read back from the [AD7192](#) when the load cell is attached. In practice, a digital post filter is used in a weigh scale system. The additional averaging that is performed in the post filter will further improve the number of noise-free counts at the expense of a reduced data rate.

## COMMON VARIATIONS

Note: All noise specifications in this section are given for a PGA gain of 128.

The [AD7192](#) is a high precision ADC for high-end weigh scales. Other suitable ADCs are the [AD7190](#) and [AD7191](#). The [AD7190](#) is pin-for-pin compatible with the [AD7192](#). However, its rms noise is slightly lower. The [AD7190](#) has an rms noise of 8.5 nV for an output data rate of 4.7 Hz while the [AD7192](#) has an rms noise of 11 nV at this output data rate. The [AD7191](#) is a pin programmable device. It has four output data rates and four gain settings. Due to its pin programmability and reduced feature set, it is an easy to use device. Its rms noise is the same as the [AD7192](#)'s rms noise.

For medium-end weigh scales, the [AD7799](#) is a suitable device. At an output data rate of 4.17 Hz, the [AD7799](#) has an rms noise of 27 nV.

Finally, for low-end weigh scales, the [AD7798](#), [AD7781](#), and [AD7780](#) are suitable devices. The [AD7798](#) has the same features set as the [AD7799](#). At 4.17 Hz, its rms noise is 40 nV. The [AD7780](#) and [AD7781](#) have one differential analog input and are pin programmable, allowing an output data rate of 10 Hz and 17.6 Hz and a gain of 1 or 128. The rms noise is 44 nV when the output data rate is 10 Hz.

As with any high accuracy circuit, proper layout, grounding, and decoupling techniques must be employed. See [Tutorial MT-031, Grounding Data Converters and Solving the Mystery of AGND and DGND](#) and [Tutorial MT-101, Decoupling Techniques](#) for more details.

## LEARN MORE

Kester, Walt. 1999. *Sensor Signal Conditioning*. Sections 2, 3, 4. Analog Devices.

MT-004 Tutorial, *The Good, the Bad, and the Ugly Aspects of ADC Input Noise—Is No Noise Good Noise?* Analog Devices.

MT-022 Tutorial, *ADC Architectures III: Sigma-Delta ADC Basics*, Analog Devices.

MT-023 Tutorial, *ADC Architectures IV: Sigma-Delta ADC Advanced Concepts and Applications*, Analog Devices.

MT-031 Tutorial, *Grounding Data Converters and Solving the Mystery of "AGND" and "DGND"*, Analog Devices.

MT-101 Tutorial, *Decoupling Techniques*, Analog Devices.

## Data Sheets and Evaluation Boards

[AD7190 Data Sheet](#)

[AD7191 Data Sheet](#)

[AD7192 Data Sheet](#)

[AD7192 Evaluation Board](#)

[AD7780 Data Sheet](#)

[AD7781 Data Sheet](#)

[AD7798 Data Sheet](#)

[AD7799 Data Sheet](#)

[ADP3303 Data Sheet](#)

**REVISION HISTORY**

7/13—Rev. 0 to Rev. A

Changes to Circuit Description Section .....3

9/09—Revision 0: Initial Version

(Continued from first page) "Circuits from the Lab" are intended only for use with Analog Devices products and are the intellectual property of Analog Devices or its licensors. While you may use the "Circuits from the Lab" in the design of your product, no other license is granted by implication or otherwise under any patents or other intellectual property by application or use of the "Circuits from the Lab". Information furnished by Analog Devices is believed to be accurate and reliable. However, "Circuits from the Lab" are supplied "as is" and without warranties of any kind, express, implied, or statutory including, but not limited to, any implied warranty of merchantability, noninfringement or fitness for a particular purpose and no responsibility is assumed by Analog Devices for their use, nor for any infringements of patents or other rights of third parties that may result from their use. Analog Devices reserves the right to change any "Circuits from the Lab" at any time without notice, but is under no obligation to do so. Trademarks and registered trademarks are the property of their respective owners.

©2009–2013 Analog Devices, Inc. All rights reserved. Trademarks and registered trademarks are the property of their respective owners.  
CN08474-0-7/13(A)



www.analog.com