

# design

# FAQs

## Driver Amplifiers For Analog-To-Digital Converters

Don Tuite  
Analog/Power Editor

FREQUENTLY ASKED QUESTIONS

ED ONLINE 20791

### What amplifiers are used to drive analog-to-digital converters (ADCs)?

Possibilities include single-ended and differential inputs and outputs, plus voltage feedback (VFB) or current feedback (CFB) in the control loop. Specialized amplifiers may provide level shifting, interstage isolation, single-ended to differential conversion, differential to single-ended conversion, plus attenuation or gain.

### What are the considerations with VFB and CFB amplifiers?


With CFBs, closed-loop gain is largely independent of frequency. Also, CFB amps provide faster slew rate and lower distortion and perform well at higher gains than VFB amps. VFBs can offer lower noise and better dc performance than CFB amps. Other tradeoffs lie in design constraints. With a VFB op amp, the circuit designer has considerable freedom in choosing the value of the feedback resistor, although higher resistance values may limit stability. CFB amplifier datasheets specify the feedback resistor values. CFBs therefore lend themselves to applications that require higher gain levels.

### What are the advantages of differential ADC drivers?

These drivers facilitate single-ended-to-differential and differential-to-differential conversions, common-mode level shifting, and amplification of differential signals. They also exhibit lower distortion and faster settling time than single-ended drivers.

### How can a differential VFB ADC driver differ from a single-ended amplifier?

In addition to the usual invert-

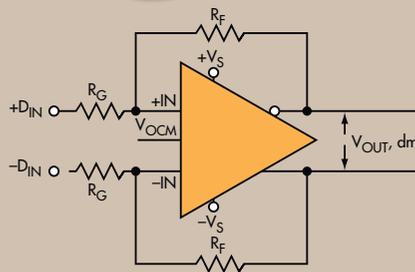

1. Some differential voltage feedback amplifiers include an additional  $V_{OCM}$  input that allows the common-mode voltage of the output signal to be shifted.

ing and non-inverting inputs, some differential VFB ADC drivers have another input,  $V_{OCM}$ , that shifts the common-mode voltage of the differential output (Fig. 1). Like a VFB op amp, closed-loop gain is set by means of input and feedback resistances, but there must be separate, matched resistors for the inverting and non-inverting inputs.

The internal common-mode feedback loop produces outputs that are highly balanced over a wide frequency range


without requiring tightly matched external components. Thus, differential outputs are very close to the ideal of being identical in amplitude and are exactly  $180^\circ$  out of phase. Also, if it is necessary, preserving the dc content of a signal can be accomplished via the  $V_{OCM}$  function.

### When would I need a single-ended, attenuating, level-translating ADC driver? How does it work?

Industrial applications often involve sensors driven by  $\pm 10\text{-V}$  signals. That's a problem with single-ended input ADCs fabricated to today's smaller design rules because those ADCs are constrained to a smaller input signal swing. A level-translating ADC driver takes a large signal, reduces the amplitude, and level-shifts the output common-mode voltage so it is compatible with low-voltage, single-supply ADCs (Fig. 2). For example, a  $20\text{-V}$  p-p ( $\pm 10\text{-V}$ ) input signal riding on  $0\text{ V}$  might be converted to a  $4\text{-V}$  p-p signal riding on  $2.5\text{ V}$ .

There are a number of other ways to perform level-translation. It has been accomplished using multiple amplifiers, single differential drivers like those described above, or ADC drivers designed for level translation. The approach using a single differential driver is simpler than the multi-amplifier approach, and the special-function level translation driver approach is simpler yet.

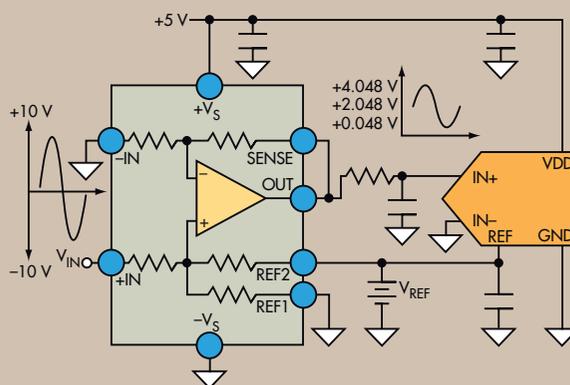Such amps use internally laser-trimmed resistors, ensuring high gain accuracy, along with high common-mode rejection and low offset. A final advantage is that, since the amp and ADC use the same supply voltage as the ADC, there is no need for multiple power supplies.



2. A level-translating driver, optimized for specific ADCs, provides a convenient way to accurately match the wide voltage output of sensors excited by  $\pm 10\text{ V}$  (common in industrial applications) to a single-ended ADC input with a more restricted voltage range.

# ANALOG DEVICES

# product Q&As

## If a driver has a 1-GHz, -3-dB bandwidth, can I use it at that frequency to drive converter inputs?

If you're driving a high-resolution ADC, look beyond the -3-dB spec and consider gain flatness and, in particular, harmonic distortion as a function of frequency. Recall that in a VFB amp, the -3-dB bandwidth figure simply reflects the half-power point after the amp's open-loop gain starts its -6-dB/octave roll-off. That provides a rough figure for comparing amplifiers.

Your concern as a mixed-signal circuit designer must be to minimize the effect of amplifier distortion on the ADC's effective number of bits (ENOB) performance. ENOB is a function of signal-to-noise ratio (SNR) + distortion (SINAD) across the whole analog signal chain:  $ENOB = (SINAD - 1.76) / 6.02$ . So, look to the data sheet graphs of harmonic distortion to make your decision.

## Why would I want to use an active driver instead of a passive transformer?

The main reasons are to get better pass-band flatness and to isolate the signal from the noisy ADC input. Transformers have a rather "lumpy" frequency response. An amplifier should produce less variability, typically  $\pm 0.1$  dB over the frequency range. If the design calls for wideband gain, an amplifier provides a better match than a transformer to the ADC's inputs. Still looking at frequency response, some amplifiers provide dc coupling. Transformers can't deal with slowly varying signals.

Because transformers are passive devices and provide no interstage isolation, noise generated on the secondary coil of the transformer from the ADC input will pass through it back to the original signal source. In contrast, amplifiers buffer the signal source with a low output impedance, providing 70 to 80 dB of interstage isolation from the ADC input back to the original signal source.

On the other hand, a consideration that favors transformers is that at higher frequencies, they may maintain better SNR and spurious-free dynamic range (SFDR). Nevertheless, within the first or second Nyquist zone, a transformer or an amplifier can be used.

## Drivers That Maximize ADC Performance

### VOLTAGE FEEDBACK DIFFERENTIAL ADC DRIVER OFFERS DESIRABLE DISTORTION/POWER CONSUMPTION RATIO AT 70 MHz

The ADA4939-1 achieves 82-dB spurious-free dynamic range (SFDR) at 70 MHz while consuming less than 120 mW of power on a single 3.3-V supply. The device can be used in either single-ended-to-differential or differential-to-differential configuration.



### ULTRALOW-DISTORTION CURRENT-FEEDBACK DIFFERENTIAL ADC DRIVER

The ADA4927 is a low-noise, ultralow-distortion, high-speed, current-feedback differential amplifier that is an ideal choice for driving high-performance ADCs with resolutions up to 16 bits from dc to 100 MHz.

### SINGLE-ENDED, ATTENUATING, LEVEL-TRANSLATING ADC DRIVER

The AD8275 is a  $G = 0.2$  difference amplifier that can be used to translate  $\pm 10$ -V signals to a +4-V level. The device has fast settle time and low distortion, making it suitable for driving 16-bit SAR ADCs.

To view Analog Devices' complete list of ADC drivers, please visit [www.analog.com/ADCdrivers](http://www.analog.com/ADCdrivers).

Differential ADC Drivers									
Part #	Supply Voltage (V)	-3 dB BW (MHz)	Slew Rate (V/ $\mu$ s)	HD2/HD3 (-dBc)	@ BW (MHz)	Voltage Noise (nV/ $\sqrt$ Hz)	IS/Amp (mA Typ)	IS/Amp (mA Typ)	Price (\$U.S./1K)
ADA4938-1	5, $\pm 5$	1000	4700	82/82	50	2.6	37	16-LFCSP	3.84
ADA4939-1	3, 5	1400	6800	83/97	70	2.3	36.5	16-LFCSP	3.84
ADA4927-1	5, $\pm 5$	2300	5000	87/89	100	1.4	20	16-LFCSP	3.79
AD8139	3, 5, $\pm 5$	410	800	85/89	1	2.25	24.5	8-LFCSP/SOIC	3.63
AD8138	3, 5, $\pm 5$	320	1150	94/114	5	5	20	8-SOIC/MSOP	3.8
ADA4937-1	3, 5	1900	6000	84/91	70	2.2	39.5	16-LFCSP	3.84
AD8352	3 to 5.5	2500	9000	82/84	140	2.7	37	16-LFCSP	3.49
AD8132	3, 5, $\pm 5$	350	1200	83/98	5	8	12	8-SOIC/MSOP	1.67
ADA4941-1	2.7 to 12	30	22	101/98	0.1	10.2	2.2	8-LFCSP/SOIC	2.42

Difference Amplifier for Driving ADCs									
Part #	Supply Voltage (V)	-3 dB BW (MHz)	Settling Time to 0.001% (ns)	Input Voltage (V <sub>PP</sub> )	Output Voltage (V <sub>PP</sub> )	Output Type	Voltage Noise (nV/ $\sqrt$ Hz)	Package	Price (\$U.S./1K)
AD8275	3.3 to 15	15	450	20	4	Single-ended	40	8-MSOP	1.6

**EXPERIENCE THE DIGI-KEY DIFFERENCE**

VISIT US FOR ALL YOUR ANALOG DEVICES PRODUCTS AT [DigiKey.com/ADI](http://DigiKey.com/ADI) TODAY!