

# **CMOS DAC APPLICATION GUIDE**

**3<sup>RD</sup> Edition**

**by**

**Phil Burton**



Copyright © 1984 by Analog Devices, Inc. Printed in U.S.A.

All rights reserved. This publication, or parts thereof, must not be reproduced in any form without permission of the copyright owner.

Information furnished by Analog Devices, Inc., is believed to be accurate and reliable. However no responsibility is assumed by Analog Devices, Inc., for its use.

Analog Devices, Inc., makes no representation that the interconnection of its circuits as described herein will not infringe on existing or future patent rights, nor do the descriptions contained herein imply the granting of licenses to make, use, or sell equipment constructed in accordance therewith.

Specifications and prices are subject to change without notice.

G872b-8-1/89



## ACKNOWLEDGEMENTS

This booklet is a complete revision of a 1978 text by Jim Wilson and Jerry Whitmore. Jerry's interest has been maintained in the material and he was one of a team of reviewers for this text. Other reviewers included Bill Hunt, Don Travers, Trevor Emmens, John Wynne and Dan Sheingold, all of whom made useful contributions. Dan deserves special mention for his painstaking correction of the text and the many valuable suggestions he made on presentation.

John Wynne, aided by Mike Murray, had the unenviable task of building and testing all the circuits and made a number of corrections and improvements. Quite a number of the applications circuits were suggested by Norm. Bernstein.

Geraldine White and Gay Moynihan were responsible for typing the drafts and overcoming the daily trials and tribulations, not least of which included a lightning strike at the heart of the word processor.

Finally, it should be acknowledged that this text has been molded by my five years at Analog Devices. Everyone I worked with (and against) during that time has made some contribution to my thoughts and to this text.

Phil Burton,  
N.I.H.E.,  
Limerick,  
Ireland.

October, 1984



# TABLE OF CONTENTS

<b>1.0</b>	<b>INTRODUCTION TO CMOS DACs</b>	<b>1</b>
1.1	Introduction	1
1.2	A Basic DAC	1
1.3	Multiplying Properties	2
1.4	Codes and Terminology	2
1.5	Whole Numbers, Fractions and Justification	3
<b>2.0</b>	<b>INSIDE CMOS DACs</b>	<b>5</b>
2.1	Introduction	5
2.2	The Basic Design of CMOS DACs	5
2.3	CMOS DAC Parameters	7
2.3.1	Output Leakage Current (ILKG)	7
2.3.2	Gain Error	8
2.3.3	Power Supply Rejection Ratio	8
2.3.4	Output Capacitance	8
2.3.5	Settling Time and Propagation Delays of CMOS DACs	8
2.3.6	Multiplying Feedthrough Error	9
2.3.7	Digital-to-Analog Glitch Impulse	9
2.3.8	Distortion and Noise	9
2.3.9	Supply Voltage ( $V_{DD}$ )	9
2.4	Equivalent Circuit of a CMOS DAC	10
2.4.1	Feedback Capacitor Selection	10
2.4.2	Noise Gain of CMOS DACs	10
2.5	Latch-Up in CMOS	10
2.6	Protecting CMOS Against Misuse	11
2.6.1	Electrostatic Discharge (ESD)	11
<b>3.0</b>	<b>BASIC APPLICATIONS CIRCUITS FOR CMOS DACS OPERATED IN THE CONVENTIONAL CURRENT-STEERING MODE</b>	<b>13</b>
3.1	Unipolar (Current-Steering)	13
3.2	Op Amps for Current-Steering Mode DACs	13
3.3	Bipolar Output (Offset Binary and 2's Complement Coding)	14
3.4	Bipolar Output (Sign + Magnitude Coding)	15
3.5	Single Supply DAC with Offset Scale	15
3.6	Changing the Gain of CMOS DACs	16
3.7	Voltage References	16
<b>4.0</b>	<b>SINGLE SUPPLY OPERATION FOR CMOS DACs USING THE VOLTAGE-SWITCHING MODE</b>	<b>19</b>
4.1	Single supply Unipolar DAC	19
4.2	Single Supply DAC with Offset Scale (Voltage-Switching)	20
4.3	Op Amps for Voltage-Switching DAC Circuits	21
4.4	Op Amp Input Stages for Single Supply	21
<b>5.0</b>	<b>THE LOGIC INTERFACE</b>	<b>23</b>
5.1	Level Shifters	23
5.2	Microprocessor Compatible DACs	23

5.3	Practical Interface Design . . . . .	25
5.3.1	Data and Address Bus Connections . . . . .	25
5.3.2	Power Supply, Ground Connections and Circuit Board Layout . . . . .	25
6.0	<b>APPLICATIONS</b> . . . . .	27
6.1	Basic Applications Circuits . . . . .	27
6.1.1	DAC as a Multiplier and Attenuator . . . . .	27
6.1.2	DAC as a Divider or Programmable Gain Element . . . . .	27
6.1.3	Programmable Integrator Circuit . . . . .	28
6.2	D/A Converters and Programmable Power Supplies . . . . .	29
6.2.1	D/A Converter with Minimal Leakage Current . . . . .	30
6.2.2	Dual 8-Bit DAC – Single + 5V Supply . . . . .	30
6.2.3	Low Cost 14-Bit Resolution D/A Converter . . . . .	30
6.2.4	A 16-Bit D/A Converter . . . . .	32
6.2.5	Simple Programmable Power Supply . . . . .	32
6.3	CMOS DAC as a Calibration Trimmer . . . . .	32
6.3.1	Simple Potentiometer Connection . . . . .	34
6.3.2	Dual DAC Trims Gain Error . . . . .	34
6.3.3	Precision Gain Summing Amplifier . . . . .	35
6.3.4	Instrumentation Amplifier . . . . .	35
6.3.5	Programmable Power Supply Using 723 Voltage Regulator . . . . .	36
6.4	Programmable Current Sources . . . . .	38
6.4.1	Basic Current Source Circuits . . . . .	38
6.4.2	4-20mA Loop Circuits . . . . .	40
6.5	Low Frequency Function Generation . . . . .	41
6.5.1	Function Generation via DACs . . . . .	41
6.5.2	Triangle to Sine Conversion . . . . .	42
6.5.3	Interpolation Methods of Function Generation . . . . .	43
6.6	Medium Frequency Function Generators and Oscillators . . . . .	46
6.6.1	Triangle/Square Wave Generator . . . . .	46
6.6.2	Triangle/Rectangle Wave Generator with Programmable Waveform . . . . .	47
6.6.3	State Variable Sine Wave Oscillators . . . . .	47
6.6.4	Digitally Programmable Oscillators and Frequency Modulators . . . . .	48
6.6.5	Programmable One-Shots and Pulse Generators . . . . .	50
6.6.6	Phased Locked Loop Stabilization . . . . .	51
6.7	Digitally Controlled Filters . . . . .	52
6.7.1	Simple Low Pass Filters . . . . .	52
6.7.2	State Variable Filters . . . . .	52
6.8	Audio Applications of CMOS DACs . . . . .	55
6.8.1	Audio Attenuators (Volume Control) . . . . .	55
6.8.2	Audio Balance and Panners . . . . .	55
6.9	Microprocessor Interfaces . . . . .	56
6.9.1	AD7545 to 8-Bit Data Bus Systems . . . . .	56
6.9.2	MCS48 Microcontroller to AD7542 Interface . . . . .	58
6.9.3	AD7542 to 8-Bit Data Bus Systems . . . . .	58
6.10	Miscellaneous Systems Applications . . . . .	59
6.10.1	Resolver-to-Digital Converter . . . . .	59
6.10.2	Co-Ordinate Conversion . . . . .	59
6.10.3	Using CMOS DACs in an AGC System . . . . .	61

<b>APPENDIX</b> . . . . .	62
Key Features and Connections for Analog Devices CMOS DACS . . . . .	62



## REFERENCES

Except where stated, copies of references are not available from Analog Devices.

1. Burton D.P., "Gain Error and Gain Temperature Coefficient of CMOS Multiplying DACs". Application Note available from Analog Devices.
2. Zurada J. & Goodman K., "Equivalent Circuit of Multiplying DAC using R-2R Ladder Network". Electronics Letters, 1980, Vol. 16, pp. 925-927.
3. Regan T., "CMOS DACs Work Backwards to Provide Voltage Outputs". Electronic Design, Sept. 16, 1982, pp. 117-121.
4. Brokaw P., "Input Resistor Stabilises MDACs Gain". EDN, January 7, 1981, pp. 210-211.
5. Travers D., "Applications of High Performance BIFET Op Amps". Application Note available from Analog Devices.
6. Toomey P. & Hunt. W., "AD7528 Dual 8 bit CMOS DAC Application Note". Available from Analog Devices.
7. Williams J., "MDACs Control Frequency not just Amplitude of Signals". Electronic Design, March 19, 1981, pp. 259-261.
8. Williams J., "Exploit D/A Converters in Unusual Controller Designs". EDN, Nov. 25, 1981, pp. 111, 118.
9. Watson D., "Synthesise Low Frequency Sine Waves with High Frequency Crystals". Electronic Design, April 30, 1981, pg. 163.
10. Toomey P., "Improve Function Generators with Matched D/A Converters". EDN, May 12, 1982, pp. 161-166. Article Reprint available from Analog Devices.
11. Burton D.P., "Methods for Generating Complex Waveforms and Vectors Using Multiplying D/A Converters". Application Note available from Analog Devices.
12. Awad S. & Guerin B., "Programmable Sine Generator is Linearly Controlled". Electronics, July 28, 1981, pp. 138-139.
13. Morgan D.R., "Control 10 to 10,000HZ Digitally and Get Complementary Output Frequencies". Electronic Design, January 18, 1977.
14. Hughes G. & Hawley S.A., "Current Mirror Linearises Remote Controlled Timer". Electronics, August 11, 1981, pg. 117.
15. Sydnor D., "Multiplying DAC Stabilises PLL Parameters". Microwaves, March 1981, pp. 71-72.
16. Zurada J.M., "Application of Multiplying Digital to Analog Converter to Digital Control of Active Filter Characteristics". IEE Proc., Vol. 128, Pt.G. No. 2, April 1981, pp. 91-92.
17. Tuthill M. & Wynne J., "Monolithic 16 bit DAC aids High Resolution Process Control". Electronic Design, June 11, 1981.
18. Boyes G.F., "Synchro and Resolver Conversion", Pub. 1980. Available from Analog Devices, Inc. (U.S.A.), Memory Devices Ltd., (U.K.).
19. Mayer A., "Low Cost Co-ordinate Converter Rotates Vectors Easily". Electronics, Sept. 22, 1981, pp. 133-134.
20. Pollock N., "Electronic Compass using a Fluxgate Sensor". Wireless World, Oct., 1982, pp. 49-54.

21. Burton D.P., & Wilson J., "Electronic Wattmeter". Electronic Engineering Times, Sept. 4, 1978, pg. 74.
22. Burton D.P., "Denser CMOS DACs cut Hardware, Software". Electronic Design, Sept. 16, 1982, pp. 133-139.
23. Gray A., "Improved 8 bit Micro Interface for 12 bit peripherals". New Electronics, Sept. 6, 1983, pg. 18.
24. Whitmore J., "Digital to Analog Converter Controls Active Filter", Electronics, January 23, 1975, pg. 86.
25. Bhar T.N. and McMahon E.J., "Electrostatic Discharge Control – Successful Methods for Microelectronic Design and Manufacturing". Hayden Book Co. Inc., Rochelle Park, N.J., 1983.
26. "ESD Prevention Manual", Analog Devices Publication No. E825-5 – 3/84. Available from Analog Devices.
27. Stevastopoulos N., et al., "An Unusual Circuit Configuration Improves CMOS MDAC Performance", EDN, March 5, 1979, pp. 77-81.
28. Jung W., "Audio Application Ideas for CMOS DACs", Analog Dialogue, Vol. 10.1, pg. 16.
29. Wynne J., "Simple Interface between D/A Converter and Microcomputer Leads to Programmable Sine-Wave Oscillator", Application Note available from Analog Devices.
30. Curtin M., "Interfacing the AD7549 to the MCS-48 and MCS-51 Microcomputer Families", Application Note available from Analog Devices.