

PRACTICAL POWER SOLUTIONS



Acknowledgments:

Thanks are due the many technical staff members of Analog Devices in Engineering, Marketing, and Applications who provided invaluable inputs during this project.

Special thanks go to Wayne Rewinkle, Matt Kessler, Brian Goeres, and Hank Zumbahlen who provided major contributions and also reviewed all the material.

Walt Kester, January 2009
Analog Devices Central Applications Department

Direct questions to Linear.Apps@analog.com, with a subject line of "Practical Power Solutions"

**Copyright © 2009 By Analog Devices, Inc.
Printed in the United States of America**

ISBN-13: 978-0-916550-00-4

All rights reserved. This book, or parts thereof, must not be reproduced in any form without permission of the copyright owner. Information furnished by Analog Devices, Inc., is believed to be accurate and reliable. However, no responsibility is assumed by Analog Devices, Inc., for its use.

Analog Devices, Inc., makes no representation that the interconnections of its circuits as described herein will not infringe on existing or future patent rights, nor do the descriptions contained herein imply the granting of licenses to make, use, sell equipment constructed in accordance therewith. Specifications are subject to change without notice.

Practical Power Solutions

Table of Contents

SECTION 1: POINT-OF-LOAD POWER	1.0
Fixed Power Point-of-Load Applications	1.1
"Fixed Power" and "Portable Power" Applications	1.2
Power Distribution System-1 (Down We Go in Voltage)	1.3
Power Distribution System-2 (Down We Go in Voltage)	1.4
Fixed Power Signal Chain Functional Blocks	1.5
Intermediate Bus Structure and Point of Load Regulation Offer Flexibility and Efficiency	1.6
Two Popular Methods of Regulation: Linear and Switching	1.7
Linear Regulators vs. Switchers	1.8
Linear Regulators	1.9
Types of Linear Regulators	1.10
PFET LDO vs. PNP LDO	1.11
ADP1706/ADP1707/ADP1708 CMOS LDO Dropout Voltage vs. Load Current	1.12
Linear Regulator Specifications	1.13
Regulator Output Error	1.14
LDO Power Supply Rejection	1.15
Stability Issues with Traditional PNP or PMOS LDOs	1.16
Stabilizing the Regulator Loop Using the Zero Created by the Output Capacitor and its ESR	1.17
Zoned Load Capacitor ESR Can Create an LDO Applications Nightmare	1.18
Bipolar LDOs Use anyCAP Design	1.19
Analog Device's CMOS LDOs	1.20
Transient Response to Current Load Step	1.21
Linear Regulator Load Current Step Transient Response for ADP1715/ADP1716	1.22
Other Useful Features for Low Dropout Linear Regulators	1.23
ADP1707 Simultaneous Voltage Tracking	1.24
ADP1707 Ratiometric Voltage Tracking	1.25
Switching Regulators and Controllers	1.26
Step-Down (Buck) Converter	1.27
Step-Up (Boost) Converter	1.28
DC-to-DC Converter Terminology	1.29
Step-Down DC-to-DC Converters: Synchronous Rectification	1.30
What Topology Depends Primarily on Output Current (Approximate Values Given Below)	1.31
Other Switching Topologies	1.32
Isolated Topologies: Asynchronous Buck-Boost-Flyback	1.33
Key Specifications	1.34
Key Specifications (Continued)	1.35
Switching Frequency Considerations	1.36
Methods for Designing Switchers	1.37
Fundamental Switcher Calculations: This is Only the Beginning!	1.38
Stability and Transient Considerations	1.39
Power Losses in Switching Supplies Determine Efficiency	1.40
Powering FPGAs	1.41
FPGA Power Supply Considerations	1.42
Proper Application of Power to FPGA	1.43
Power Supply Must Charge Bulk Capacitance and Supply Inrush Current Monotonically	1.44
Sequencing/Power-On Issues with FPGAs	1.45
Simultaneous, Ratiometric, and Sequential Supply Sequencing Methods	1.46
Xilinx Virtex-4 FPGA Power Supplies	1.47
Switching Supply Error Budget Must Include Transient in Most FPGA Applications	1.48
ADP1829 Load Transient Response	1.49
ADP1829 Dual, Interleaved, Step-Down DC-to-DC Controller with Tracking	1.50

Practical Power Solutions

Table of Contents

Powering DSPs	1.51
Typical Low Power DSP and FPGA Voltage and Current Requirements.....	1.52
ADSP-BF534/ADSP-BF536/ADSP-BF537 IDD Typical Dynamic Current.....	1.53
ADSP-BF534/ADSP-BF536/ADSP-BF537 Maximum Static Current.....	1.54
Blackfin Power Solutions.....	1.55
A Simple Solution to a Tricky Problem: Replacing 1.8 V Core Supply with 1.2 V Supply.....	1.56
ADIsimPower	1.57
What is ADIsimPower?.....	1.58
ADIsimPower Value Advantages.....	1.59
Vendor Database.....	1.60
Application Space Covered by ADIsimPower.....	1.61
ADIsimPower Video	1.62
ADIsimPower Step 1: Enter Your Design Criteria.....	1.63
ADIsimPower Step 2: View All Design Solutions.....	1.64
ADIsimPower Step 3: View Solution Details.....	1.65
ADIsimPower Step 3: View Solution Details (Continued).....	1.66
ADIsimPower Step 4: Build Your Design.....	1.67
Technical Reference Material	1.68
Analog Devices' Textbook References.....	1.69
Other Textbook References.....	1.70
SECTION 2: SYSTEM POWER MANAGEMENT AND PORTABLE POWER	2.0
Designing a Typical System Power Chain	2.1
A Typical System Using AC Power.....	2.2
End Power Requirements for System.....	2.3
General Guidelines for Power Trains.....	2.4
Choice of AC Power Adapter.....	2.5
After Choosing a 12 V Power Bus, What is the Next Step?.....	2.6
Powering the High Current Devices from a Dual Synchronous Buck Controller.....	2.7
Finishing the Design using the 5 V Intermediate Bus and More POL Regulators.....	2.8
Overall System Efficiency Calculations.....	2.9
Efficiency Comparison: ADP2107 Synchronous Regulator vs. ADP1864 Asynchronous Controller.....	2.10
Design Solutions Using ADIsimPower.....	2.11
Efficiency of ADP1864 Asynchronous Buck Controller vs. ADP2107 PFM Synchronous Buck Regulator.....	2.12
Microprocessor Supervisory Functions	2.13
Simple Reset and Power-On Reset Generator.....	2.14
ADM6710 Low Voltage Quad Supervisory Circuit.....	2.15
Adding an External Reset and a Watchdog Timer to the Reset Generator.....	2.16
Reset Generator and Battery Backup Circuit.....	2.17
Online Supervisory Parametric Search.....	2.18
Results from Supervisory Parametric Search.....	2.19
Power Supply Monitoring and Sequencing	2.20
Comparators as Voltage Monitors.....	2.21
Sequencing Supplies: I/O Before Core.....	2.22
Sequencing Supplies: Core Before I/O.....	2.23
Basic Sequencing Using ADM1085 Simple Sequencer and Regulator Enables.....	2.24
ADM1185 Quad Voltage Monitor and Sequencer.....	2.25
ADM1185 Typical Monitoring and Sequencing Application.....	2.26
Timing Diagram for ADM1185.....	2.27
ADM1066 Super Sequencer.....	2.28
State Machine Based Sequencing Engine Core.....	2.29
ADM1066 Super Sequencer.....	2.30
Closed-Loop Supply Margining Using ADM1062/ADM1066.....	2.31

Practical Power Solutions

Table of Contents

Hot Swap Controllers	2.32
What is a Hot Swap Controller?.....	2.33
Hot Swap Techniques.....	2.34
Functions of a Hot Swap Controller.....	2.35
Components of a Hot Swap Controller.....	2.36
How the Hot Swap Controller Works for Normal Power Up.....	2.37
How the Hot Swap Controller Works for Power Up Into a Fault.....	2.38
Soft Start Gives Linear Inrush Current Control.....	2.39
Hot Swap Controller and Power Monitoring ADM1175, ADM1176, ADM1177, ADM1178.....	2.40
ADM117x/ADM119x Solution for Digital Power Measurement.....	2.41
Temperature Monitoring	2.42
Types of Temperature Sensors.....	2.43
Basic Relationship for IC Temperature Sensors.....	2.44
Classic Band Gap Temperature Sensor.....	2.45
Analog Temperature Sensors are Now Integrated into Many Different Parts.....	2.46
Low Cost, 2.7 V to 5.5 V, Micropower Temperature Switches in SOT-23.....	2.47
Digital Isolation and Isolated Power	2.48
Digital Isolators Based on <i>i</i> Coupler Technology.....	2.49
Construction of the <i>i</i> Coupler Digital Isolator.....	2.50
Unidirectional and Bidirectional Transmission.....	2.51
<i>i</i> Coupler Simplifies True Bidirectional Isolation.....	2.52
True Bidirectional Isolation Using the ADuM1250 Digital Isolator.....	2.53
ADuM5240 Dual-Channel Isolator with <i>iso</i> Power Integrated DC-to-DC Converter.....	2.54
<i>iso</i> Power Digital Isolator Implements Isolated Power.....	2.55
Isolated SPI Interface Using <i>i</i> Coupler Technology and Optocouplers.....	2.56
Completely Isolated Turbidity Sensor and ADC.....	2.57
Digital Power Applications	2.58
Digital Power Management and Digital Power Control.....	2.59
Digital Control Loop Features.....	2.60
Typical Application of ADP1043 Secondary-Side Controller.....	2.61
Programmability and Monitoring (Through I2C).....	2.62
Powering Portable Systems	2.63
Portable Power Considerations.....	2.64
The Energy System: Lithium Ion (Li-Ion).....	2.65
Techniques for Portable Power.....	2.66
Processor Power Distribution with Separate Core and I/O Voltage.....	2.67
Typical Application using a Switching Regulator and an LDO in Cascade.....	2.68
Point-of-Use Regulation Using LDOs with Low VIN – VOUT.....	2.69
Buck-Boost Regulators Often Needed for Low Voltage Batteries.....	2.70
Integrated Camera Module Solution.....	2.71
ADP1653 Flash LED Driver Requires Boost Regulator.....	2.72
Basic Switched Capacitor Voltage Inverter and Voltage Doubler.....	2.73
ADP3605 120 mA Switched Capacitor Inverter with Regulated Output.....	2.74
ADM8845 Charge Pump Driver for LCD Displays with White LED Backlights.....	2.75
Technical References	2.76
Analog Devices' Technical References.....	2.77

Practical Power Solutions

Table of Contents

SECTION 3: POWER FOR MIXED ANALOG/DIGITAL SYSTEMS	3.0
General Guidelines for Powering Analog Circuits	3.1
Power Supply Rejection (PSR) vs. Frequency is a Key Specification	3.2
Definition of Ripple Free Dynamic Range	3.3
Determine the Device's Sensitivity to Ripple by Calculating the RFDR at the Switching Frequency	3.4
Example Calculation of Maximum Allowable Power Supply Ripple Voltage	3.5
Measuring Ripple	3.6
Powering Amplifiers	3.7
Typical Weigh Scale Application of Instrumentation Amplifier	3.8
PSR for Representative In-Amps	3.9
Instrumentation Amplifier Characteristics	3.10
In-Amp Input and Power Supply Filtering	3.11
Industry-Standard OP07 and OP27 Precision Bipolar Op Amps PSR (RTI)	3.12
OP1177 Modern, Precision, Bipolar Op Amp PSR (RTI)	3.13
ADA4937-1: 1.9 GHz, Low Distortion, 16-Bit, SiGe Differential ADC Driver (RTO)	3.14
Amplifier PSR Summary	3.15
Powering ADCs	3.16
Defining Dynamic PSR of an ADC in Terms of its Spectral Output	3.17
Example Calculation of Maximum Allowable Power Supply Ripple	3.18
Multichannel Data Acquisition System on a Chip	3.19
AD7641:18-Bit, 2 MSPS, PulSAR ADC	3.20
Integrator and Digital Filter Reduce the Effects of Power Supply Ripple in Σ - Δ ADCs	3.21
Sigma-Delta Power Considerations	3.22
AD9246 14-Bit, 125 MSPS Pipelined ADC	3.23
Test Setup to Evaluate Switching Supply Effect on AD9246 14-bit, 125 MSPS ADC	3.24
Switching Power Supply Details	3.25
Modified AD9246 Evaluation Board Showing Switching Supply Boards	3.26
ADP2106 Switching Regulator Output Measured at AVDD of AD9246	3.27
Noise Floor of ADC for Linear and Switching Supplies with Input Grounded FFT Data Shows Spurs to 2MHz	3.28
Analysis of AD9246 ADC PSR	3.29
SNR and SFDR of 14-Bit AD9246 for Linear and Switching Supplies, $f_s = 125$ MSPS	3.30
SNR and SFDR of AD9446 16-bit, 80 MSPS ADC for Linear and Switching Supplies, $f_s = 80$ MSPS	3.31
Pipelined ADC PSR Summary	3.32
Sampling Clock Jitter and Aperture Jitter Increase ADC Noise	3.33
ADC SNR as a Function of Analog Input Frequency and Clock Jitter	3.34
Using a Phase-Locked Loop (PLL) and Bandpass Filter to Condition a Noisy Clock Source	3.35
Powering Precision Analog Microcontrollers	3.36
ADuC7026 Precision Analog Microcontroller with 12-Bit Analog I/O, ARM7TDMI MCU	3.37
Powering the Analog Devices' ADuC702x Family of Precision Analog Microcontrollers	3.38
Voltage References	3.39
Shunt and Series Voltage References	3.40
XFET Reference Architecture	3.41
Band Gap and XFET Reference Ripple Rejection Ratio	3.42
Voltage Reference Noise	3.43
Reference Noise Requirements for Various System Accuracies (1/2 LSB / 100kHz BW Criteria)	3.44
References Should be Stable with Capacitive Loads	3.45
External Reference for SAR ADC Requires Energy Storage Capacitor to Prevent Errors	3.46
Reference Temperature Drift Requirements for Various System Accuracies (1/2 LSB Criteria, 100°C Span)	3.47
Low Noise Reference Driving a Sigma-Delta ADC	3.48
Voltage Reference Summary	3.49

Practical Power Solutions

Table of Contents

Powering Clock Circuits.....	3.50
Power Supply Ripple Modulates PLL Output.....	3.51
AD9858: 1 GSPS DDS with Phase Detector and Analog Multiplier.....	3.52
Determining if Spurs are Coming from Power Supply in DAC/DDS Systems.....	3.53
Superposition of Four DDS Output Carriers with 150 kHz AM Modulation on AVDD Power Supply.....	3.54
DDS RFDR/PSR Analysis (Very Approximate).....	3.55
Reducing Power Supply Noise by Bulk Filtering.....	3.56
Buck Converter with Input Filter.....	3.57
Buck Converter with Output Ripple Filter.....	3.58
Boost Converter with Output Ripple Filter.....	3.59
LC Filter Attenuation Approximation.....	3.60
Simulated Gain of LC Network Using NI Multisim Analog Devices Edition.....	3.61
Ferrite Bead Impedance Compared to a 1 μ H Inductor.....	3.62
Reducing Ripple and Noise by Localized Decoupling and Filtering.....	3.63
What is Proper Localized Decoupling?.....	3.64
Power Supply Rejection Ratio vs. Frequency for the AD8000 1.5 GHz Op Amp.....	3.65
Effects of Decoupling on Performance of the AD8000 Op Amp.....	3.66
FFT Plot for the AD9445 Evaluation Board with Proper Decoupling.....	3.67
AD9445 Pinout Diagram.....	3.68
FFT Plot for an AD9445 Evaluation Board with Caps Removed from the Analog Supply.....	3.69
FFT Plot for an AD9445 Evaluation Board with Caps Removed from the Digital Supply.....	3.70
Resonant Circuit Formed by Power Supply Decoupling Network.....	3.71
Reducing Power Supply Noise Using LDO Post Regulators.....	3.72
Reducing Ripple Using an LDO as a Post Regulator.....	3.73
ADP1708 1 A CMOS LDO PSR.....	3.74
Powering the ADuC7026 MicroConverter with the ADP1710 150mA LDO.....	3.75
LDO Regulator Noise.....	3.76
Reducing Power Supply Noise by Physical Separation from Analog Circuits.....	3.77
Types of Coupling.....	3.78
ADC/FPGA System Evaluation Board Power Design (Physical Separation Avoids Noise).....	3.79
ADC/FPGA System Board Layouts (Physical Separation Avoids Noise).....	3.80
Optimum PCB Layout Begins with Critical Component Placement (Physical Separation Avoids Noise).....	3.81
Noise and Ripple Reduction Techniques Summary.....	3.82
Reducing Noise in Mixed-Signal Circuits by Proper Grounding.....	3.83
Digital Currents Flowing in Analog Return Path Create Error Voltages.....	3.84
Simple Four Layer Board Stack with Split Analog and Digital Ground Planes.....	3.85
Simple Four Layer Board Stack with Single Ground Plane.....	3.86
Maintaining Low Impedance to Power Supply.....	3.87
ADC Grounding: The Wrong Way.....	3.88
Split Ground Planes, Connected at System PS.....	3.89
Split Ground Planes, Connected at ADC.....	3.90
Single Ground Plane.....	3.91
Technical References.....	3.92
Analog Devices' Textbook References.....	3.93
Other Textbook References.....	3.94

Practical Power Solutions

Table of Contents

SECTION 4: HARDWARE DESIGN TECHNIQUES	4.0
Passive Components	4.1
Capacitors	4.2
A Real Capacitor Equivalent Circuit Includes Parasitic Elements	4.3
"Bathtub" Impedance of 100 μ F Capacitors	4.4
Response of a Capacitor to a Current Step	4.5
Capacitor Data Sheet : What Do Specs Mean?	4.6
Capacitors for Power Designs: Energy Storage	4.7
Capacitors for Power Designs: Filtering	4.8
Boost Converter with Output Pi Filter	4.9
Capacitor Functions in Buck Converter	4.10
Capacitor Functions in a Boost Converter	4.11
Capacitor Functions in Buck-Boost Regulators	4.12
Parallel Capacitors	4.13
Popular Capacitor Types	4.14
Aluminum Electrolytic Capacitors	4.15
Solid Tantalum Capacitors	4.16
OS-CON (Sanyo)	4.17
POSCAP (Polymer Organic Semiconductor Capacitor)	4.18
Impedance of Various 100 μ F Capacitors	4.19
Ceramic Capacitors	4.20
Which Ceramic Capacitor Provides More Capacitance?	4.21
Inductor Basics	4.22
Wire and Strip Inductance Calculations	4.23
Inductor Basic Current/Voltage Relationship	4.24
Inductor Model	4.25
Inductor Power Losses	4.26
Inductor Functions in Switching Converters	4.27
Inductor Specifications	4.28
Inductor Cores and Their Characteristics	4.29
Inductor Selection Considerations	4.30
Saturation of Inductors	4.31
Shielded or Unshielded?	4.32
New Inductor Technology: Multilayer Ceramic Inductors for Power	4.33
Coupled inductors	4.34
Calculation of Sheet Resistance and Linear Resistance	4.35
Mismatched Resistor TCs Can Induce Temperature-Related Gain Errors	4.36
Current Sense Resistors Require Kelvin Sensing	4.37
Sense Resistor Considerations	4.38
Active Components	4.39
MOSFET Basics	4.40
N-Channel vs. P-Channel	4.41
MOSFET Parameters of Interest for Switching Converters	4.42
Calculating Power in MOSFETs Conduction Loss	4.43
Calculating Power in MOSFETs: Switching Loss	4.44
MOSFET Switching Loss (Continued)	4.45
Is MOSFET Power Dissipation Too High?	4.46
Snubber Selection for Buck Converters	4.47
Snubber Selection for Buck Converters	4.48
Effect of Snubber on the Switch Node for a Buck Converter	4.49
Diode Rectifiers	4.50
Diode Parallel and Series Connections	4.51

Practical Power Solutions

Table of Contents

Power Supply Layout and Grounding	4.52
Parasitics to Deal with in PCB Layout.....	4.53
Printed Circuit Board Resistance.....	4.54
Relative Dielectric Constant, ϵ_r , for Common PCB Materials.....	4.55
Kirchoff's Law Helps Analyze Voltage Drops Around a Complete Circuit.....	4.56
A More Realistic View of the Impedance Between Grounds.....	4.57
Switching Currents Flowing in Analog Return Path Create Error Voltages.....	4.58
Magnetic Field Lines and Inductive Loop (Right Hand Rule).....	4.59
Magnetic Field Passing Through a Loop Area Creates Magnetic Flux.....	4.60
Effects of Opening a Switch.....	4.61
The Effects of Switching on Loop Area for Buck Converters.....	4.62
Buck Converter Layout.....	4.63
Boost Converter Layout.....	4.64
Synchronous Buck Converter Layout.....	4.65
ADP1821 Synchronous Buck Layout.....	4.66
ADP1821 Synchronous Buck Layout Details-1.....	4.67
ADP1821 Synchronous Buck Layout Details-2.....	4.68
Asynchronous Buck Switching Controller Layout	4.69
Details of ADP1864 Double-Sided Board Layout.....	4.70
Return Current Takes the Path of Least Impedance.....	4.71
Effects of Component Orientation.....	4.72
Shielding	4.73
Reflection and Absorption Are the Two Principal Shielding Mechanisms.....	4.74
Conductivity and Permeability for Various Shielding Materials.....	4.75
Thermal Design	4.76
Thermal Design Basics.....	4.77
ADP1706 1 A LDO Power Dissipation.....	4.78
Thermal Resistance of Popular Packages.....	4.79
Heat Sink Basics.....	4.80
TO-220 and TO-263 (D2PAK) Packages.....	4.81
Thermal Resistance of TO-263 (D2PAK) vs. Drain Pad Area - No Airflow.....	4.82
Thermal Resistance of AAVID 573300 Surface Mount Heat Sink vs. Airflow.....	4.83
Technical References	4.84
Analog Devices' Textbook References.....	4.85
Other Textbook References.....	4.86

