SYSTEM APPLICATIONS GUIDE

PRECISION SENSOR SIGNAL CONDITIONING AND TRANSMISSION 1

MULTIPLEXING SIGNALS WITH ANALOG SWITCHES 2

PROGRAMMABLE GAIN AMPLIFIERS 3

HIGH ACCURACY SAMPLE AND HOLD CIRCUITRY 4

VOLTAGE REFERENCES FOR HIGH ACCURACY SYSTEMS 5

HIGH ACCURACY A/D CONVERSION 6

THE AD1B60: AN INTELLIGENT, DIGITIZING SIGNAL CONDITIONER 7

AUDIO APPLICATIONS 8

INTRODUCTION TO HIGH SPEED SIGNALS AND SYSTEMS 9

HIGH SPEED SIGNAL AMPLIFICATION 10

VIDEO SIGNAL TRANSMISSION AND PROCESSING 11

SELECTING THE RIGHT HIGH SPEED ADC 12

INTERFACING TO HIGH SPEED ADCs 13

SIGMA-DELTA ADCs AND DACs 14

WIDE DYNAMIC RANGE ADC APPLICATIONS 15

TECHNIQUES FOR VERIFYING HIGH SPEED ADC PERFORMANCE 16

HIGH SPEED DACs AND DIRECT DIGITAL SYNTHESIS 17

SIGNAL COMPUTING APPLICATIONS IN COMMUNICATIONS 18

MOTOR CONTROL CIRCUITS 19

INDEX I

ANALOG DEVICES TECHNICAL REFERENCE BOOKS

PUBLISHED BY PRENTICE HALL

- Analog-Digital Conversion Handbook
- Digital Signal Processing Applications Using the ADSP-2100 Family
- Digital Signal Processing in VLSI
- DSP Laboratory Experiments Using the ADSP-2101
- ADSP-2100 Family User's Manual

PUBLISHED BY ANALOG DEVICES

- System Applications Guide
- Amplifier Applications Guide
- Mixed Signal Design Seminar Notes
- High-Speed Design Seminar Notes
- Nonlinear Circuits Handbook
- Transducer Interfacing Handbook
- Synchro & Resolver Conversion
- THE BEST OF *Analog Dialogue*, 1967-1991

SYSTEM APPLICATIONS GUIDE

ACKNOWLEDGMENTS

Thanks are due the many technical staff members of Analog Devices in Engineering and Marketing who provided invaluable inputs during this project. Particular credit is due the individual authors whose names appear at the beginning of their material.

James M. Bryant served as co-editor and contributed greatly to the technical clarity, accuracy, and style of the entire book.

Linda Grimes Brandon of Brandon's WordService prepared the new illustrations and typeset the text. Ernie Lehtonen of the Analog Devices' art department supplied many camera-ready drawings. Judith Douville compiled the index, and printing was done by R. R. Donnelley and Sons, Inc.

Walt Kester
1993

Copyright © 1993 by Analog Devices, Inc.
Printed in the United States of America

All rights reserved. This book, or parts thereof, must not be reproduced in any form without permission of the copyright owner.

Information furnished by Analog Devices, Inc., is believed to be accurate and reliable. However, no responsibility is assumed by Analog Devices, Inc., for its use.

Analog Devices, Inc., makes no representation that the interconnections of its circuits as described herein will not infringe on existing or future patent rights, nor do the descriptions contained herein imply the granting of licenses to make, use, or sell equipment constructed in accordance therewith.

Specifications are subject to change without notice.

ISBN 0-916550-13-3

ANALOG DEVICES
SYSTEM APPLICATIONS GUIDE

SECTION 1
PRECISION SENSOR SIGNAL CONDITIONING AND TRANSMISSION

- Precision Signals and System Error Sources
- Sensor Output Signal Conditioning Examples
- Remote Sensor Application Problems
- Shielding Long Cables Effectively Against Noise Pickup
- Filtering and Protection Against EMI/RFI
- Input-Stage RFI Rectification Sensitivity
- RFI Rectification: An Analytical Approach
- Input Overvoltage Protection
- Transmitting Precision Signals in Noisy Environments
- Isolating Transducers

SECTION 2
MULTIPLEXING SIGNALS WITH ANALOG SWITCHES

- Parasitic Latchup Mechanism and Prevention Techniques
- The Anatomy of the Analog Switch
- Trench-Isolated LC^{2}MOS Analog Switch Family Offers Many Benefits
- Applying the Analog Switch

SECTION 3
PROGRAMMABLE GAIN AMPLIFIERS

SECTION 4
HIGH ACCURACY SAMPLE AND HOLD CIRCUITRY

SECTION 5
VOLTAGE REFERENCES FOR HIGH ACCURACY SYSTEMS

- A Low Noise Discrete Bandgap Design
- An Ultra Low Noise Reference Circuit
- Effects of Output Loading on Reference Outputs

SECTION 6
HIGH ACCURACY A/D CONVERSION

- Signal Conditioning Transducer Input ADCs
- Single Supply ADCs
- Serial Output ADCs
- Complete Data Acquisition on a Chip
- Ultra-High Resolution DAS on a chip

SECTION 7
THE AD1B60: AN INTELLIGENT, DIGITIZING SIGNAL CONDITIONER

- The Analog State-of-the-Art
- What are Digital Signal Conditioners?
- An Embedded Microcontroller Gives the AD1B60 "Intelligence"
- Built-In Circuits Makes Acquiring the Sensor Signals Simple

- Communication Ports
- Digital Command and Control
- Conversion Modes
- Calibrating the AD1B60
- The AD1B60 in Thermocouple Applications
- Configuring the AD1B60 for Voltage Inputs
- Configuring the AD1B60 for RTD Applications
- Using the AD1B60 in an Industrial Environment
- Supplying Power to the AD1B60
- Layout Techniques for Maximum Performance
- The AD1B60 Evaluation Board
- Using Digital Algorithms in Signal Conditioning Circuitry

SECTION 8
AUDIO APPLICATIONS

- Audio Preamplifiers:
  Mic Preamplifiers, RIAA Phono Preamplifiers,
  Tape Preamplifiers
- Audio Line Level Stages:
  Audio Line Receivers, Audio Line Drivers and Buffers
- DC Servo Controlled Audio Stages
- Speaker Crossovers
- Digital Audio for Studio Applications:

The AD1879 18 Bit Sigma-Delta Audio ADC, Applications for Audio DACs in Compact Disc (CD) Player Electronics

- DAC Architectures
- Stereo Codecs for Multimedia and Business Audio Applications
- Signal Computing Audio Chipsets and Algorithms
- Personal Sound Systems Using the AD20msp614 Audio Chipset

SECTION 9
INTRODUCTION TO HIGH SPEED SIGNALS AND SYSTEMS

- High Speed Signal Levels, Impedances, and Noise
- Dynamic Range of High Speed Systems
- Defining High Speed System Dynamic Range

SECTION 10
HIGH SPEED SIGNAL AMPLIFICATION

- High Speed Amplifier Architectures
- Current Feedback Amplifiers
- Comparison Between Voltage Feedback and Current Feedback Op Amps
- High Speed Buffer Amplifiers
- High Speed Op Amp Noise Models
- Op Amp DC Model
- Level Shifting High Speed Signals Using Op Amps

SECTION 11
VIDEO SIGNAL TRANSMISSION AND PROCESSING

- Driving Capacitive Loads With Wideband Op Amps:
  Out-of-Loop Resistive Compensation for Driving Capacitive Loads, In-the-Loop Resistive Compensation for Driving Capacitive Loads, Using Op Amps With Internal Capacitive-Load Compensation
- Cable Driving at Video Frequencies
- Video Signal Processing:
  Differential Gain and Phase Specifications, Video Line Drivers, High Speed Differential Signal Transmission, Video Line Receivers Using the AD830 Active Feedback Amplifier Topology, A Composite Video Sync Tip DC Restorer, A Video Sync Stripper Circuit
- Maintaining Transmission Line Impedances on the PC Board

SECTION 12
SELECTING THE RIGHT HIGH SPEED ADC

- Discrete Time Sampling of Analog Signals
- Properly Specifying the ADC Sampling Rate and the Antialiasing Filter
- Properly Specifying the ADC Resolution and Dynamic Range Requirements
- High Speed Flash Converters and Error Sources
- High Speed Subranging ADCs and Error Sources
- Aperture Delay Time (or Effective Aperture Delay Time)
- Errors Due to Aperture Jitter
- Transient Response or Settling Time

- Overvoltage Recovery Time
- Metastability and Bit Error Rates in ADCs

SECTION 13
INTERFACING TO HIGH SPEED ADCs

- Driving the High Speed ADC Input and Generating Reference Voltages
- Capturing High Speed ADC Output Data
- Demultiplexing High Speed ADC Outputs
- Dealing With 16-bit Precision Sampling ADCs
- Data Output Considerations for Precision Sampling DSP ADCs
- Protecting the ADC Input From Overdrive and Preventing Latchup
- Sampling Clock Generation
- Power Supplies, Ground Planes, Decoupling, and Layout
- Prototyping High Performance Analog Circuitry

SECTION 14
SIGMA-DELTA ADCs AND DACs

- Sigma-Delta Overview
- Oversampling
- Sigma-Delta Modulators and Quantization Noise Shaping
- Digital Filtering and Decimation

- Idling Pattern and Tonal Considerations for Sigma-Delta ADCs
- Higher Order Modulator Loops
- Description of the AD776 Third-Order Sigma-Delta ADC
- Description of the AD1879 18 Bit Sigma-Delta Audio ADC
- Sigma-Delta DACs
- THE AD28msp02 SIGMA-DELTA CODEC
- Multistage Noise Shaping (MASH) Sigma-Delta Converters
- Multi-Bit Sigma-Delta Converters
- Sigma-Delta Summary

SECTION 15
WIDE DYNAMIC RANGE ADC APPLICATIONS

- Achieving Wide Dynamic Range in Digital Spectral Analysis
- Use of Dither Signals to Increase ADC Dynamic Range
- Direct IF to Digital Conversion Applications Using Undersampling Techniques
- Bandpass Sigma-Delta Techniques for Direct IF-To-Digital Conversion
- Achieving Wide Dynamic Range Using Variable Gain Amplifiers
- Wide Dynamic Range Ultrasound Systems

SECTION 16
TECHNIQUES FOR VERIFYING HIGH SPEED ADC PERFORMANCE

- Analog Techniques for Evaluation of ADC Static Transfer Functions

- Analog Techniques for Evaluating ADC Dynamic Transfer Function
- Bench Testing High Speed ADCs Using DSP Techniques
- FFT Testing
- Troubleshooting the FFT Output

SECTION 17
HIGH SPEED DACs AND DIRECT DIGITAL SYNTHESIS

- Settling Time
- Glitch Impulse Area
- Harmonic Distortion and Spurious Free Dynamic Range
- DACs Designed for Maximum Dynamic Range
- Wide Dynamic Range DDS Systems
- Injecting Digital Dither in DDS Systems to Increase SFDR
- Deglitching DACs Using SHAs
- Sin(x)/x Frequency Rolloff Effect

SECTION 18
SIGNAL COMPUTING APPLICATIONS IN COMMUNICATIONS

- Introduction to Signal Computing:
  Applications of Signal Computing, Signal Computing Hardware, Software: Open Architecture the Key, What It All Means
- High Performance Modems for Data Transmission

- The AD28msp01 PSTN Signal Port for V.32 Modems
- The AD20msp500-Series of Software Programmable PSTN Communications Chipsets and the ADAT-DSI01 DataPump Algorithm Toolkit
- Digital Telephone Answering Machine Solution Using Signal Computing From Analog Devices
- Digital Mobile Radio Overview
- The GSM System

SECTION 19
MOTOR CONTROL CIRCUITS

- AC Induction Motors
- Variable Voltage Variable Frequency Control
- Vector Control
- Slip Control
- High Performance Dynamic Control
- General Description of AD2S100/110 AC Vector Processors
- GAMANA - A Project in Motion
- GAMANA VT
- GAMANA GMCDS
- Chipsets / Algorithms
- Applications

INDEX

SYSTEM APPLICATIONS GUIDE

PRECISION SENSOR SIGNAL CONDITIONING AND TRANSMISSION 1

MULTIPLEXING SIGNALS WITH ANALOG SWITCHES 2

PROGRAMMABLE GAIN AMPLIFIERS 3

HIGH ACCURACY SAMPLE AND HOLD CIRCUITRY 4

VOLTAGE REFERENCES FOR HIGH ACCURACY SYSTEMS 5

HIGH ACCURACY A/D CONVERSION 6

THE AD1B60: AN INTELLIGENT, DIGITIZING SIGNAL CONDITIONER 7

AUDIO APPLICATIONS 8

INTRODUCTION TO HIGH SPEED SIGNALS AND SYSTEMS 9

HIGH SPEED SIGNAL AMPLIFICATION 10

VIDEO SIGNAL TRANSMISSION AND PROCESSING 11

SELECTING THE RIGHT HIGH SPEED ADC 12

INTERFACING TO HIGH SPEED ADCs 13

SIGMA-DELTA ADCs AND DACs 14

WIDE DYNAMIC RANGE ADC APPLICATIONS 15

TECHNIQUES FOR VERIFYING HIGH SPEED ADC PERFORMANCE 16

HIGH SPEED DACs AND DIRECT DIGITAL SYNTHESIS 17

SIGNAL COMPUTING APPLICATIONS IN COMMUNICATIONS 18

MOTOR CONTROL CIRCUITS 19

INDEX I